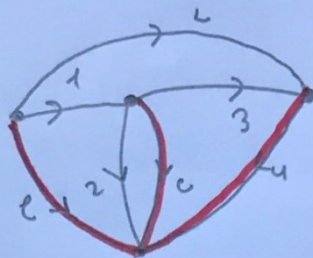


Graf



$$T = \{e, c, 4\}$$


(1) State variables $\begin{pmatrix} v_c \\ i_c \end{pmatrix}$

(2)
$$i_c + i_2 - i_1 + i_3 = 0$$

$$v_L + v_4 - e = 0$$

(3)
$$C \frac{dv_c}{dt} = i_1 - i_2 - i_3$$

$$L \frac{di_c}{dt} = e - v_4$$

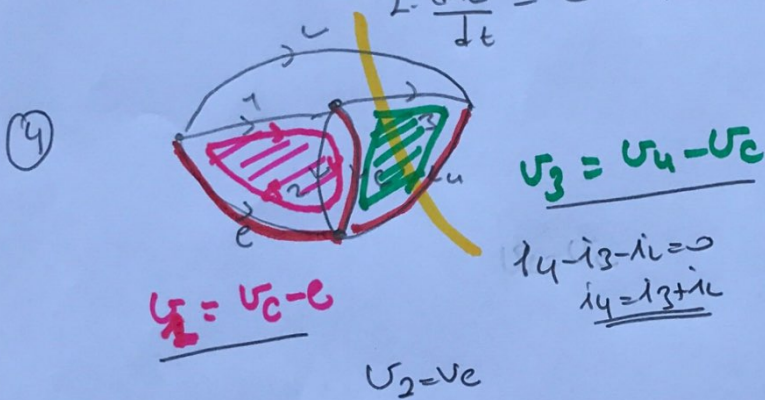

(5)
$$C \frac{dv_c}{dt} = G_1(v_c - e) - G_2 v_c - G_3(v_4 - v_c)$$

$$L \frac{di_c}{dt} = e - v_4$$

$v_4 = ?$

$$i_4 = i_3 + i_c$$

$$v_4 = G_4 i_4 = G_4(i_3 + i_c)$$

$$= G_4(G_3 v_3 + i_c)$$

$$v_4 = G_4(G_3(v_4 - v_c) + i_c)$$

$$v_4 = G_4 G_3 v_4 - G_4 G_3 v_c + G_4 i_c$$

$$(1 - G_4 G_3) v_4 = -G_4 G_3 v_c + G_4 i_c$$

$$v_4 = \frac{-G_4 G_3 v_c + G_4 i_c}{1 - G_4 G_3}$$


$$C \frac{dv_c}{dt} = G_1(v_c - e) - G_2 v_c - G_3 \left(-\frac{G_4 G_3 v_c + G_4 i_c}{1 - G_4 G_3} - v_c \right)$$

$$L \frac{di_c}{dt} = e + \frac{G_4 G_3 v_c - G_4 i_c}{1 - G_4 G_3}$$



3

$\frac{dc}{dt}$

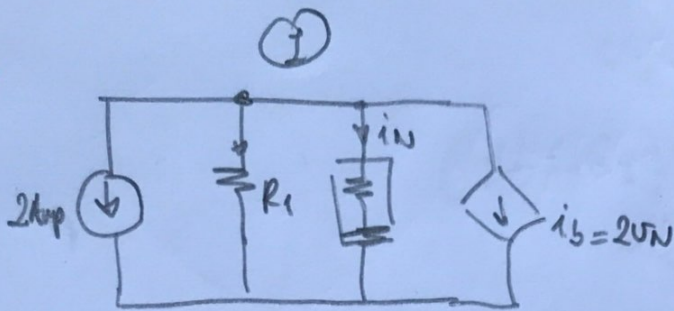

$$\textcircled{1} \rightarrow +2 + i_{R1} + i_N + i_b = 0$$

$$2 + \frac{v_N}{R1} + v_N + 2v_N = 0$$


$$v_N^2 + 3v_N + 2 = 0$$

$$(v_N + 1)(v_N + 2) = 0$$

$$Q_1 = \{ v_N = -1, i_N = 1 \}$$

$$Q_2 = \{ v_N = -2, i_N = 4 \}$$

$\frac{dc}{dt}$

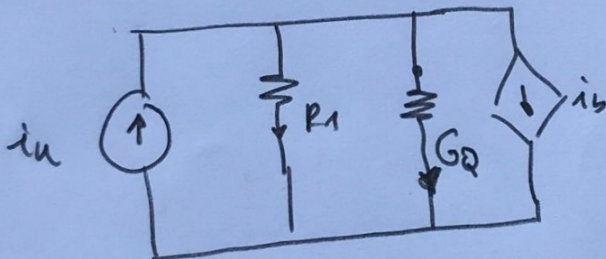

$$G_{Q1} = \frac{2v_N^2}{2v_N} \Big|_{Q1}$$

$$= 2v_N \Big|_{Q1}$$

$$= -2 \text{ S}$$

$$G_{Q2} = 2v_N \Big|_{Q2}$$

$$= -4 \text{ S}$$

Q_1 case

$$-i_u + i_{R1} + i_{G_Q} + i_b = 0$$

$$-i_u + \frac{v_N}{1} + (-2) \cdot v_N + 2v_N = 0$$

$$v_N = 0.1 \text{ Smwt}$$

Q_2 case

$$-i_u + \frac{v_N}{1} + (-4) \cdot v_N + 2v_N = 0$$

$$v_N = -0.1 \text{ Smwt}$$

Q_1 case $v_N = \underline{-1 + 0.1 \text{ Smwt}}$

Q_2 case $v_N = \underline{-2 - 0.1 \text{ Smwt}}$