

Dr. Mustak E. Yalcin

Circuit and System Analysis

Exercise for Week-4

1. The input to the circuit shown in Figure 1 is the current

$$i_s(t) = 80 \cos(250t) \text{ mA.}$$

The steady-state mesh current in the right mesh is

$$i_2 = 66.56 \cos(250t + 33.7^\circ) \text{ mA.}$$

Determine the value of the resistance R .

2. For the circuit of Figure 2, find the value of C required so that $Z = 590 \Omega$ when $f = 1 \text{ MHz}$ ($1 \text{ MHz} = 10^6 \text{ Hz}$).

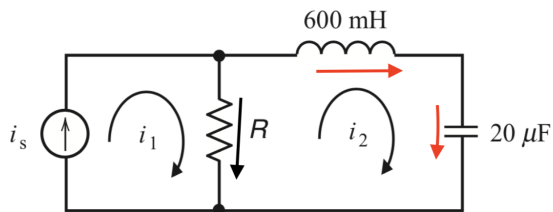


Figure 1

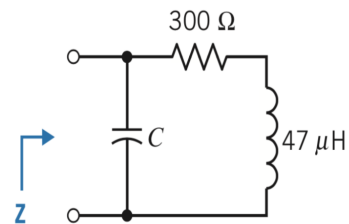


Figure 2