

**Circuit and System Analysis
Homework II**

1)

- Find the y - parameters in s - domain for the circuit given in Figure 1.
- Obtain the Norton equivalent circuit with respect to terminals 2 and 2' while connecting a current source $i_1 = \sin(2t + 30^\circ)$ across the terminals 1 and 1'.
- Let an admittance $Y = -5 + j2$ mho be connected across terminals 2 and 2'. Determine the active, reactive and average powers absorbed by the 2- terminal.

2) Determine the transfer function, I_0/I_1 , for circuit given in Figure 2.

3)

- Find the h - parameters in s - domain for the circuit given in Figure 3.
- When $Z_1 = Z_2 = Z_3 = 1$ and $Z_4 = \frac{1}{s}$, and connecting a resistance, $R = 1\Omega$, across terminals 2 and 2', determine the input impedance, $Z_{11'}(s)$.

4)

- Using the block diagram given in Figure 4.b, obtain a block diagram for the circuit shown in Figure 4.a.
- Reducing the block diagram obtained in part 4-a, find the transfer function, $I_0(s)/I_k(s)$.

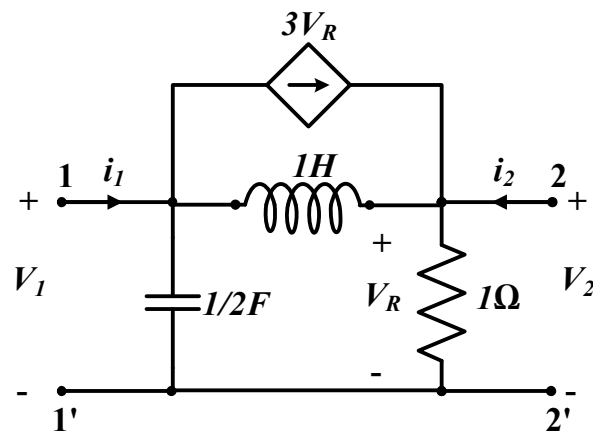


Figure 1

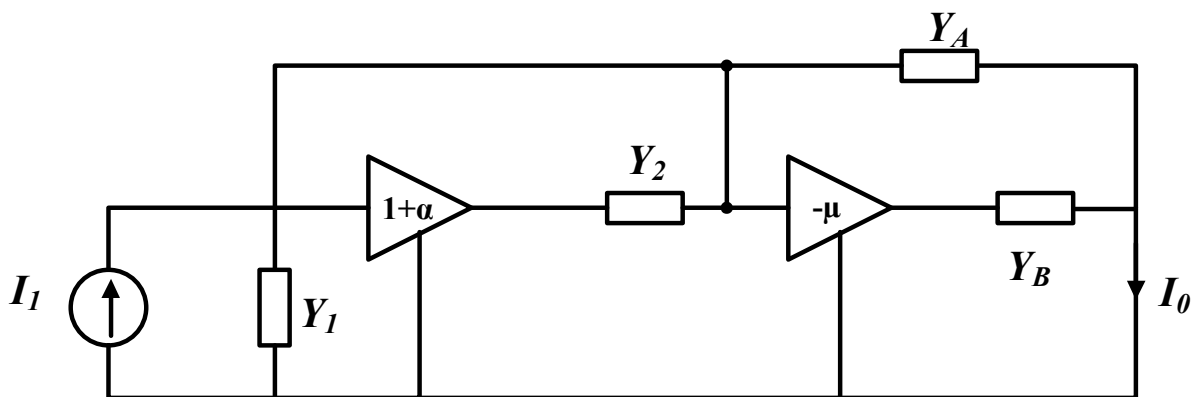


Figure 2

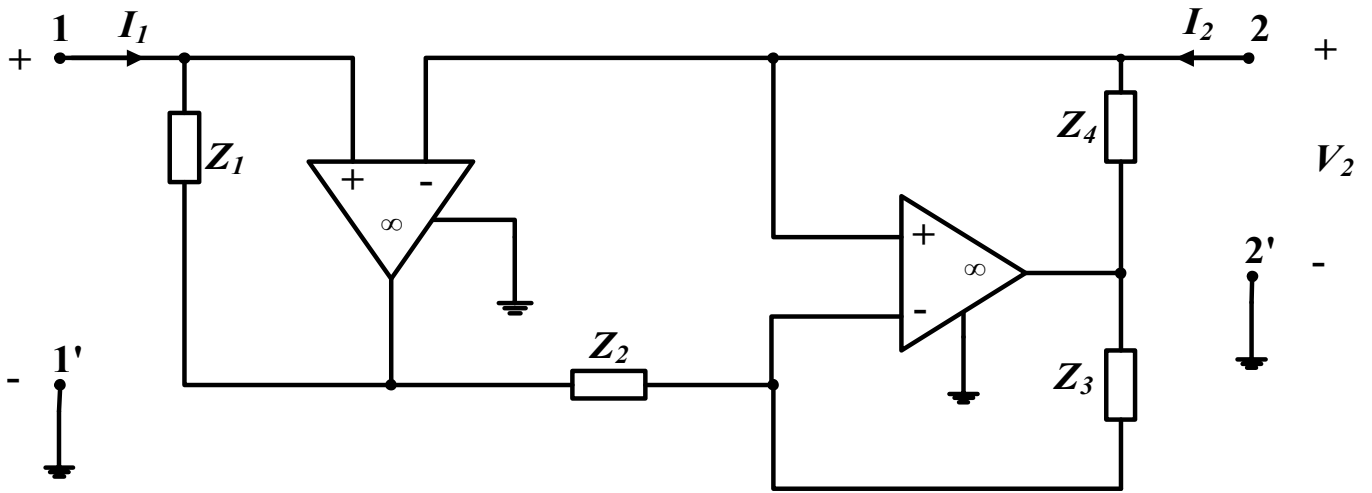


Figure 3

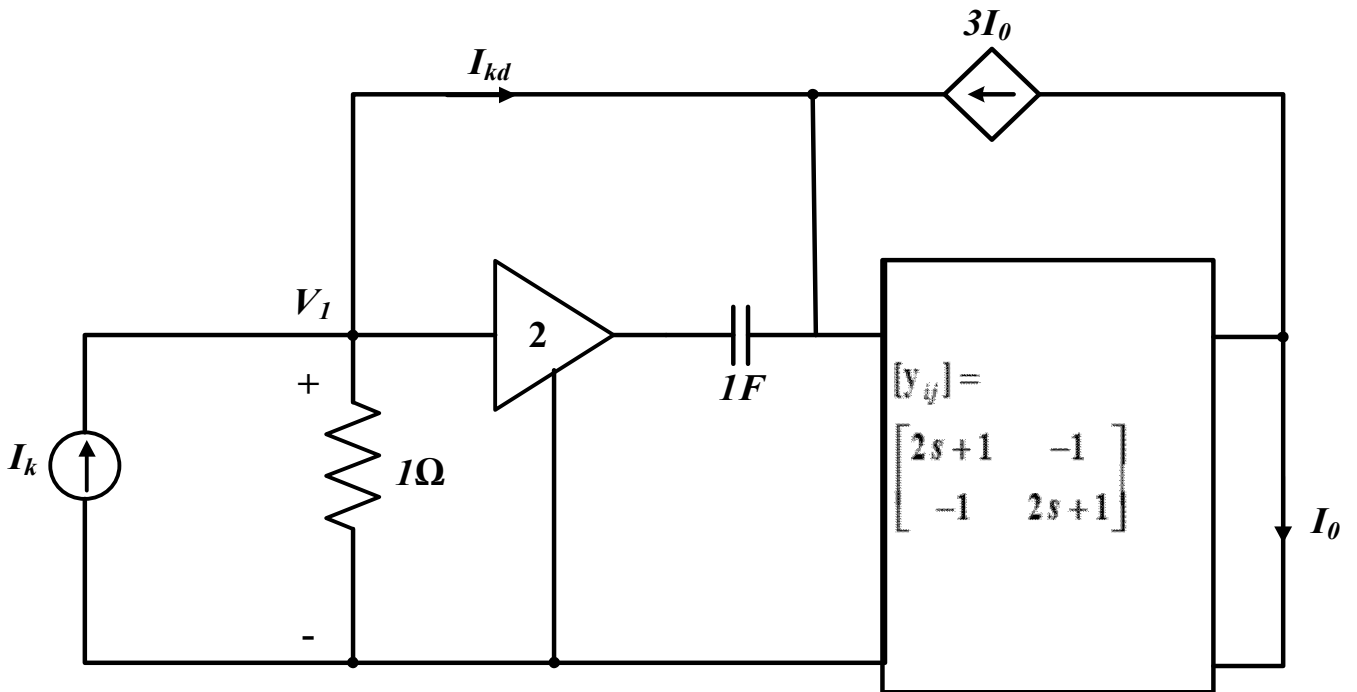


Figure 4.a

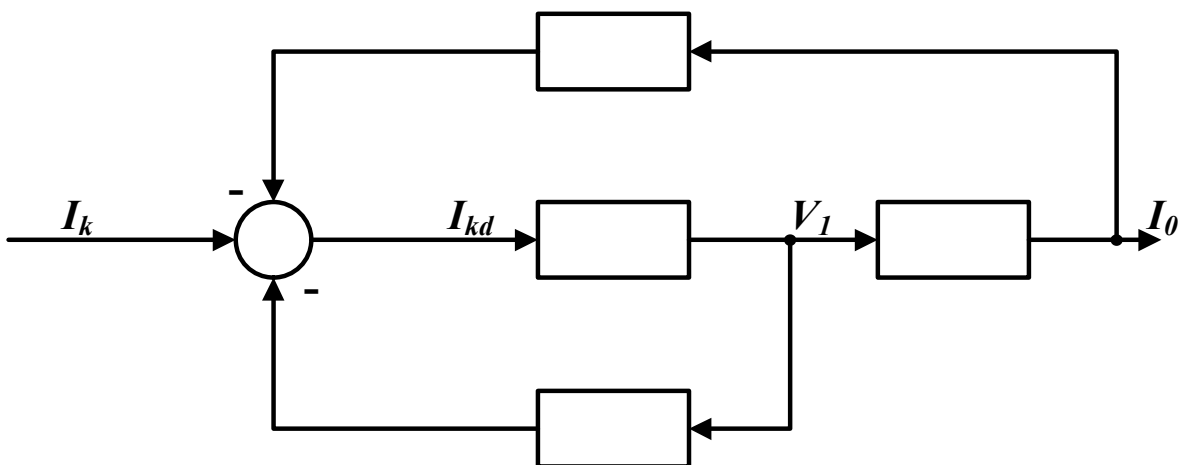


Figure 4.b