

Prof. Dr. H. Hakan Kuntman

ELE509E

Current-Mode Analog Circuit Design

Final Project

Design a current operational amplifier using n-well 0.5 μ m CMOS technology. The circuit symbol of the current operational amplifier is illustrated in Figure 1.



Figure-1

The definition equations are given by

$$\begin{bmatrix} V_{IN+} \\ V_{IN-} \\ I_{O+} \\ I_{O-} \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ K & -K & 0 & 0 \\ -K & K & 0 & 0 \end{bmatrix} \begin{bmatrix} I_{IN+} \\ I_{IN-} \\ V_{O+} \\ V_{O-} \end{bmatrix}$$

where K is the open-loop gain; V_{IN+} , V_{IN-} , I_{IN+} , I_{IN-} are the voltages and currents of the input terminals, V_{O+} , V_{O-} , I_{O+} , I_{O-} denote the voltages and currents of the output terminals. The current operational amplifier to be designed must provide the following properties given in Table 1.

Table 1

Open-loop gain (dB)	> 80
Unity gain bandwidth (MHz)	>50
Input resistance (k. Ohm)	< 1
Output resistance (M. Ohm)	>10
Supply voltages	$\pm 2.5V$

Design a current operational amplifier providing the above mentioned properties with n-well 0.5 μ m CMOS technology.

a- Determine the dimensions and biasing currents of the transistors.

Using SPICE simulations :

b- Plot the DC transfer characteristic of the circuit; $I_{O+} = f(I_{IN+} - I_{IN-})$, $I_{O-} = f(I_{IN+} - I_{IN-})$.

c- Plot the open-loop frequency response the current gain $\{I_{O+}/(I_{IN+} - I_{IN-}), I_{O-}/(I_{IN+} - I_{IN-})\}$ without applying any compensation, determine the poles of the transfer function.

d- Compensate the frequency response to obtain a slope of -20dB/dec. Investigate the stability of the circuit.

- e- Investigate the DC transfer characteristics $V_{O+} = f(I_{IN+}-I_{IN-})$, $V_{O-} = f(I_{IN+}-I_{IN-})$ for several load resistance values,
- f- Investigate the frequency response of input and output impedances.
- h- Summarize the performance parameters of the current operational amplifier in a Table.
- i- Evaluate your design and your results.

Explanations: The current operational amplifier can be realized by the use of the blocks illustrated in Figure 2. (DO-CCII structure designed in a previous homework can be also used for the output stage).

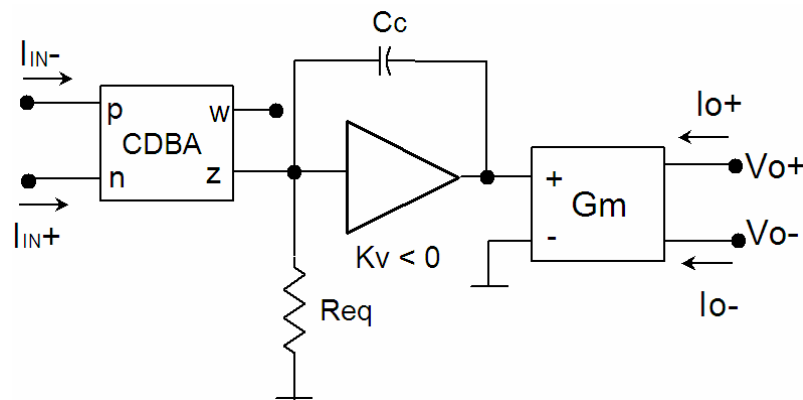


Figure-2

References:

- [1] G. Palmisano, G. Palumbo and S. Pennisi, CMOS Current Amplifiers, Sec. 1., pp. 1-44, Kluwer Academic Publishers, 1999.
- [2] A.T. Bekri, Current Mode Amplifiers, Current Operational Amplifiers (Seminar Notes for ELE509E: Current-Mode Analog Circuit Design, İstanbul Technical University, 2004.
- [2] I. Myderrizi, Cascadable Current Mode Multipurpose Filters Employing Current Differencing Amplifier (CDBA), Seminar Notes for ELE509E: Current-Mode Analog Circuit Design, İstanbul Technical University, 17. 12.2004.
- [4] N. Tarım, H. Kuntman, "A High Performance Current Differencing Buffered Amplifier", Proceedings of the 13th International Conference on Microelectronics (ICM'2001), pp.153-156, Rabat, Morocco, October 29-31, 2001.
- [5] U. Çam and H. Kuntman, A new CMOS realisation of four terminal floating nullor (FTFN), International Journal of Electronics, Vol. 87, No.7, pp 809-817, 2000.
- [6] S. Kılınc, U. Çam, Current-Mode Oscillator Configuration Using Single Current Operational Amplifier, ELECO 2003: Third International Conference on Electrical and Electronics Engineering, pp.107-111, Dec., 2003, Bursa, Turkey
- [7] Acar C., Özoğuz S., "A new versatile building block: current differencing amplifier suitable for analog signal-processing filters". Microelectronics Journal 30 (1999) 157-160