

# ELE509E

## Current-Mode Analog Circuit Design

### Homework 1 (24.10.2003)

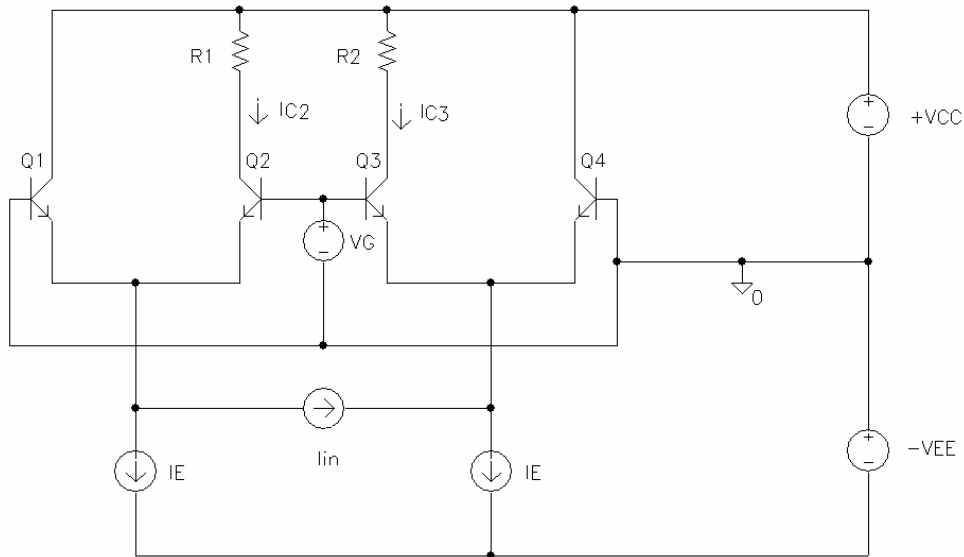


Figure 1

The current gain of the AGC circuit illustrated in Figure 1 is related to the control voltage  $V_G$  as

$$\frac{I_{out}}{I_{in}} = \frac{\exp\left(\frac{V_G}{V_T}\right)}{\exp\left(\frac{V_G}{V_T}\right) + 1} \quad (1)$$

Choose appropriate values for the biasing currents  $I_E$ , supply voltages  $+V_{CC}$ ,  $-V_{EE}$  and load resistors  $R_1$ ,  $R_2$ .

Using SPICE simulation results

- prove Eqn.1 comparing SPICE simulations with theoretical values calculated from (1).
- draw the plots of  $I_{C2}$ ,  $I_{C3}$  against  $I_{in}$  taking the control voltage  $V_G$  as parameter,
- specify the limits of the input current  $I_{in}$ ,
- specify the limits of the control voltage  $V_G$ ,
- draw the frequency response of the current gain and determine the bandwidth of the amplifier taking the control voltage  $V_G$  as parameter.
- Give a detailed evaluation of your results.