

ELE509E

Current-Mode Analog Circuit Design

Homework 4 (12.12.2003)

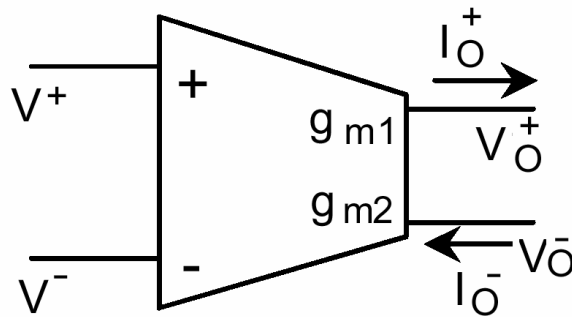


Figure 1. Circuit symbol of dual output transconductor

Design a CMOS dual output transconductor (DO-OTA) with inverting and noninverting outputs. The circuit will be operated in the frequency range of several MHz and used for analog signal processing. The circuit will provide

1. the transconductances $g_{m1} = g_{m2} = 50\mu\text{A/V}$,
2. output terminal resistances $R_{O1}, R_{O2} > 10 \text{ M}\Omega$,

The supply voltages are given as $V_{DD} = 2.5\text{V}$, $-V_{SS} = -2.5\text{V}$. The model parameters of the MOS transistors are given in Table 1.

- a) Specify the CMOS DO-OTA structure, determine transistor dimensions.

Using SPICE simulation results

- b) draw the plots of I_o^+ and I_o^- against V_{IN} (the outputs are short-circuited to the ground, V_{IN} is defined as $V_{IN} = V^+ - V^-$),
- c) specify the limits of the operation region, the limits of the output currents.
- d) draw the frequency response of the transconductances and determine the bandwidth,
- e) draw the plots of V_o^+ and V_o^- against V_{IN} (the outputs are open-circuited),
- f) specify the limits of the operation region, the limits of the output voltages,
- g) draw the frequency response of the voltage gain and determine the bandwidth,
- h) draw the plot of the terminal impedances against the frequency,
- i) investigate the large signal behaviour of the DO-OTA by applying to the input a sinusoidal voltage and observing the total harmonic distortion THD at the outputs

- for different input levels; draw the plot of THD against v_{in} for each output terminal. (Connect adequate load resistances to the output terminals.)
- j) Investigate the dependence of the transconductances on the biasing current. Draw the plots of g_{m1} and g_{m2} against biasing current.
 - k) Give a detailed evaluation of your results.

Table 1. Transistor parameters of 0.5 μ m CMOS process

```
.MODEL NT NMOS LEVEL=3
+UO=460.5 TOX=1.0E-8 TPG=1 VTO=.62 JS=1.8E-6 XJ=.15E-6 RS=417 RSH=2.73
LD=0.04E-6 ETA=0 +VMAX=130E3 NSUB=1.71E17 PB=.761 PHI=0.905
THETA=0.129 GAMMA=0.69 KAPPA=0.1 AF=1 +WD=.11E-6 CJ=76.4E-5 MJ=0.357
CJSW=5.68E-10 MJSW=.302 CGSO=1.38E-10 CGDO=1.38E-10 +CGBO=3.45E-10
KF=3.07E-28 DELTA=0.42 NFS=1.2E11

.MODEL PT PMOS LEVEL=3
+UO=100 TOX=1E-8 TPG=1 VTO=-.58 JS=.38E-6 XJ=0.1E-6 RS=886 RSH=1.81
LD=0.03E-6 ETA=0 +VMAX=113E3 NSUB=2.08E17 PB=.911 PHI=0.905
THETA=0.120 GAMMA=0.76 KAPPA=2 AF=1 +WD=.14E-6 CJ=85E-5 MJ=0.429
CJSW=4.67E-10 MJSW=.631 CGSO=1.38E-10 CGDO=1.38E-10 +CGBO=3.45E-10
KF=1.08E-29 DELTA=0.81 NFS=0.52E11
```