

ELE509E
Current-Mode Analog Circuit Design
Homework 1 (22.10.2004)

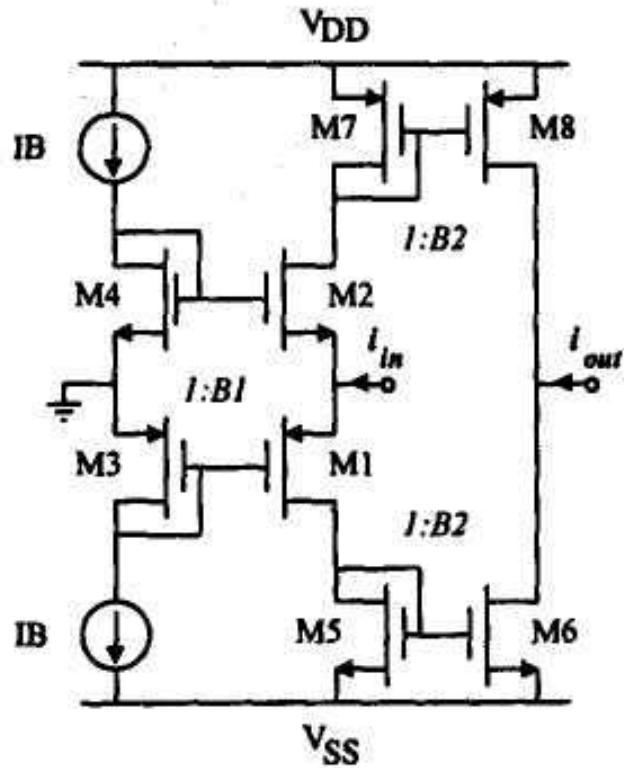


Figure 1

A CMOS current amplifier is shown in Figure 1. The supply voltages and the biasing currents are given as $V_{DD} = 2.5V$, $-V_{SS} = -2.5V$, $I_B = 50\mu A$. The dimensions for M1, M2, M3 and M4 are illustrated in Table 1 and the model parameters of the MOS transistors are given in Table 2.

- Realize the current sources I_B providing a biasing current of $50\mu A$, determine the transistor dimensions.
- Determine the dimensions for M5, M6, M7 and M8 to provide a current gain of 3.

Using SPICE simulation results

- draw the plot of I_{OUT} against I_{IN} ,
- specify the limits of the input current I_{IN} and the output current I_{OUT} ,
- draw the frequency response of the current gain and determine the bandwidth of the amplifier,
- draw the plot of the input impedance against the frequency,

- g) draw the plot of the output impedance against the frequency,
- h) investigate the large signal behaviour of the amplifier by applying a sinusoidal input current in the passband of the amplifier and observing the total harmonic distortion THD at the output for different input levels; draw the plot of THD against i_{in} ,
- i) investigate the dependence of the output voltage upon the load resistance R_L keeping the input level constant, observe the harmonic distortion THD at the output for each load resistance value; draw the plot of V_O against R_L ,
- j) Give a detailed evaluation of your results.

Table 1. Transistor dimensions

Transistor	L [μm]	W [μm]
M1	1	10
M2	1	10
M3	1	10
M4	1	10

Table 2. Transistor parameters of 0.5 μm CMOS process

```
.MODEL NT NMOS LEVEL=3
+UO=460.5 TOX=1.0E-8 TPG=1 VTO=.62 JS=1.8E-6 XJ=.15E-6 RS=417 RSH=2.73
LD=0.04E-6 ETA=0 +VMAX=130E3 NSUB=1.71E17 PB=.761 PHI=0.905
THETA=0.129 GAMMA=0.69 KAPPA=0.1 AF=1 +WD=.11E-6 CJ=76.4E-5 MJ=0.357
CJSW=5.68E-10 MJSW=.302 CGSO=1.38E-10 CGDO=1.38E-10 +CGBO=3.45E-10
KF=3.07E-28 DELTA=0.42 NFS=1.2E11

.MODEL PT PMOS LEVEL=3
+UO=100 TOX=1E-8 TPG=1 VTO=-.58 JS=.38E-6 XJ=0.1E-6 RS=886 RSH=1.81
LD=0.03E-6 ETA=0 +VMAX=113E3 NSUB=2.08E17 PB=.911 PHI=0.905
THETA=0.120 GAMMA=0.76 KAPPA=2 AF=1 +WD=.14E-6 CJ=85E-5 MJ=0.429
CJSW=4.67E-10 MJSW=.631 CGSO=1.38E-10 CGDO=1.38E-10 +CGBO=3.45E-10
KF=1.08E-29 DELTA=0.81 NFS=0.52E11
```