

ELE509E
Current-Mode Analog Circuit Design
Homework 2 (19.11.2004)

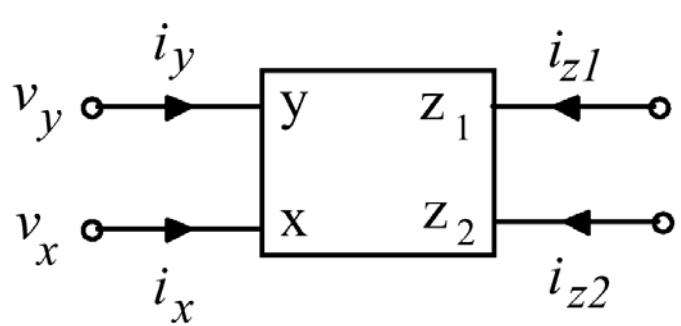


Figure 1. Circuit symbol of DOCCII.

A dual output current conveyor (DOCCII) is described by

$$\begin{bmatrix} V_X \\ I_Y \\ I_{Z1} \\ I_{Z2} \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ k & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_X \\ V_Y \\ V_{Z1} \\ V_{Z2} \end{bmatrix}$$

$k = \pm 1$. For $k = 1$ a DOCCII with two noninverting Z outputs is obtained. For $k = -1$ the Z_2 terminal yields an inverted output signal.

Design a CMOS dual output current conveyor with inverting and noninverting outputs..

1. Terminal output resistances $R_{Z1}, R_{Z2}, R_Y > 10 \text{ M.Ohms}, R_X < 10 \text{ Ohms}$.
2. Voltage tracking error $\epsilon_V < 0.1\%$, current tracking error $\epsilon_I < 0.1\%$,
3. BW of the voltage gain ($A_V = v_x/v_y$) $f_{V3db} > 10 \text{ MHz}$,
4. BW of the current gain ($A_{I1} = i_{z1}/i_x, A_{I2} = i_{z2}/i_x$) $f_{I3db} > 50 \text{ MHz}$,

The supply voltages are given as $V_{DD} = 2.5V, -V_{SS} = -2.5V$. The model parameters of the MOS transistors are given in Table 1.

a - Specify the CMOS DOCCII structure, determine transistor dimensions.

Using SPICE simulation results

- a) draw the plots of V_X against V_Y, I_{Z1} and I_{Z2} against I_X ,
- b) specify the limits of the operation region,

- c) draw the frequency response of the voltage gain and determine the bandwidth,
- d) draw the frequency response of the current gain and determine the bandwidth,
- e) draw the plot of the terminal impedances against the frequency,
- f) investigate the large signal behaviour of the DOCCII by applying to Y terminal a sinusoidal input voltage in the passband and observing the total harmonic distortion THD at the X, Z1 and Z2 terminals for different input levels; draw the plot of THD against i_{in} for each terminal. (Connect adequate load resistances to the X, Z1 and Z2 terminals.
- g) Give a detailed evaluation of your results.

Table 1. Transistor parameters of 0.5μm CMOS process

```

.MODEL NT NMOS LEVEL=3
+UO=460.5 TOX=1.0E-8 TPG=1 VTO=.62 JS=1.8E-6 XJ=.15E-6 RS=417 RSH=2.73
LD=0.04E-6 ETA=0 +VMAX=130E3 NSUB=1.71E17 PB=.761 PHI=0.905
THETA=0.129 GAMMA=0.69 KAPPA=0.1 AF=1 +WD=.11E-6 CJ=76.4E-5 MJ=0.357
CJSW=5.68E-10 MJSW=.302 CGSO=1.38E-10 CGDO=1.38E-10 +CGBO=3.45E-10
KF=3.07E-28 DELTA=0.42 NFS=1.2E11

.MODEL PT PMOS LEVEL=3
+UO=100 TOX=1E-8 TPG=1 VTO=-.58 JS=.38E-6 XJ=0.1E-6 RS=886 RSH=1.81
LD=0.03E-6 ETA=0 +VMAX=113E3 NSUB=2.08E17 PB=.911 PHI=0.905
THETA=0.120 GAMMA=0.76 KAPPA=2 AF=1 +WD=.14E-6 CJ=85E-5 MJ=0.429
CJSW=4.67E-10 MJSW=.631 CGSO=1.38E-10 CGDO=1.38E-10 +CGBO=3.45E-10
KF=1.08E-29 DELTA=0.81 NFS=0.52E11

```