

## INDUSTRIAL APPLICATIONS OF POWER ELECTRONICS

2012 – 2013 FALL

MIDTERM EXAM


## QUESTIONS

1. Some concepts which are related with SMPS circuits are given. Briefly explain “PWM”, “duty cycle”, “switching frequency”, “CCM”, “DCM”, “output voltage ripple” and “inductor volt-second balance”.
2. What is magnetically coupled SMPS? What is the purpose of these circuits? Briefly explain the magnetizing inductor phenomena and indicate the importance of magnetizing inductor for a flyback converter.
3. Sketch the circuit schema of the boost converter and explain the operation principle. Sketch sub-circuits for CCM operation, and develop the expressions for voltage conversion ratio, peak inductor current and average switch current.
4. Boost converter is convenient for photovoltaic applications. A resistive load of  $15\Omega$  is supplied by a CCM operating boost converter whose input source is a photovoltaic module with 45V and 5A. Switching frequency of the converter is 75kHz.
  - a. Assuming the ideal conditions, calculate the power this converter.
  - b. Calculate the output voltage and required duty cycle.
  - c. Calculate the inductor value for 0,25A peak-to-peak inductor current.
  - d. Plot the capacitor current and find the output voltage ripple for 150 $\mu$ F capacitor value.
5. An electronic circuit which operates at 5V and draws a current of 10A is supplied by a 12V battery through a buck converter. The converter is wanted to be operate at DCM. Switching frequency of the converter is given as 35kHz.
  - a. What is the critical inductor value for this converter?
  - b. Select an inductor value and calculate duty cycle.
  - c. Plot the capacitor current and calculate the capacitor value to obtain  $\Delta v_o = 0,025V$ .
6. A forward converter with tertiary winding is supplied by 20V source and a  $10\Omega$  resistive load is given. Turns ratio of the transformer is  $N_1/N_2/N_3 = 3/13/1$ . Magnetizing inductor is 10mH.
  - a. Sketch the principal circuit schema and indicate the importance of magnetizing inductor and the tertiary winding.
  - b. What is the maximum duty cycle of this converter? Find the output voltage for  $D_{max}$ .
  - c. Calculate the maximum and minimum filter inductor current for  $L = 330\mu H$ .
  - d. Plot the magnetizing inductor current and input current of the converter.

**GOOD LUCK !**


# IAPE Midterm Exam Solution (23.11.2012)

3)

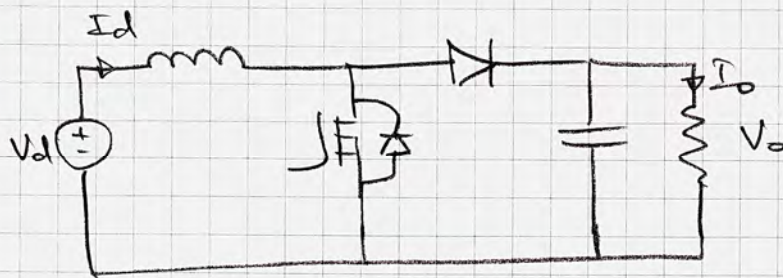


Mosfet ON  $\rightarrow$  inductor stores energy, capacitor feeds the load.  
 Mosfet OFF  $\rightarrow$  stored energy is transferred to output.

Sub-circuit 1  
 $D \cdot T_s$

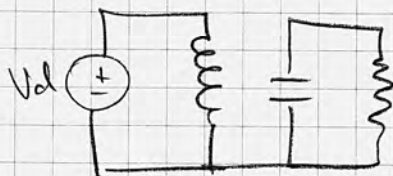

Sub-circuit 2,  
 $(1-D) T_s$

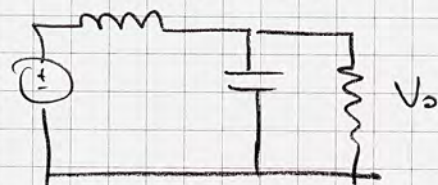

Applying IVSB (inductor Volt second Balance)

$$V_d \cdot D \cdot T_s + (V_d - V_o) (1-D) T_s = 0$$

$$V_d D + V_d + V_o D - V_d \cdot D - V_o = 0.$$

$$\frac{V_o}{V_d} = \frac{1}{1-D}.$$


Average inductor current is  $I_L = I_d$

$$I_{L, \max} = I_d + \frac{\Delta I_L}{2} = I_d + \frac{V_d D}{2L f_s}$$

$$I_{L, \min} = I_d - \frac{\Delta I_L}{2} = I_d - \frac{V_d D}{2L f_s}$$

$$\Delta I_L = \frac{V_d}{L} \cdot D \cdot T_s$$

Average switch current

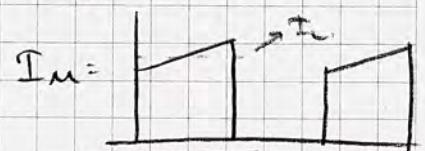

$$I_m = I_L \cdot D = I_d \cdot D.$$



4) PV supplies 45V @ 5A.


a)  $P_{in} = P_o = 45 \cdot 5 = 225 \text{ W}$

b)  $R = 15 \Omega$      $P_o = \frac{V_o^2}{R} \Rightarrow V_o = \sqrt{P_o \cdot R} = 58,1 \text{ V.}$

$$\frac{V_o}{V_d} = \frac{1}{1-D} \Rightarrow D = 1 - \frac{V_d}{V_o} = 1 - \frac{45}{58,1} = 0,225$$

c)  $\Delta i_L = 0,25$      $\Delta i_L = \frac{V_d \cdot D}{L \cdot f_s} \Rightarrow L = \frac{V_d \cdot D}{\Delta i_L \cdot f_s} = \frac{45 \cdot 0,225}{0,25 \cdot 75000} = 540 \mu\text{H.}$

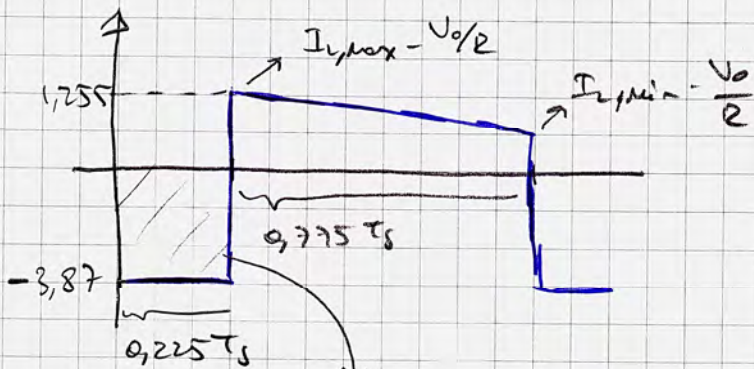d) Subcircuit 1  $\rightarrow i_c = -V_o/R$   
Subcircuit 2  $\rightarrow i_c = i_L - V_o/R.$



$$\Delta Q = i_c \cdot \Delta t = \frac{3,87 \cdot 0,225}{75000} = 11,61 \mu\text{C}$$

$$C = \frac{\Delta Q}{\Delta V_o} \Rightarrow \Delta V_o = \frac{\Delta Q}{C} = \frac{11,61 \mu\text{C}}{150 \mu\text{F}} = 0,077 \text{ V} = 77 \text{ mV.}$$



5) Electronic Load  $5V @ 10A \Rightarrow R = 0,5$

Buck Converter is used; (DCM operation)

a)  $L_{crit} = \frac{R(1-D)}{2f_s}$   $D = V_o/V_d = 5/12 = 0,417$

$$= \frac{0,5(1-0,417)}{2 \cdot 35000} = 4,17 \mu H$$

b)  $L$  must be selected less than  $L_{crit}$  for DCM operation;

$L = 3 \mu H$  (selected)

$$K = \frac{2Lf_s}{R} = \frac{2 \cdot 3 \mu \cdot 35000}{0,5} = 0,42$$


$$D = \sqrt{\frac{K}{\left(\frac{V_d}{V_o}\right)\left(\frac{V_d}{V_o}-1\right)}} = \sqrt{\frac{0,42}{\left(\frac{12}{5}\right)\left(\frac{12}{5}-1\right)}} = 0,354$$

$$\Delta_1 = \frac{D}{2} \left( \sqrt{1 + \frac{4K}{D^2}} - 1 \right) = 0,495$$

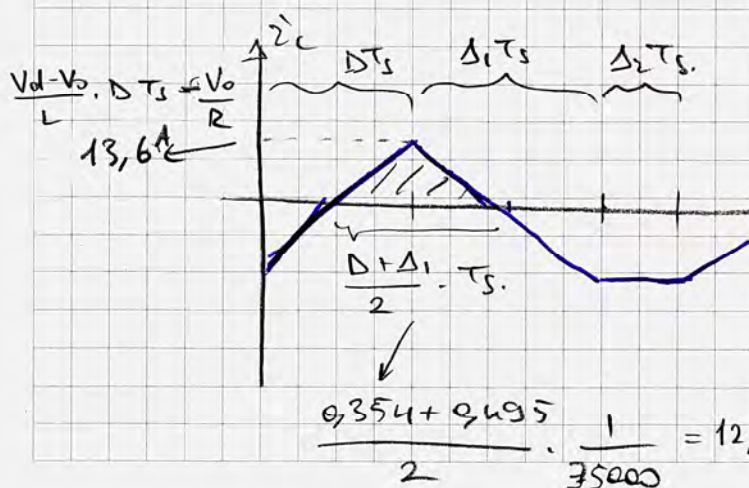c) Sub-circuit 1  $\rightarrow \dot{i}_c = \dot{i}_L - V_o/R$

Sub-circuit 2  $\rightarrow \dot{i}_c = \dot{i}_L - V_o/R$

Sub-circuit 3  $\rightarrow \dot{i}_c = -V_o/R$




only positive or negative sections are calculated, in this waveform it is easier to calculate positive part.

$$\Delta Q = \frac{12,13 \mu \cdot 13,6}{2} = 82,484 \mu C$$

$$C = \frac{\Delta Q}{\Delta V_o} = \frac{82,484 \mu}{0,025} = 3,3 mF$$



6) a)

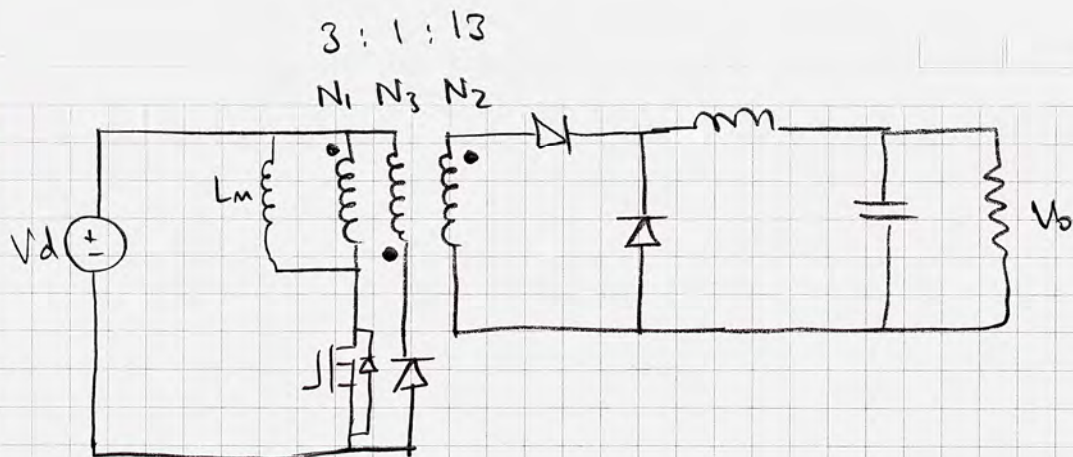

b) 
$$D_{max} = \frac{N_1}{N_1 + N_3} = \frac{3}{3+1} = \frac{3}{4} = 0,75$$


This duty cycle can't be greater than 0,75 because this is the limit time for resetting the  $L_m$  (magnetizing inductor)

$$V_o = V_d \cdot \frac{N_2}{N_1} \cdot D = 20 \cdot \frac{13}{3} \cdot 0,75 = 65V.$$

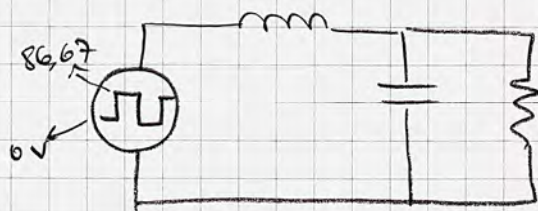c) For this part, forget about the input side; output side of a power converter is a "Buck Converter"

MOSFET is ON  $\rightarrow$  reflected secondary voltage =  $\frac{20}{3} \cdot 13 = 86,67V$

MOSFET is OFF  $\rightarrow$  " " " = 0V.



$$\langle i_L \rangle = I_L = \frac{V_o}{R} = \frac{65}{10} = 6,5A,$$

$$\Delta i_L = \frac{(86,67 - 65)}{L} \cdot D \cdot T_s = \frac{21,67}{400\mu} \cdot 0,75 \cdot \frac{1}{150000} = 0,27A,$$

$$I_{L,max} = 6,5 + \frac{0,27}{2} = 6,635A.$$


$$I_{L,min} = 6,5 - \frac{0,27}{2} = 6,365A.$$



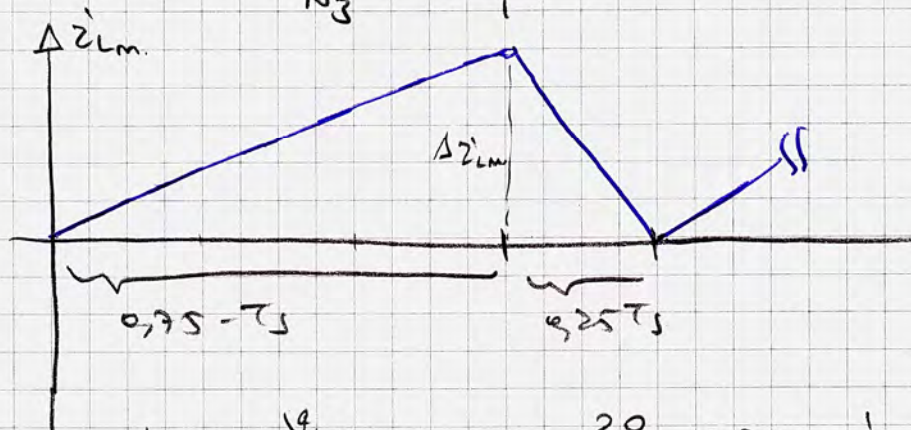d) For regenerating inductor;

$$V_{LM} = 20V \quad (\text{MOSFET is ON})$$

$$V_{LM} = -V_d \cdot \frac{N_1}{N_3} = -\frac{20 \cdot 3}{1} = -60V \quad (\text{MOSFET is OFF})$$



$$\Delta i_{LM} = \frac{V_{LM}}{L} \cdot D \cdot T_s = \frac{20}{10m} \cdot 0.75 \cdot \frac{1}{150000} = 0.01A.$$