

① Single phase half-wave uncontrolled rectifier with cap. filter

An electronic load operates from a linear regulator with 15V. Load resistor value is 3Ω . Linear regulator must be supplied by a 1 ϕ half-wave uncontrolled rectifier ^{with cap. filter} and output voltage of the rectifier must have a minimum average value of 20V with $\Delta V_{PP} = 2V$. Utility voltage is $220V \pm 5\%$.

① * Sketch the complete circuit diagram.



② suggest a transformer ratio? for the worst case of utility voltage?

$$220 \cdot (0.95) = 209V$$

$$V_{o,max} = 21V$$


$$V_{ac,max} = 209 \cdot \sqrt{2} = 295V$$

$$\frac{V_{ac,max}}{V_{o,max}} = \frac{n_1}{1} = \frac{295}{21} \approx 14$$

* For the minimum utility voltage, calculate the required cap. value.

for output voltage $\rightarrow V_{o,min} = 19V$. $\Delta V_{pp} = 2V$.
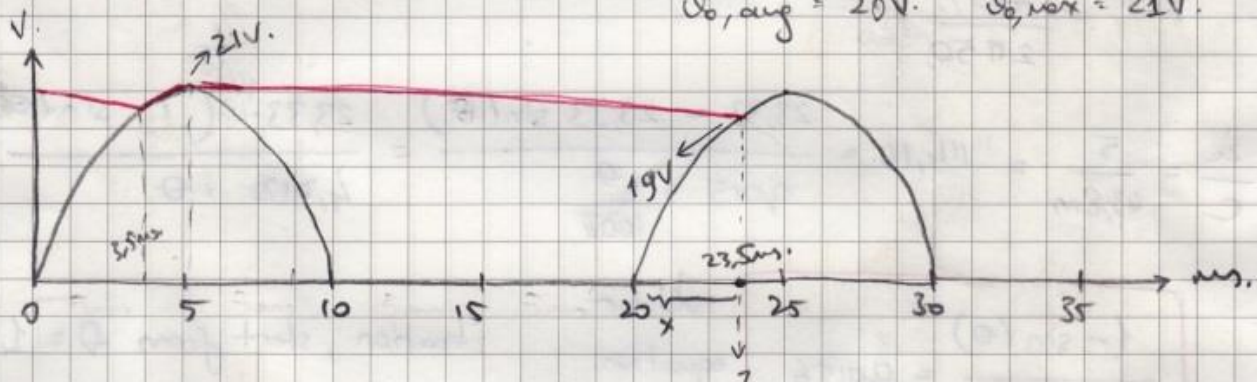
$$V_{o,avg} = 20V \quad V_{o,max} = 21V$$



$$V_s = V_{ac} \cdot \sin(\omega t) = \frac{1}{\sqrt{2}} = \frac{220 \cdot 0.95 \cdot \sqrt{2}}{\sqrt{2}} \cdot \sin(\omega t) = 21.11 \sin(\omega t)$$

$$21.11 \sin(\omega t) = 19$$

$$\sin(\omega t) = 0.89$$

$$\omega t \approx 63^\circ \approx 3.5ms \approx 1.1rad$$

capacitor voltage decreases linearly and supplies output current itself.

$$I_o = 15/3 = 5A$$

(21,11-19)

capacitor eq.

$$i_c = C \cdot \frac{dV_c}{dt}$$

5A $\rightarrow (0,015 + 0,0035)$

$$C = \frac{5 \cdot (0,0185)}{2,11} = 43,8 \text{ mF.}$$

* diode conduction angle/time $\rightarrow 1,5 \text{ ms} / 27^\circ$ cap. " " $\rightarrow 18,5 \text{ ms} / 333^\circ$ * calculate and sketch output voltage for $220\text{V} + 5\%$.

$$V_{o,\max} = V_{ac,\max} \cdot \frac{1}{14} = \frac{220 \cdot 1,05 \cdot \sqrt{2}}{14} = 23,33 \text{ V.}$$

$$i_c = C \cdot \frac{dV_c}{dt}$$

known $\rightarrow$ unknown

$$\frac{dV_c}{dt} = \frac{V_{o,\max} - V_{o,\min}}{15 \text{ ms} + x}$$

known $= 23,33 \text{ V.}$
these two are related!

$$23,33 \sin(\omega t) = V_{o,\min} \quad \omega t = \theta$$

$$x = \frac{\theta}{2\pi 50}$$

$$\frac{i_c}{C} = \frac{5}{43,8 \text{ m}} = 114,16 = \frac{23,33 - 23,33 \sin(\theta)}{0,015 + \frac{\theta}{100\pi}} = \frac{23,33 \cdot 100\pi \cdot (1 - \sin(\theta))}{4,712 + \theta}$$

$$\frac{1 - \sin(\theta)}{4,712 + \theta} = 0,0156 \quad \text{nonlinear equation.}$$

iteration, start from $\theta = 1,1 \text{ rad}$

first $\frac{1 - \sin(1,1 \text{ rad})}{4,712 + 1,1} = 0,0187$

$$0,0187 > 0,0156 \rightarrow \theta = 1,2 \text{ rad}$$

second $\frac{1 - \sin(1,2)}{4,712 + 1,2} = 0,0115$

$$0,0115 < 0,0156 \rightarrow \theta = 1,15 \text{ rad.}$$

third $\frac{1 - \sin(1,15)}{4,712 + 1,15} = 0,0149$

$$0,0149 < 0,0156 \rightarrow \theta = 1,14 \text{ rad.}$$

$$\text{last} \rightarrow 0,0156 \quad \theta = 1,14 \text{ rad.}$$

$$\theta = 1,14 \text{ rad} = 65,32^\circ = 3,63 \text{ ms.}$$


$$V_{o, \min} = 23,33 \sin(1,14 \text{ rad}) = 21,19 \text{ V.}$$

$$\Delta V_o = 23,33 - 21,19 = 2,14 \text{ V.}$$

$$V_{o, \text{avg}} = \frac{23,33 + 21,19}{2} = 22,26 \text{ V.}$$

★ Single Phase full-wave uncontrolled rectifier w/out cap. filter

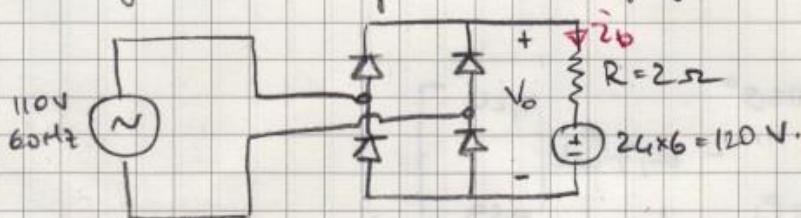
A utility voltage of 110 V_{ac} ^{160 Hz} supplies and charges a battery ^{(24V x 6 series) ramp} through a full wave rectifier w/out cap. filter and 2Ω current limiting resistor.



★ if all diodes have $0,7 \text{ V}$ threshold voltages find the conduction angles.

2 diodes conducting

$$120 + 2 \cdot 0,7 = 121,4 \text{ V.}$$

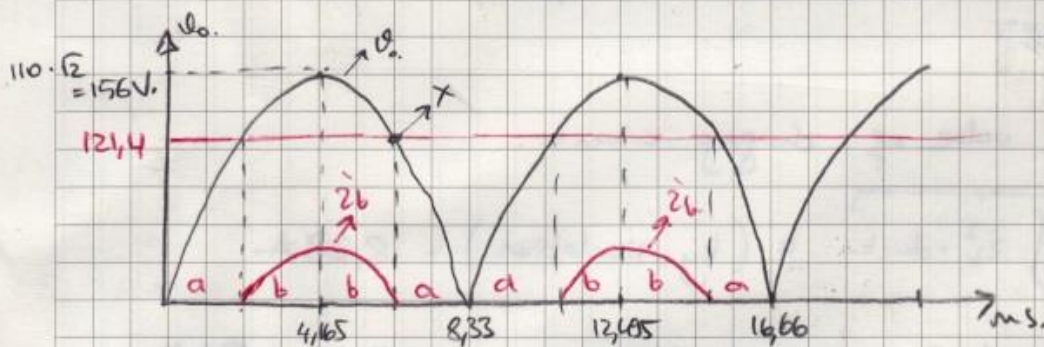

$$V_o = 156 \cdot \sin(\omega t) = 121,4 \text{ V} \Rightarrow \omega t = 51,1^\circ = 0,89 \text{ rad.} = 2,37 \text{ ms.}$$

$$a = 2,37 \text{ ms}$$

$$b = 1,795 \text{ ms.}$$

$$x = 2b + a = 5,96 \text{ ms.}$$

charging occurs $\rightarrow$ 2,37 ms to 5,96 ms

$$51,1^\circ \text{ to } 128,9^\circ$$

$$0,89 \text{ rad to } 2,24 \text{ rad.}$$

* plot the charging current and calculate the average value.

$$i_b = \frac{156 \sin(\omega t) - 121,4}{2} = 78 \sin(\omega t) - 60,7$$

conducts from $51,1^\circ$ to $128,9^\circ$.

$$\begin{aligned} \langle i_b \rangle &= \frac{2}{T} \int_{51,1^\circ (0,89 \text{ rad})}^{128,9^\circ (2,24 \text{ rad})} (78 \sin(\omega t) - 60,7) d\omega t \\ &= \frac{1}{\pi} \int_{51,1^\circ (0,89 \text{ rad})}^{128,9^\circ (2,24 \text{ rad})} (78 \sin(\omega t) \cdot d\omega t - 60,7 \cdot d\omega t) \end{aligned}$$

$$\begin{aligned} &= \frac{1}{\pi} \left[(78 (-\cos \omega t)) \Big|_{51,1^\circ}^{128,9^\circ} - 60,7 \omega t \Big|_{0,89}^{2,24} \right] \\ &= \frac{48,98 + 48,98 - 135,97 + 54,02}{\pi} = 5,15 \text{ A.} \end{aligned}$$

* calculate the rms value of charging current.

$$i_{b,rms} = \sqrt{\frac{1}{T} \int i_b^2 \cdot d\omega t} = (\text{by simulation}) = 8,29 \text{ A.}$$

* find the time required to charge battery from 100Ah to 160Ah.

$$160 - 100 = 60 \text{ Ah.}$$

$$\langle i_b \rangle = I_b \text{ into battery}$$

$$\frac{60 \text{ Ah}}{5,1 \text{ A}} = 11,76 \text{ h} = 11 \text{ hours } 45 \text{ minutes.}$$

* calculate the charging resistor loss, diode losses and complete efficiency?

$$P_{\text{diode}} = 2,55 \cdot 0,7 \cdot 4 = 7,14 \text{ W}$$

for one diode $\frac{\langle i_b \rangle}{2}$ is flowing = 2,55 A.

$$P_R = i_{b,\text{rms}}^2 \cdot R = 8,29^2 \cdot 2 = 137,45 \text{ W}$$

$$P_{\text{batt}} = 120 \cdot 5,1 = 612 \text{ W.}$$

$$\text{efficiency} = \frac{P_{\text{batt}}}{P_{\text{batt}} + P_R + P_{\text{diode}}} = \frac{612}{612 + 137,45 + 7,14} = 80,89\%$$