

3 PHASE RECTIFIERS

UNCONTROLLED

RESISTIVE
INDUCTIVE

CONTROLLED


RESISTIVE

THIS DOCUMENT IS WRITTEN BY
RES. ASST. FURKAN BAŞKURT

BASKURTF@ITU.EDU.TR
[HTTP://WEB.ITU.EDU.TR/BASKURTF](http://web.itu.edu.tr/baskurtf)

3 PHASE RECTIFIERS

UNCONTROLLED

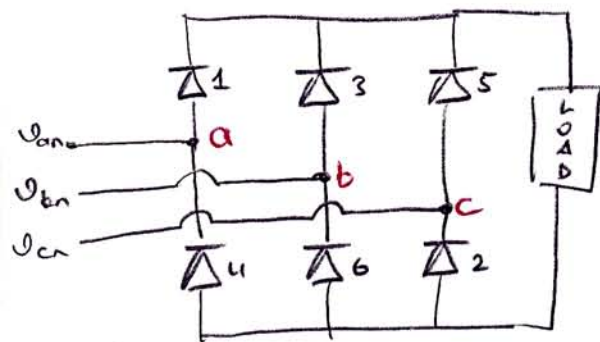


$$V_{an} = V_{max} \sin(\omega t)$$

$$V_{bn} = V_{max} \sin(\omega t - 120^\circ)$$

$$V_{cn} = V_{max} \sin(\omega t - 240^\circ)$$

Actually, between a-b, b-c and c-a points, phase-to-phase voltages can be seen.

Rectifier is modified...

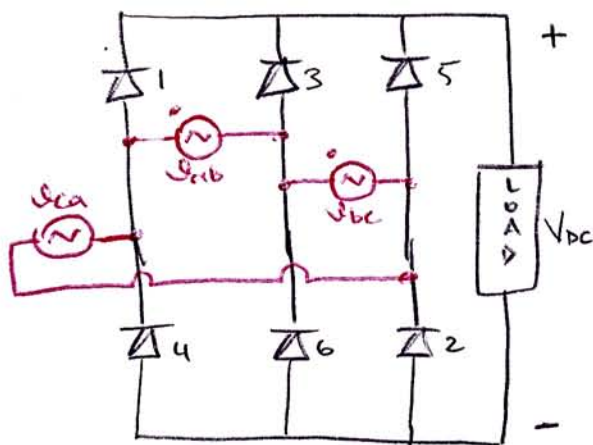

$$V_{ab} = V_{an} - V_{bn} = V_{max} \sqrt{3} \sin(\omega t + 30^\circ)$$

$$V_{bc} = V_{bn} - V_{cn} = V_{max} \sqrt{3} \sin(\omega t + 150^\circ)$$

$$V_{ca} = V_{cn} - V_{an} = V_{max} \sqrt{3} \sin(\omega t + 270^\circ)$$

All phase-to-phase voltages are rectified and the greatest of three rectified voltages appear on the load.

From the figure; phase voltages, phase-to-phase voltages, rectified phase-to-phase voltages and load voltage can be seen respectively.

For rectified voltages;

- V_{ab} is greatest for $30^\circ \sim 90^\circ$ and $210^\circ \sim 270^\circ$
- V_{bc} is greatest for $150^\circ \sim 210^\circ$ and $330^\circ \sim 390^\circ (-30^\circ)$
- V_{ca} is greatest for $90^\circ \sim 150^\circ$ and $270^\circ \sim 330^\circ$





Diode conduction times are determined by the greatest and lowest phase voltages for higher and lower side diodes respectively.


For higher side diodes;

- D1 conducts for $30^\circ \sim 150^\circ$
- D3 conducts for $150^\circ \sim 270^\circ$
- D5 conducts for $270^\circ \sim 390^\circ (-30^\circ)$

For lower side diodes;

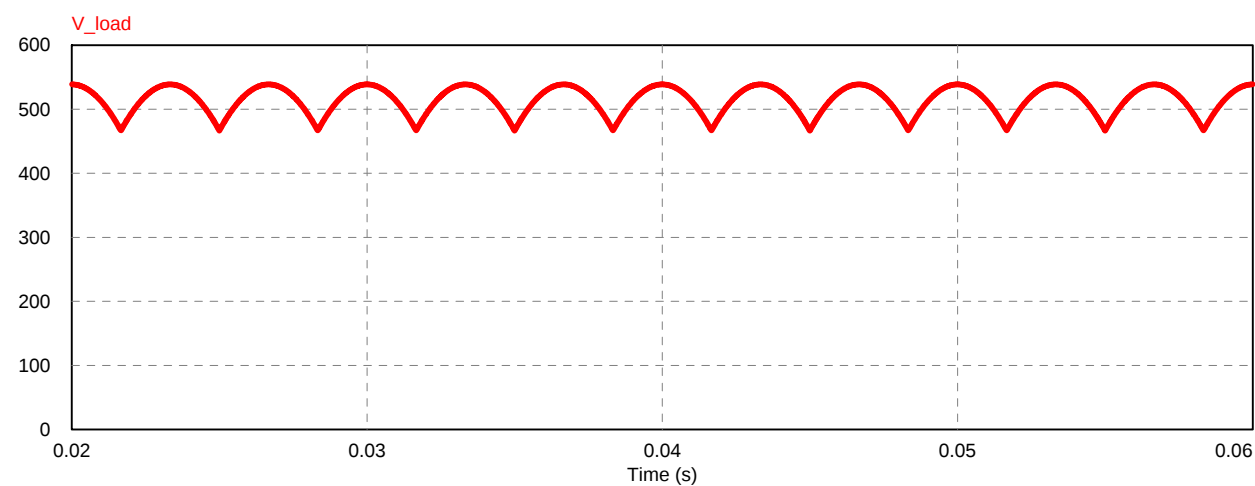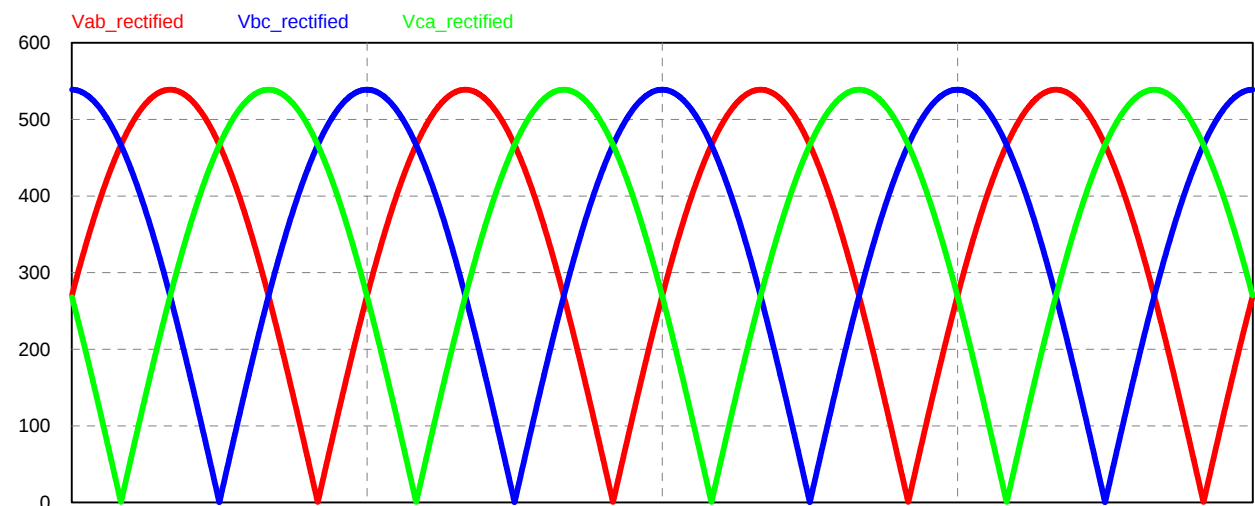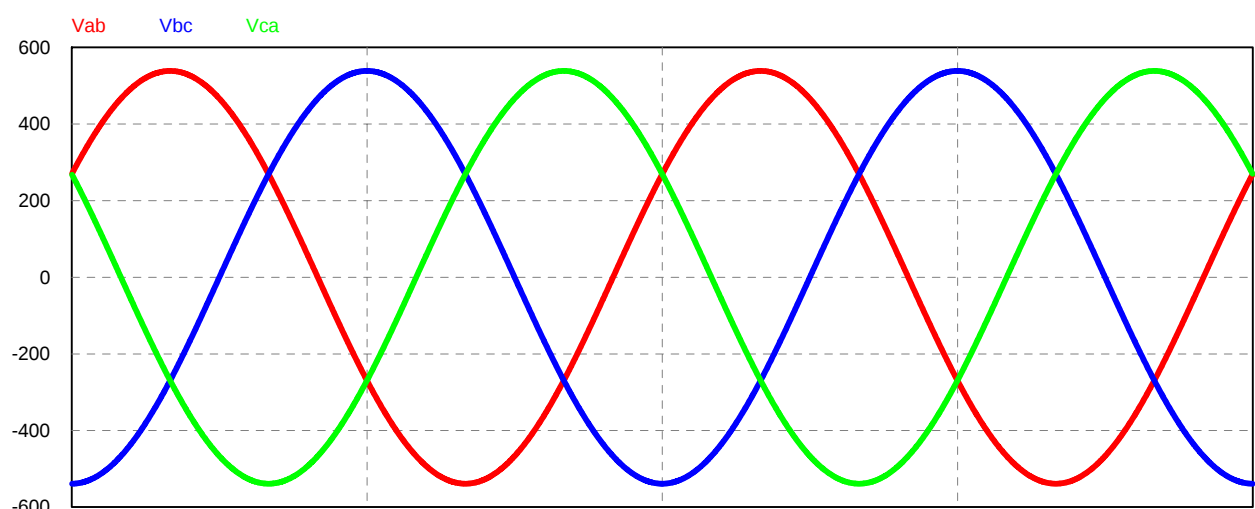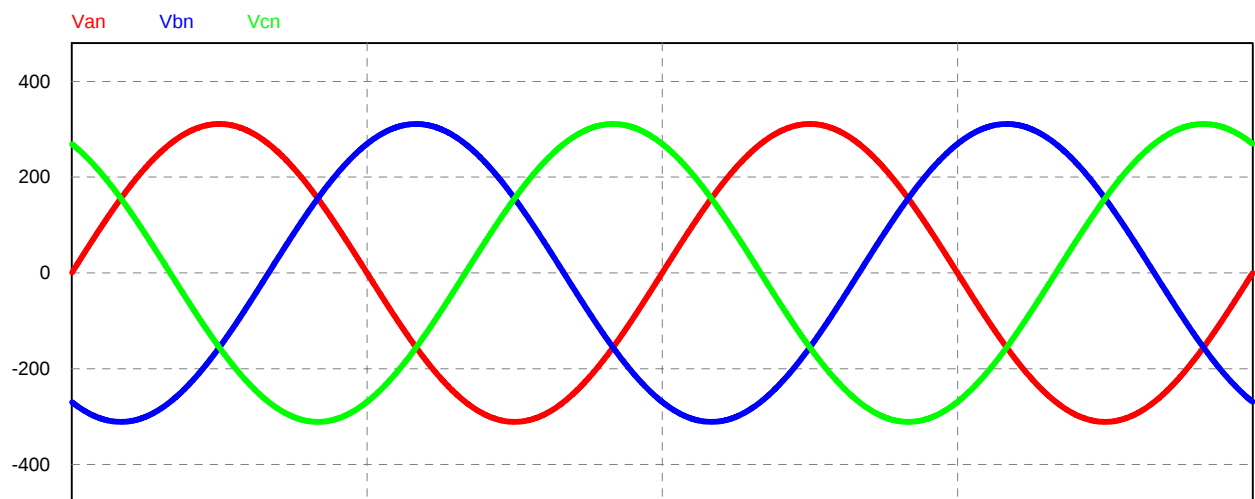- D4 conducts for $210^\circ \sim 330^\circ$
- D6 conducts for $-30^\circ \sim 90^\circ$
- D2 conducts for $90^\circ \sim 210^\circ$



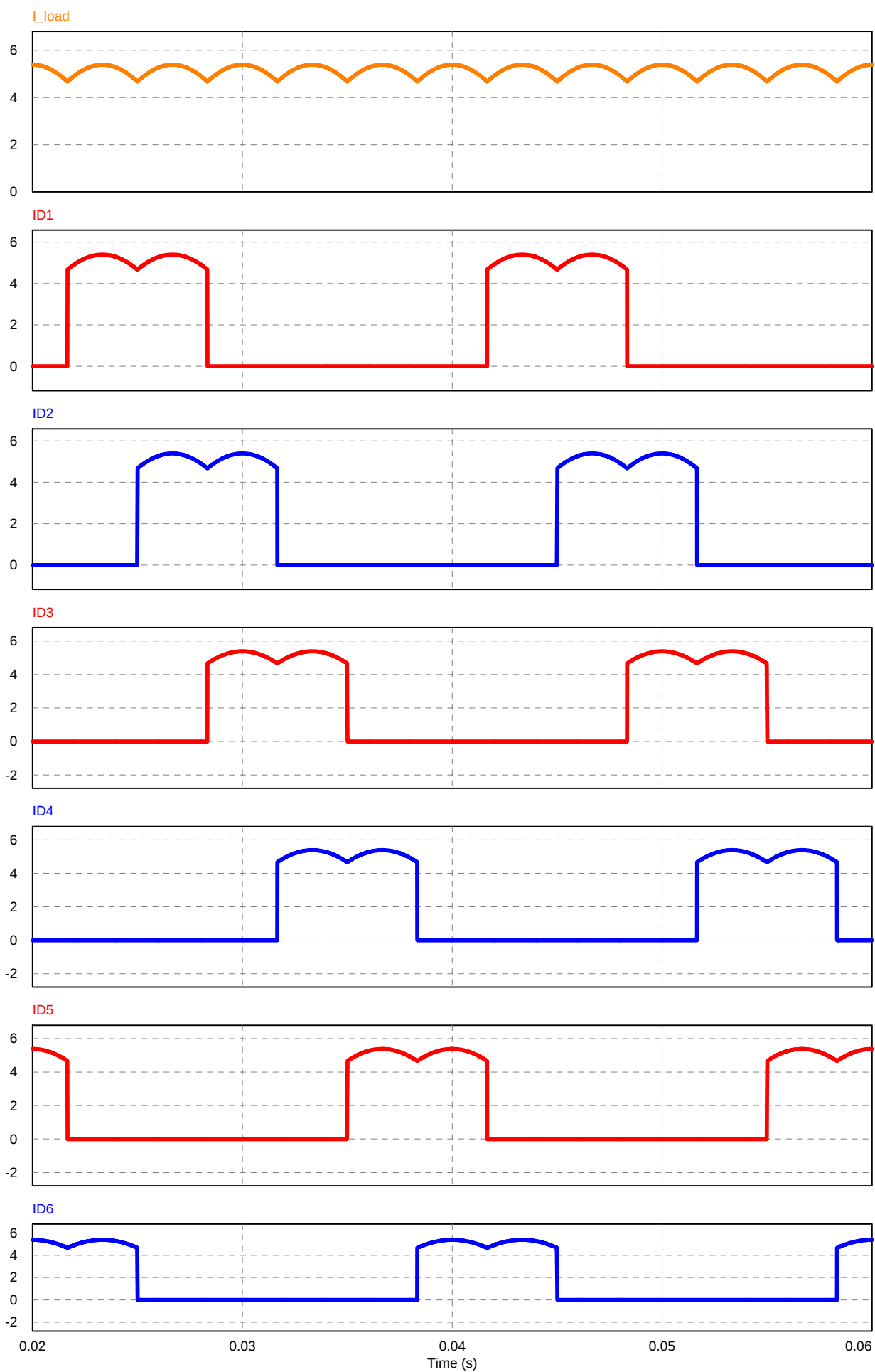

Load Voltage Average Value

Since the load voltage is repetitive for 60° time intervals, the average (DC) load voltage can be calculated as below.

$$\begin{aligned}\frac{1}{\pi/3} \int_{\pi/3}^{2\pi/3} V_{\max} \sqrt{3} \cdot \sin(\omega t) \cdot d\omega t &= \frac{V_{\max} 3\sqrt{3}}{\pi} \left[(-\cos(\omega t)) \right]_{\pi/3}^{2\pi/3} \\ &= \frac{V_{\max} 3\sqrt{3}}{\pi} \left(-(-0,5) - (-0,5) \right) = \frac{V_{\max} 3\sqrt{3}}{\pi} \\ &= 1,654 V_{\max}.\end{aligned}$$


Load Voltage RMS Value

$$\begin{aligned}\sqrt{\frac{1}{\pi/3} \int_{\pi/3}^{2\pi/3} (V_{\max} \sqrt{3})^2 \cdot \sin^2(\omega t) \cdot d\omega t} &= \sqrt{\frac{3V_{\max}^2}{\pi} \cdot \left[\frac{1}{2} \left(\omega t - \frac{\sin 2\omega t}{2} \right) \right]_{\pi/3}^{2\pi/3}} \\ &= \sqrt{\frac{9V_{\max}^2}{2\pi} \left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \right)} = 1,65544 V_{\max}\end{aligned}$$

For Resistive Load Condition

Average Load Current $I_{DC} = \frac{V_{DC}}{R}$

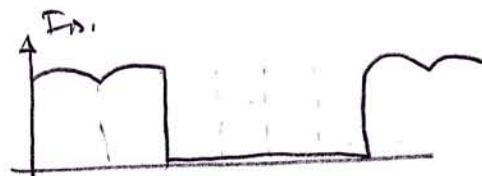Average Diode Current $I_D = \frac{I_{DC}}{3} = \frac{V_{DC}}{3R}$



RMS Diode Current

$$\begin{aligned}I_{D,rms} &= \sqrt{\frac{2}{2\pi} \int_{\pi/3}^{2\pi/3} \left(\frac{V_{\max} \sqrt{3}}{R} \right)^2 \sin^2(\omega t) \cdot d\omega t} = \sqrt{\frac{3V_{\max}^2}{\pi R^2} \left[\frac{1}{2} \left(\omega t - \frac{\sin 2\omega t}{2} \right) \right]_{\pi/3}^{2\pi/3}} \\ &= \sqrt{\frac{3V_{\max}^2}{2\pi R^2} \left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \right)} = 0,9558 \cdot \frac{V_{\max}}{R}\end{aligned}$$

For Inductive Load Condition

Load average and RMS voltages are same with resistive load condition. But current waveforms are different.

Since the output voltage is nearly DC, the current is always continuous.

$$V_{DC} = 1.654 V_{max}$$

$$V_{rms} = 1.65544 V_{max}$$

$$I_{DC} = 1.654 V_{max} / R$$


General solution of a AC excited RL load current is given;

$$i_{load} = \frac{V_x}{Z} \sin(\omega t - \phi) + A \cdot e^{-(R/L)t}$$

- $V_x = V_{max} \sqrt{3}$ for our notation
- $Z = \sqrt{R^2 + \omega^2 L^2}$
- $\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$ rad

"A" is a constant which can be calculated from load voltage waveform.

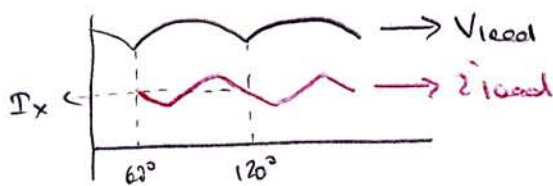For a RL loaded 3 ϕ uncontrolled rectifier;



When $\omega t = 60^\circ = \pi/3$, it is assumed that $i_{load} = I_x$, "A" is;

$$A = \left[I_x - \frac{V_x}{Z} \sin\left(\frac{\pi}{3} - \phi\right) \right] e^{(R/L)(\frac{\pi}{3\omega} - t)}$$

i_{load} is written again;

$$i_{load} = \frac{V_x}{Z} \sin(\omega t - \phi) + \left[I_x - \frac{V_x}{Z} \sin\left(\frac{\pi}{3} - \phi\right) \right] e^{(R/L)(\frac{\pi}{3\omega} - t)} e^{-(R/L)t}$$

under steady-state; $i_{load}(\omega t = \frac{\pi}{3}) = i_{load}(\omega t = \frac{2\pi}{3}) = I_x$

$$I_x = \frac{V_x}{Z} \cdot \frac{\sin(\frac{2\pi}{3} - \phi) - \sin(\frac{\pi}{3} - \phi) e^{-(R/L)(\pi/3\omega)}}{1 - e^{-(R/L)(\pi/3\omega)}}$$

I_x is inserted into i_{load} and i_{load} is rewritten.

$$i_{load} = \frac{V_x}{Z} \left[\sin(\omega t - \phi) + \frac{\sin(\frac{2\pi}{3} - \phi) - \sin(\frac{\pi}{3} - \phi) e^{(R/L)(\frac{\pi}{3\omega} - t)}}{1 - e^{-(R/L)(\pi/3\omega)}} \cdot e^{(R/L)(\frac{\pi}{3\omega} - t)} \right] \text{ for } \frac{\pi}{3} < \omega t < \frac{2\pi}{3}$$

$60^\circ < \omega t < 120^\circ$

Example: A 3 ϕ uncontrolled bridge rectifier is supplying the 20- Ω resistive load from line voltage of 380V/50Hz.

- Calculate mean load voltage and current. (V_{dc} and I_{dc})

$$V_{max} = V_{rms} \cdot \sqrt{2} = 380 \cdot \sqrt{2} = 537,4 \text{ V}$$

$$V_{dc} = 1,654 \cdot V_{max} = 1,654 \cdot 537,4 = 888,86 \text{ V}$$

$$I_{dc} = V_{dc} / R = 888,86 / 20 = 44,44 \text{ A}$$

- Calculate average and rms diode current (per diode)

$$I_{D,av} = \frac{I_{dc}}{3} = \frac{44,44}{3} = 14,81 \text{ A}$$


$$I_{D,rms} = 0,9558 \cdot \frac{V_{max}}{R} = 0,9558 \cdot \frac{537,4}{20} = 25,68 \text{ A}$$

- Draw the source current for one phase, calculate rms phase current.

$i_a \rightarrow$ source current from "phase a"

I_{D1} (diode 1 current is drawn from "phase a")

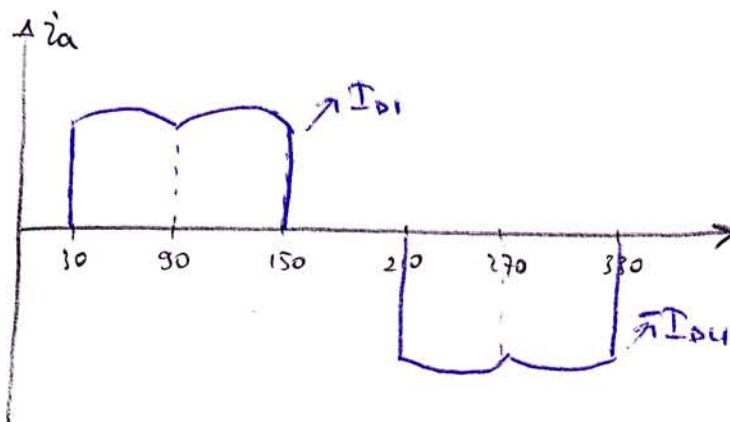I_{D4} (diode 4 current is supplied to "phase a")



$$I_{a,rms} = \sqrt{2} \cdot I_{D,rms} = \sqrt{2} \cdot 25,68 = 36,32 \text{ A}$$

- Calculate the P_{DC} power of the circuit.

$$P_o = V_{dc} \cdot I_{dc} = 888,86 \cdot 44,44 = 39501 \text{ W}$$

- Calculate the power factor of the circuit.

$$PF = \frac{P_{o,rms}}{P_{i,rms}} = \frac{V_{rms}^2 / R}{3 \cdot V_{a,rms} \cdot I_{a,rms}} = \frac{(1,65544 \cdot 537,4)^2 / 20}{3 \cdot 380 \cdot 36,32} = 0,955743$$

(power factor is defined as power consumed at output resistor over input rms power)

Example: A 3 ϕ uncontrolled bridge rectifier is supplying an inductive load with $R=60$ and $L=25\text{mH}$, from $220\text{V}/50\text{Hz}$ utility.

- Calculate average load voltage and current.

$$V_{\max} = 220\sqrt{2} = 311,13\text{V}$$

$$V_{\text{DC}} = 1,654 \cdot V_{\max} = 1,654 \cdot 311,13 = 514,6\text{V}$$

$$I_{\text{DC}} = V_{\text{DC}}/R = 8,577\text{A}$$

- Write the expression for load current.

$$V_x = V_{\max}\sqrt{3} = 311,13\sqrt{3} = 538,89\text{V}$$

$$Z = \sqrt{\omega^2 L^2 + R^2} = \sqrt{4\pi^2 50^2 0,025^2 + 60^2} = 60,51\Omega$$

$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right) = 7,458^\circ = 0,13\text{rad}$$

$$\left. \begin{array}{l} 60^\circ < \omega t < 120^\circ \\ \frac{\pi}{3} < \omega t < \frac{2\pi}{3} \\ \frac{\pi}{3\omega} < t < \frac{2\pi}{3\omega} \end{array} \right\} \begin{aligned} i_{\text{load}} &= \frac{538,89}{60,51} \cdot \left[\sin(\omega t - 7,458^\circ) + \frac{\sin(120^\circ - 7,458^\circ) - \sin(60^\circ - 7,458^\circ)}{1 - e^{-\left(\frac{60}{0,025}\right)\left(\frac{\pi}{6\pi 50} - t\right)}} \cdot e^{\left(\frac{60}{0,025}\right)\left(\frac{\pi}{6\pi 50} - t\right)} \right] \\ &= 8,906 \left[\sin(\omega t - 7,458^\circ) + \frac{0,9236 - 0,7938}{1 - e^{-8}} \cdot e^{(8 - 2400t)} \right] \\ &= 8,906 \left[\sin(\omega t - 7,458^\circ) + 0,12984 \cdot e^{(8 - 2400t)} \right] \end{aligned}$$

- calculate i_{load} for $\omega t = 60^\circ, 70^\circ, 80^\circ, 90^\circ, 100^\circ, 110^\circ, 120^\circ$

$$i_{\text{load}}(60^\circ) = 8,906 \left[\sin(60^\circ - 7,458^\circ) + 0,12984 e^{(8 - 2400 \cdot \frac{\pi}{3\omega})} \right] = 8,226\text{A}$$

$$i_{\text{load}}(70^\circ) = 8,2076\text{A} \quad i_{\text{load}}(80^\circ) = 8,5761\text{A} \quad i_{\text{load}}(90^\circ) = 8,8518\text{A}$$

$$i_{\text{load}}(100^\circ) = 8,9028\text{A} \quad i_{\text{load}}(110^\circ) = 8,6949\text{A} \quad i_{\text{load}}(120^\circ) = 8,226\text{A}$$

- calculate rms load current with discrete current values.

$$\sqrt{\frac{i_{\text{load}}^2(60^\circ) + i_{\text{load}}^2(70^\circ) + i_{\text{load}}^2(80^\circ) + i_{\text{load}}^2(90^\circ) + i_{\text{load}}^2(100^\circ) + i_{\text{load}}^2(110^\circ)}{6}} = i_{\text{RMS}}$$

$$i_{\text{RMS}} = \sqrt{\frac{441,7968}{6}} = 8,581\text{A}$$





$$i_{D,\text{RMS}} = i_{\text{RMS}} \cdot \sqrt{1/3}$$

$$i_{a,\text{RMS}} = i_{D,\text{RMS}} \sqrt{2}$$


$$i_{a,\text{RMS}} = i_{\text{RMS}} \sqrt{2/3}$$

- calculate power factor of the rectifier.
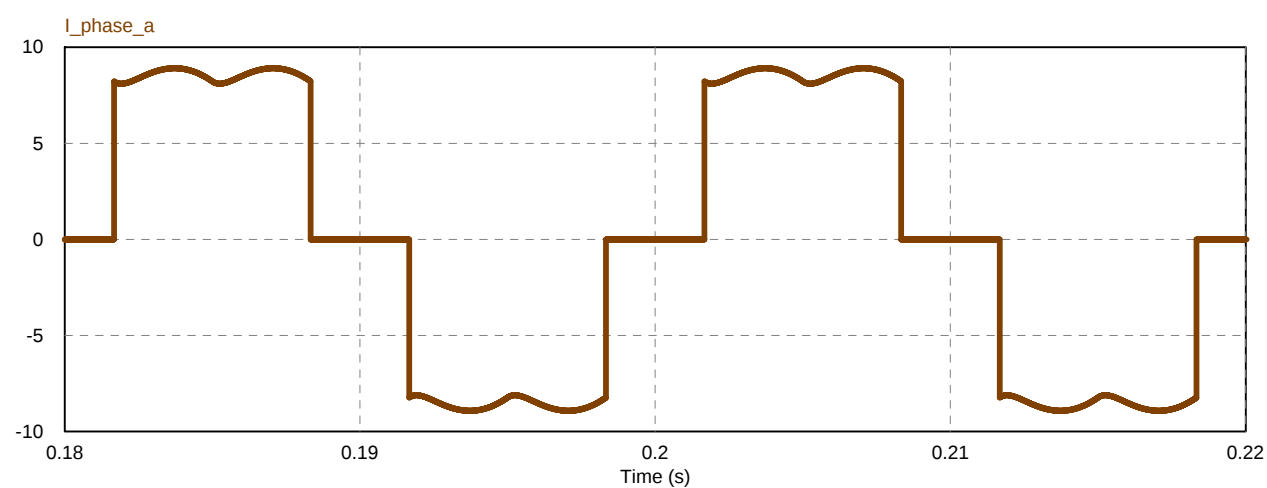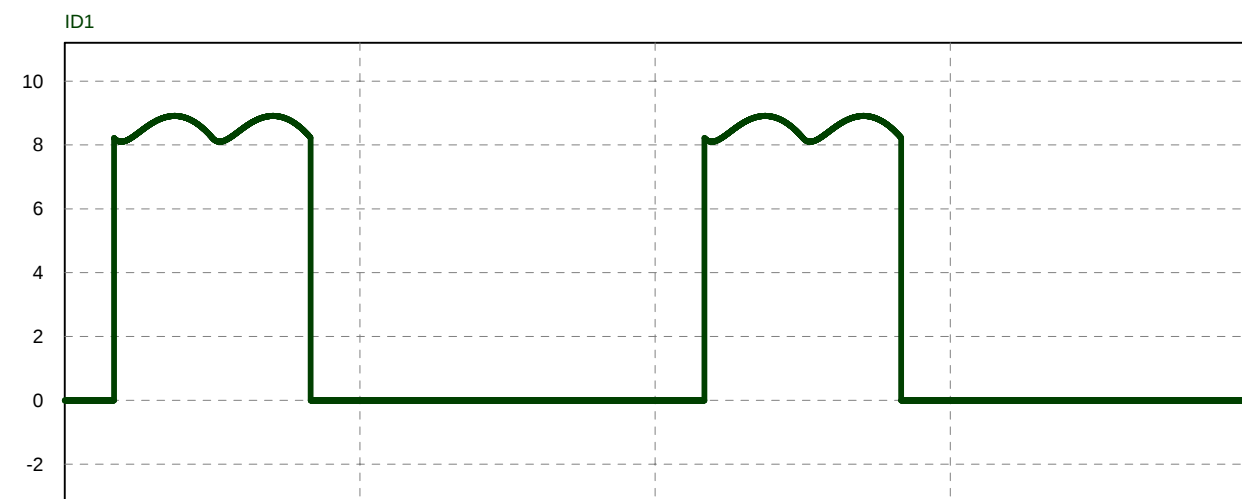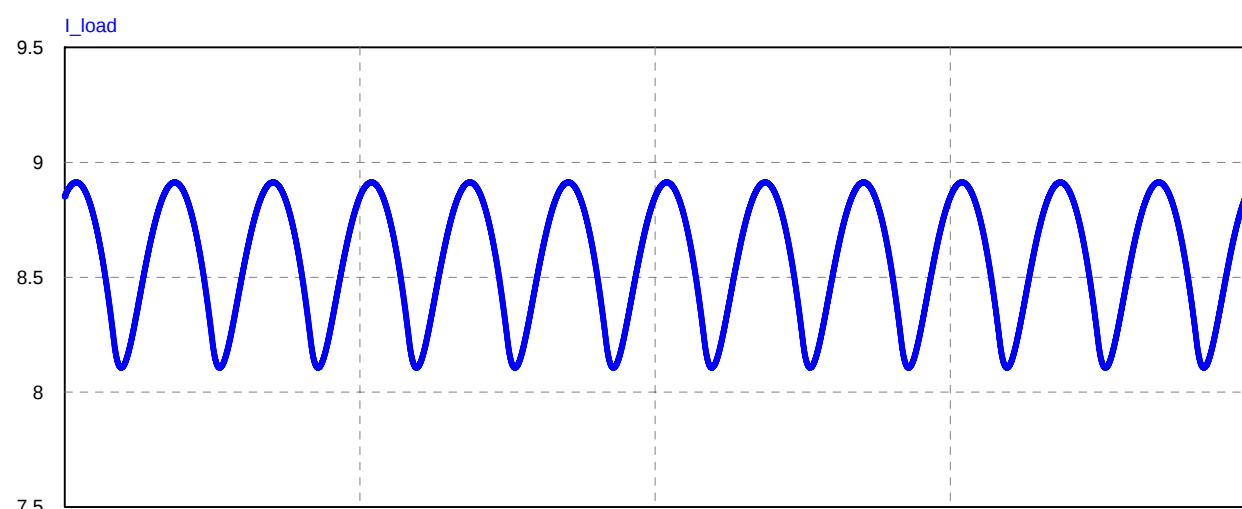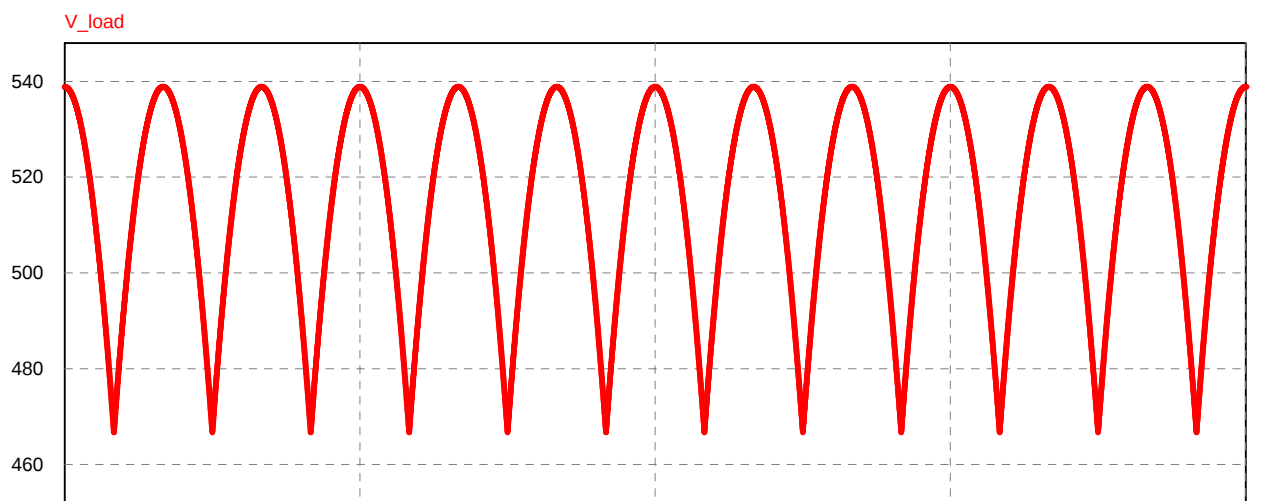
$$\text{PF} = \frac{i_{\text{RMS}}^2 \cdot R}{3 \cdot 220 \cdot i_{a,\text{RMS}}} = \frac{8,581^2 \cdot 60}{3 \cdot 220 \cdot 7,006} = 0,9554$$



- CONTROLLED RECTIFIERS -

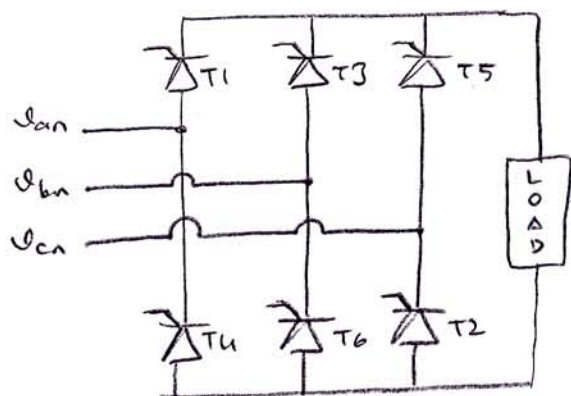

α angle is the control parameter.

As it is seen from uncontrolled rectifiers, if there are thyristors replaced with diodes, conduction angles become;

$T_1 \rightarrow$	$30^\circ \sim 150^\circ$
$T_2 \rightarrow$	$90^\circ \sim 210^\circ$
$T_3 \rightarrow$	$150^\circ \sim 270^\circ$
$T_4 \rightarrow$	$210^\circ \sim 330^\circ$
$T_5 \rightarrow$	$270^\circ \sim 330^\circ$
$T_6 \rightarrow$	$-30^\circ \sim 90^\circ$

α angle is defined for T_1 , T_1 starts to conduct at 30° .
if $\alpha = 0^\circ$, gate signal must be applied to thyristor 1 at $\alpha + 30^\circ$.
(α_1)

other thyristors requires gate signal 60° later from α_1 .

$$\alpha_2 = T_2 \rightarrow \alpha + 30^\circ + 60^\circ = \alpha + 90^\circ = \alpha_2$$

$$\alpha_3 = T_3 \rightarrow \alpha + 30^\circ + 120^\circ = \alpha + 150^\circ = \alpha_3$$


This converter operates as rectifier for $\alpha \leq 90^\circ$

and operates as inverter for $\alpha \geq 90^\circ$

At $\alpha = 90^\circ$, average output voltage is zero.

for $\alpha \leq 90^\circ$, average output voltage is positive

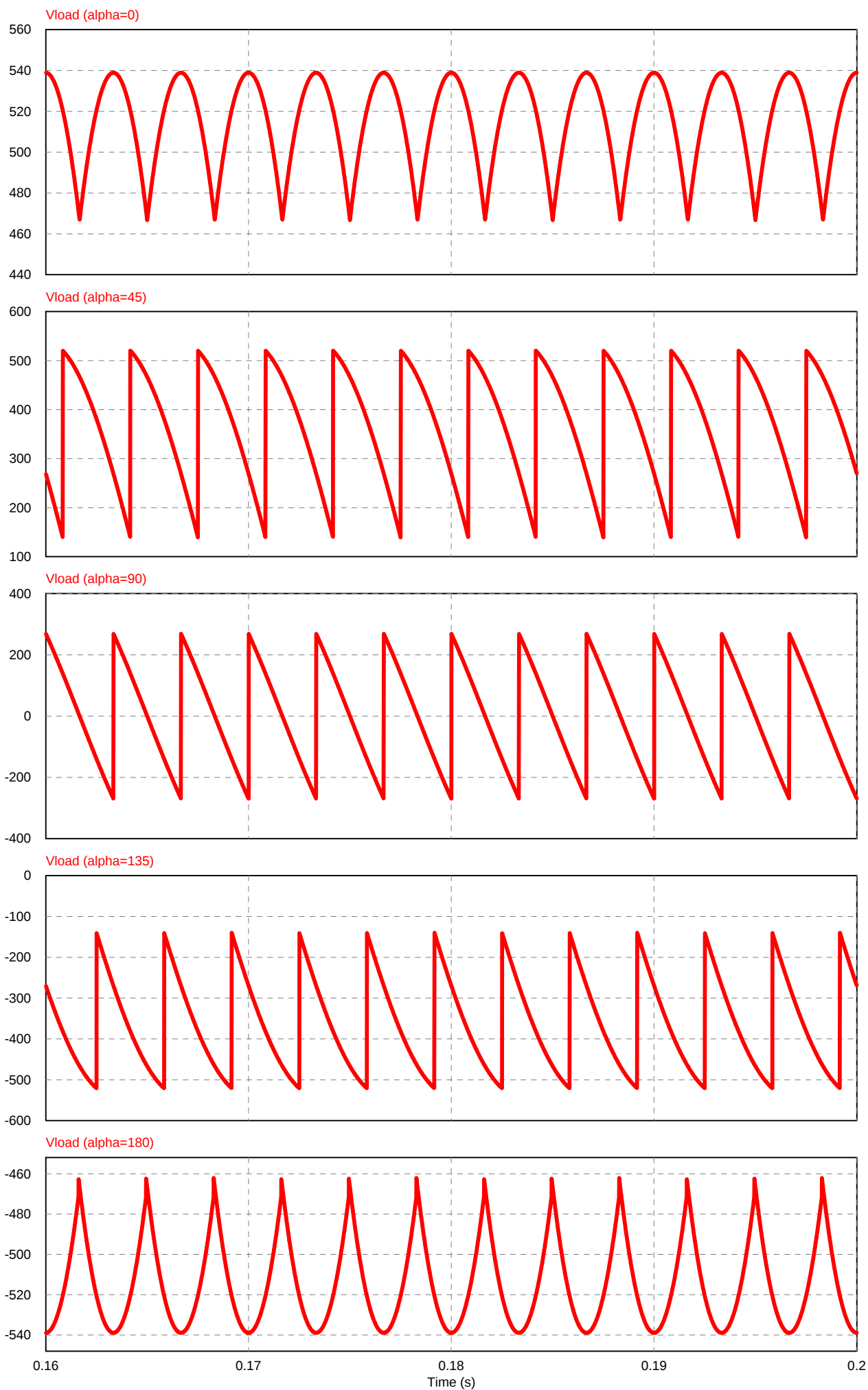for $\alpha \geq 90^\circ$, average output voltage is negative.



Load Voltage Average Value

Phase to phase voltages are seen on the load. It is known that, 60° of the phase-to-phase voltage was the starting point at uncontrolled rectifiers. For the controlled rectifiers, the starting point becomes $60^\circ + \alpha$ ($\frac{\pi}{3} + \alpha$). Also every switch conducts current for 60° ($\frac{\pi}{3}$). Therefore; the finish point becomes $60^\circ + \alpha + 60^\circ$ ($\frac{\pi}{3} + \alpha + \frac{\pi}{3} = \frac{2\pi}{3} + \alpha$).

$$\begin{aligned}
 V_{DC} &= \frac{1}{\pi/3} \int_{\pi/3+\alpha}^{\frac{2\pi}{3}+\alpha} V_{max} \sqrt{3} \cdot \sin(\omega t) \cdot d\omega t = \frac{V_{max} 3\sqrt{3}}{\pi} \left[(-\cos(\omega t)) \right]_{\pi/3+\alpha}^{\frac{2\pi}{3}+\alpha} \\
 &= \frac{V_{max} 3\sqrt{3}}{\pi} \left[\underbrace{(-\cos(\frac{2\pi}{3}+\alpha)) - (-\cos(\frac{\pi}{3}+\alpha))}_{\left(\cos \frac{\pi}{3} \cdot \cos \alpha - \sin \frac{\pi}{3} \cdot \sin \alpha \right) - \left(\cos \frac{2\pi}{3} \cdot \cos \alpha - \sin \frac{2\pi}{3} \cdot \sin \alpha \right)} \right] \\
 &= \frac{V_{max} 3\sqrt{3}}{\pi} \left[\frac{\cos \alpha}{2} - \frac{\sin \alpha \sqrt{3}}{2} + \frac{\cos \alpha}{2} + \frac{\sin \alpha \sqrt{3}}{2} \right] = \frac{V_{max} 3\sqrt{3}}{\pi} \cos \alpha
 \end{aligned}$$

Load Voltage RMS value

$$\begin{aligned}
 V_{rms} &= \sqrt{\frac{1}{\pi/3} \int_{\pi/3+\alpha}^{\frac{2\pi}{3}+\alpha} (V_{max} \sqrt{3})^2 \cdot \sin^2(\omega t) \cdot d\omega t} = \sqrt{\frac{9V_{max}^2}{\pi} \left[\frac{1}{2} \left(\omega t - \frac{\sin 2\omega t}{2} \right) \right]_{\pi/3+\alpha}^{\frac{2\pi}{3}+\alpha}} \\
 &= \frac{3V_{max}}{\sqrt{2\pi}} \sqrt{\left(\frac{2\pi}{3} + \alpha - \frac{\sin(\frac{4\pi}{3} + 2\alpha)}{2} \right) - \left(\frac{\pi}{3} + \alpha - \frac{\sin(\frac{2\pi}{3} + 2\alpha)}{2} \right)} \\
 &\quad \underbrace{\frac{\pi}{3} + \frac{\sin(\frac{2\pi}{3} + 2\alpha) - \sin(\frac{4\pi}{3} + 2\alpha)}{2}}_{= \frac{\pi}{3} + \frac{2 \cdot \sin(-\frac{\pi}{3}) \cdot \cos(\pi + 2\alpha)}{2}} \\
 &= \frac{3V_{max}}{\sqrt{2\pi}} \sqrt{\left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha \right)}
 \end{aligned}$$

For Resistive Load Condition

Load current waveform is identical to load voltage waveform.

Therefore,

$$I_{DC} = V_{OC}/R = \frac{V_{max} 3\sqrt{3}}{\pi R} \cdot \cos \alpha$$

$$I_{RMS} = V_{RMS}/R = \frac{3V_{max}}{R\sqrt{2\pi}} \sqrt{\left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha\right)}$$

Current of per diode

$$I_{D,DC} = \frac{I_{DC}}{3} = \frac{V_{max}\sqrt{3}}{\pi R} \cdot \cos \alpha$$

$$I_{D,RMS} = I_{RMS} \cdot \sqrt{1/3} = \frac{3V_{max}}{R\sqrt{6\pi}} \cdot \sqrt{\left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha\right)}$$

RMS current per phase

$$I_{a,RMS} = \sqrt{2} \cdot I_{D,RMS} = \frac{3V_{max}}{R\sqrt{3\pi}} \sqrt{\left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha\right)}$$

Example: At a factory room, pure resistive heater is used with $R = 3 \Omega$. Supply of the factory is 3ϕ $110V/60Hz$ utility. The heater is supplied with 3ϕ controlled rectifier to control the temperature.

- calculate V_{DC} and V_{RMS} for $\alpha = 0^\circ, 30^\circ, 60^\circ$.

$$V_{DC} = \frac{V_{max} 3\sqrt{3}}{\pi} \cos \alpha$$

$$V_{RMS} = \frac{3V_{max}}{\sqrt{2\pi}} \sqrt{\left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha\right)}$$

$$V_{DC}(\alpha=0^\circ) = \frac{110\sqrt{2} \cdot 3\sqrt{3}}{\pi} \cdot \cos 0 = 257,3V$$

$$V_{RMS}(\alpha=0^\circ) = \frac{3 \cdot 110\sqrt{2}}{\sqrt{2\pi}} \sqrt{\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 0} = 257,5V$$

$$V_{DC}(\alpha=30^\circ) = 222,83V$$

$$V_{RMS}(\alpha=30^\circ) = 226,52V$$

$$V_{DC}(\alpha=60^\circ) = 128,65V$$

$$V_{RMS}(\alpha=60^\circ) = 145,91V$$

- calculate P_o for $\alpha = 0^\circ, 30^\circ, 60^\circ$.

$$P_o(\alpha=0^\circ) = V_{RMS}^2(0^\circ)/R = 257,5^2/3 = 22,1 kW$$

$$P_o(\alpha=30^\circ) = V_{RMS}^2(30^\circ)/R = 226,52^2/3 = 17,1 kW$$

$$P_o(\alpha=60^\circ) = V_{RMS}^2(60^\circ)/R = 145,91^2/3 = 7,1 kW$$

- calculate one phase current (RMS) for $\alpha = 0^\circ, 30^\circ, 60^\circ$.

$$i_{a,RMS}(\alpha=0^\circ) = \frac{3V_{max}}{R\sqrt{3\pi}} \sqrt{\left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha\right)} = \frac{3 \cdot 110\sqrt{2}}{3\sqrt{3\pi}} \cdot \sqrt{\left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos(2 \cdot 0)\right)} = 70,01 A$$

$$i_{a,RMS}(\alpha=30^\circ) = 61,65 A \quad i_{a,RMS}(\alpha=60^\circ) = 39,71 A$$

- calculate power factor for $\alpha = 0^\circ, 30^\circ, 60^\circ$

$$PF(\alpha=0^\circ) = \frac{V_{RMS}^2/R}{3 \cdot V_{a,RMS} \cdot i_{a,RMS}} = \frac{22,1 kW}{3 \cdot 110 \cdot 70,01} = 0,9566$$

$$PF(\alpha=30^\circ) = \frac{V_{RMS}^2/R}{3 \cdot V_{a,RMS} \cdot i_{a,RMS}} = \frac{17,1 kW}{3 \cdot 110 \cdot 61,65} = 0,8405$$

$$PF(\alpha=60^\circ) = \frac{V_{RMS}^2/R}{3 \cdot V_{a,RMS} \cdot i_{a,RMS}} = \frac{7,1 kW}{3 \cdot 110 \cdot 39,71} = 0,5418$$

- if the heater is wanted to give $10kW$ to the room, what must the α be?

$$10kW = \frac{V_{RMS}^2}{R}$$

$$V_{RMS} = 173,21V$$

$$\frac{3V_{max}}{\sqrt{2\pi}} \sqrt{\left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha\right)} = V_{RMS}$$

$$\left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha\right) = \left(\frac{173,21 \sqrt{2\pi}}{3 \cdot 110 \sqrt{2}}\right)^2 \quad \dots \alpha = 51,06^\circ$$