

ELE509E

Current-Mode Analog Circuit Design

Homework 3 (16.11.2009)

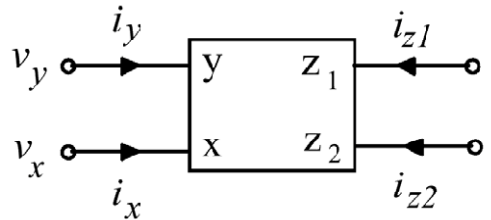


Figure 1. Circuit symbol of DOCCII.

A dual output current conveyor (DOCCII) is described by

$$\begin{bmatrix} V_X \\ I_Y \\ I_{Z1} \\ I_{Z2} \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ k & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_X \\ V_Y \\ V_{Z1} \\ V_{Z2} \end{bmatrix}$$

$k = \pm 1$. For $k = 1$ a DOCCII with two noninverting Z outputs is obtained. For $k = -1$ the Z_2 terminal yields an inverted output signal.

Design a CMOS dual output current conveyor with inverting and noninverting outputs.

1. Terminal input and output resistances $R_{Z1}, R_{Z2}, R_Y > 10 \text{ M}\Omega$, $R_X < 10 \Omega$.
2. Voltage tracking error $\epsilon_v < 0.1\%$, current tracking error $\epsilon_i < 0.1\%$,
3. BW of the voltage gain ($A_v = v_x/v_y$) $f_{v3db} > 10 \text{ MHz}$,
4. BW of the current gain ($A_{i1} = i_{z1}/i_x, A_{i2} = i_{z2}/i_x$) $f_{i3db} > 50 \text{ MHz}$,

Choose an adequate CMOS realization technology. The model parameters of the MOS transistors can be obtained from the WEB site.

- a- Specify the CMOS DOCCII structure, determine transistor dimensions.
Using SPICE simulation results
- b- draw the plots of V_X against V_Y , I_{Z1} and I_{Z2} against I_X ,
- c- specify the limits of the operation region,
- d- draw the frequency response of the voltage gain and determine the bandwidth,
- e- draw the frequency response of the current gain and determine the bandwidth,
- f- draw the plot of the terminal impedances against the frequency,
- g- investigate the large signal behaviour of the DOCCII by applying to Y terminal a sinusoidal input voltage in the passband and observing the total harmonic distortion THD at the X, Z_1 and Z_2 terminals for different input levels; draw the plot of THD against i_{in} for each terminal. (Connect adequate load resistances to the X, Z_1 and Z_2 terminals.
- h- Give a detailed evaluation of your results.