

ELE509E

Current-Mode Analog Circuit Design

Final Project

Design a current-mode sixth-order Butterworth LP filter with a cut-off frequency of 3 MHz. Use the second order CCCII+ based filter topology illustrated in Figure 1. The overall filter can be obtained by cascading these second-order sections, as shown in Figure 2.

- a) Choose a suitable CCCII+ realization topology (BJT or CMOS). Specify the supply voltages.
- b) Determine the biasing currents, resistance and capacitance values.

Using SPICE simulation results

- a) draw the frequency and phase responses of the filter for ideal and actual cases, determine the actual cut-off frequency,
- b) compare the simulated frequency and phase responses with the theoretical results.
- c) Investigate the large signal behaviour of the filter by applying a sinusoidal input current in the pass band of the filter and observing the total harmonic distortion THD at the output for different input levels; draw the plot of THD against i_{in} ,
- d) investigate the dependence of the output voltage upon the load resistance R_L keeping the input level constant, observe the harmonic distortion THD at the output for each load resistance value; draw the plots of THD against R_L and V_O against R_L .
- e) Investigate the tunability of the realized filter.
- f) Give a detailed evaluation of your results.

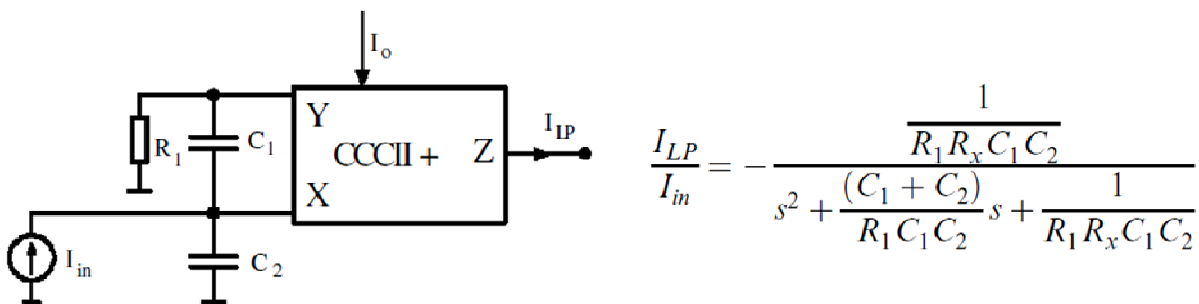


Figure 1. CCCII+ based second-order LP filter topology

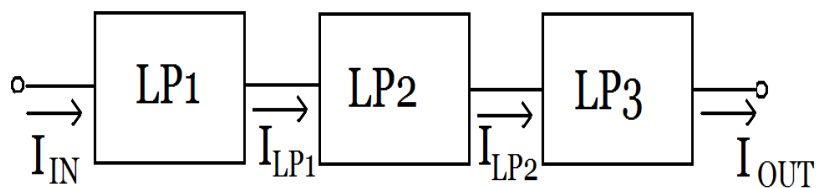


Figure 2. 6th order LP filter obtained by cascading second-order sections.

References:

- Minaei S., Çiçekoğlu, O, Kuntman, H., and Türköz, S., 2001. "High Output Impedance Current-Mode Low pass, Band pass and High pass Filters Using Current Controlled Conveyors". *International Journal of Electronics*. 88 (8), 915-922.

Normalized Butterworth polynomials

<i>n</i>	<i>Factors of polynomial $P_n(s)$</i>
1	$(s + 1)$
2	$(s^2 + 1.414s + 1)$
3	$(s + 1)(s^2 + s + 1)$
4	$(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$
5	$(s + 1)(s^2 + 0.618s + 1)(s^2 + 1.618s + 1)$
6	$(s^2 + 0.518s + 1)(s^2 + 1.414s + 1)(s^2 + 1.932s + 1)$
7	$(s + 1)(s^2 + 0.445s + 1)(s^2 + 1.247s + 1)(s^2 + 1.802s + 1)$
8	$(s^2 + 0.390s + 1)(s^2 + 1.111s + 1)(s^2 + 1.663s + 1)(s^2 + 1.962s + 1)$
