

# Current-Mode Analog Circuit Design

Current-Mode Oscillators

Realization of DO-OTA-C oscillators

Realization of FTFN-Based Current-Mode Oscillators

Hakan Kuntman, 2009

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

- Sinusoidal oscillators play an important role in instrumentation, communication and signal processing applications.
- Sinusoidal oscillators based on OTA-C structures have attracted considerable attention in recent years because they offer several advantages over conventional op-amp based oscillators as well as providing the evaluation of fully integrated oscillators in VLSI design with CMOS technology.
- OTAs :
- provide highly linear electronic tunability of their transconductance ( $gm$ )
- require just a few or even no resistors for their internal circuitry
- have more reliable high frequency performance
- OTAs are increasingly replacing operational amplifiers

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

- A general sinusoidal oscillator circuit can be described by a second order characteristic equation as follows:

$$(s^2 + bs + \Omega_o^2)I_{out} = 0$$

- $b = 0$  is oscillation condition and  $\Omega_o$  is oscillation frequency.

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

- The general biquadratic transfer function is

$$H(s) = \frac{I_o(s)}{I_i(s)} = \frac{a_2s^2 + a_1s + a_0}{s^2 + b_1s + b_0}$$

- There are two possible methods of obtaining sinusoidal oscillator from this transfer function.
- In the first method the characteristic equation of the oscillator is obtained by
$$(s^2 + bs + \Omega_o^2)I_{out} = 0$$
- Equating input current of filter,  $i_n(s)$  to zero.
- In this case the following oscillator characteristic equation is obtained:

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

- The second way is connecting the output terminal of filter to the input terminal.
- The resulting oscillator characteristic equation is expressed as:

$$\left[ s_2 + \left( \frac{b_1 - a_1}{1 - a_2} \right) s + \left( \frac{b_0 - a_0}{1 - a_2} \right) \right] \cdot I_o(s) = 0$$

- If the oscillation condition is satisfied by equating the coefficient of  $s$  to zero, this two equation yields undamped oscillators.


# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

- In this study nine DO-OTA-C sinusoidal oscillator structures
- are obtained by converting filters [10-13] into oscillators.
- The equation giving the oscillation condition of an oscillator must include both positive and negative terms to obtain stable oscillation which can be achieved by equating the oscillation condition term to zero.
- Negative and positive resistors implemented with CMOS DO-OTAs are added to oscillator networks.
- These configurations have oscillation frequencies controlled by transconductance gain without affecting oscillation condition and capability of operation at high frequencies.
- All of the proposed topologies are very attractive in both monolithic integrated technology

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

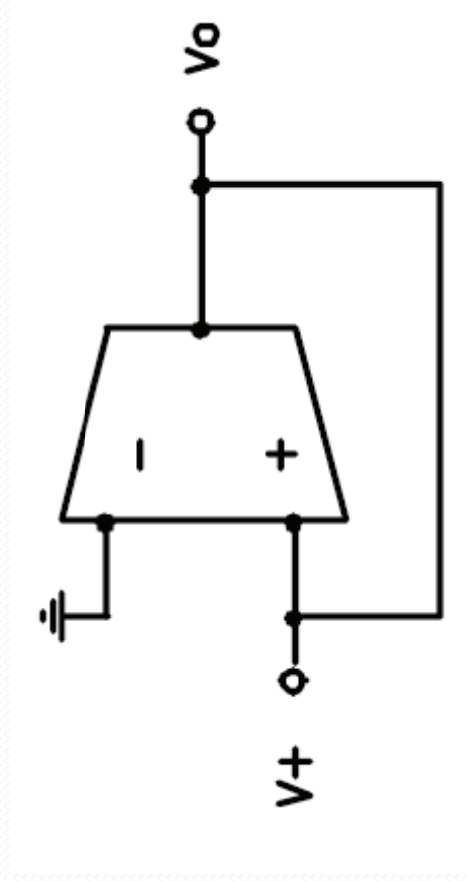


Negative resistor implemented with OTA

$$R_n = -\frac{1}{g_m}$$

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

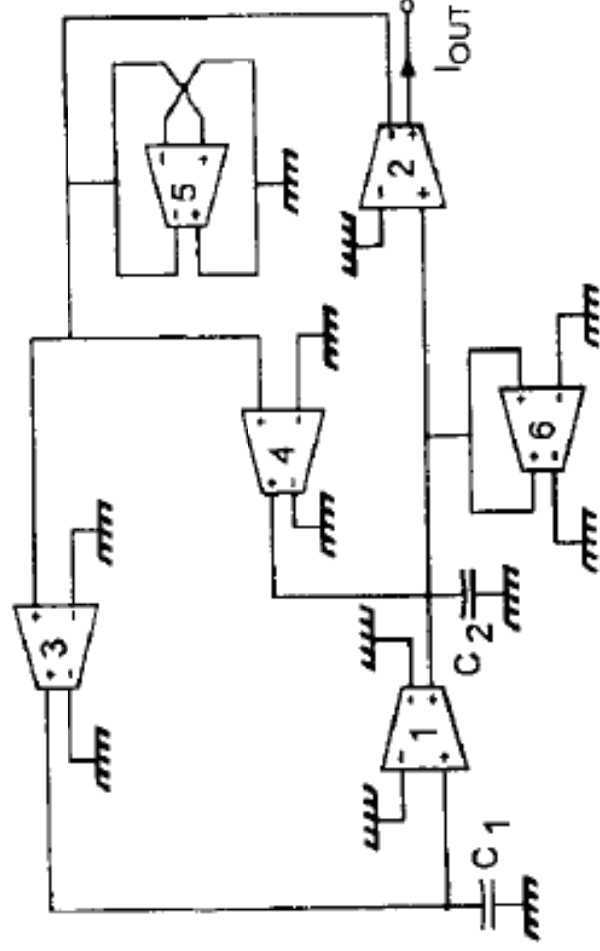

(a)

b

$$\frac{g_{m2} \cdot g_{m4} - g_{m6}}{g_{m5}} \cdot C_2$$


$\Omega_0^2$

$$\frac{g_{m1} \cdot g_{m2} \cdot g_{m3}}{C_1 C_2 g_{m5}}$$



# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

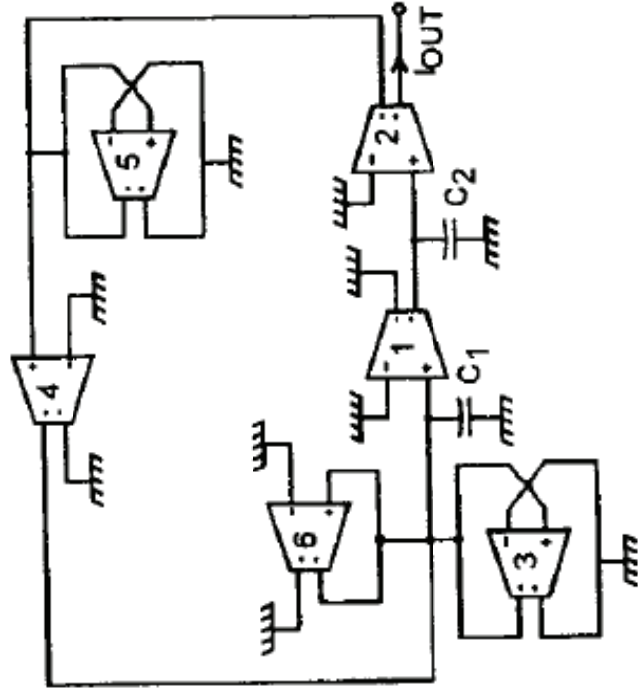


(b)

$b$	$\Omega_0^2$
$\frac{g_{m3} - g_{m6}}{C_1}$	$\frac{g_{m1} \cdot g_{m2} \cdot g_{m4}}{C_1 C_2 g_{m5}}$

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

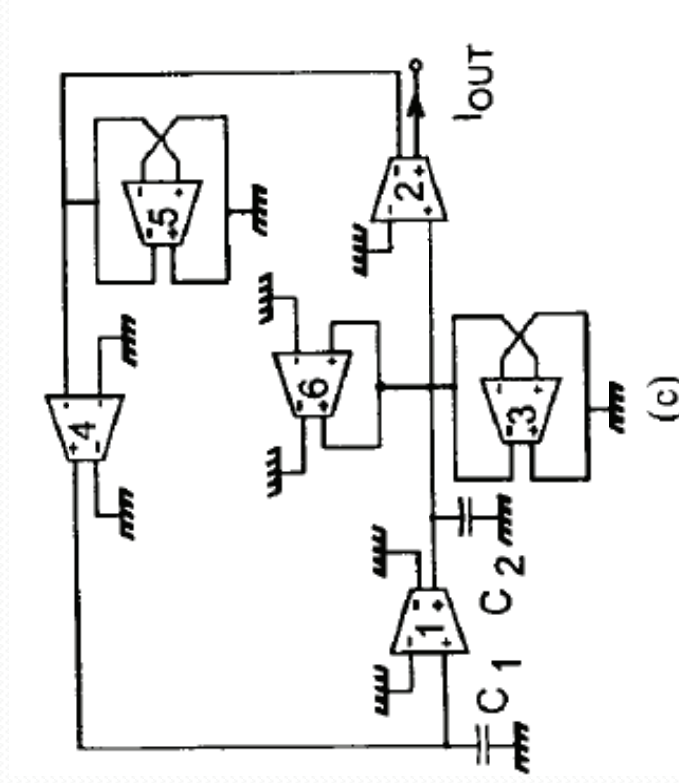


$$b \quad \Omega_0^2$$


---


$$\frac{g_{m3} - g_{m6}}{C_2} \quad \frac{g_{m1} g_{m2} g_{m4}}{C_1 C_2 g_{m5}}$$

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

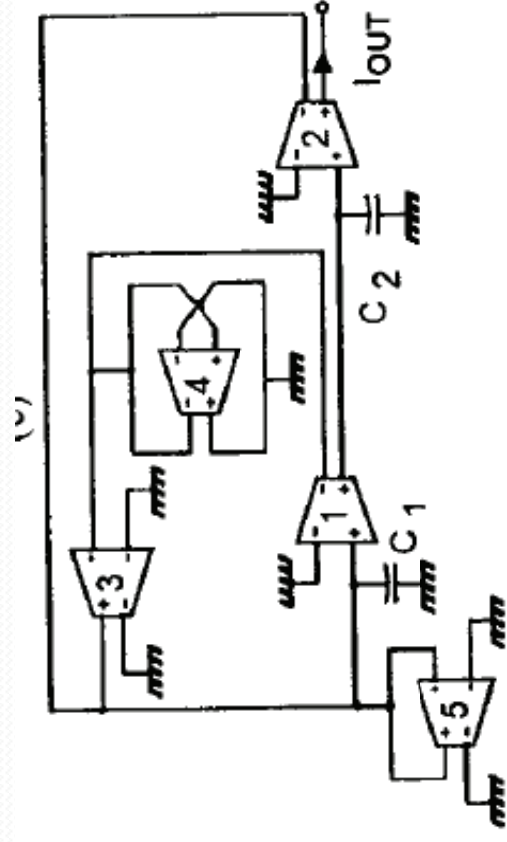


(d)

$b$	$\Omega_0^2$
$\frac{g_{m1}g_{m3}}{g_{m4}} - g_{m5}$	$\frac{g_{m1} \cdot g_{m2}}{C_1 C_2}$

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

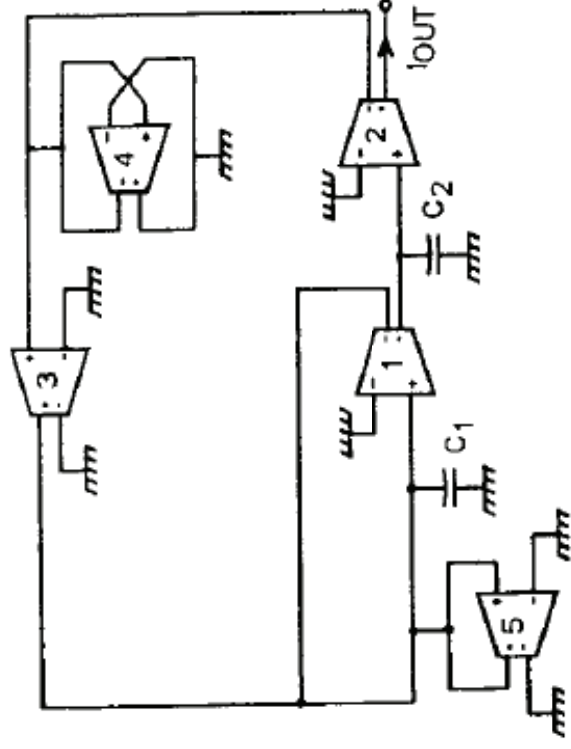

(e)

$b$


$\Omega_0^2$

$$\frac{g_{m1} - g_{m5}}{C_1}$$

$$\frac{g_{m1} g_{m2} g_{m3}}{C_1 C_2 g_{m4}}$$

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

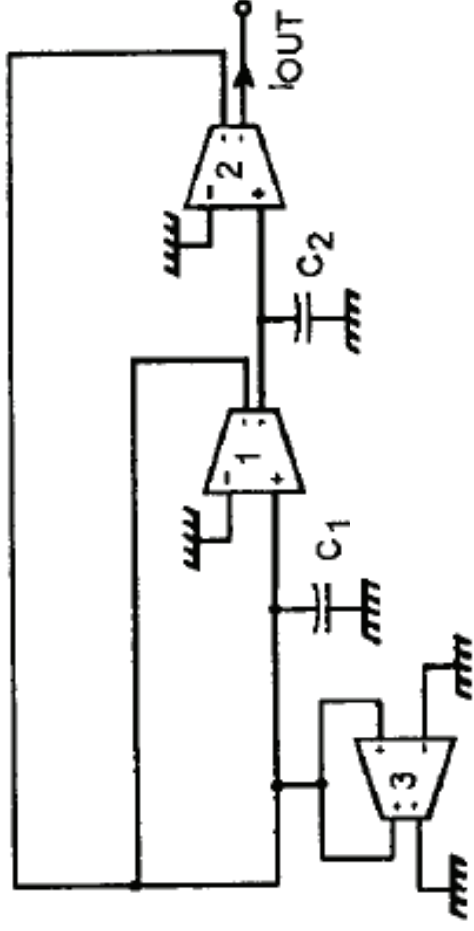


(f)

$b$	$\Omega_0^2$
$\frac{g_{m1} - g_{m3}}{C_1}$	$\frac{g_{m1} \cdot g_{m2}}{C_1 C_2}$

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

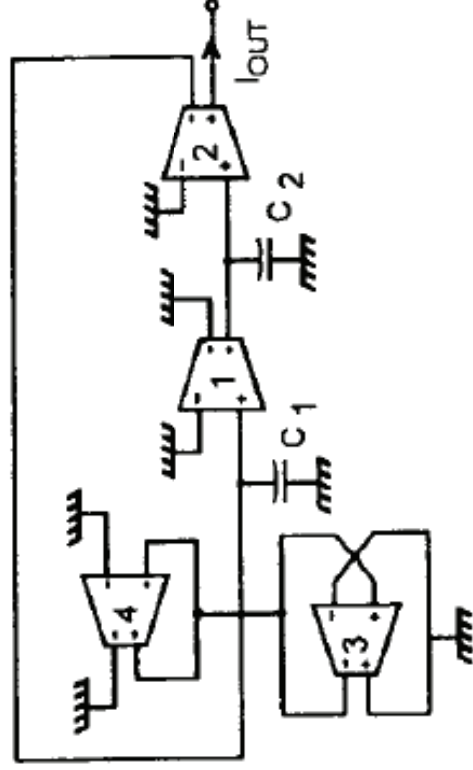

(B)

$b$


$\Omega_0^2$

$$\frac{g_{m3} - g_{m4}}{C_1}$$

$$\frac{g_{m1} \cdot g_{m2}}{C_1 C_2}$$

# Current-Mode Analog Circuit Design


## Realization of DO-OTA-C oscillators

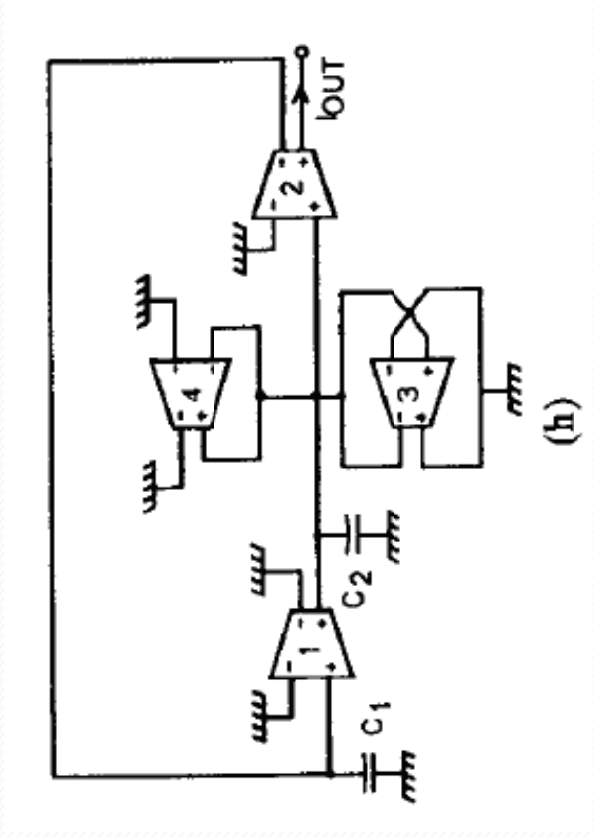

$b$	$\Omega_0^2$
$\frac{g_{m3} - g_{m4}}{C_2}$	$\frac{g_{m1} \cdot g_{m2}}{C_1 C_2}$

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

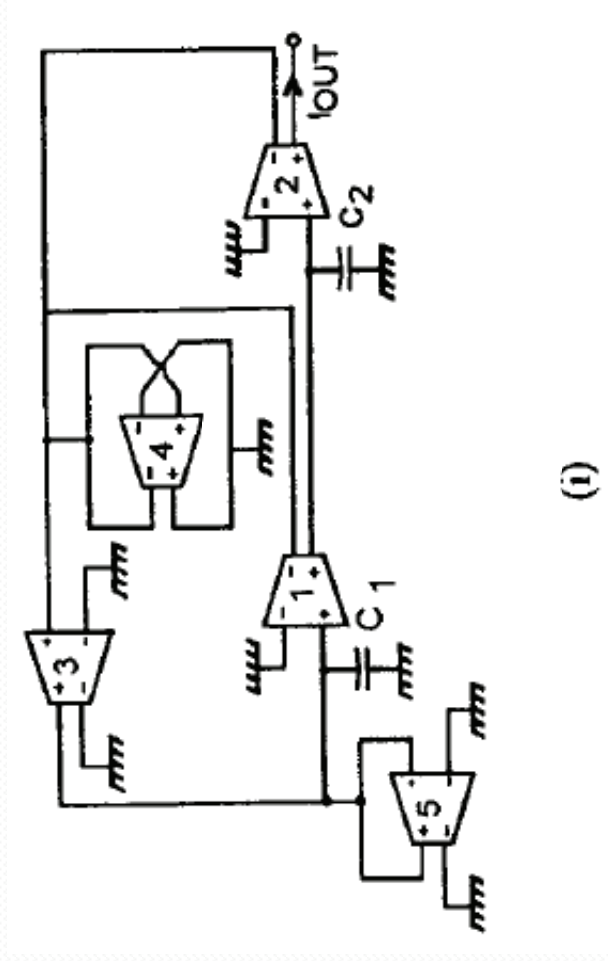

$b$	$\Omega_0^2$
$\frac{g_{m1}g_{m3}}{g_{m4}} - g_{m5}$	$\frac{g_{m1} \cdot g_{m2} \cdot g_{m3}}{C_1 C_2 g_{m4}}$



# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

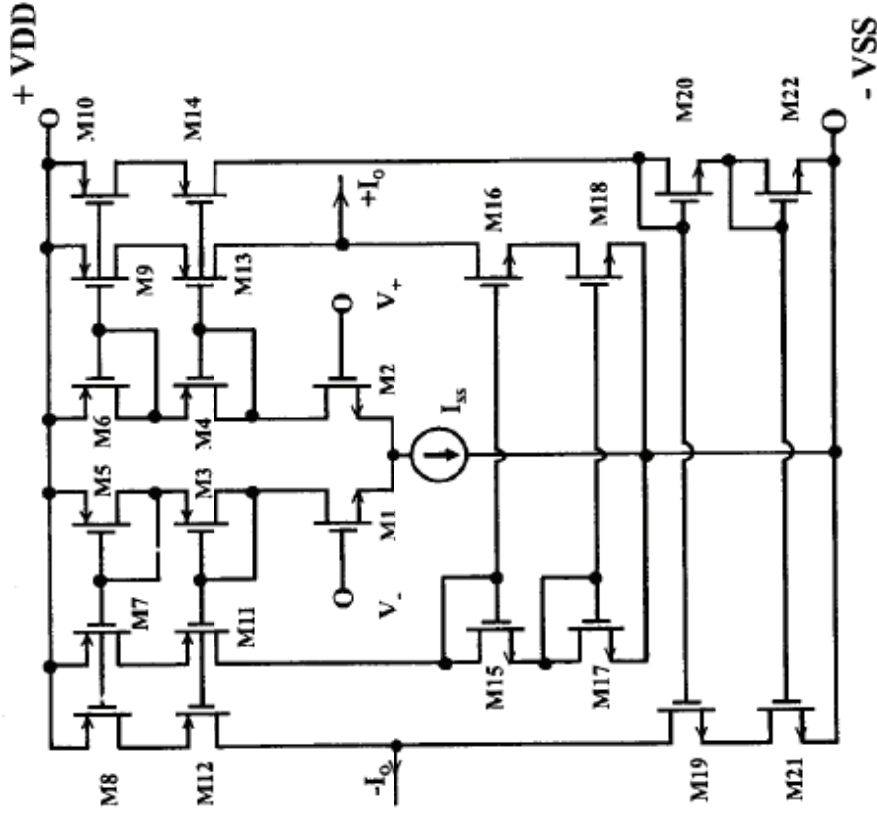


Fig. 3. CMOS cascade DO-OTA structure used for SPICE simulations.

For all simulations the capacitances of C1 and C2 are taken as  $C1 = C2 = 50 \text{ pF}$ .


The biasing current of the OTAs is chosen as  $I_{SS} = 500 \mu\text{A}$  which yields an OTA transconductance of  $450 \mu\text{A/V}$

Theoretical and simulation results of oscillation frequency obtained for proposed oscillator topologies

Topology	Theory	Simulation with actual CMOS DO-OTAs
Fig. 1a	1.342 MHz	1.297 MHz
Fig. 1b	1.433 MHz	1.358 MHz
Fig. 1c	1.488 MHz	1.431 MHz
Fig. 1d	1.472 MHz	1.37 MHz
Fig. 1e	1.433 MHz	1.355 MHz
Fig. 1f	1.433 MHz	1.365 MHz
Fig. 1g	1.433 MHz	1.36 MHz
Fig. 1h	1.433 MHz	1.35 MHz
Fig. 1i	1.537 MHz	1.509 MHz

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

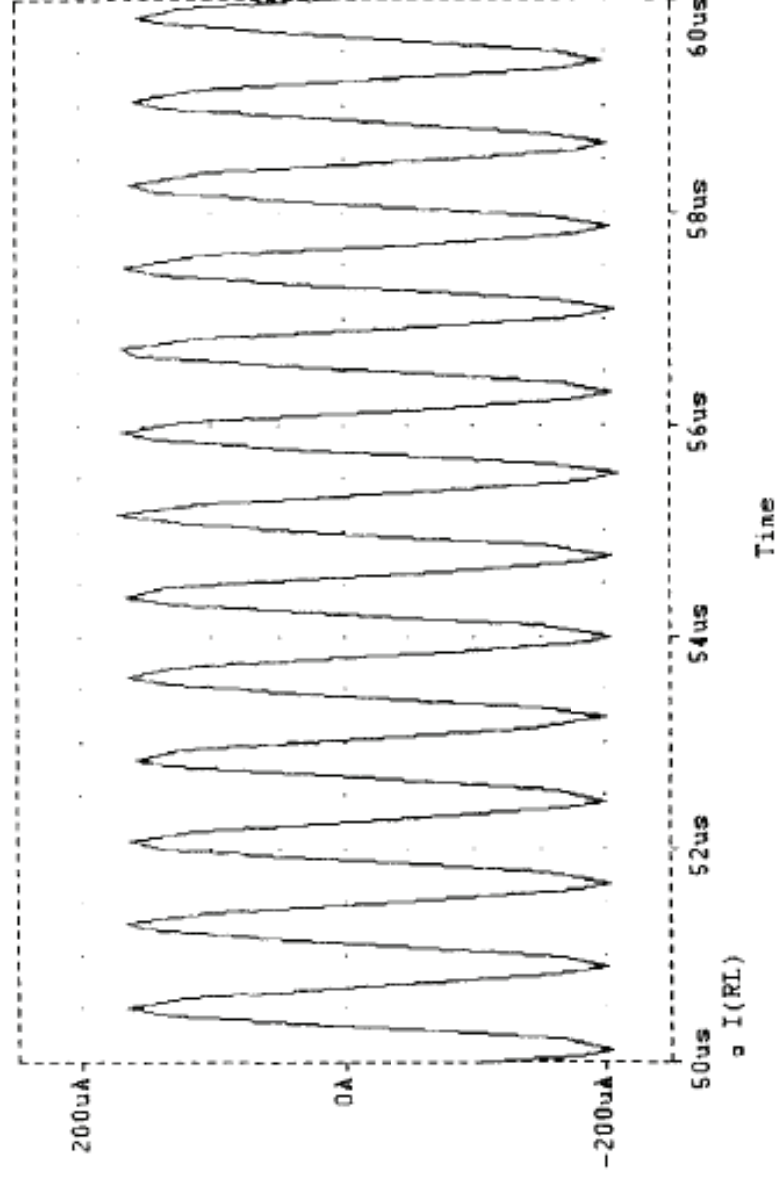

Simulated waveform for output current of oscillator topology illustrated in Fig. 1a,  $C_1 = C_2 = 50\text{ pF}$ ,  $R_L = 1000\ \Omega$ .

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

SPICE simulation results of output current and output voltage performed for different load resistance values

Fig. 1a	$I_{OUTPP}$	$V_{OUTPP}$	Frequency
$R_L = 1 \Omega$	376.255 $\mu$ A	376.255 $\mu$ V	1.297 MHz
$R_L = 1 \text{ k}\Omega$	372.208 $\mu$ A	372.208 mV	
$R_L = 10 \text{ k}\Omega$	398.098 $\mu$ A	3.98098 V	
Fig. 1b			
$R_L = 1 \Omega$	616.392 $\mu$ A	616.392 $\mu$ V	1.358 MHz
$R_L = 1 \text{ k}\Omega$	709.969 $\mu$ A	709.968 mV	
$R_L = 10 \text{ k}\Omega$	668.157 $\mu$ A	6.6815 V	
Fig. 1c			
$R_L = 1 \Omega$	656.413 $\mu$ A	656.413 $\mu$ V	1.431 MHz
$R_L = 1 \text{ k}\Omega$	649.716 $\mu$ A	649.716 mV	
$R_L = 10 \Omega$	602.833 $\mu$ A	6.0283 V	
Fig. 1d			
$R_L = 1 \Omega$	1006.509 $\mu$ A	1006.509 $\mu$ V	1.37 MHz
$R_L = 1 \text{ k}\Omega$	1007.313 $\mu$ A	1007.313 mV	
$R_L = 5 \text{ k}\Omega$	975.762 $\mu$ A	4.8788 V	
Fig. 1e			
$R_L = 1 \Omega$	718.012 $\mu$ A	718.012 $\mu$ V	1.355 MHz
$R_L = 1 \text{ k}\Omega$	720.880 $\mu$ A	720.880 mV	
$R_L = 10 \text{ k}\Omega$	688.346 $\mu$ A	6.8835 V	

# Current-Mode Analog Circuit Design

## Realization of DO-OTA-C oscillators

Fig. 1f

$R_L = 1\Omega$  731.044  $\mu\text{A}$  731.451  $\mu\text{V}$  1.365 MHz

$R_L = 1\text{k}\Omega$  774.261  $\mu\text{A}$  774.261 mV

$R_L = 10\text{k}\Omega$  747.489  $\mu\text{A}$  7.4761 V

Fig. 1g

$R_L = 1\Omega$  714.922  $\mu\text{A}$  714.922  $\mu\text{V}$  1.36 MHz

$R_L = 1\text{k}\Omega$  736.624  $\mu\text{A}$  736.624 mV

$R_L = 10\text{k}\Omega$  699.877  $\mu\text{A}$  6.796 V

Fig. 1h

$R_L = 1\Omega$  679.074  $\mu\text{A}$  679.074  $\mu\text{V}$  1.35 MHz

$R_L = 1\text{k}\Omega$  704.037  $\mu\text{A}$  704.037 mV

$R_L = 10\text{k}\Omega$  675.921  $\mu\text{A}$  6.7592 V

Fig. 1i

$R_L = 1\Omega$  642.317  $\mu\text{A}$  642.317  $\mu\text{V}$  1.509 MHz

$R_L = 1\text{k}\Omega$  650.343  $\mu\text{A}$  650.343 mV

$R_L = 10\text{k}\Omega$  576.071  $\mu\text{A}$  5.7607 V

# Current-Mode Analog Circuit Design

## Realization of FTFN-Based Current-Mode Oscillators


- **Current-Mode High Output Impedance Sinusoidal Oscillator Configuration Employing Single FTFN**
- a new oscillator configuration providing high output impedance,
- employing single FTFN, five resistors and two capacitors.

The proposed circuits permit

- Noninteractive control of oscillation frequency and
- oscillation condition,
- low active and passive sensitivities

# Current-Mode Analog Circuit Design
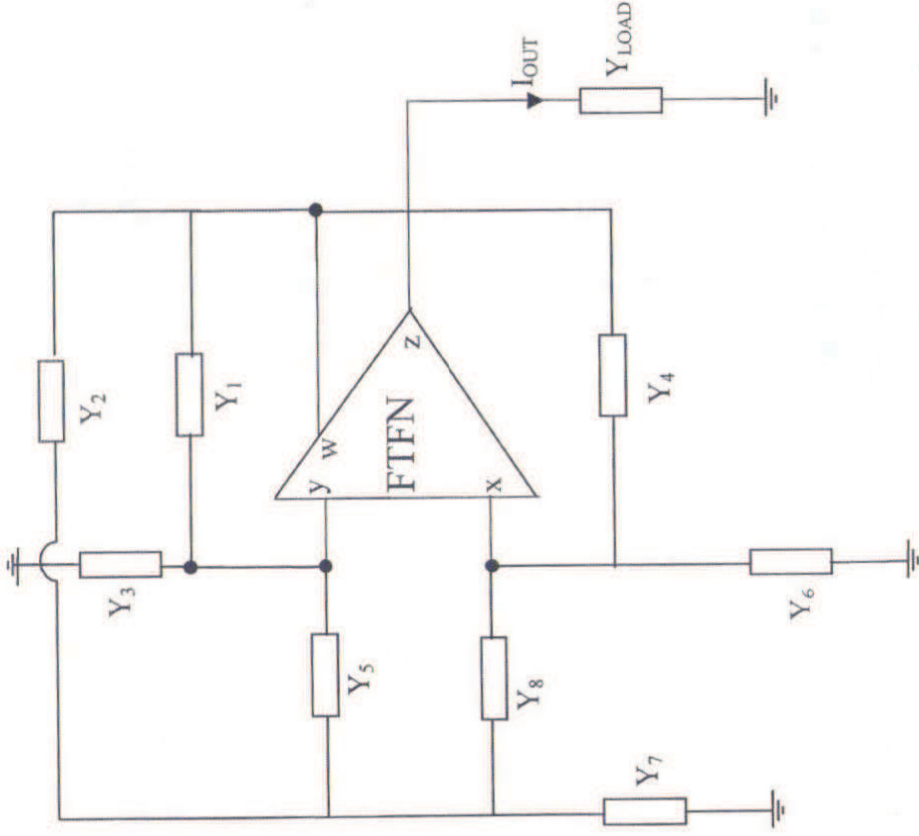
## Realization of FTFN-Based Current-Mode Oscillators



$$\begin{aligned} & Y_1 Y_6 (Y_2 + Y_5 + Y_7 + Y_8) + Y_1 Y_7 Y_8 + Y_2 Y_5 Y_6 \\ & - Y_3 Y_4 (Y_2 + Y_5 + Y_7 + Y_8) \\ & - Y_4 Y_5 Y_7 - Y_2 Y_3 Y_8 = 0 \end{aligned} \quad (2)$$

The general form of the proposed oscillator configuration.

# Current-Mode Analog Circuit Design

## Realization of FTFN-Based Current-Mode Oscillators

Taking the FTFN non-idealities into consideration, the port relations

$$V_x = \beta V_y \quad I_{o2} = \alpha I_{o1}$$

where  $\beta = 1 - \varepsilon_v$ ,  $\varepsilon_v$  ( $|\varepsilon_v| \ll 1$ ) denotes voltage tracking error and  $\alpha = 1 - \varepsilon_i$ ,  $\varepsilon_i$  ( $|\varepsilon_i| \ll 1$ ) denotes current tracking error of the FTFN respectively.

$$\begin{aligned} & \beta[Y_1 Y_6(Y_2 + Y_5 + Y_7 + Y_8) + Y_1 Y_7 Y_8 + Y_2 Y_5 Y_6] \\ & - Y_3 Y_4(Y_2 + Y_5 + Y_7 + Y_8) - Y_4 Y_5 Y_7 - Y_2 Y_3 Y_8 \\ & - (\beta - 1)[Y_4(Y_1 Y_2 + Y_1 Y_5 + Y_1 Y_8 + Y_1 Y_7 \\ & + Y_2 Y_5 + Y_5 Y_8) \\ & + Y_8(Y_1 Y_2 + Y_1 Y_5 + Y_2 Y_5)] = 0 \end{aligned}$$

# Current-Mode Analog Circuit Design

## Realization of FTFN-Based Current-Mode Oscillators

- From equation (2) many oscillators can be derived.
- In this study two subsets of possible circuits are presented.
- Table 1 shows the selected passive elements for single resistance controlled oscillators.
- It is clearly observed from Table 1 for all proposed oscillators, oscillation condition and oscillation frequency can be independently adjusted by a resistor.

Table 1. Oscillation condition and oscillation frequency of single resistance-controlled oscillators (2C-5R).

No.	$Y_1$	$Y_2$	$Y_3$	$Y_4$	$Y_5$	$Y_6$	$Y_7$	$Y_8$	Oscillation Condition	Oscillation Frequency
1	$G_1$	$G_2$	—	$G_4$	$G_5$	$G_6$	$G_7$	$G_8$	$C_8G_1G_6 + C_7G_1G_6 = C_7G_5G_4$	$\omega_0 = \sqrt{\frac{G_6(G_1G_2+G_1G_5+G_2G_5)}{C_7C_8G_1}}$
2	$G_1$	$G_2$	$G_3$	—	$G_5$	$G_6$	$G_7$	$G_8$	$C_7G_1G_6 + C_8G_1G_6 = C_8G_3G_2$	$\omega_0 = \sqrt{\frac{G_6(G_1G_2+G_1G_5+G_2G_5)}{C_7C_8G_1}}$
3	—	$C_2$	$G_3$	$G_4$	$G_5$	$G_6$	$G_7$	$G_8$	$C_8G_3G_4 + C_2G_3G_4 = C_2G_6G_5$	$\omega_0 = \sqrt{\frac{G_4(G_3G_7+G_5G_7+G_3G_5)}{C_2C_8G_3}}$
4	$G_1$	$C_2$	$G_3$	$G_4$	$G_5$	—	$G_7$	$G_8$	$C_8G_3G_4 + C_2G_3G_4 = C_8G_1G_7$	$\omega_0 = \sqrt{\frac{G_4(G_3G_7+G_5G_7+G_3G_5)}{C_2C_8G_3}}$
5	—	$G_2$	$G_3$	$G_4$	$C_5$	$G_6$	$C_7$	$G_8$	$C_5G_3G_4 + C_7G_3G_4 = C_5G_2G_6$	$\omega_0 = \sqrt{\frac{G_3(G_2G_8+G_4G_8+G_2G_4)}{C_5C_7G_4}}$
6	$G_1$	$G_2$	$G_3$	$G_4$	$C_5$	—	$C_7$	$G_8$	$C_5G_3G_4 + C_7G_3G_4 = C_7G_1G_8$	$\omega_0 = \sqrt{\frac{G_3(G_2G_8+G_4G_8+G_2G_4)}{C_5C_7G_4}}$
7	$G_1$	$C_2$	—	$G_4$	$C_5$	$G_6$	$G_7$	$G_8$	$C_2G_1G_6 + C_5G_1G_6 = C_5G_4G_7$	$\omega_0 = \sqrt{\frac{G_1(G_7G_8+G_6G_8+G_6G_7)}{C_2C_5G_6}}$
8	$G_1$	$C_2$	$G_3$	—	$C_5$	$G_6$	$G_7$	$G_8$	$C_2G_1G_6 + C_5G_1G_6 = C_2G_3G_8$	$\omega_0 = \sqrt{\frac{G_1(G_7G_8+G_6G_8+G_6G_7)}{C_2C_5G_6}}$



# Current-Mode Analog Circuit Design

## Realization of FTFN-Based Current-Mode Oscillators

Table 2 shows the selected passive elements of single frequency oscillators in which the number of resistors is reduced by one compared to the oscillators in Table 1.

Table 2. Oscillation condition and oscillation frequency of single frequency oscillators (2C-4R).

No.	$Y_1$	$Y_2$	$Y_3$	$Y_4$	$Y_5$	$Y_6$	$Y_7$	$Y_8$	Oscillation Condition	Oscillation Frequency
1	$G_1$	$G_2$	$G_3$	—	—	$G_6$	$C_7$	$C_8$	$C_8G_1G_6 + C_7G_1G_6 = C_8G_3G_2$	$\omega_0 = \sqrt{\frac{G_2G_6}{C_8C_7}}$
2	—	$C_2$	$G_3$	$G_4$	$G_5$	$G_6$	—	$C_8$	$C_2G_3G_4 + C_8G_3G_4 = C_2G_5G_6$	$\omega_0 = \sqrt{\frac{G_4G_5}{C_2C_8}}$
3	—	$G_2$	$G_3$	$G_4$	$C_5$	$G_6$	$C_7$	—	$C_5G_3G_4 + C_7G_3G_4 = C_5G_2G_6$	$\omega_0 = \sqrt{\frac{G_2G_4}{C_8C_7}}$
4	$G_1$	$C_2$	$G_3$	—	$C_5$	$G_6$	—	$G_8$	$C_2G_1G_6 + C_5G_1G_6 = C_2G_3G_8$	$\omega_0 = \sqrt{\frac{G_1G_8}{C_2C_5}}$
5	$G_1$	—	—	$G_4$	$G_5$	$G_6 + C_6$	$C_7$	—	$C_6G_1G_5 + C_7G_1G_6 = C_7G_4G_5$	$\omega_0 = \sqrt{\frac{G_6G_4}{C_6C_7}}$
6	$G_1$	$C_2$	$G_3$	—	—	$C_6$	$G_7$	$G_8$	$C_6G_1G_8 + C_6G_1G_7 = C_2G_3G_8$	$\omega_0 = \sqrt{\frac{G_8G_7}{C_2C_6}}$
7	$G_1$	—	—	$G_4$	$C_5$	$G_6 + C_6$	$G_7$	—	$C_5G_1G_6 + C_6G_1G_7 = C_5G_4G_7$	$\omega_0 = \sqrt{\frac{G_6G_7}{C_5C_6}}$
8	$G_1$	—	$G_3$	$G_4 + C_4$	—	—	$C_7$	$G_8$	$C_4G_3G_8 + C_7G_3G_4 = C_7G_1G_8$	$\omega_0 = \sqrt{\frac{G_4G_8}{C_4C_7}}$

# Current-Mode Analog Circuit Design

## Realization of FTFN-Based Current-Mode Oscillators


### Experimental Results and Discussions

- To confirm theoretical analysis, all the proposed circuits were experimentally tested.
- SPICE simulations were performed for the proposed circuits.
- The FTFN circuit was constructed with two AD844 IC of Analog Devices as shown in Fig. 3.
- The supply voltages were taken as  $V_{DD} = 10\text{ V}$  and  $V_{SS} = -10\text{ V}$ .
- As an example, the experimental wave-form of second circuit in Table 1 is shown in Fig. 4.
- The passive elements of the oscillator were chosen as  $R_1 = R_2 = R_5 = R_6 = 10\text{ k}\Omega$ ,  $R_3 = 5\text{ k}\Omega$ ,  $C_7 = C_8 = 1\text{ nF}$  and the oscillation frequency was measured as 28 kHz.

# Current-Mode Analog Circuit Design

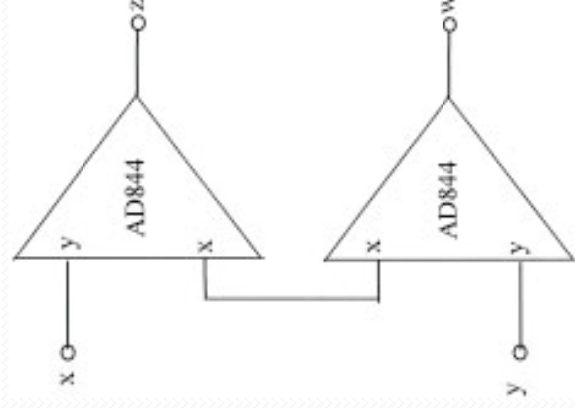
## Realization of FTFN-Based Current-Mode Oscillators

Realization of an FTFN with commercial AD844 IC (used as positive type CCII).




# Current-Mode Analog Circuit Design
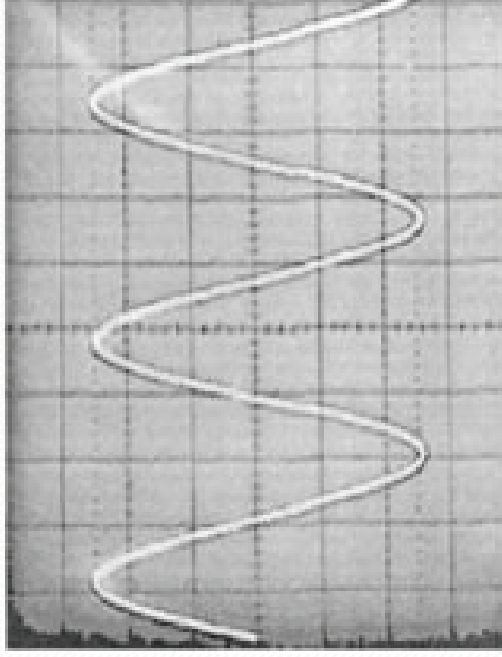
## Realization of FTFN-Based Current-Mode Oscillators



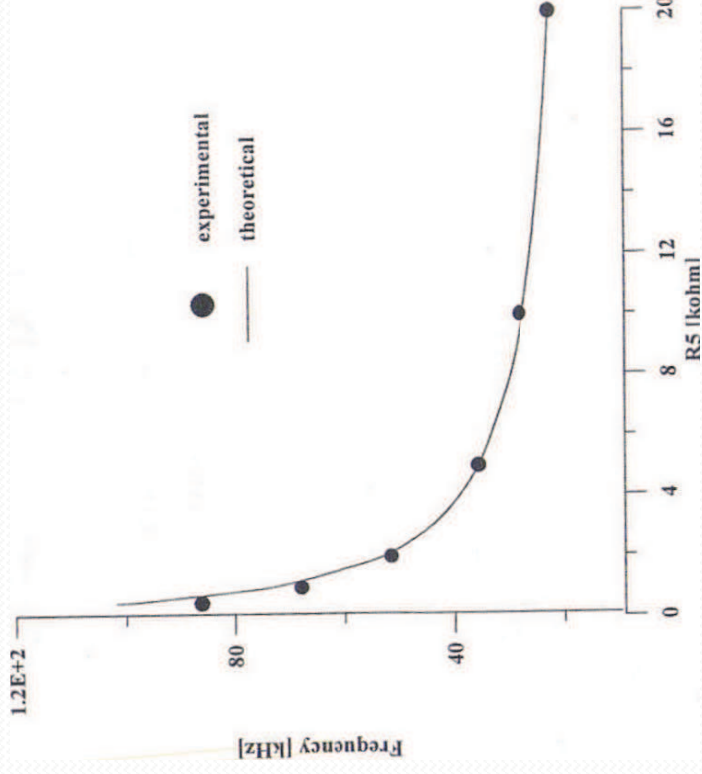Experimental wave-form of the second circuit in Table 1 vertical: 1 div.0.1 mA, horizontal: 1 div.10).



Variation of the oscillation frequency with R5 of the second oscillator circuit given in Table 1.



## References

- A. Ozpinar, Yeni DO-OTA-C osilattir topolojileri, M.Sc. Thesis, Istanbul Technical University, Institute of Science and Technology, 1998.
- H. Kuntman, A. Özpinar, On the realization of DO-OTA-C oscillators, *Microelectronics Journal* 29 (1998) 9.91-997
- U. Cam, A. Toker, O. Cicekoglu and H. Kuntman, Current-Mode High Output Impedance Sinusoidal Oscillator Configuration Employing Single FTFN, *Analog Integrated Circuits and Signal Processing*, 24, 231-238, 2000.