

# The Current Conveyors, Current Followers and Current-mode Feedback Amplifiers

Çağlar Kılıkçier

504081236

# CCI

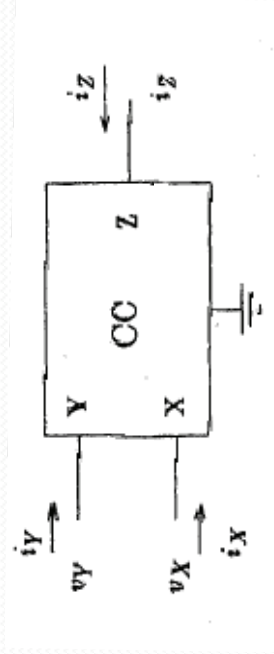


Figure 1: Black Box of CC

$$\begin{bmatrix} i_Y \\ v_X \\ i_Z \end{bmatrix} = \begin{bmatrix} 0 & a & 0 \\ 1 & 0 & 0 \\ 0 & \pm 1 & 0 \end{bmatrix} \begin{bmatrix} v_Y \\ i_X \\ v_Z \end{bmatrix}$$

Figure 2: Hybrid equations the CCI

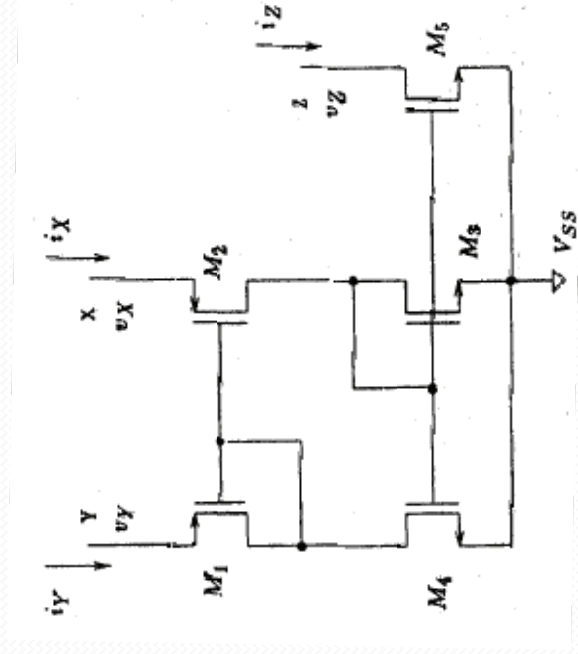


Figure 3: First order CMOS implementation CCI



# CCI

- Operation of the device can be described as if a voltage is applied to input terminal Y, an equal potential will appear on the input terminal X.
- As well, an input current  $I$  being forced into terminal X will result in an equal amount of current flowing into terminal Y.
- As a result the current  $I$  will be conveyed to output terminal Z which has the characteristics of a current source of value  $I$  with high output impedance that we can figure out all from figure 1, 2 and 3

# CCII


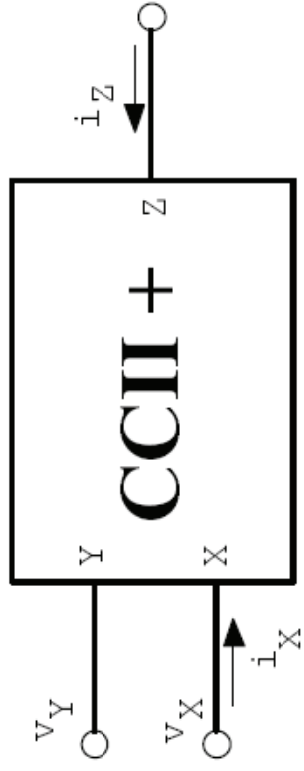


Figure 4: CCII+ and CCII-

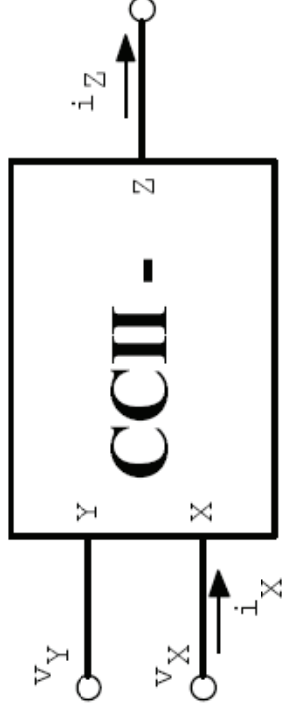

$$\begin{bmatrix} i_Y \\ v_X \\ i_Z \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 \\ 1 & 0 & 0 \\ 0 & \pm 1 & 0 \end{bmatrix} \begin{bmatrix} v_Y \\ i_X \\ v_Z \end{bmatrix}$$

Figure 5: Hybrid equations the CCII

$$\begin{aligned} v_X &= v_Y \\ i_Y &= 0 \\ i_Z &= \mp i_X \end{aligned}$$

# CCII

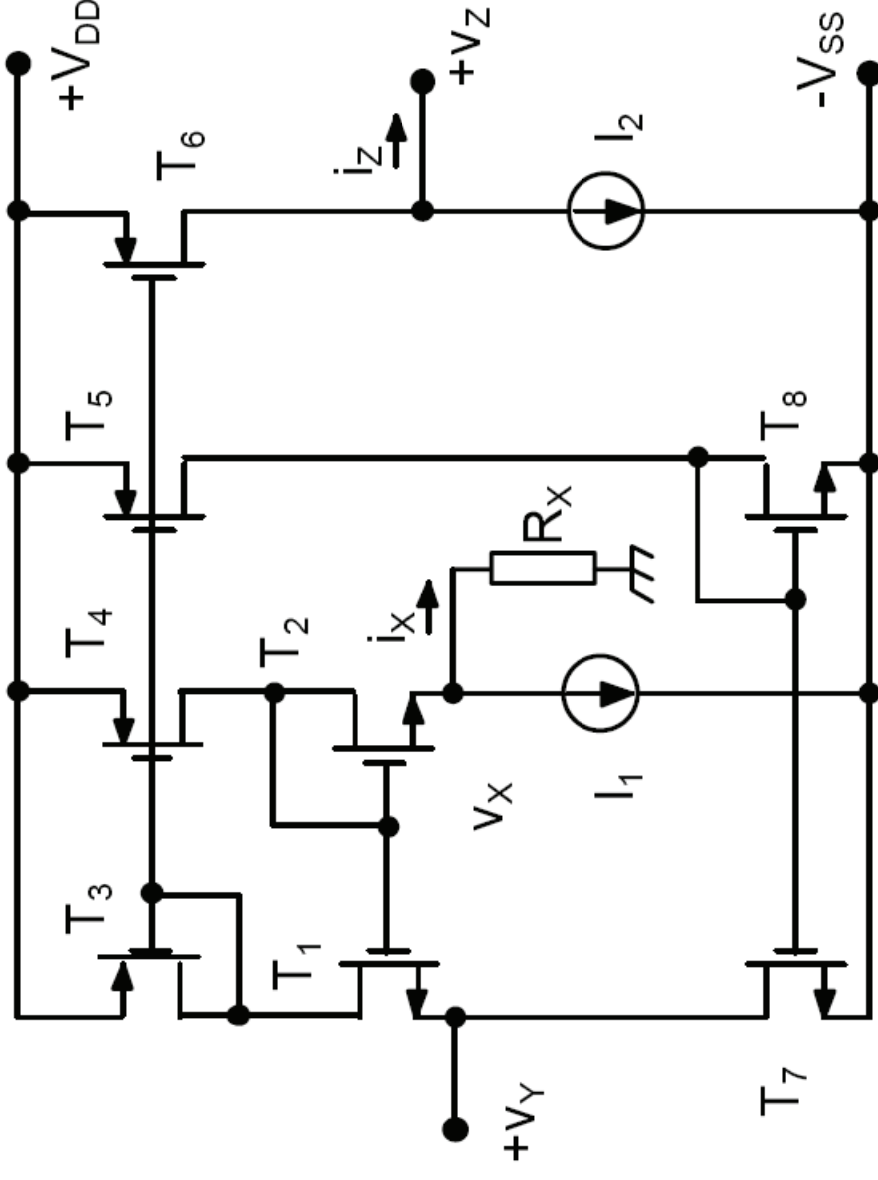


Figure 6: CMOS implementation CCII+



# CCII

- $T_3$ - $T_6$  PMOS transistors and  $T_7$ - $T_8$  NMOS transistors are used as current mirrors.
- $I_1$  current source creates the biasing current for the circuit.
- Assuming that transistors are equal, current mirrors have unity gain and all of the transistors are working in active region

# CCII

- We can describe the circuit as the  $T_3 - T_4$  transistors accomplishes driving equal currents from  $T_1$  and  $T_2$  so  $V_{gs1} = V_{gs2}$  which is meaning  $V_Y$  will be equal to  $V_X$ .
- $I_X$  current which is flowing from  $R_X$  also flows from  $T_2$  transistor and  $T_3 - T_4$  current mirror.
- In case of  $V_X > 0$  current  $I_X = V_X / R_X$  will flow out from  $T_2$ 's source and so  $T_3 - T_4$  current sources value will be  $I_1 + i_X$ .



## CCII

- This current will be reflected to the  $T_1$ 's source through  $T_5$  transistor and  $T_7$ - $T_8$  current mirror to compensate source current changes of  $T_1$  so  $I_Y$  will be zero all the time .
- At the same time  $T_6$  transistor will reflect  $I_1+i_X$  current to the  $Z$  node in case of  $I_1$  being equal to the  $I_2$ ,  $i_Z=i_X$  current flows out from node  $Z$





## CCII

- As noticeable  $i_z$  currents direction is same as the  $i_x$  current so we call this type of circuits positive current conveyors (CCII+).
- If  $i_z$  currents direction is opposite of the  $i_x$  current then we call it negative current conveyors (CCII-).
- An CCII- can be described similarly and it is shown figure 7.

# CCII

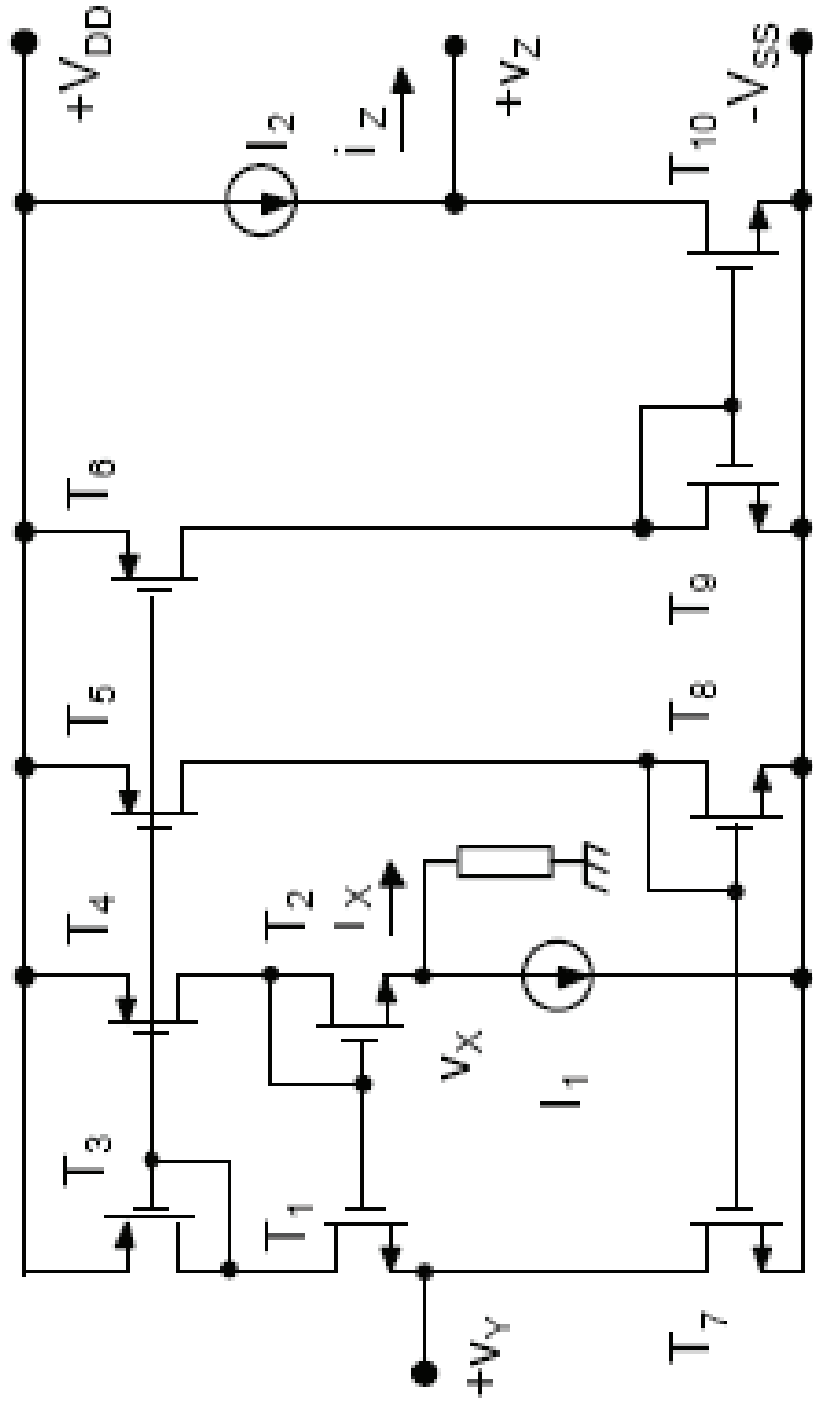


Figure 7: CMOS implementation CCII-

# CCII

- Also there are other topologies which we can create  
CCII's these are shown in figures 8,9 and 10.

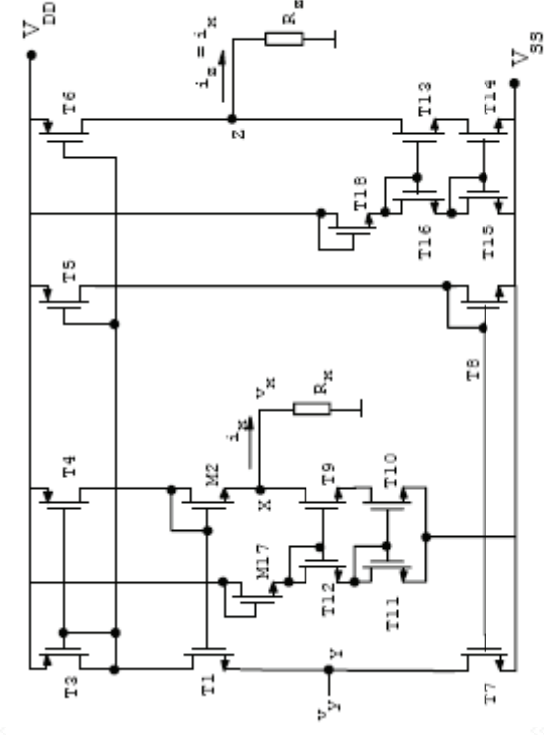
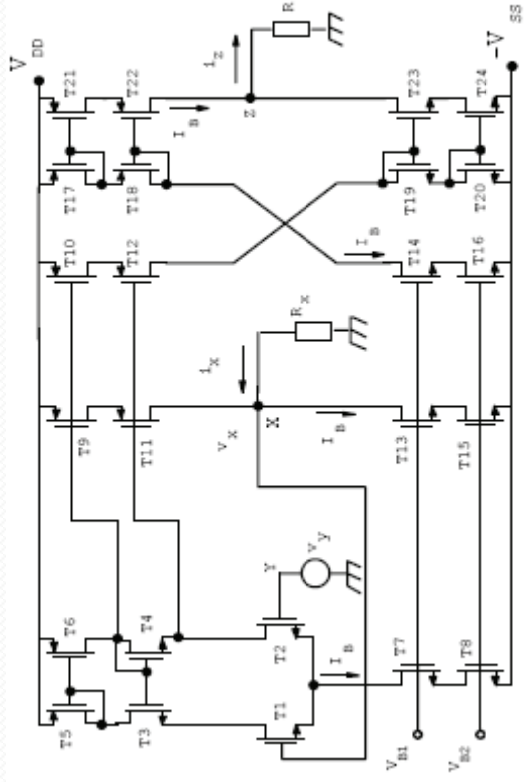


Figure 8: CMOS implementation CCII- Figure 9: CMOS implementation CCII+

# CCII

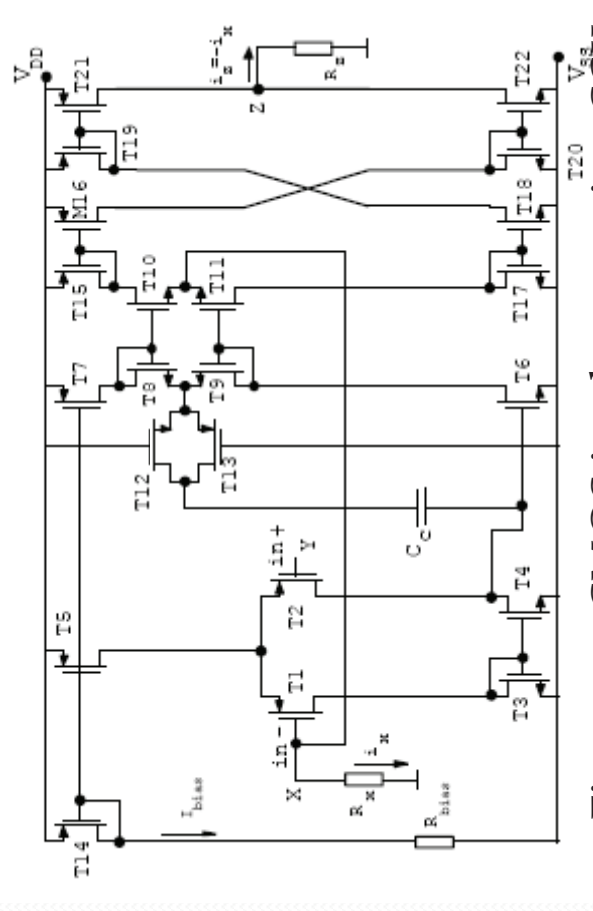


Figure 10: CMOS implementation CCII-

# CCII

- Last but not the least there are current conveyor realisations using VOA's

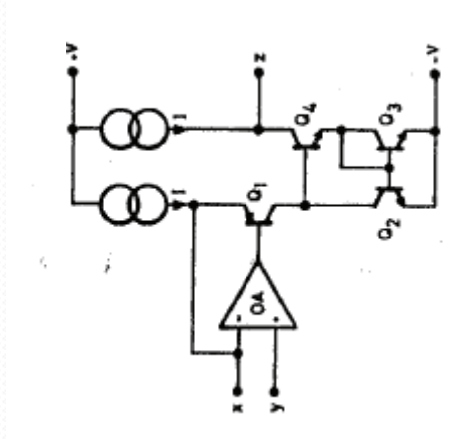


Figure 11: Bakhitiar and Aronhimes's CC

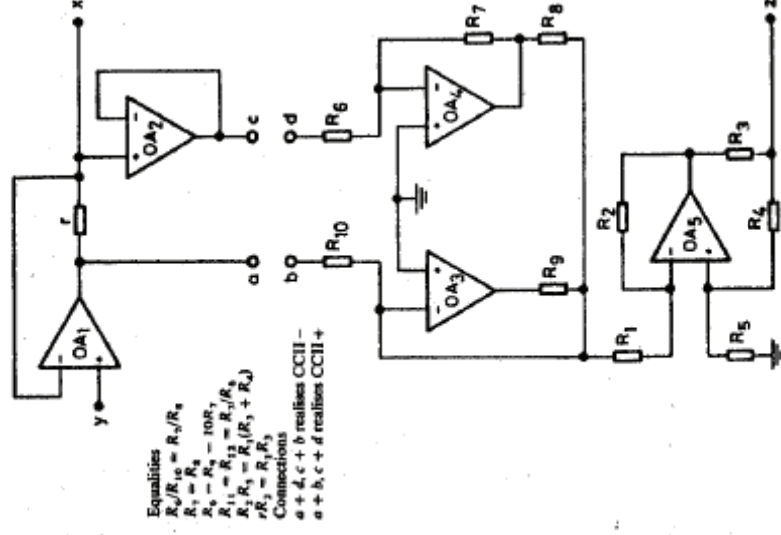


Figure 12: Pookaiyaudom and Srisarakham's single ended CCII+

# CCII Applications

	Characterization	Realization Using Current Conveyor
2-Port Realized		
Voltage-Controlled Voltage-Source	$G = \begin{bmatrix} 0 & 0 \\ j & 0 \end{bmatrix}$	
Voltage-Controlled Current-Source	$Y = \begin{bmatrix} 0 & 0 \\ g & 0 \end{bmatrix}$	
Current-Controlled Current-Source	$H = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix}$	
Current-Controlled Voltage-Source	$Z = \begin{bmatrix} 0 & 0 \\ r & 0 \end{bmatrix}$	
NIC	$G = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$	
NIV	$Y = \begin{bmatrix} 0 & g^1 \\ g^2 & 0 \end{bmatrix}$	
Gyrator	$Y = \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix}$	

Figure 13: Applications of CCII to active network synthesis

# CCII Applications

Functional Element	Function	Realization Using Current Conveyor
Current Amplifier	$I_o = (R_1/R_2)I_i$	
Current Differentiator	$I_o = CR \frac{dI_i}{dt}$	
Current Integrator	$I_o = 1/CR \int I_i dt$	
Current Summer	$I_o = - \sum_j^n I_j$	
Weighted Current Summer	$I_o = - \sum_j^n I_j R_j/R$	

Figure 14: Applications of CCII to analog computaion



# CCII Applications

- Also with the adjoint network concept Active-RC circuits can be converted to equivalent current conveyor circuits
- Adjoint network concept simply means we can change the voltage mode circuits to current mode circuits by reciprocal or interreciprocal networks



# CCII Applications(Adjoint network concept )

## Reciprocal network

- Same network can be used as in figure 15

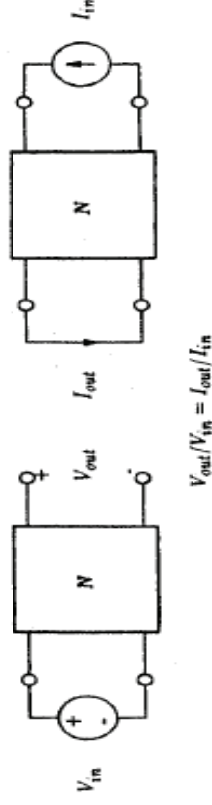


Figure 15: Reciprocal N network

## Interreciprocal network

- A adjoint network  $N_A$  can be used as in figure 16

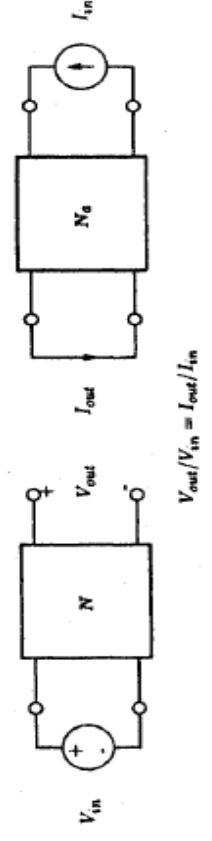


Figure 16: Interreciprocal N and  $N_A$  network

# CCII Applications(Adjoint network concept )

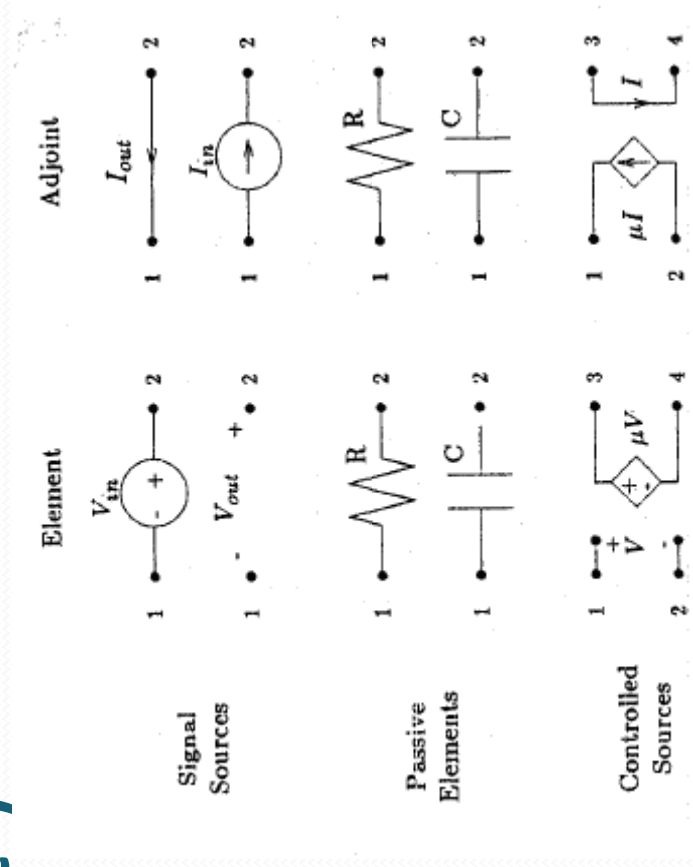


Figure 17: Some electrical elements and their corresponding adjoint elements

# CCII Applications(Adjoint network concept )

- In figure 18 we see a voltage mode circuit with adjoint network concept. we can change this circuit into the circuit in figure 19

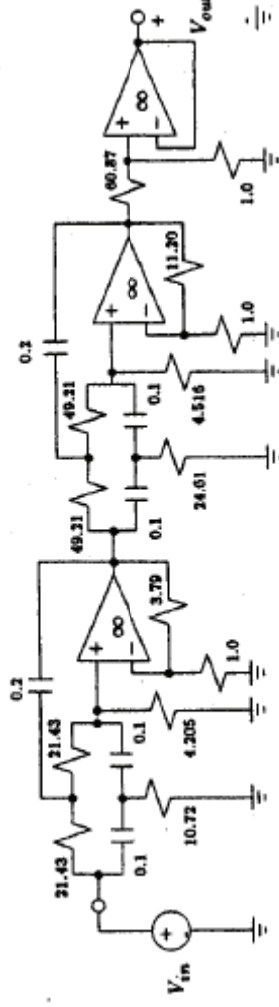


Figure 18: 4-th order HP elliptic filter as a cascade op-amp

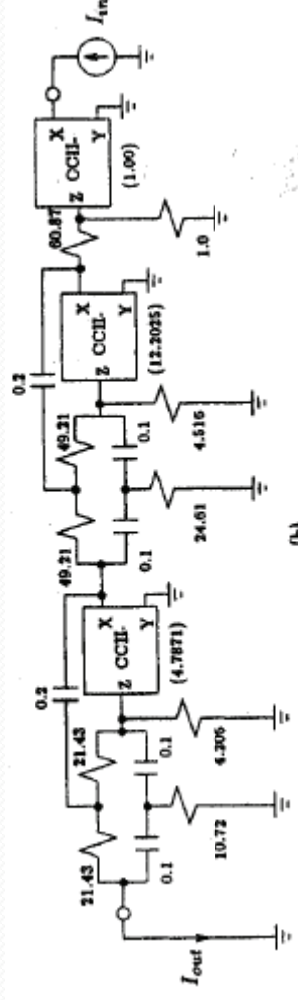


Figure 19: 4-th order HP elliptic filter as a corresponding CCII equivalent



# Current Followers

- Current followers are structures that are configured into unity gain current controlled current sources.
- They are circuits with extremely low input impedance, extremely high output impedance.
- It is expected to produce a current drive to load equal in value to the short circuit current obtainable from the input signal source.
- Generally they can be categorised into two groups.



# Current Followers

- One group considers techniques that make two equal in-phase output currents available by current mirroring the VOA's supply currents with respect to the positive and negative supply voltages, and summing them to a single ended output.
- Figure 20 is an example of this group, an supply current sensing current follower, its performance can be given as  $i_{O1}/i_S = 1/(1 + jf(K_1 + 1)/GB)$  where  $K_1$  is  $(R_O + R_L)/R_O$ .

# Current Followers

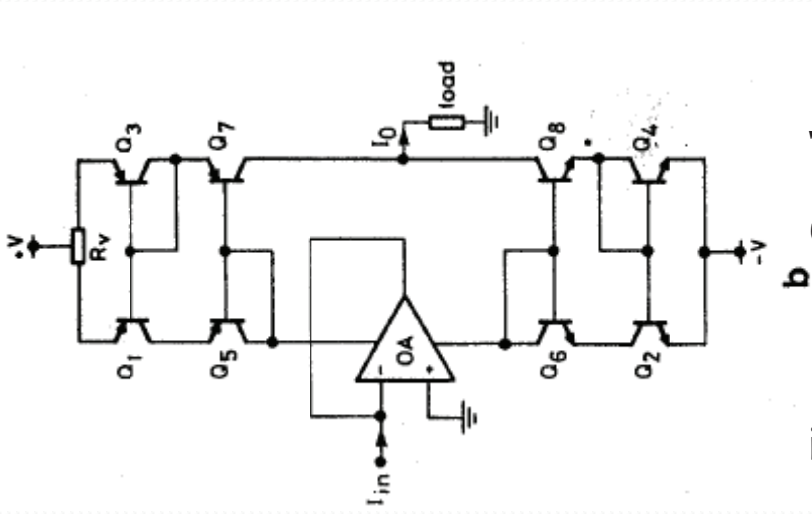


Figure 20: Supply current sensing current follower

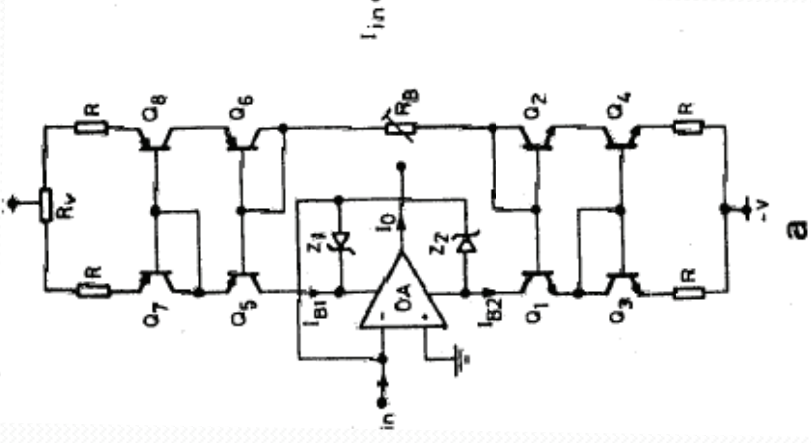


Figure 21: Floating VOA current follower



# Current Followers

- The other group provides the VOA with two equal but opposite output currents, with characteristics similar to that of a floating VOA (Nullor).
- An example of this group circuit, floating VOA current follower shown in figure 21.
- Current transfer performance of the circuit in figure 21 can be given  $i_o/i_s = \lambda(j\omega) / (1+jf/GB) \times (1+jf.K_2/GB)$  where  $\lambda(j\omega)$  is the frequency dependent current transfer of the current mirror and  $K_2$  is  $(1+R_O/R_S)$  assuming bandwidth is determined by the VOA.

# Current-Mode Feedback

## Amplifiers (Translinear class AB current amplifier)

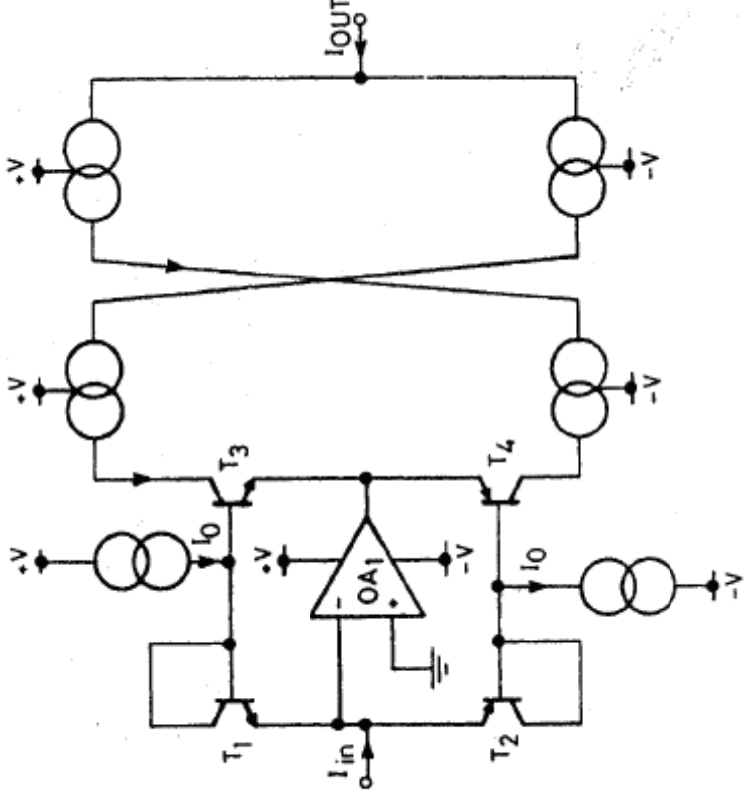


Figure 22: Translinear class AB current amplifier



# Current-Mode Feedback

## Amplifiers<sub>(Translinear class AB current amplifier)</sub>

- In figure 22 an operational amplifier OA1 is embedded within the translinear cell from T1 to T4.
- The d.c. Current source and sink ensures that all four BJTs are actively biased with current  $I_O$ , providing the desirable class AB input/output performance.
- The voltage following action of the translinear cell provides negative feedback around OA1 ensuring that the output of OA1 is a virtual ground and the input impedance of the amplifier is low.

# Current-Mode Feedback

## Amplifiers (Translinear class AB current amplifier)

- Current gain of this circuit  $A = \beta_3 = \beta_4 = \beta$  is provided by the transistors  $T_3$  and  $T_4$ .
- Four current mirrors are needed to translate the phase-split output currents from  $T_3$  and  $T_4$  to the output node and create the correct phase relationship.
- Total current gain of this circuit can be given  $\lambda^2 \beta$  and the output impedance is determined by the  $R_O$  of the current mirrors.

# Current-Mode Feedback Amplifiers

- In figure 23 we are seeing an alternative feedback structure to achieve voltage gain

$$V_{O}/V_{in} = -(\lambda/(\lambda + 1)) \cdot R_2/R_1 \quad \text{and}$$

output resistance

$$R_{out} = R_2 / (\lambda + 1)$$

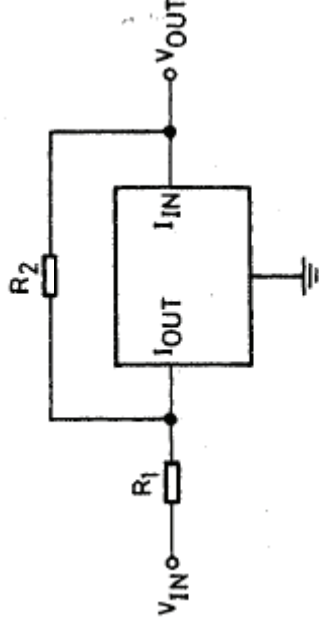


Figure 23: Alternative closed-loop voltage amplifier

# Current-Mode Feedback

## Amplifiers (Transimpedance Operational Amplifier)

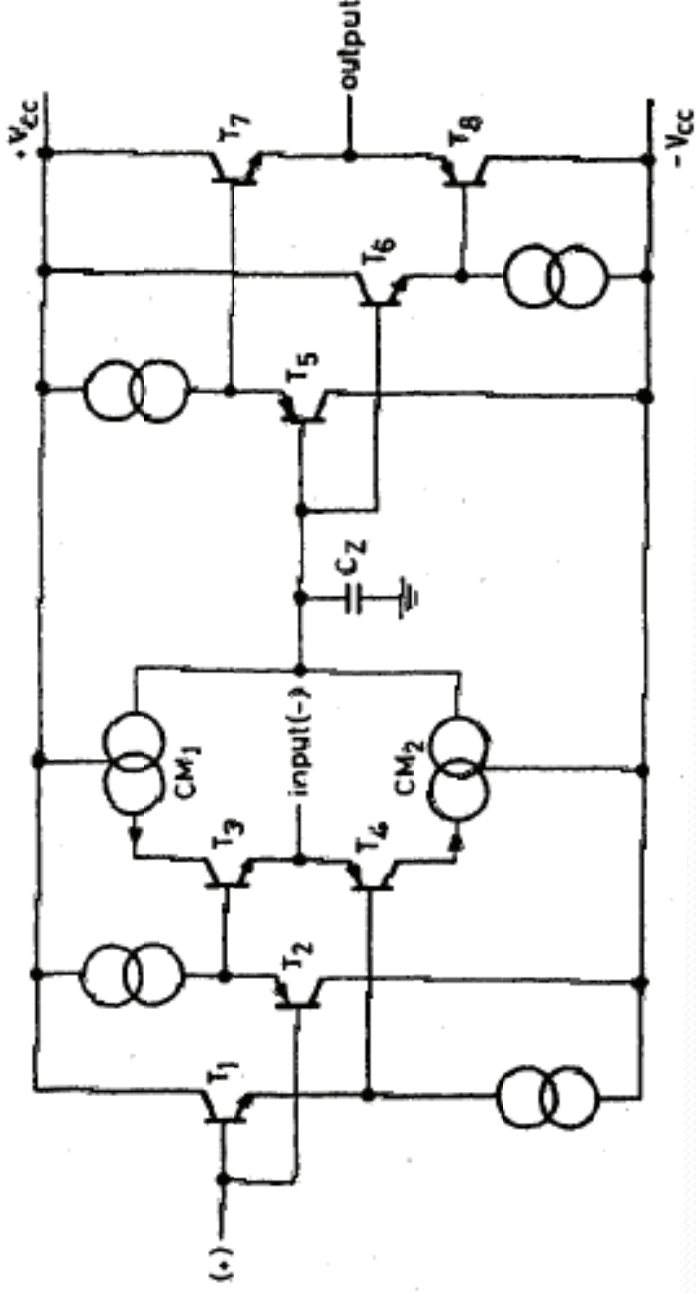


Figure 24: "Current feedback" transimpedance operational amplifier



# Current-Mode Feedback

## Amplifiers (Transimpedance Operational Amplifier)

- Examining the circuit in figure 24, noninverting input corresponds to the Y terminal of the current conveyor and inverting input corresponds to the X input of current conveyor and the Z node, although not accessible in the device, is the output mode of the current conveyor.

# Current-Mode Feedback Amplifiers(OFC)

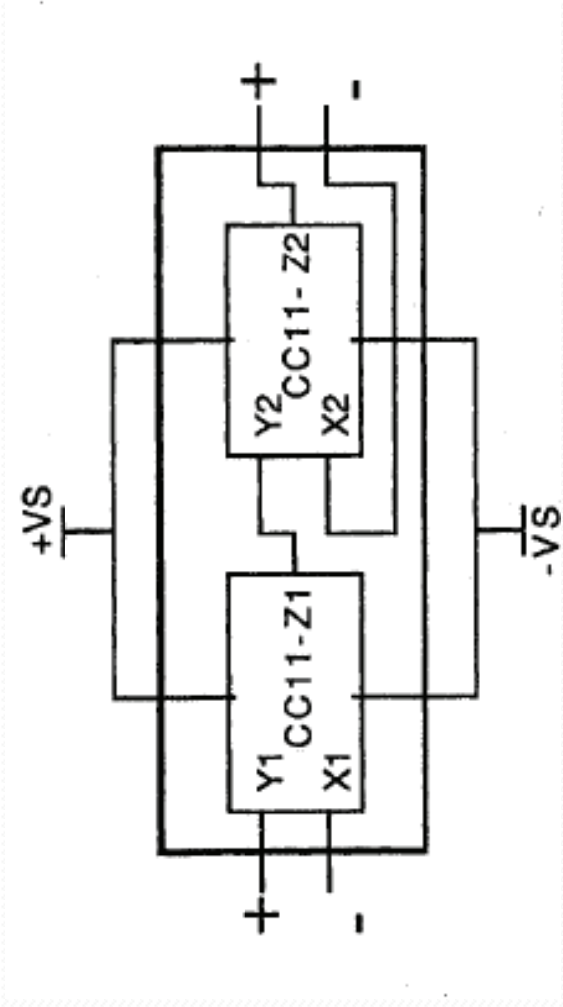


Figure 25: Operational Floating Conveyor

# Current-Mode Feedback

## Amplifiers(OFC)

- Operational floating conveyor is a four port general purpose analogue building block, it has similar transmission properties to the current-feedback op-amp and current conveyor but with an additional output which allows accurate output sampling.
- Figure 25 consist of two series connected CCII-.
- $X_1$  and  $Y_1$  of the first CCII as inverting and non-inverting input terminals respectively and  $X_2$  and  $Z_2$  of the second conveyor as inverting and non-inverting output terminals respectively

# Current-Mode Feedback

## Amplifiers(OFC)

- This result in a very elegant hybrid of amplifier stages between different input and output ports.
- As an example there is high open-loop transimpedance gain between  $X_2$  and  $X_1$ , current gain between  $Z_2$  and  $X_1$ , voltage gain between  $X_2$  and  $Y_1$  and transadmittance gain between  $Z_2$  and  $Y_1$  assuming a load termination at  $X_2$  and  $Z_2$  in all of the cases.
- This transmission of multiple transfer functions allows four main amplifier types to be accurately configured in closed loop.



# Current-Mode Feedback Amplifiers(OFC)

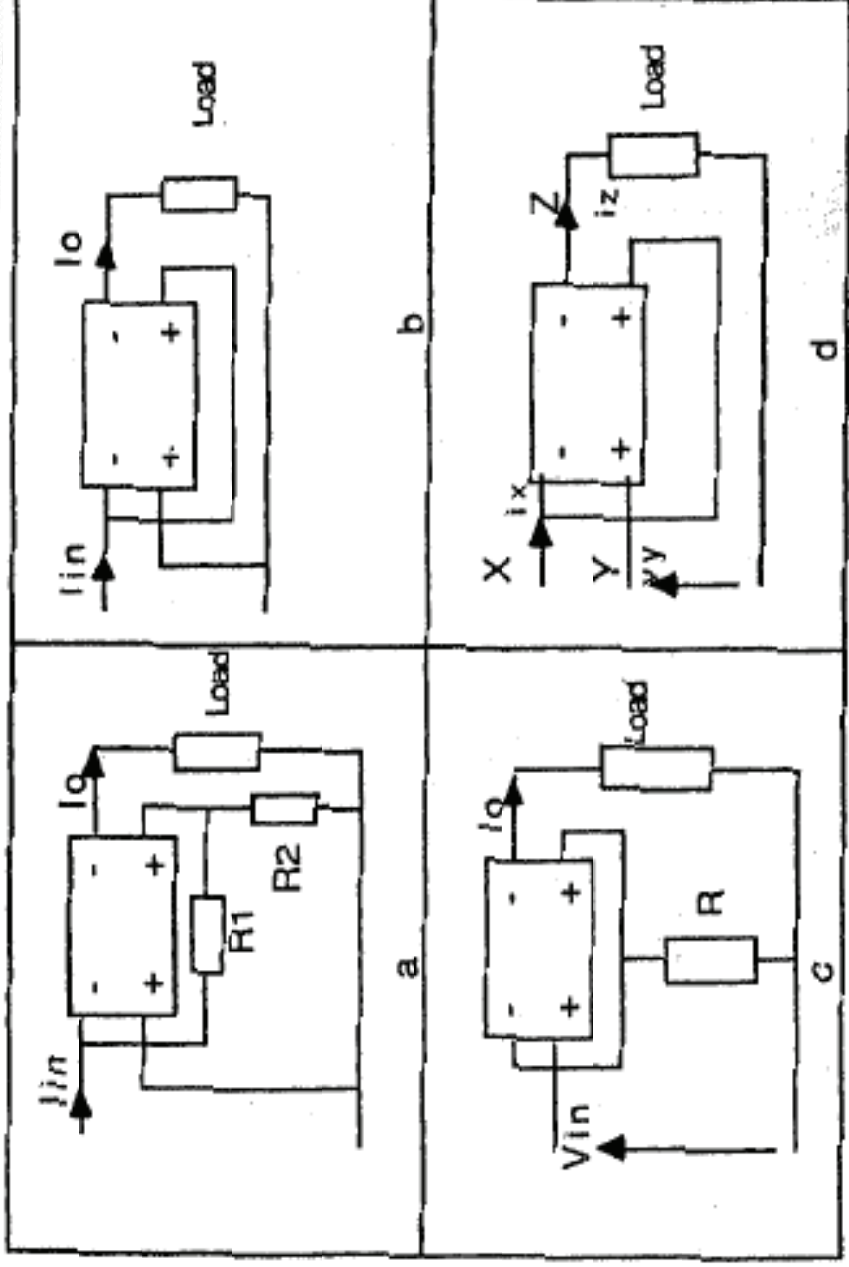


Figure 26: Closed loop controlled current output circuits applications

# Current-Mode Feedback

## Amplifiers(OFC)

- In figure 26 this types of applications are given, in figure 26.a it is a current amplifier ( $I_O/I_{iN}=1+R_1/R_2$ ), in figure 26.b it is a current follower ( $I_O/I_{iN}=1$ ), in figure 26.c we see a transconductance amplifier ( $I_O/V_{iN}=-1/R$ ) and in 26.d there is a current conveyer.



# References

- C. Toumazou, F.J. Lidge & D.G. Haigh, *Analogue IC Design: The Current Mode Approach*, Peter Peregrinus LTD., 1998.
- H. Hakan Kuntman, *Analog MOS Tümdrevre Tekniđi* (Ders Kitabı), İTÜ Kütüphanesi, Sayı 1587, 1997.