

$$\frac{i_{out}}{i_2} = \frac{G_2 G_3}{s^2 C_1 C_2 + s(C_1 + C_2)G_2 + G_2 G_3}$$

$$i_5 = i_4 = 0$$

$$\frac{i_{out}}{i_4} = \frac{s C_1 G_3}{s^2 C_1 C_2 + s G_2 (C_1 + C_2) + G_2 G_3}$$

$$i_5 = i_2 = 0$$

$$\frac{i_{out}}{i_5} = \frac{s^2 C_1 C_2}{s^2 C_1 C_2 + s G_2 (C_1 + C_2) + G_2 G_3}$$


$$i_2 = -i_5$$

$$i_4 = i_5 \frac{G_2 (C_1 + C_2)}{G_3 C_1}$$

• Kutup açısıl frekansı, değer katsayısı

$$\omega_o = \sqrt{\frac{G_2 G_3}{C_1 C_2}}$$
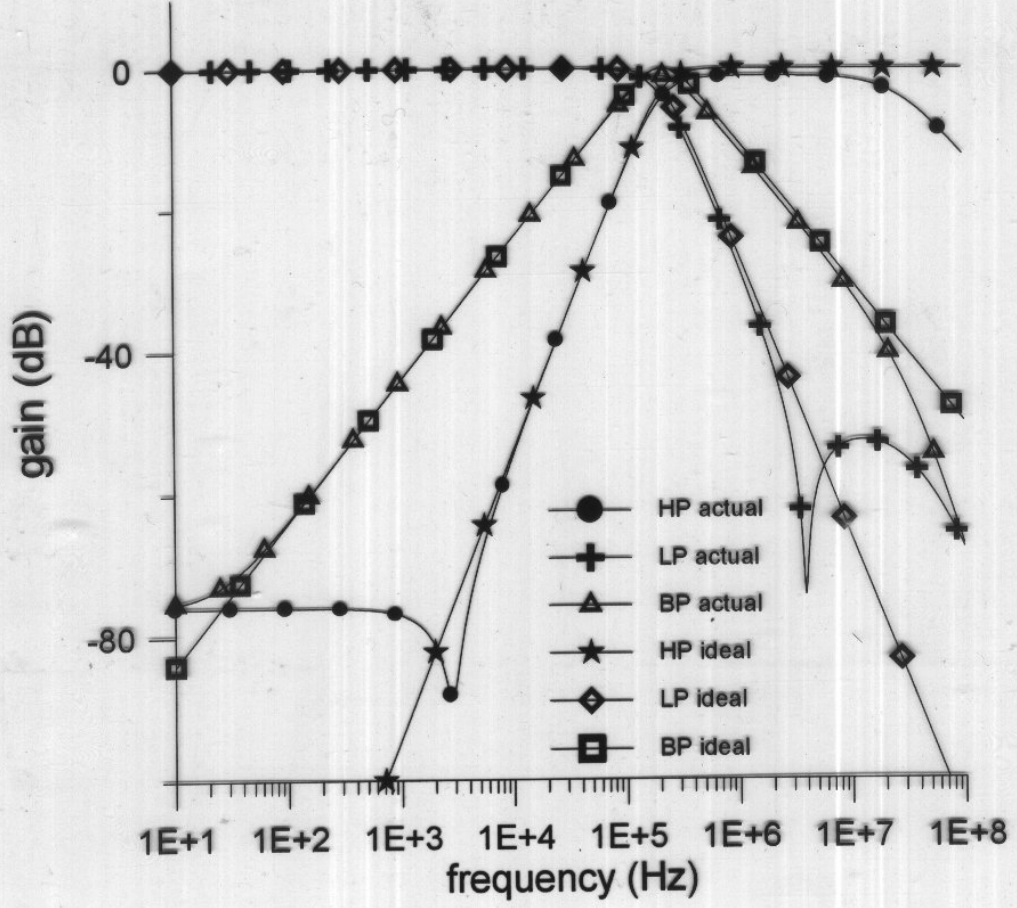
$$Q = \frac{1}{(C_1 + C_2)} \sqrt{\frac{C_1 C_2 G_3}{G_2}}$$



•HP, LP ve BP süzgeç frekans eğrileri