

# Chapter3: Signal conditioning

**Signal conditioning circuits are used to process the output signal from sensors of a measurement system to be suitable for the next stage of operation**

**The function of the signal conditioning circuits include the following items: Signal amplification (opamp), Filtering (opamp), Interfacing with  $\mu$ P (ADC), Protection (Zener & photo isolation), Linearization, Current – voltage change circuits, resistance change circuits (Wheatstone bridge), error compensation**

# Operational Amplifiers



Operational amplifiers are the basic element of many signal conditioning modules

- Generally the opamp has the following properties:

**Gain:** being of the order greater than 100000, ideally = infinite


**Input impedance:** ideally infinite

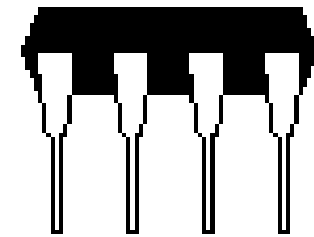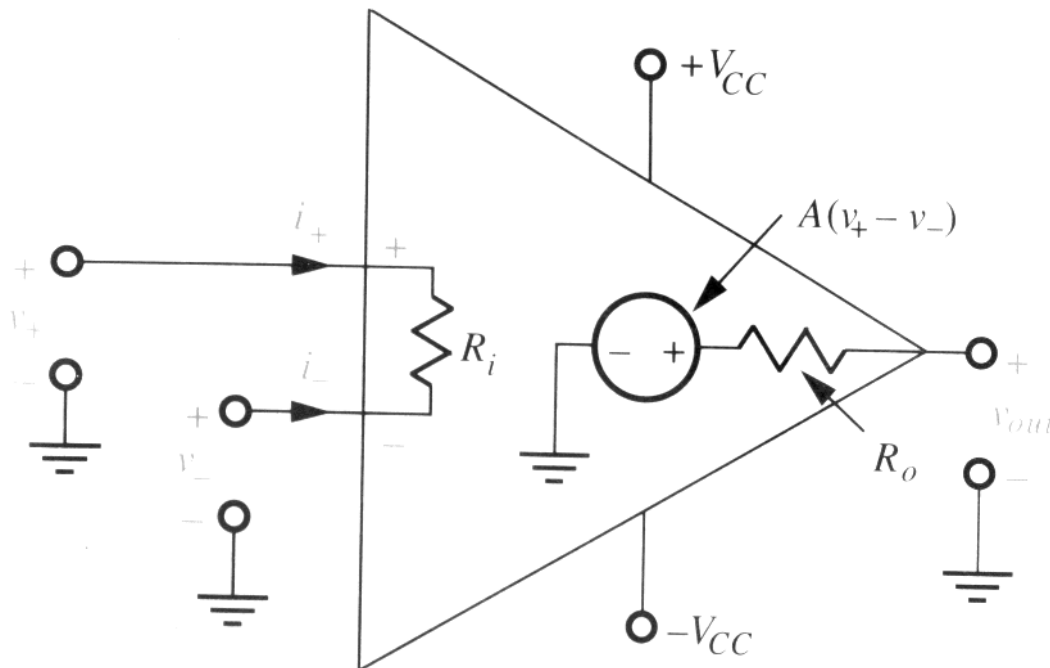**output impedance:** ideally zero; practical values 20-100 $\Omega$




# Opamp Circuit Configurations (1)

## Non-Inverting Amp

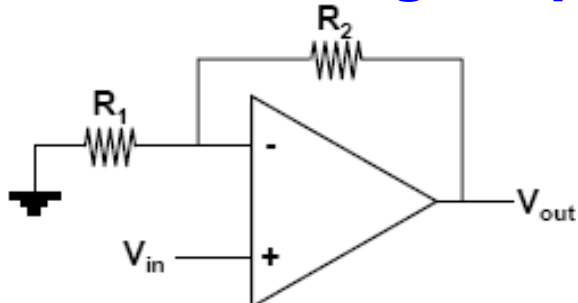


$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

## Inverting Amp

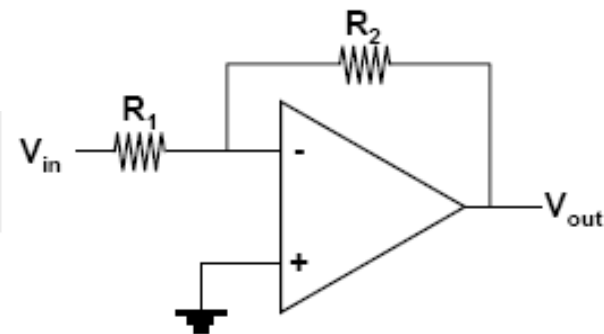

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$


## Voltage Follower

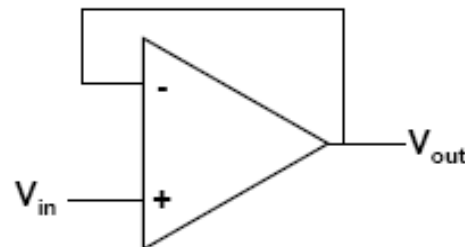


$$V_{out} = V_{in}$$

## Voltage Comparator

– digitize input

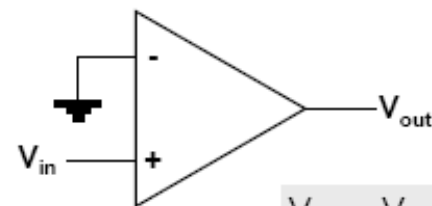


$$V_{out} = V_{CC} \text{sign}(V_{in})$$

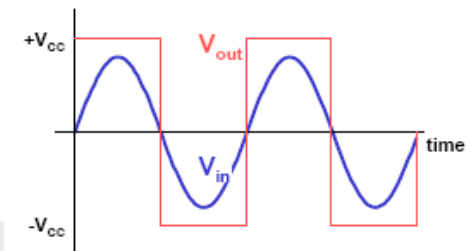
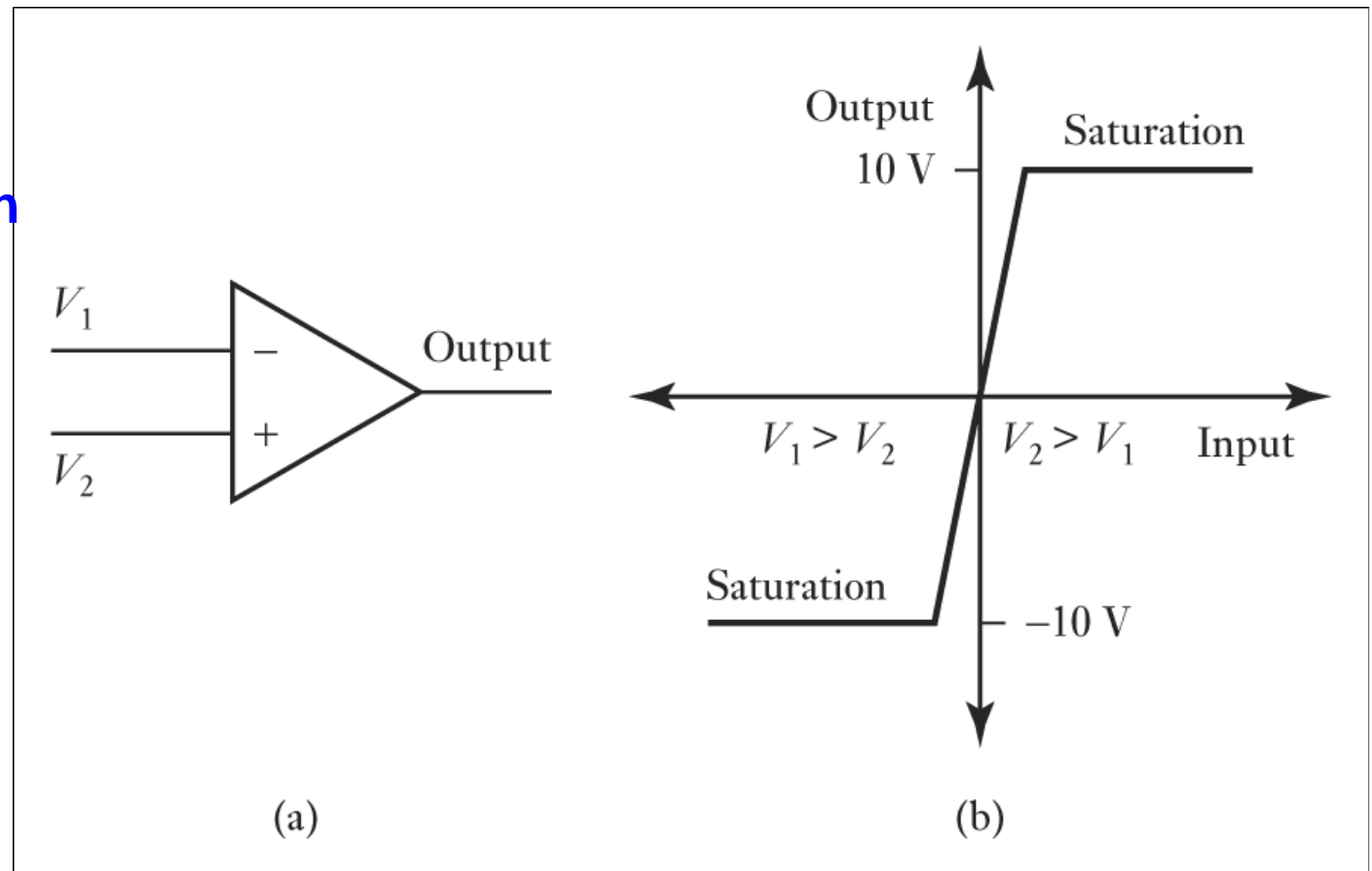
# Opamp as comparator (1)


The output indicates which of the two voltages is high ( $V_1$  or  $V_2$ ).  
When used with no feedback connection

If the voltage applied to  $v_1$  is greater than  $V_2$  then the output is constant voltage equal to (-10V) if ( $V_2 > V_1$ ) then the output is constant voltage = (+10V). This can be used in the following example:



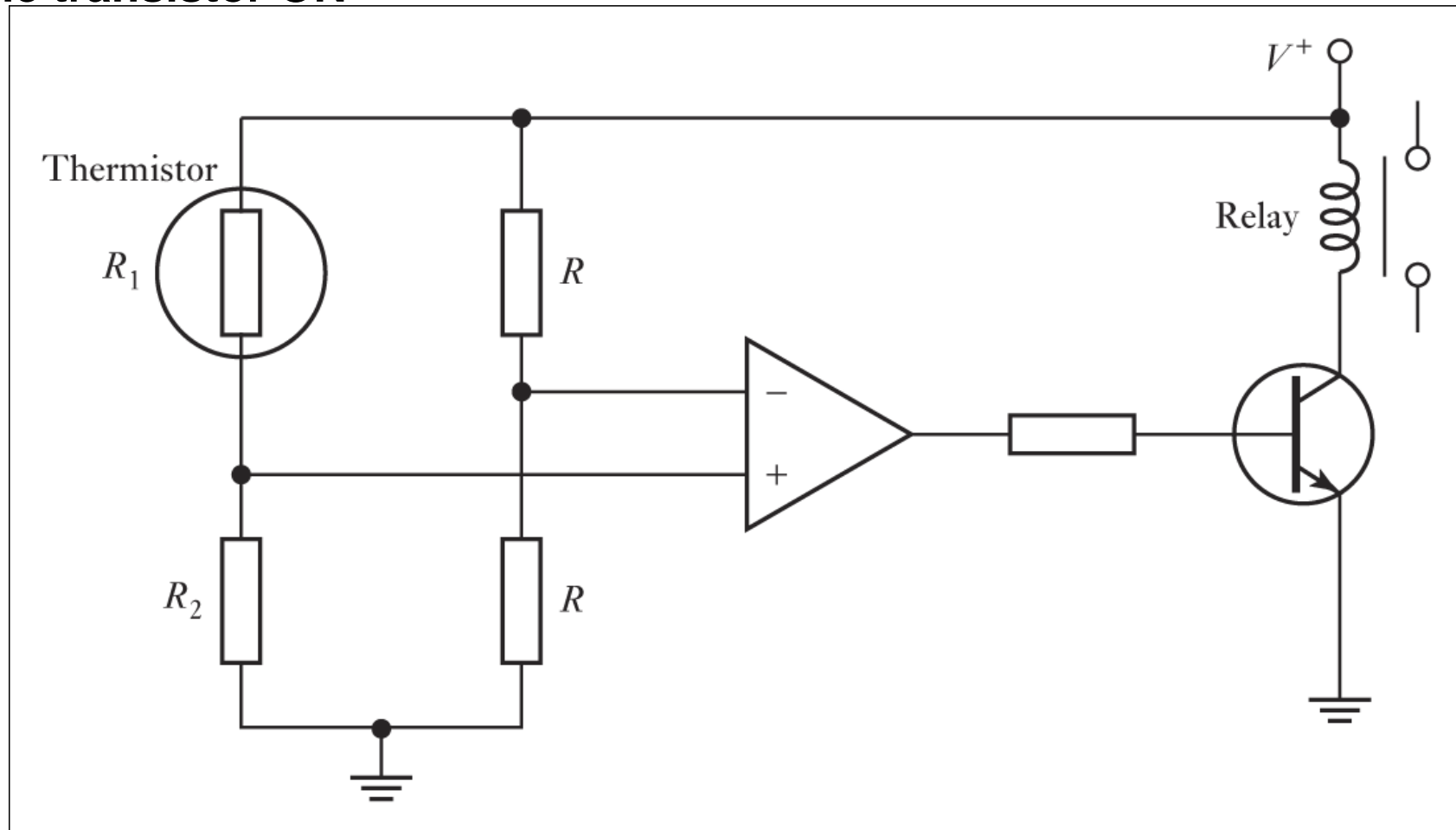
## Opamp as comparator (2)

The circuit is designed to control temperature with a certain range. When the temp. is below certain value, the thermistor  $R_1$  is more than  $R_2$  and the bridge is out of balance, it gives an output at its lower saturation limit which keeps the transistor OFF. When temperature rises and  $R_1$  falls the opamp switch to +ive saturation value and switch the transistor ON




# Opamp Circuit Configurations (2)

- Summing Amp

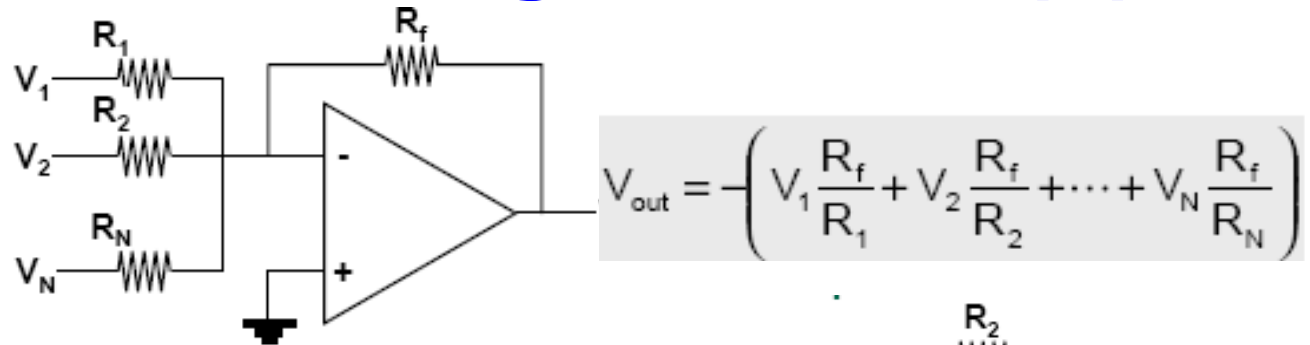


- Differential Amp

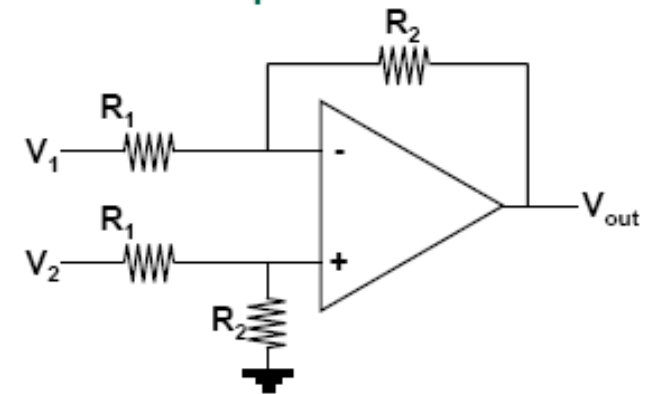
$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$



- Integrating Amp

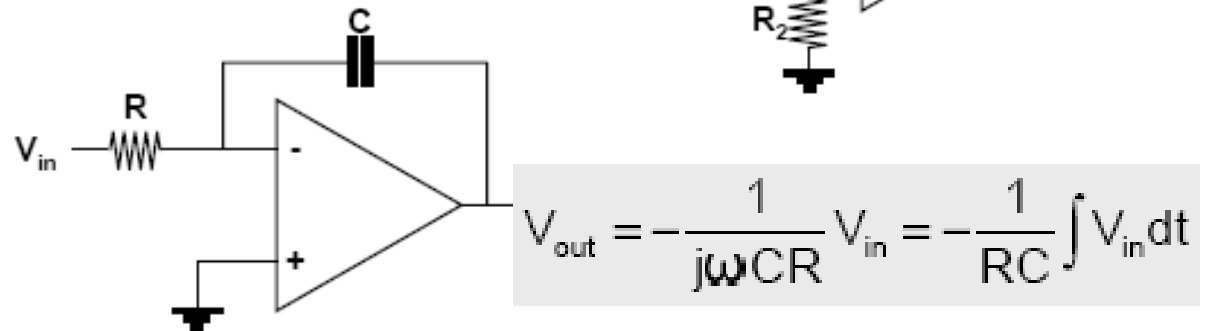

- Differentiating Amp

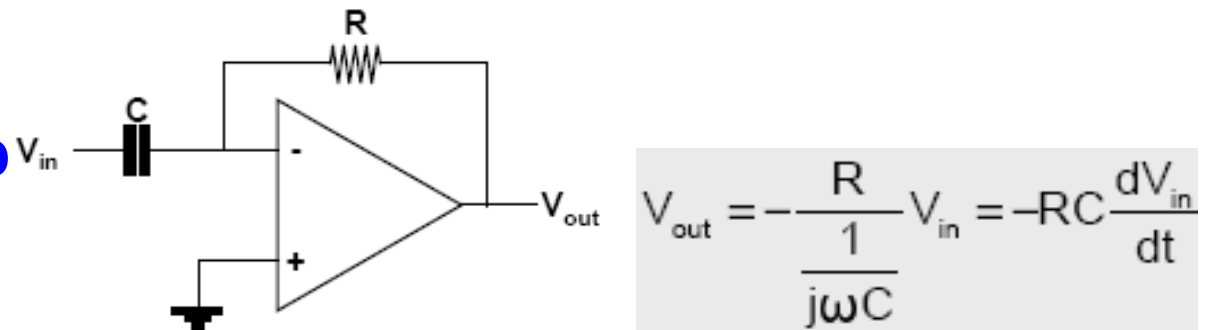

## Differential Opamp Circuit Example (3)

The difference in voltage between the emfs of the two junctions of the thermocouple is being amplified.

If a temperature difference between the thermocouple junctions of  $10^{\circ}\text{C}$  produces an emf difference of  $530\text{ }\mu\text{V}$ , then the values of  $R_1$  and  $R_2$  can be chosen to give a circuit with an output of  $10\text{mV}$ .


For the circuit we have  $V_{\text{out}} = (V_2 - V_1)R_2/R_1$

$$10 \times 10^{-3} = \frac{R_2}{R_1} \times 530 \times 10^{-6}$$

$$\frac{R_2}{R_1} = 18.9$$



So if we select  
 $R_1$  as  $10\text{ k Ohm}$   
then

$R_2 = 189\text{ k Ohm}$

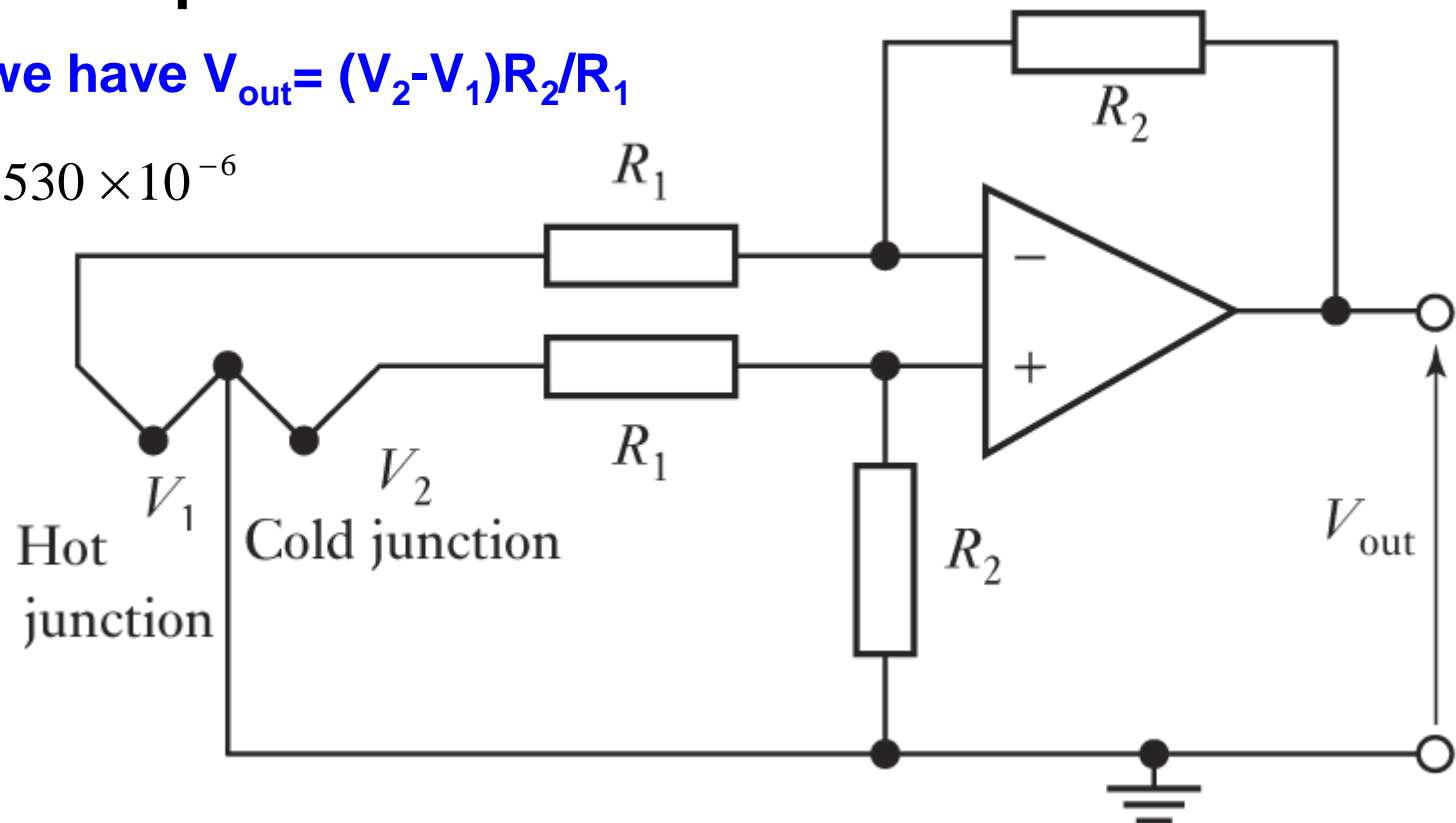


# Opamp Circuit Configurations (4)

Current-to-Voltage

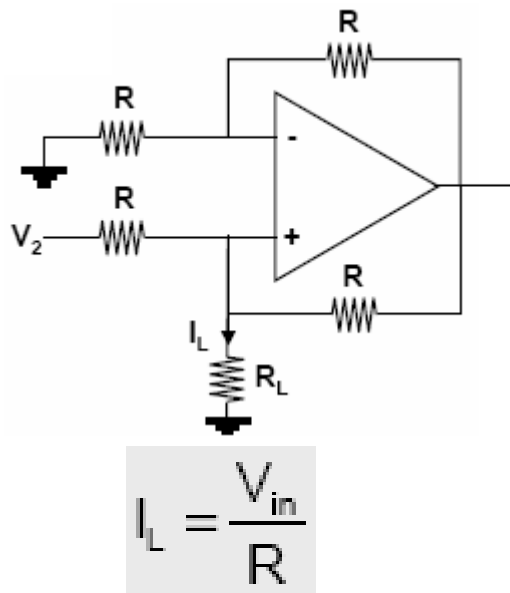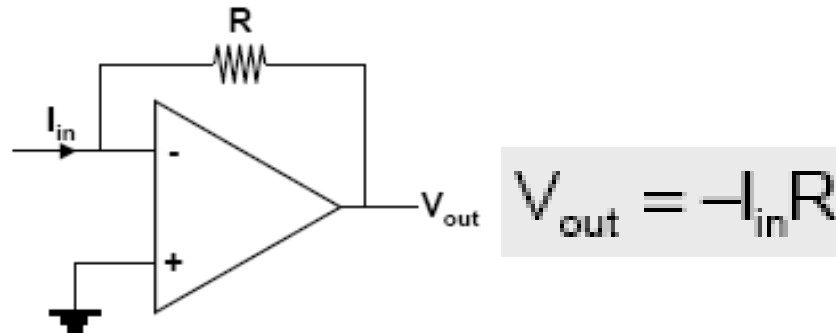

Voltage-to-Current

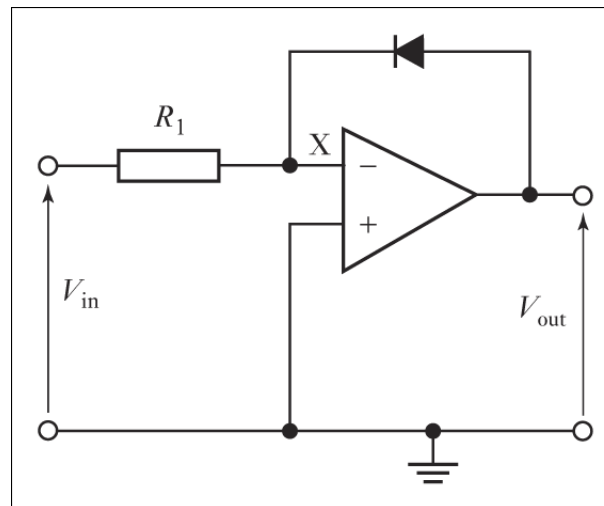

Logarithmic amplifier

$$V_{out} = k \ln(V_{in})$$


The voltage- current relationship can be approximated by:

$V = C \ln(I) = C \ln(V_{in}/R) = k \ln(V_{in})$ ; so if  $V_{in} = A \exp(at)$  then

$V_{out} = K \ln(A \exp(at)) = k \ln A + at$  which is linear relationship



# Instrumentation Amplifier

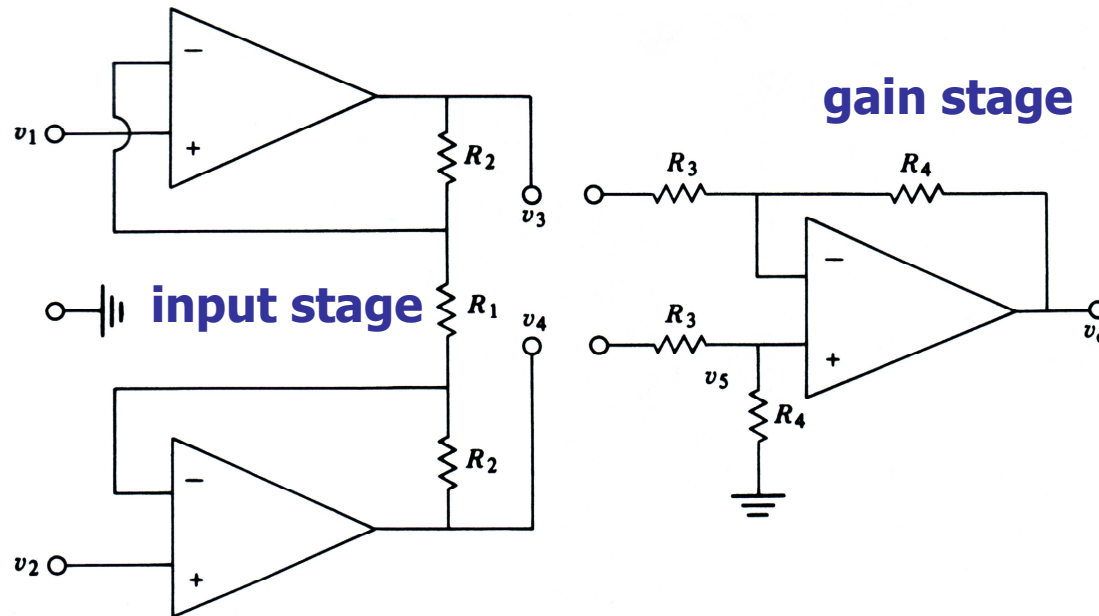


- It is available as single IC is designed to have:
  - **high input impedance (300M ohm)**
  - **High common mode rejection gain (more than 100 dB)**
  - **High voltage gain**

***total differential gain***

$$G_d = \frac{2R_2 + R_1}{R_1} \left( \frac{R_4}{R_3} \right)$$

# Instrumentation Amplifier

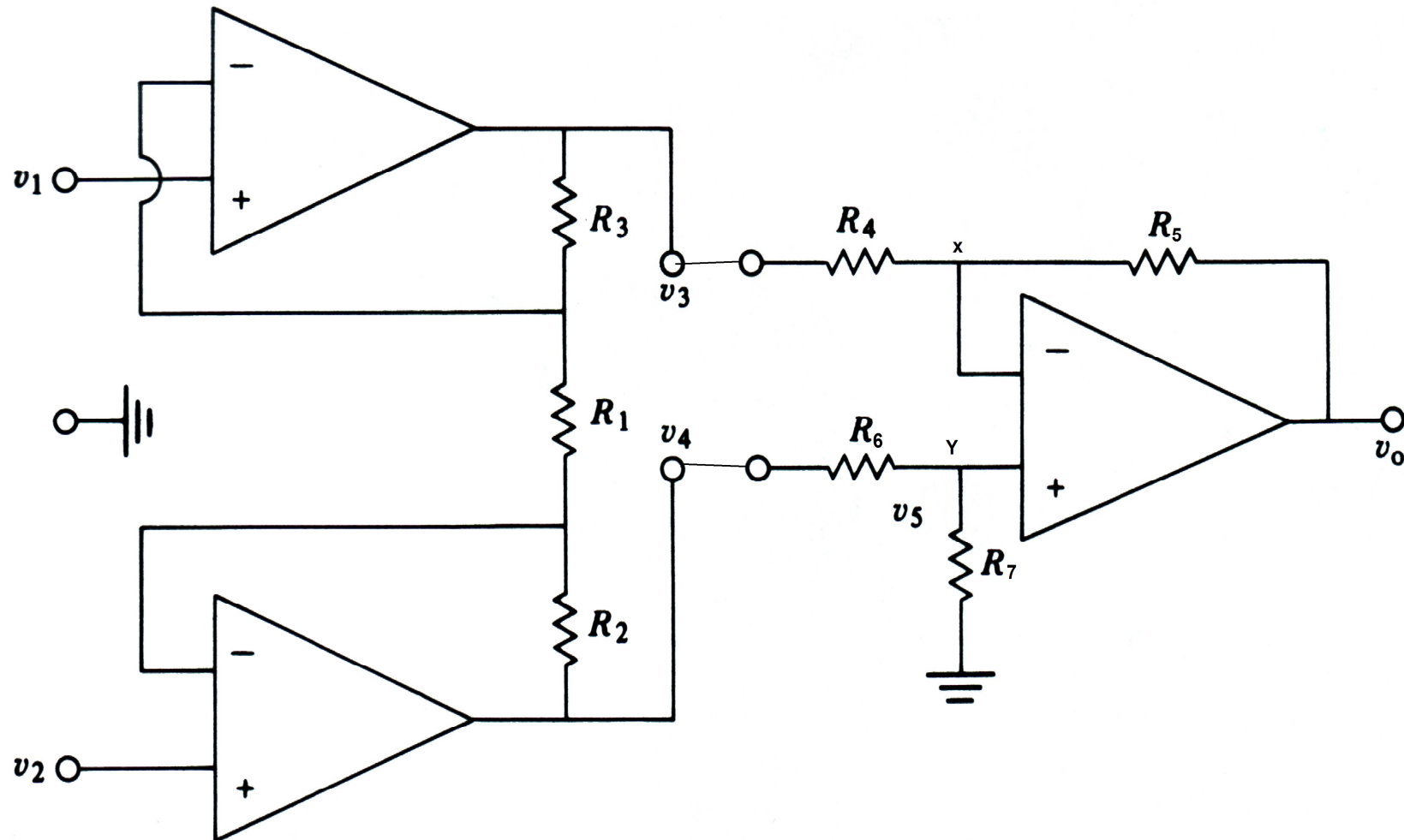

By selection suitable resistance ratios show that this circuit is capable of rejecting common mode noise.???

See Mechatronics, Bolton

# Signal conditioning: Wheatstone Bridge

- One of the most used signal conditioning circuit. It can be used to convert a resistance change to a voltage change as in the following example:

At balanced condition  $V_0 = 0$  and in result

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

When not balanced  $V_{BD} =$


$$V_{BD} = V_0 = V_s \left( \frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$

$$V_0 + \delta V_0 = V_s \left( \frac{R_1 + \delta R_1}{R_1 + \delta R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$

$$\delta V_0 = V_s \left( \frac{R_1 + \delta R_1}{R_1 + \delta R_1 + R_2} - \frac{R_1}{R_1 + R_2} \right)$$

if  $\delta R_1$  is much smaller than  $R_1$
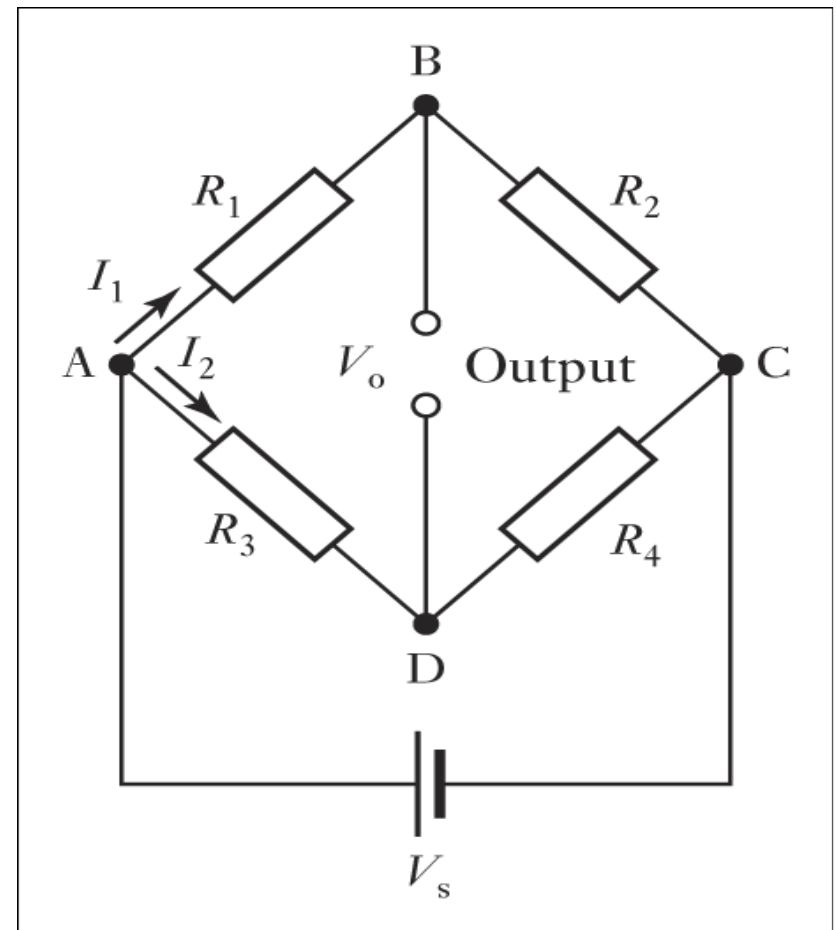
$$\text{then we can write } \delta V_0 = \frac{\delta R_1}{R_1 + R_2} V_s$$



# Signal conditioning: Wheatstone Bridge

Eg. A platinum resistance temperature sensor has a resistance of 100 ohm at 0 °C is placed in one arm of a Wheatstone bridge with each of the other arms also being 100 ohm. If the resistance temperature coefficient of the platinum is 0.0039/K, find the output voltage from the bridge per degree change in temp. if the load across the output can be assumed to be infinite.  $V_s=6.0$  volt.

The variation of the resistance of the platinum with temperature can be represented as  $R_t = R_0 (1 + \alpha T)$

**Sol.**

Change in resistance =  $R_t - R_0 = R_0 \alpha T$

$= 100 \times 0.0039 \times 1 = 0.39$  ohm/k

Since the resistance change is small compared to the 100 ohm, the approximate equation can be used. Hence:


$$\delta V_0 = \frac{\delta R_1}{R_1 + R_2} V_s = \frac{0.39 \times 6.0}{100 + 100} = 0.012V / \text{degree } K$$

# Signal conditioning: Wheatstone Bridge

## Compensation for leads


In many measurement system involving a resistive sensor, the actual sensing element may be affected by the connecting leads. so to compensate for such effects Wheatstone bridge may be used as arranged in the figure

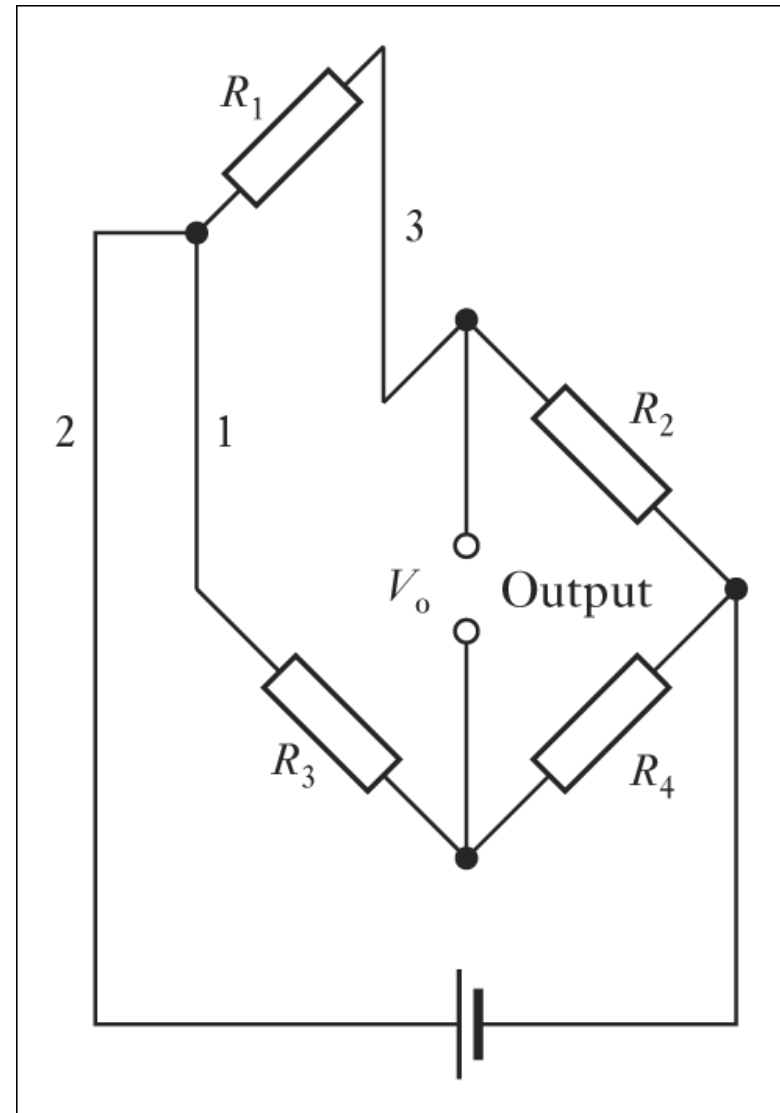**Connecting Lead 1 to  $R_3$  and Lead 3 to  $R_1$  (the sensor) and so if  $R_1$  is equal to  $R_3$  and of the same size and type then the leads effect can be canceled out.**


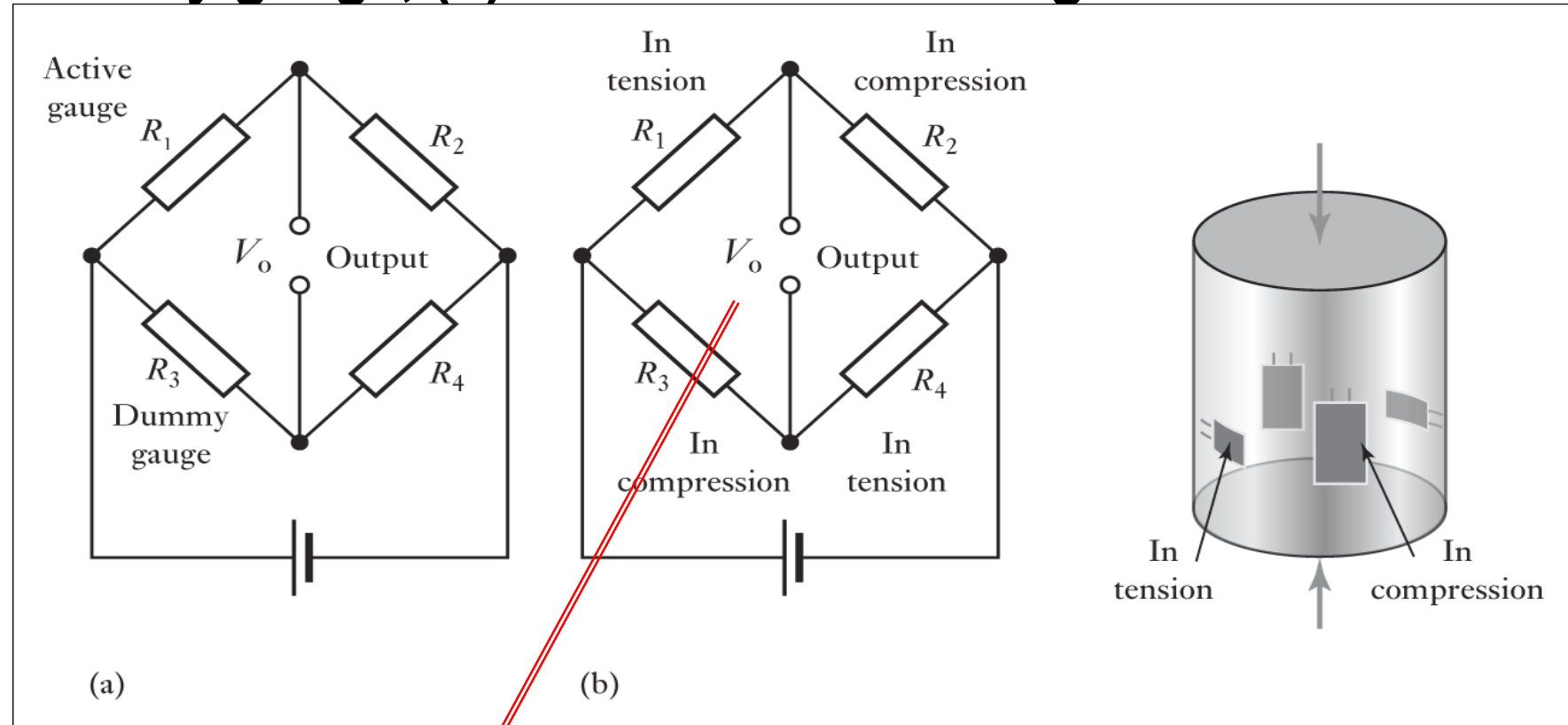
# Signal conditioning: Wheatstone Bridge

Temperature compensation with strain gauges: (a) use of dummy gauge, (b) four active arm bridge



$$V_o = \frac{V_s R_1 R_4}{(R_1 + R_2)(R_3 + R_4)} = \left( \frac{\delta R_1}{R_1} - \frac{\delta R_2}{R_2} - \frac{\delta R_3}{R_3} + \frac{\delta R_4}{R_4} \right) V_s$$


Strain gauge in tension increase resistance , in compression decrease resistance which increase the output voltage

# Signal conditioning: PROTECTION

- Normally protection is provided against high current and high voltage which may damage the important components.
- **Examples of protection in mechatronics:**
  - Series resistor to limit line current
  - Fuse to break if the current does exceed a safe level
  - Zener diode circuit to protect against high voltage and wrong polarity.
  - Optoisolator to isolate circuits completely
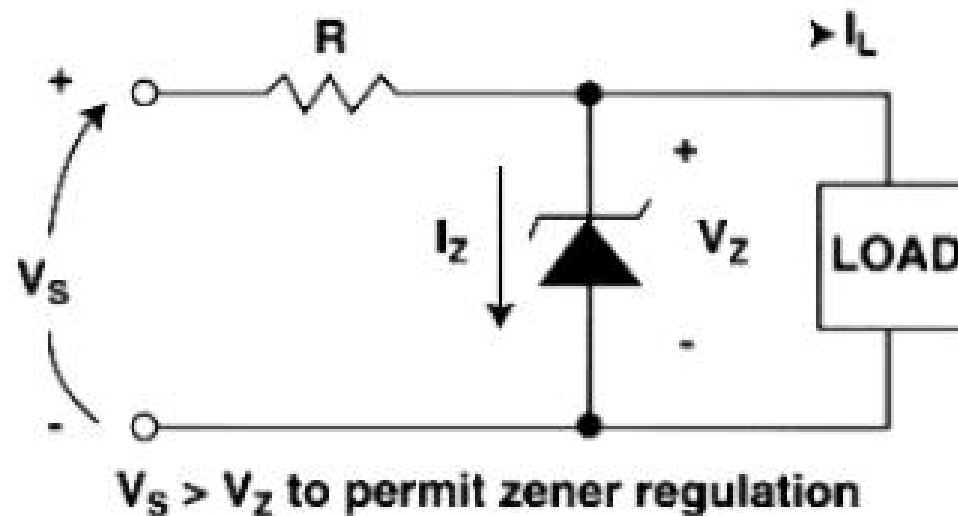
# Protection: Zener Diode


- Zener diodes operate in the breakdown region.
- Zener diodes have a specified voltage drop when they are used in reverse bias. So normally used for voltage regulation in reverse bias
- Zener has the ability to maintain a nearly constant voltage under conditions of widely varying current.




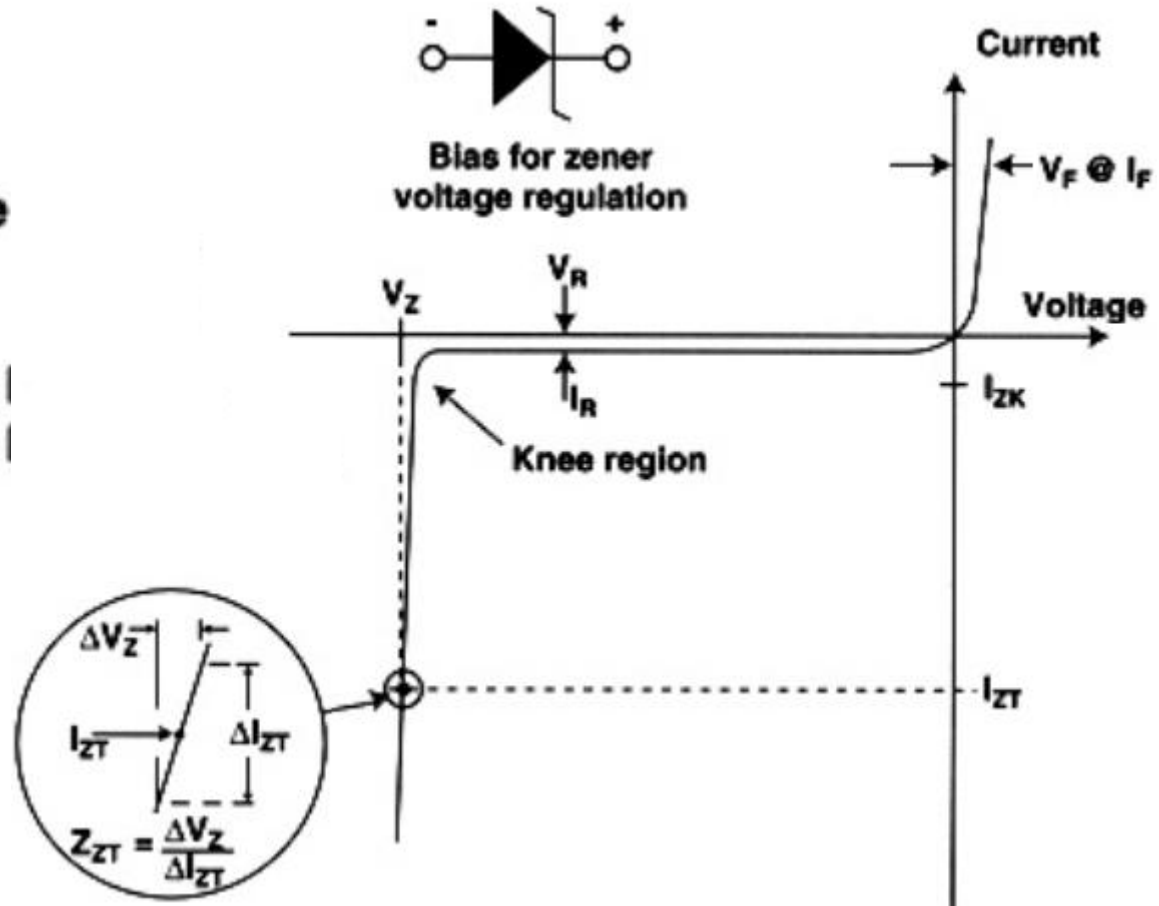
# Zener Diode characteristics

$V_Z$  = Voltage at current  $I_Z$   
 $I_{ZT}$  = Test current for voltage  
 $V_R$  = Reverse voltage  
 $I_R$  = Leakage current at  $V_R$   
 $Z_{ZT}$  = Dynamic impedance at  $I_{ZT}$   
 $Z_{ZK}$  = Dynamic impedance at  $I_{ZK}$   
 $V_F$  = Forward voltage at  $I_F$



When the reverse voltage  $V_R$  is increased, the leakage current remains essentially constant until the breakdown voltage  $V_Z$  (Zener voltage) is reached.

# Optoisolator Background

- Operation similar to relays
- Used to control high voltage devices
- Excellent noise isolation because switching circuits are electrically isolated
- Coupling of two systems with transmission of photons eliminates the need for a common ground

**Ideal for applications requiring High isolation surge voltage**


**Noise isolation**

**Small size**




**Signal cannot travel in opposite direction**

**Used to control motors, solenoids, etc.**

# Optoisolator Schematic

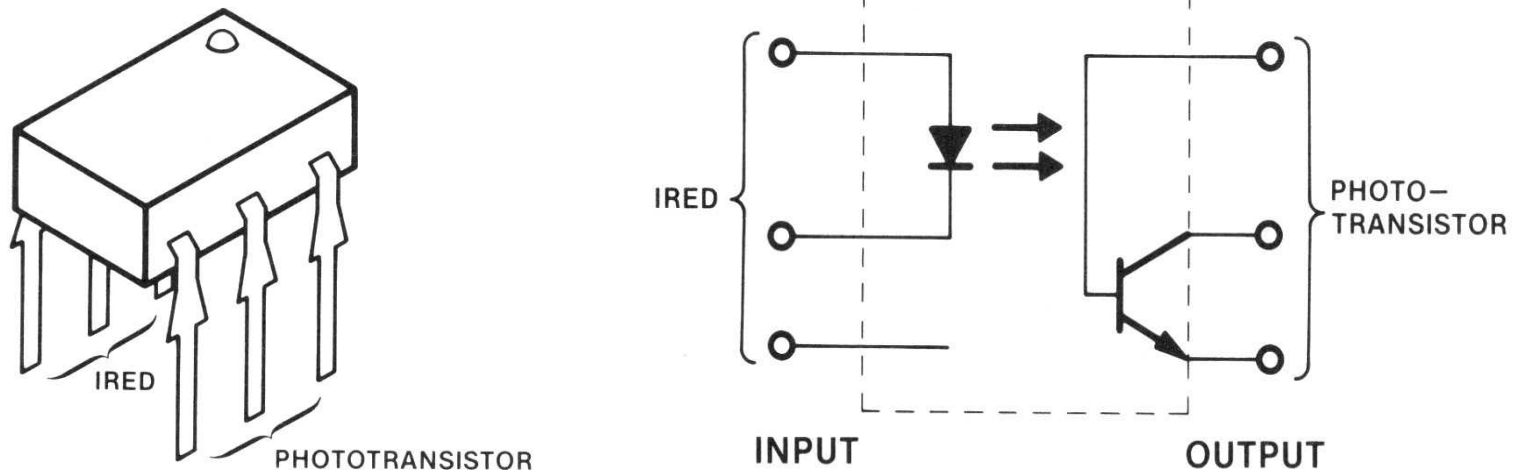


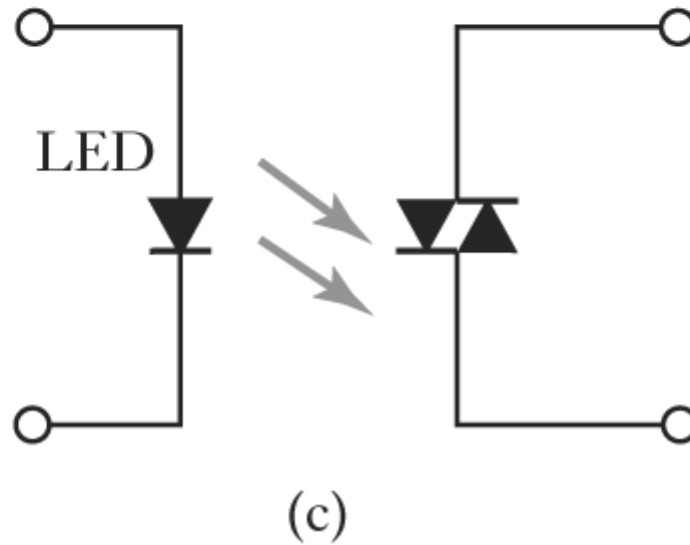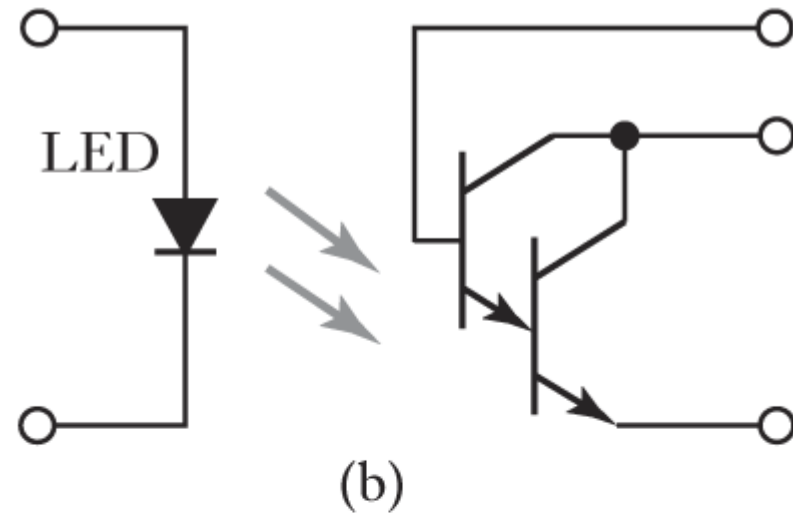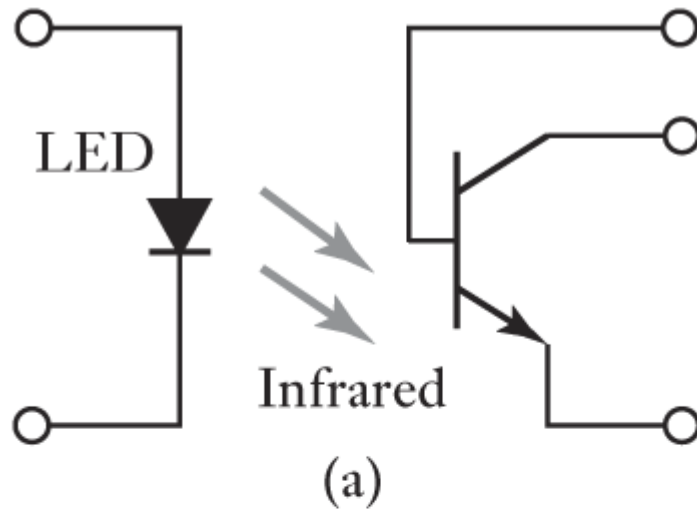- Input Stage = infrared emitting diode (IRED)
- Output Stage = silicon NPN phototransistor



**Optoisolators: (a) transistor, (b) Darlington, (c) triac**

**(see Bolton Mechatronics)**

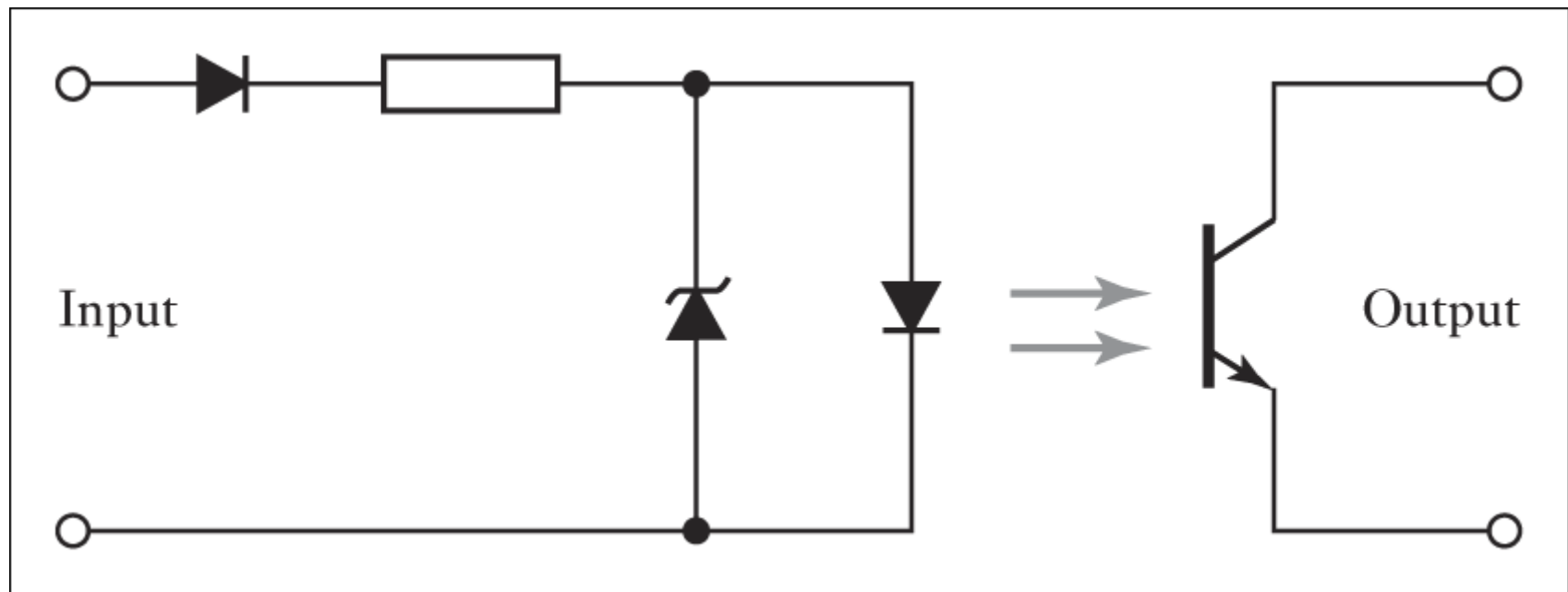

Protection circuit

# Signal conditioning: Filtering (1)

- **Filtering** is the process of removing a certain band of frequencies from a signal and permitting others to be transmitted.
- **The Pass Band:** the range of frequencies passed by the filter
- **The Stop Band:** the range not passed by the filter.
- **CUT OFF frequency:** the boundary between stopping and passing


Technically CUTOFF frequency is defined as the frequency at which the output voltage is 70.7% of that in the pass band.

**Attenuation dB (decibels )=**

$$10\log \frac{P_{out}}{P_{in}} = 20\log \frac{V_{out}}{V_{in}}$$

**The output voltage of 70.7% of that in the pass band is thus an attenuation of 3dB=20 log (0.707)**

## Signal conditioning: Filtering (2)

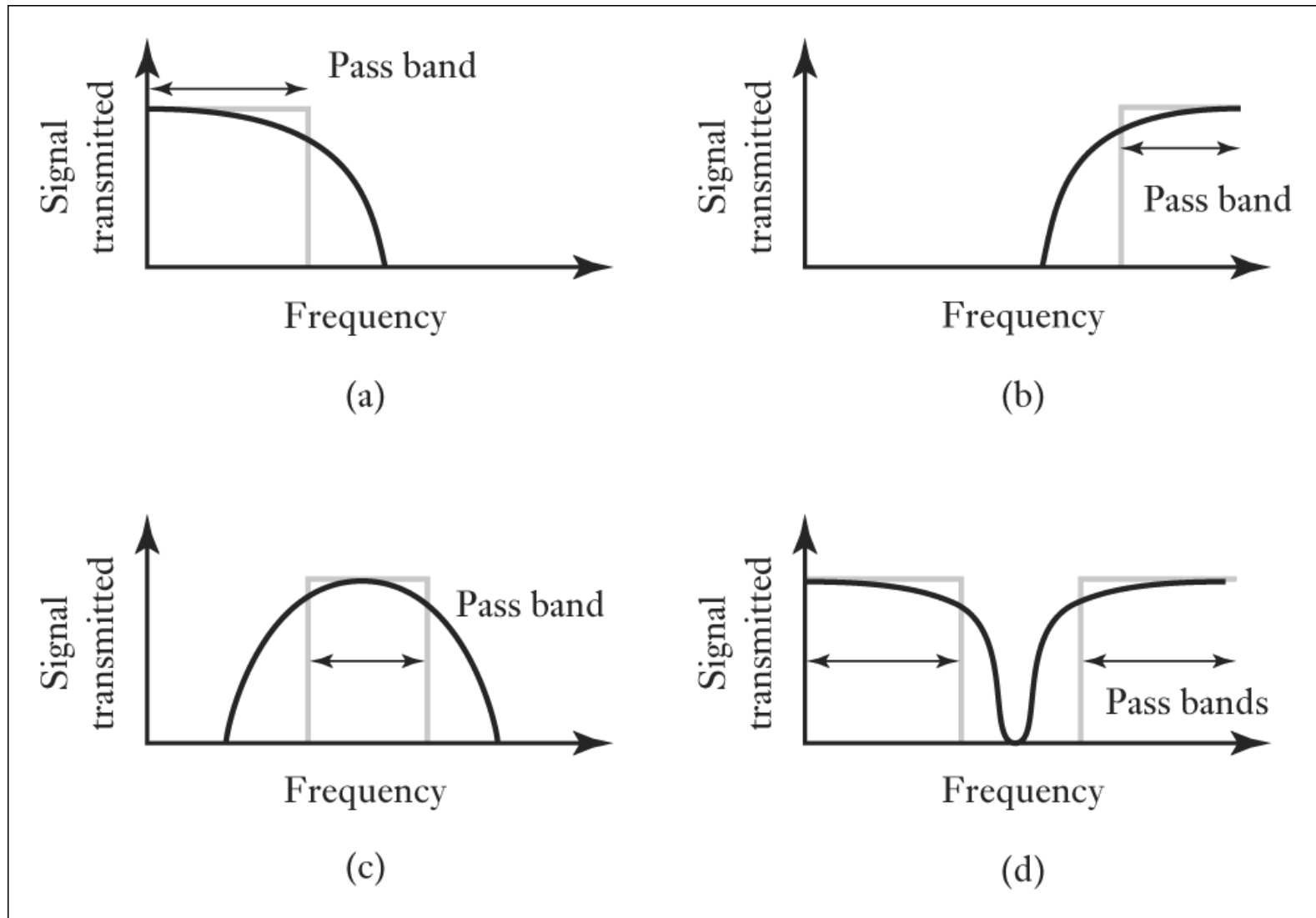


Characteristics of ideal filters: (a) low-pass filter, (b) high-pass filter, (c) band-pass filter, (d) band-stop filter

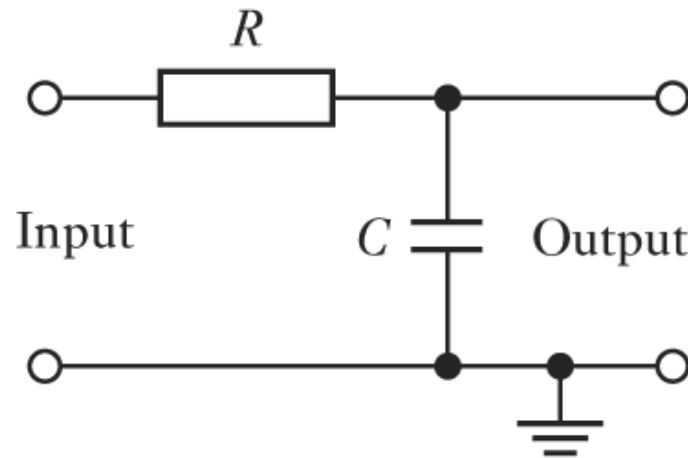
## Signal conditioning: Filtering (3)

**Passive Filters** made up using only resistors, capacitors and inductors

**Active filters** involve an operational amplifier



(a)

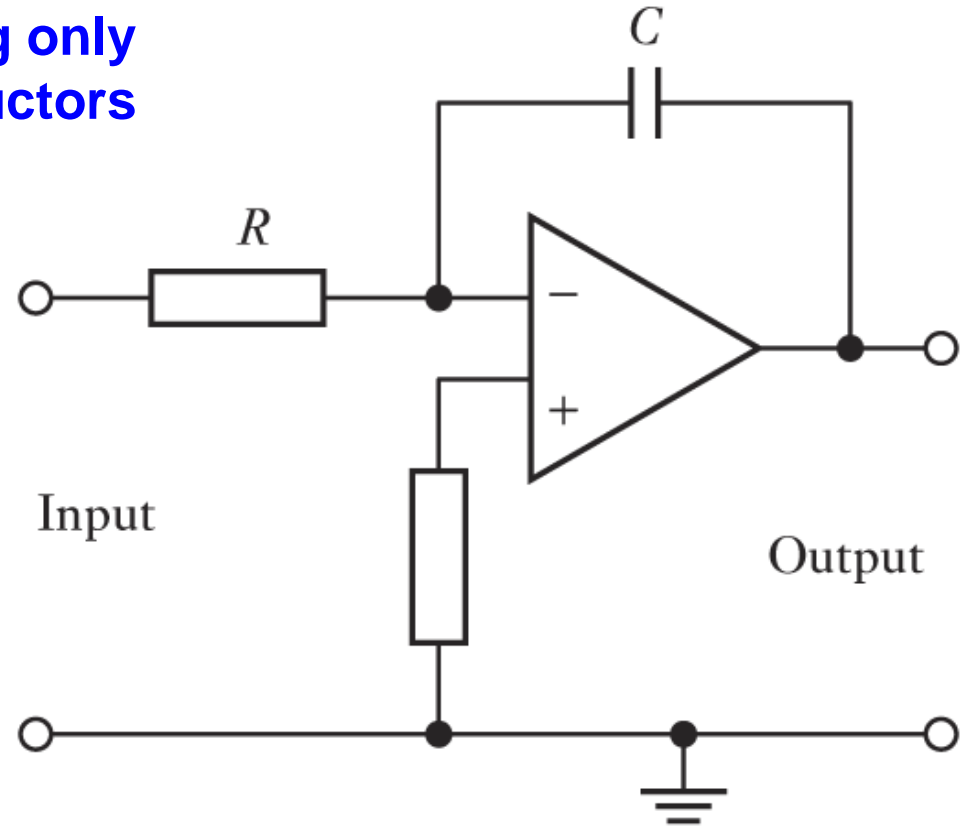

(b)

**Low-pass filter: (a) passive, (b) active using an operational amplifier**