

**Circuit and System Analysis**  
Final Exam

- For the circuit in Figure 1,  $R_1 = 1\Omega$ ,  $R_2 = 1\Omega$ ,  $C = 1F$ ,  $L = 1H$ ,  $v_k(t) = \cos(t)$  and  $i_3 = v_1$  are given. (a) Obtain  $Y_1$  and  $Y_2$  admittans. (b) Find the Thévenin equivalent circuit (in sinusoidal steady-state) with respect to the terminals  $a$  and  $b$ . (c) Calculate the load impedance to connect the terminal between  $a$  and  $b$  for maximum average power transfer. (d) Calculate the complex power and  $\cos\phi$  of the independent voltage source ( $v_k$ ) in the case of (c).
- For the circuit given in Figure 2, (a) Express  $V_o(s)$  in terms of  $V_s(s)$ ,  $R$ ,  $C$  and the initial condition  $v_C(0)$  in the Laplace domain. (b) Obtain the transfer function  $H(s) = \frac{V_o}{V_s}$ .
- The circuit which is given in Figure 3 with  $v_3 = ri_1$  and  $i_4 = gv_2$ , is in sinusoidal steady-state. Obtain modified (generalized) mesh equation to analyze the circuit.
- Find the  $y$ -parameters for the 2-port network shown in Figure 4 with  $v_3 = \alpha i_a$ . Not that  $I_1 = y_{1,1}V_1 + y_{1,2}V_2$  and  $I_2 = y_{2,1}V_1 + y_{2,2}V_2$ .

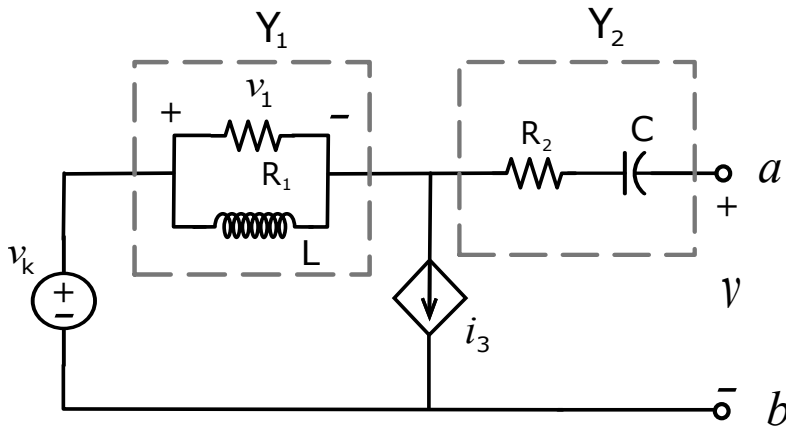


Figure 1

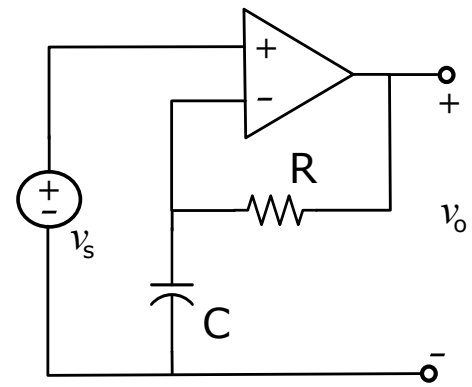


Figure 2

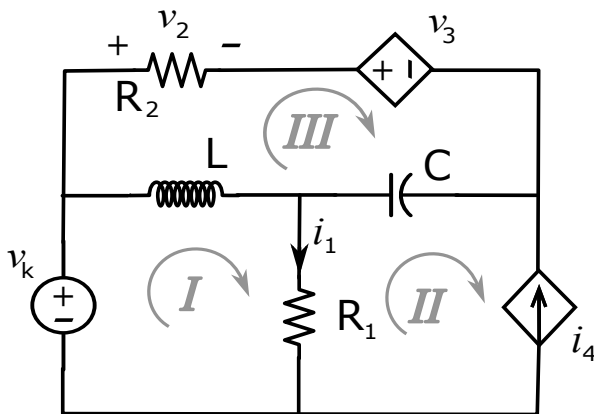


Figure 3

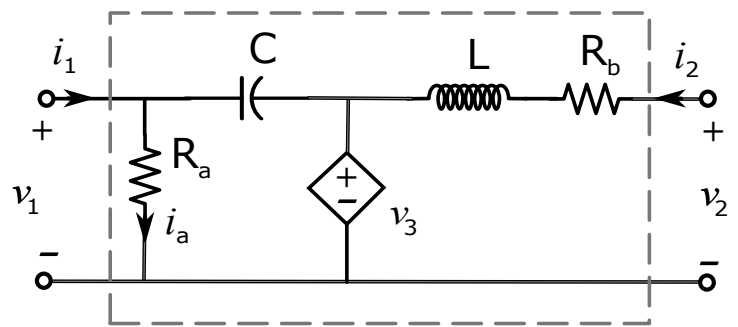


Figure 4

At the end of the exam, please hand in this sheet, along with your answers.

Good luck !