

Basic of Electrical Circuits

EHB 211E

Prof. Dr. Müştak E. Yalçın

Istanbul Technical University
Faculty of Electrical and Electronic Engineering

mustak.yalcin@itu.edu.tr

Lecture 13

1 State Equation

- Analysis of Circuits Containing RLC Elements
- Durum Denklemlerinin Elde Edilmesi
- RLC and multi-terminal elements
- Obtaining State Equations directly from the circuit

State Equation

Capacitor current and or its voltage are given by

$$C \frac{dV_C}{dt} = i_C$$

and

$$V_C(t) = \frac{1}{C} \int_{t_0}^t i_C(\tau) d\tau + V_C(0)$$


Inductor voltage and current are given by

$$L \frac{di_L}{dt} = V_L$$

and


$$i_L(t) = \frac{1}{L} \int_{t_0}^t V_L(\tau) d\tau + i_L(0)$$

State Equation

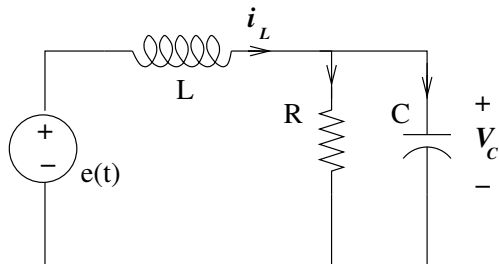

Using Branch Voltages Method

$$i_C = i_L - i_R$$

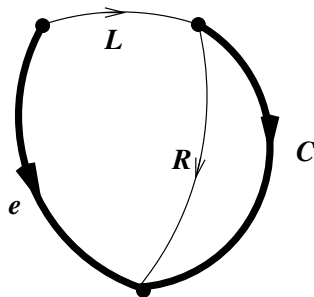

Using the definition of L and C elements

$$\begin{aligned} C \frac{dV_C}{dt} &= \frac{1}{L} \int_{t_0}^t V_L(\tau) d\tau + i_L(0) - GV_R \\ &= \frac{1}{L} \left(\int_{t_0}^t e(\tau) d\tau - \int_{t_0}^t V_C(\tau) d\tau \right) + i_L(0) - GV_R \end{aligned}$$

we have an Integro-Differential Equation !.

We can represent the same circuit by differential equations of the form

$$\begin{aligned}C \frac{dV_C}{dt} &= i_L - i_R \\L \frac{di_L}{dt} &= e - V_C\end{aligned}$$

We can write the state equations in matrix form:

$$\begin{bmatrix} \frac{dV_C}{dt} \\ \frac{di_L}{dt} \end{bmatrix} = \begin{bmatrix} -G/C & 1/C \\ -1/L & 0 \end{bmatrix} \begin{bmatrix} V_C \\ i_L \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} e$$

where $i_R = GV_R = GV_C$. This equation can be recast into the standard form

$$\begin{aligned}\dot{X} &= AX + Bu \\ y &= CX + Du\end{aligned}$$

where X is state variable vector, y is output and u is input.

Obtaining State Equations



1. Pick a proper tree :

- The voltage sources must be placed in the tree.
- If the tree is not complete, the edges corresponding to as many capacitors as possible must be placed in the tree. If a capacitor in a loops which consisting entirely of capacitors and voltage sources. The capacitor must not be placed in the tree.
- If the tree is not complete, the edges corresponding to the resistors must be chosen and as many resistors as possible must be included.
- If still the tree is not completed, then, the edges corresponding to the inductors will be chosen until the tree is completed. If an inductors in a cut set which consisting entirely of inductors and current sources, the inductor must be placed in tree.
- All the edges corresponding to the current sources must be placed in the co-tree.

2. After the selection of proper tree, the state variables are branch capacitor voltages and chord inductor currents.



3. Obtaining State Equations from the circuit: Express the voltage across each element corresponding to a branch and the current through each element corresponding to non-branch edge in terms of voltage sources, current sources, and state variables. * If not possible, assign a new voltage variable to a resistor corresponding to a branch and a new current variable to a resistor corresponding to a non-branch edge.
- a Apply KVL to the fundamental loop determined by each non-branch inductor.
 - b Apply KCL to the fundamental cut-set determined by each branch capacitor.
 - c Apply KVL to the fundamental loop determined by each resistor with a new current variable assigned in *.
 - d Apply KCL to the node or super-node corresponding to the fundamental cut-set determined by each resistor with a new voltage variable assigned in *
 - e Solve the simultaneous equations obtained from steps c and d for the new variables in terms of the voltage sources, current sources, and the state variables.
 - f Substitute the expressions obtained in step e into the equations determined in steps a and b.

Example

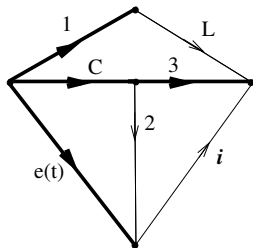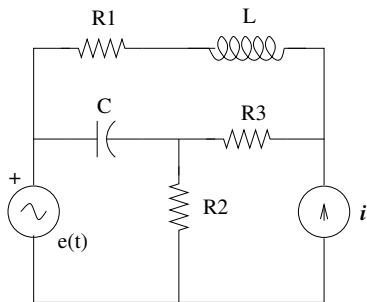

- 1 Graph is drawn and pick the proper tree.
- 2 V_C and i_L state variables.
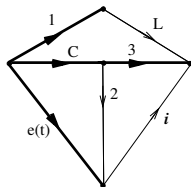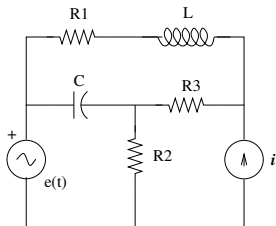
$$\dot{V}_C = f(V_C, i_L, e(t), i(t)) \quad \dot{i}_L = f(V_C, i_L, e(t), i(t))$$



- 1 KVL for the fundamental loop determined by the inductor and KCL to the fundamental cut-set determined by the capacitor.

$$i_C + i_L - i_2 + i = 0$$

$$V_L - V_3 - V_C + V_1 = 0$$

using the definition of the inductor and capacitor

$$C \frac{dV_C}{dt} = -i_L + i_2 - i$$

$$L \frac{di_L}{dt} = V_3 + V_C - V_1$$

KVL for the fundamental loop determined by R_2 and KCL to the fundamental cut-set determined by R_1 and R_3

$$\begin{aligned}R_2 i_2 &= e - V_C \\G_1 V_1 &= i_L \\G_3 V_3 &= -i_L - i\end{aligned}$$



Substitute the expressions

$$\frac{d}{dt} \begin{bmatrix} V_C \\ i_L \end{bmatrix} = \begin{bmatrix} \frac{-1}{R_2 C} & \frac{-1}{C} \\ \frac{1}{L} & \frac{-(R_3 + R_1)}{L} \end{bmatrix} \begin{bmatrix} V_C \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{1}{R_2 C} \\ 0 \end{bmatrix} e(t) + \begin{bmatrix} \frac{-1}{C} \\ -\frac{R_3}{L} \end{bmatrix} i$$

Degenerate Circuit



Circuit which contains any

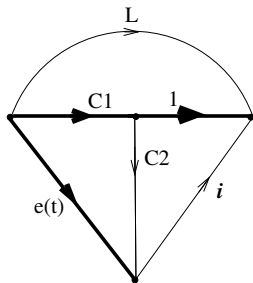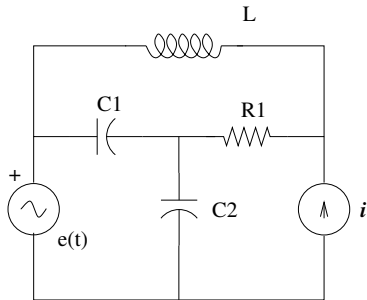- Loops consisting entirely of capacitors and voltage sources.
- Cutsets consisting entirely of inductors and current sources.





two capacitors and the voltage source make a loop.

Degenerate Circuit

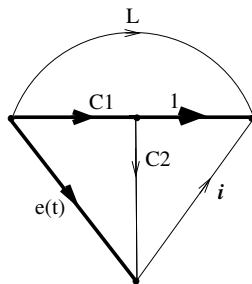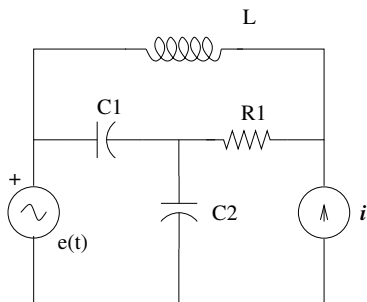

1. $C2$ must be placed to co-tree.

Degenerate Circuit

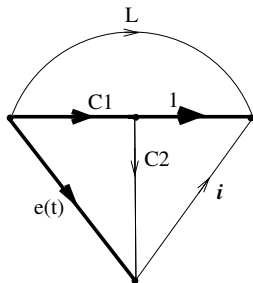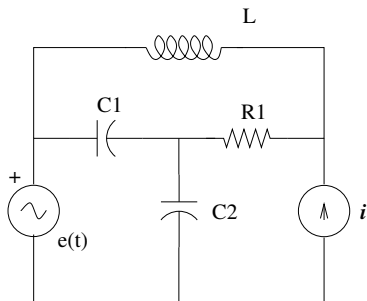

2. The state variables are V_{C1} i_L .
3. KCL and KVL

$$\begin{aligned}i_{C1} + i_L - i_{C2} + i &= 0 \\V_L - V_1 - V_{C1} &= 0\end{aligned}$$

Using the definition of C and L elements, the state equations;

$$\begin{aligned}C_1 \frac{dV_{C1}}{dt} &= -i_L - i + i_{C2} \\L \frac{di_L}{dt} &= V_1 + V_{C1}\end{aligned}$$

Degenerate Circuit

Apply KVL to the fundamental loop determined by C_2 and KCL to the fundamental cut-set determined by R_1

$$\begin{aligned}V_{C_2} &= e - V_{C_1} \\ G_1 V_1 &= -i_L - i\end{aligned}$$

In order to obtain i_{C_2} in terms of the voltage sources, current sources, and the state variables, we will use the definition of capacitor ($i_{C_2} = C_2 \frac{dV_{C_2}}{dt}$).

$$C_2 \frac{dV_{C_2}}{dt} = C_2 \frac{de}{dt} - C_2 \frac{dV_{C_1}}{dt}$$


The state equation in standard form

$$\begin{aligned}C_1 \frac{dV_{C_1}}{dt} &= -i_L - i + C_2 \frac{de}{dt} - C_2 \frac{dV_{C_1}}{dt} \\ L \frac{di_L}{dt} &= -R_1(i_L - i) + V_{C_1}\end{aligned}$$



$$\frac{d}{dt} \begin{bmatrix} V_{C_1} \\ i_L \end{bmatrix} = \begin{bmatrix} 0 & \frac{-1}{C_2 + C_1} \\ \frac{1}{L} & \frac{-R}{L} \end{bmatrix} \begin{bmatrix} V_{C_1} \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{C_2}{C_1 + C_2} \\ 0 \end{bmatrix} \frac{de}{dt} + \begin{bmatrix} \frac{-1}{C_1 + C_2} \\ \frac{-R}{L} \end{bmatrix} i$$


All the edge corresponding to the dependent voltage source must be placed in tree. All the edge corresponding to the dependent current source must be placed in co-tree.

Example

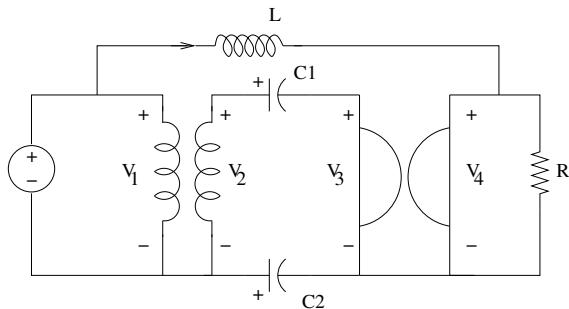


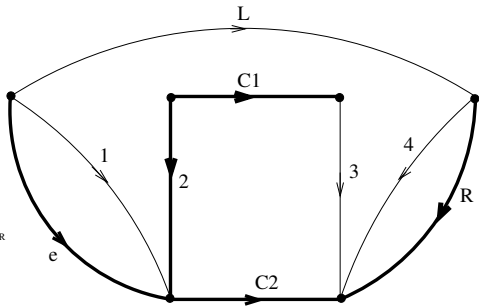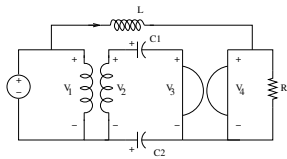Transformer $V_2 = nV_1$, $i_1 = -ni_2$ and Gyrator $i_3 = -\alpha V_4$, $i_4 = \alpha V_3$



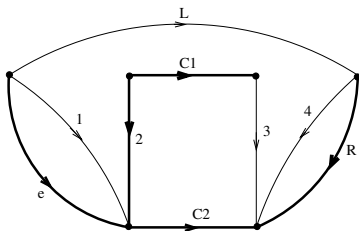

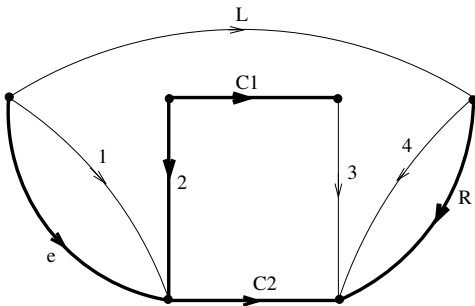1. Graph is drawn. The voltage sources e , capacitors $C1$ and $C2$ are placed to tree. The tree is not complete, edge 2 is a dependent voltage source which is placed to tree. The edges 3 and 4 are placed to co-tree.
2. V_{C1} , V_{C2} and i_L are state variable.



3. From the fundamental cut-sets and loop, we have

$$\begin{aligned}
 i_{C1} + i_3 &= 0 \\
 i_{C2} + i_L + i_3 &= 0 \\
 V_L + V_R - V_{C2} - e &= 0
 \end{aligned}$$

The state equations;

$$\begin{aligned} C_1 \frac{dV_{C1}}{dt} &= -i_3 \\ C_2 \frac{dV_{C2}}{dt} &= -i_L - i_3 \\ L \frac{di_L}{dt} &= -V_R + V_{C2} + e \end{aligned}$$

Express the i_3 and V_R as function of state variable and independent sources

$$\begin{aligned} i_R &= -i_4 + i_L = i_L - \alpha V_3 = i_L - \alpha(-V_{C1} + V_2 + V_{C2}) \\ &= i_L - \alpha(-V_{C1} + ne + V_{C2}) \\ i_3 &= \alpha V_4 = \alpha V_R = \alpha R i_R \end{aligned}$$


$$\frac{d}{dt} \begin{bmatrix} V_{C1} \\ V_{C2} \\ i_L \end{bmatrix} = \begin{bmatrix} \text{---} & \text{---} & \text{---} \\ \text{---} & \text{---} & \text{---} \\ \text{---} & \text{---} & \text{---} \end{bmatrix} \begin{bmatrix} V_{C1} \\ V_{C2} \\ i_L \end{bmatrix} + \begin{bmatrix} \text{---} \\ \text{---} \\ \text{---} \end{bmatrix} e$$

Obtaining State Equations directly from the circuit

Consider a dynamic circuit that does not contain any

- Loops consisting entirely of capacitors and voltage sources.
- Cutsets consisting entirely of inductors and current sources.

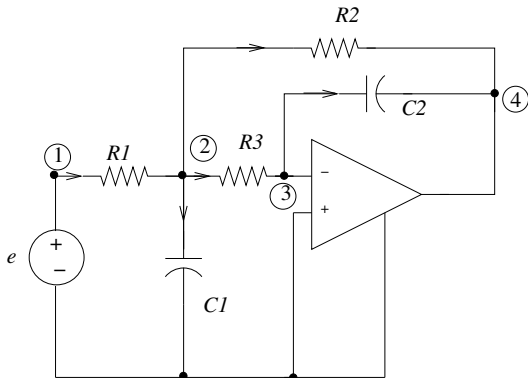The objective of the analysis is to express the currents of capacitors and the voltages of the inductors as a function of the voltages of the capacitors, the currents of the inductors and the independent sources.



$$C_1 \frac{dV_{C1}}{dt} = G_1(V_{d1} - V_{d2}) - G_3(V_{d2} - V_{d3}) - G_2(V_{d2} - V_{d4})$$

$$C_2 \frac{dV_{C2}}{dt} = G_3(V_{d2} - V_{d3})$$

$$\begin{aligned}
 V_{d1} &= e \\
 V_{d3} &= 0 \\
 V_{d2} &= V_{C1} \\
 V_{d4} &= -V_{C2}
 \end{aligned}$$

Using the above equations, the state equations;

$$\begin{aligned}
 C_1 \frac{dV_{C1}}{dt} &= G_1(e - V_{C1}) - G_3(V_{C1}) - G_2(V_{C1} + V_{C2}) \\
 C_2 \frac{dV_{C2}}{dt} &= G_3 V_{C1}
 \end{aligned}$$

In standard matrix form:

$$\frac{d}{dt} \begin{bmatrix} V_{C1} \\ V_{C2} \end{bmatrix} = \begin{bmatrix} -\frac{G_1+G_2+G_3}{C_1} & -\frac{G_2}{C_1} \\ -\frac{G_3}{C_2} & 0 \end{bmatrix} \begin{bmatrix} V_{C1} \\ V_{C2} \end{bmatrix} + \begin{bmatrix} \frac{G_1}{C_1} \\ 0 \end{bmatrix} e$$