

# Basic of Electrical Circuits

## EHB 211E

Prof. Dr. Müştak E. Yalçın

Istanbul Technical University  
Faculty of Electrical and Electronic Engineering

[mustak.yalcin@itu.edu.tr](mailto:mustak.yalcin@itu.edu.tr)

Lecture 2.



# Contents I

- First Postulate of Circuit Theory
- From Circuit to Graph
- Kirchhoff Voltage Law (KVL)
- Kirchhoff Current Law (KCL)
- Examples
- Tellegen Theorem

# First Postulate of Circuit Theory
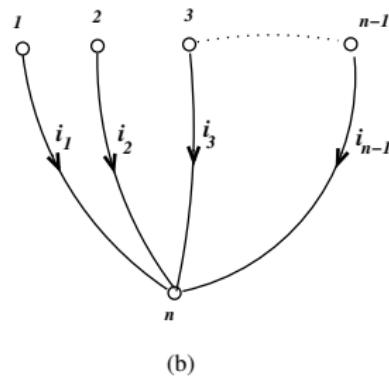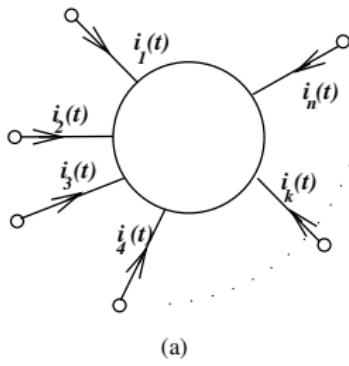
## First Postulate of Circuit Theory

All the properties of an  $n$ -terminal (or  $n - 1$ -port) electrical element can be described by a mathematical relation between a set of  $(n - 1)$  voltage and a set of  $(n - 1)$  current variables.



# First Postulate of Circuit Theory

Terminal variables and Terminal equation of n-terminal circuit element:


$$v = \begin{bmatrix} V_{1,n} \\ V_{2,n} \\ V_{3,n} \\ \vdots \\ \vdots \\ V_{n-1,n} \end{bmatrix}, i = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ \vdots \\ \vdots \\ i_{n-1} \end{bmatrix} \text{ and } f\left(v, i, \frac{dv}{dt}, \frac{di}{dt}, t\right) = 0$$

Power delivered at time  $t$  to the n-terminal circuit element:

$$P = \sum_{k=1}^n v_k i_k$$

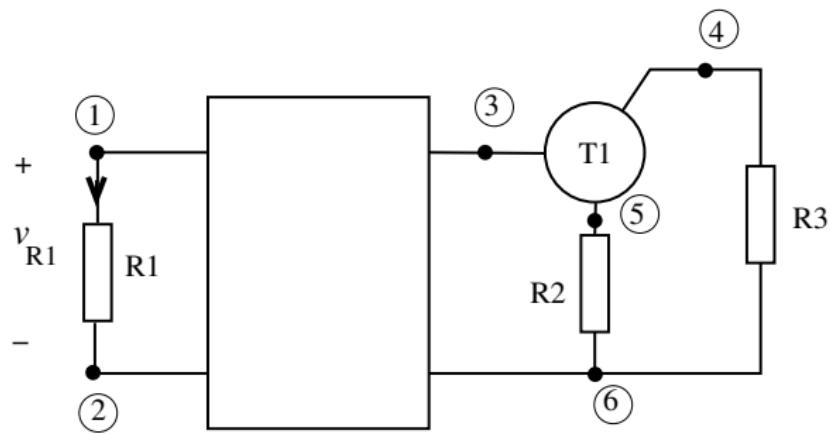
# From Circuit to Graph

For a given circuit if we replace each element by its element graph, the result is a directed circuit graph (digraph).



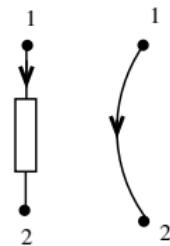
# From Circuit to Graph


For a given circuit if we replace each element by its element graph, the result is a directed circuit graph (digraph).




(a)

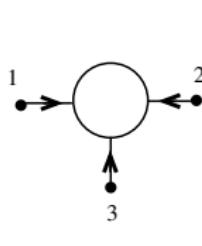



(b)

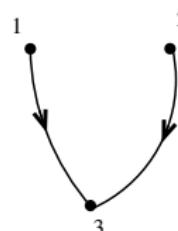



(d)

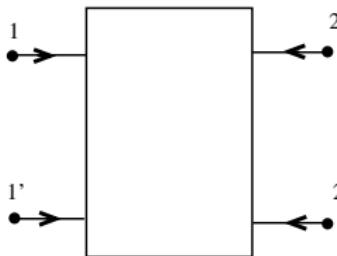


(e)

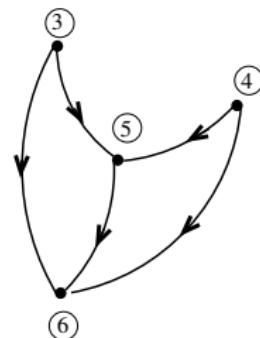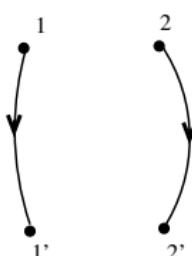

# From Circuit to Graph

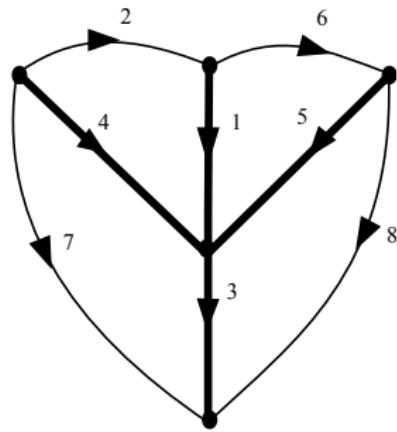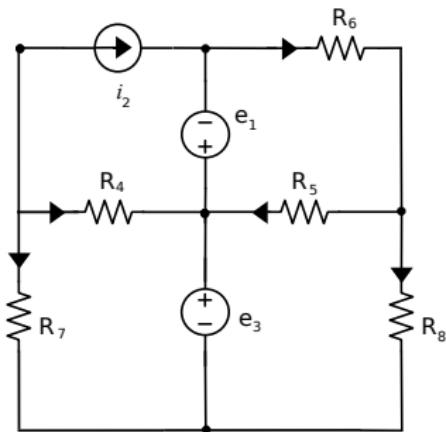

# From Circuit to Graph

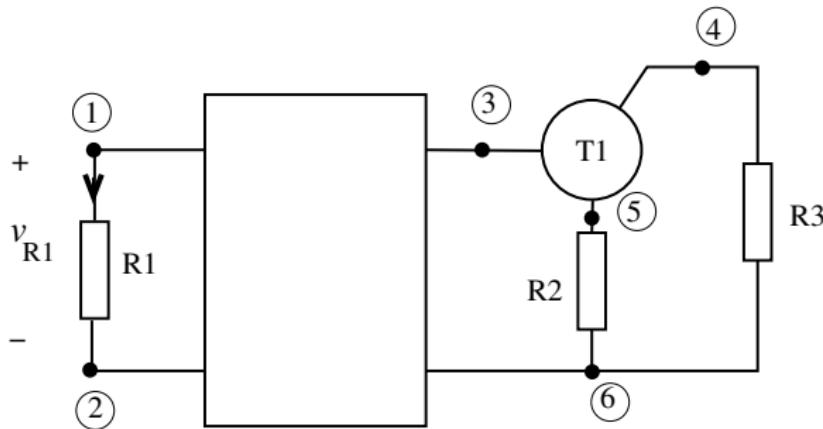


Node voltages:  $e_1, e_2, \dots, e_n$ .

Let  $v_{k,l}$  denote the voltage difference between node k and node l.

$$v_{k,l} = e_k - e_l$$

# Noda Voltage

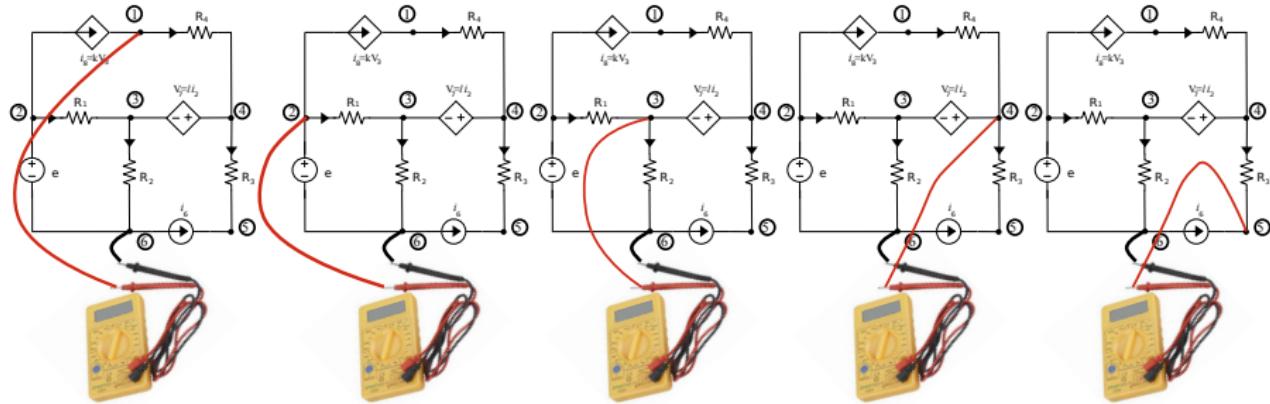

$$e_1, e_2, e_3, e_4, e_5, e_6 = 0$$


$$V_1 = e_2 - e_3; V_2 = e_3 - e_6; V_3 = e_4 - e_5; V_4 = e_1 - e_4; \dots$$

if we know the nodes voltage, we can calculate all the branch voltages!

# Kirchhoff's Law

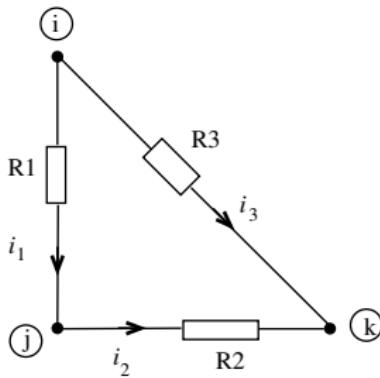
## Second Postulate of Circuit Theory: Kirchhoff Voltage Law (KVL)

For all lumped connected circuits, for all closed node sequences, for all times t, the algebraic sum of all node-to-node voltages around the chosen closed node sequence is equal to zero.



Let us consider the closed node sequence  $i - j - k - i$ .

# Kirchhoff Voltage Law (KVL)

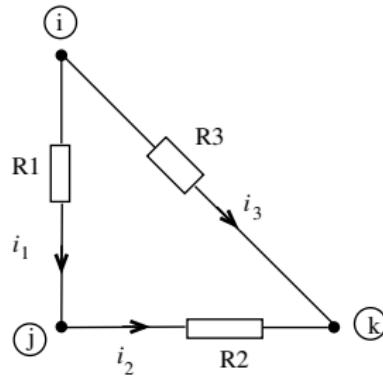

Let us consider the closed node sequence  $i - j - k - i$ .


$$V_{i,j} + V_{j,k} + V_{k,i} = 0$$

$$e_i - e_j + e_j - e_k + e_k - e_i = 0$$

# Kirchhoff Current Law (KCL)
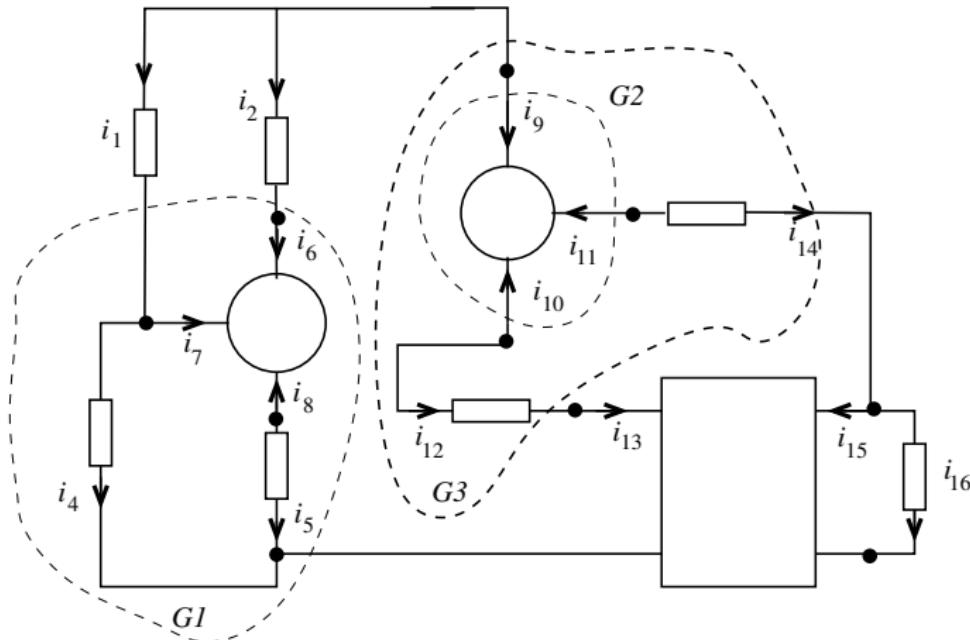
## Gaussian Surface

It is a closed surface such that it cuts only the connecting wires which connect the circuit elements.




# KCL from Electromagnetism Theory

Continuity equation;

Charge is leaving the enclosed volume

$$\int_S J \, da = -\frac{d}{dt} \int_V \rho \, dv$$

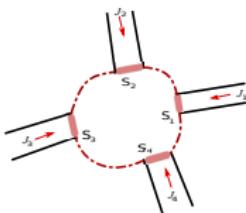The total charge inside the volume at any instant



if charge density is constant ( $\rho$ );  $\int_S J \, da = 0$ . Conductive currents are within wires so  $J_i$  is non-zero only though  $S_i$ ,


$$\int_S J \, da = \sum_{i=1}^4 \int_{S_i} J \, da = \sum_{i=1}^4 i_i = 0$$

# Kirchhoff Current Law (KCL)

## Third Postulate of Circuit Theory: Kirchhoff Current Law (KCL)

For all lumped circuits, for all gaussian surfaces  $G$ , for all times  $t$ , the algebraic sum of all the currents leaving the gaussian surface  $G$  at time  $t$  is equal to zero.

# Kirchhoff Current Law (KCL)

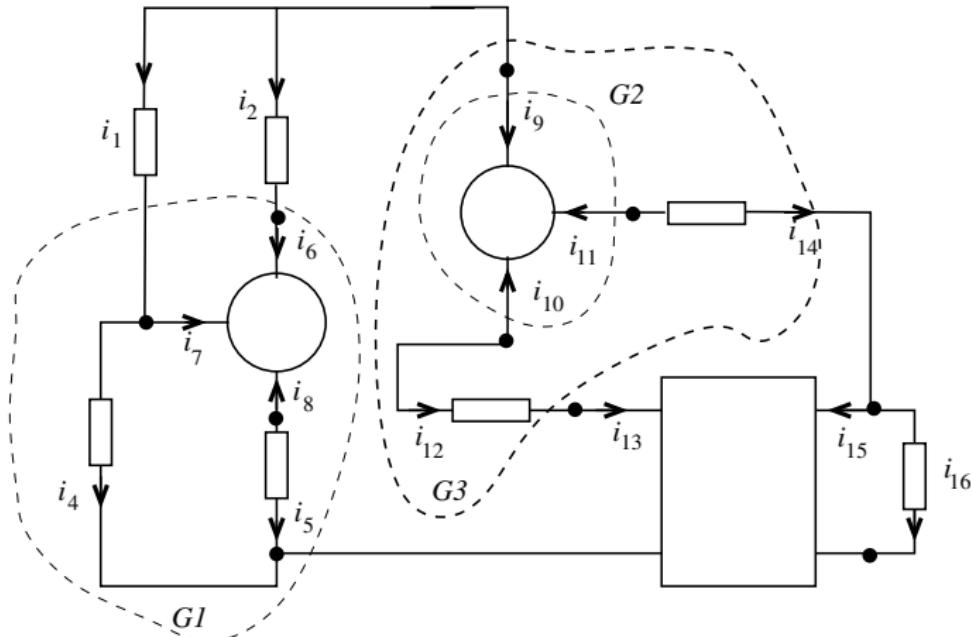

$$G1 \quad i_1 + i_2 + i_{13} = 0$$


$$G2 \quad i_9 + i_{10} + i_{11} = 0$$

$$G3 \quad i_9 - i_{12} - i_{14} = 0$$

# Kirchhoff Current Law (KCL)
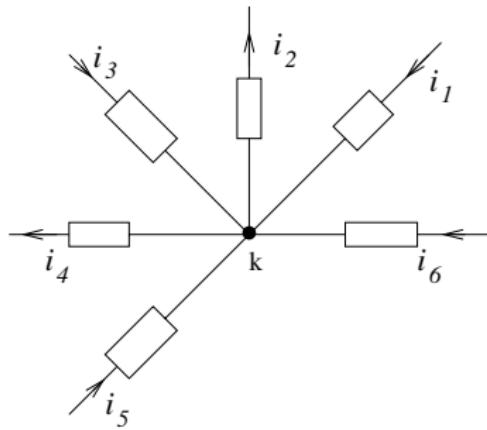
## KCL (node law)


For all lumped circuits, for all times  $t$ , the algebraic sum of the currents leaving any node is equal to zero.



For the node k:

$$i_1 - i_2 + i_3 - i_4 + i_5 + i_6 = 0$$

# Examples

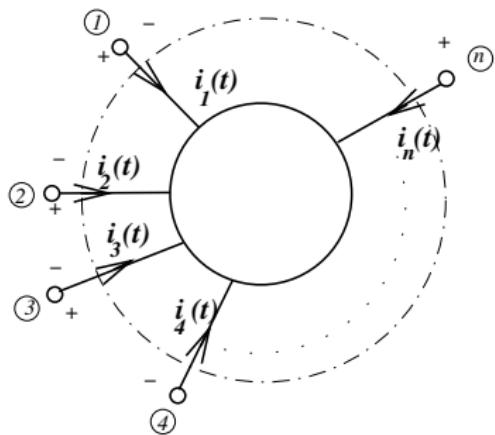


For Gaussian surface;

$$i_1 + i_2 + \dots + i_{n-1} + i_n = 0$$

$n - 1$  currents can be specified independently! Why ?

$$-i_n = i_1 + i_2 + \dots + i_{n-1}$$

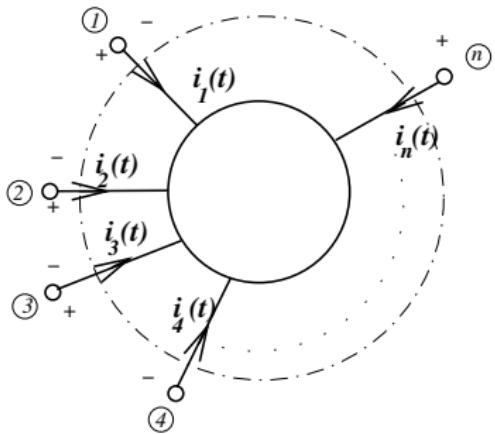


Let us consider the closed node sequence 1-2-3-...-n-1 and apply KVL (the sum of the voltages is equal to zero)

$$V_{1,2} + V_{2,3} + V_{3,4} + \dots + V_{n-1,n} + V_{n,1} = 0$$

$n - 1$  voltages can be specified independently! Why ?

$$-V_{n,1} = V_{1,2} + V_{2,3} + V_{3,4} + \dots + V_{n-1,n}$$

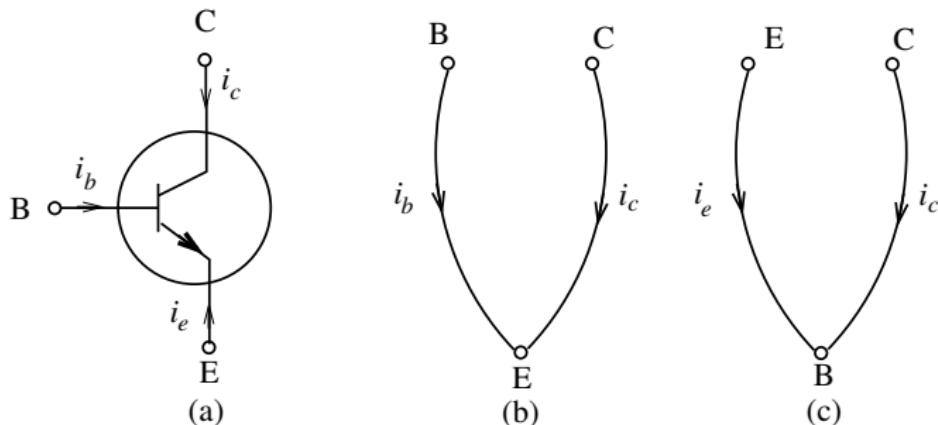**Remember :** First Postulate of Circuit Theory: All the properties of an  $n$ -terminal (or  $n - 1$ -port) electrical element can be described by a mathematical relation between a set of  $(n - 1)$  voltage and a set of  $(n - 1)$  current variables



Mathematical model is given by the terminal equation

$$\begin{bmatrix} v_{bc} \\ i_c \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_b \\ v_{ce} \end{bmatrix}$$

and terminal graph (b). Find the terminal equation in the form

$$\begin{bmatrix} v_{eb} \\ i_c \end{bmatrix} = \begin{bmatrix} ? & ? \\ ? & ? \end{bmatrix} \begin{bmatrix} i_e \\ v_{cb} \end{bmatrix}$$

if (c) is the terminal graph.

## Terminal equations

$$\begin{aligned}v_{bc} &= h_{11}i_b + h_{12}v_{ce} \\i_c &= h_{21}i_b + h_{22}v_{ce}\end{aligned}$$

KCL and KVL for the circuit element

$$\begin{aligned}i_c + i_e + i_b &= 0 \\v_{ce} + v_{eb} + v_{bc} &= 0.\end{aligned}$$

New terminal variables are  $i_e$  and  $V_{eb}$  (additional to  $i_c$  and  $V_{cb}$  ).  
Substituting KVL and KCL Eqs. into above Eqs. we obtain

$$\begin{aligned}v_{bc} &= h_{11}(-i_c - i_e) + h_{12}(-v_{eb} + v_{cb}) \\i_c &= h_{21}(-i_c - i_e) + h_{22}(-v_{eb} + v_{cb})\end{aligned}$$

$$\begin{aligned} h_{12}v_{eb} + h_{11}i_c &= -h_{11}(i_e) + (1 + h_{12})v_{cb} \\ (1 + h_{21})i_c + h_{22}v_{eb} &= -h_{21}i_e + h_{22}v_{cb} \end{aligned}$$

New terminal equations

$$\begin{bmatrix} h_{12} & h_{11} \\ h_{22} & 1 + h_{21} \end{bmatrix} \begin{bmatrix} v_{eb} \\ i_c \end{bmatrix} = \begin{bmatrix} -h_{11} & (1 + h_{12}) \\ -h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_e \\ V_{cb} \end{bmatrix}$$

and terminal graph (c) will be the new mathematical model !

# Tellegen Theorem

Tellegen's theorem is based on the fundamental law of conservation of energy!


## Tellegen Theorem

It states that the algebraic sum of power absorbed by all elements in a circuit is zero at any instant.

Tellegen's theorem asserts that

$$\sum_{k=1}^{n_e} v_k i_k = 0$$

# Tellegen Theorem

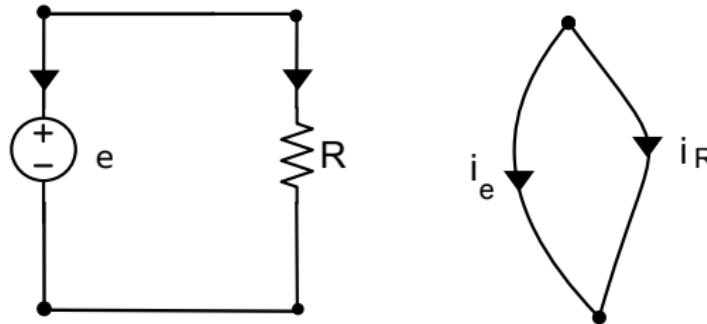

$R = 2\Omega$  and  $e = 2V$ , from KCL

$$i_e = -i_R = \frac{2}{2} = 1A$$

Lets apply Tellegen Theorem:

$$P = i_e \cdot e + V_R \cdot i_R = 2 \cdot (-1) + 2 \cdot 1$$

Power absorbed by a resistor is always positive, whereas a source may deliver power. Then in this case, the power associated with the source is negative.