

# Basic of Electrical Circuits

## EHB 211E

Prof. Dr. Müştak E. Yalçın

Istanbul Technical University  
Faculty of Electrical and Electronic Engineering

[mustak.yalcin@itu.edu.tr](mailto:mustak.yalcin@itu.edu.tr)

Lecture 5.

# Contents I

- Fundamental Loop Analysis
- Mesh Equation
- Fundamental Cut-set
- Example



# Fundamental Loop Analysis

## Fundamental Loop

Every link of  $G_T$  and the unique tree path between its nodes constitute a unique loop. This loop is called the Fundamental loop associated with the link.

Consider a link  $l$  which connects nodes 1 and 2. There is a unique tree path between 1 and 2. This path, together with the link  $l$ , constitutes a loop. There cannot be any other loop.


## Fundamental Loop Equation

The linear algebraic equations obtained by applying KVL to each Fundamental loop constitute a set of  $n_e - n_n - 1$  linearly independent equations.

Reference direction for the loop which agrees with that of the link defining the loop.



# Fundamental Loop Analysis

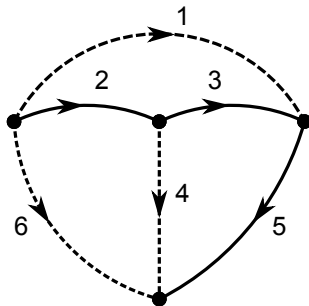

The links  $G_L = \{1, 4, 6\}$  for the chosen tree  $G_T = \{2, 3, 5\}$ . The Fundamental loop sets are  $G_{L1} = \{1, 2, 3\}$   $G_{L4} = \{4, 5, 3\}$   $G_{L6} = \{6, 2, 3, 5\}$ .

If we apply KVL to the Fundamental loops, we obtain:

$$V_1 - V_3 - V_2 = 0$$

$$V_4 - V_5 - V_3 = 0$$

$$V_6 - V_2 - V_3 - V_5 = 0$$



# Fundamental Loop Analysis

$$V = \begin{bmatrix} V_l \\ \text{---} \\ V_b \end{bmatrix} = \begin{bmatrix} V_1 \\ V_4 \\ V_6 \\ \text{---} \\ V_2 \\ V_3 \\ V_5 \end{bmatrix}$$

where  $V_l$  is link voltage vector,  $V_b$  is tree branch voltage vector. In matrix form:

$$\begin{bmatrix} 1 & 0 & 0 & | & -1 & -1 & 0 \\ 0 & 1 & 0 & | & 0 & -1 & -1 \\ 0 & 0 & 1 & | & -1 & -1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_4 \\ V_6 \\ \text{---} \\ V_2 \\ V_3 \\ V_5 \end{bmatrix} = 0$$



# Fundamental Loop Analysis

$$B = \left[ \begin{array}{ccc|ccc} 1 & 0 & 0 & -1 & -1 & 0 \\ 0 & 1 & 0 & 0 & -1 & -1 \\ 0 & 0 & 1 & -1 & -1 & -1 \end{array} \right]$$

$B$  is an  $n_b - n_n + 1 \times n_b$  matrix called the Fundamental loop matrix.

$$BV = [ I|F ] \begin{bmatrix} V_l \\ - \\ V_b \end{bmatrix} = 0$$


$$V_l = -FV_b$$

The number of Fundamental loop equations is  $n_e - n_n + 1$  (=number of links).


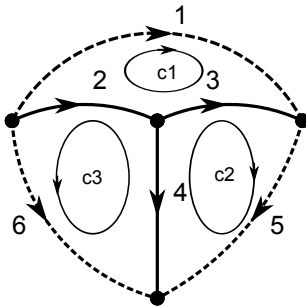
# Mesh Equation

Meshes are special case of the Fundamental loops i.e., there exists a tree such that the meshes are Fundamental loops\*\*\*\*.



There are 3 meshes. Corresponding loop sets and mesh currents (loop currents)  $G_{M1} = \{1, 2, 3\}$  and  $i_{m1}$ ;  $G_{M2} = \{3, 4, 5\}$  and  $i_{m2}$ ;  $G_{M3} = \{2, 4, 6\}$  and  $i_{m3}$ .



# Mesh Analysis

$$\begin{aligned}i_1 &= i_{m1} \\i_2 &= -i_{m3} - i_{m1} \\i_3 &= -i_{m2} + i_{m1} \\i_4 &= -i_{m3} - i_{m1} \\i_5 &= i_{m2} \\i_6 &= i_{m3}\end{aligned}$$

$$i = \begin{bmatrix} 1 & 0 & 0 & -1 & -1 & 0 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & 0 & -1 \end{bmatrix}^T = B_f^T i_c$$

where  $i = [i_1 \ i_5 \ i_6 \ i_2 \ i_3 \ i_4]^T$  is branch current vector and  $i_m = [i_{m1} \ i_{m2} \ i_{m3}]^T$  is mesh current vector.






# Fundamental Cut-set
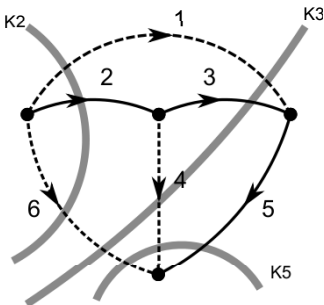
## Cut-set


is made up of links and of one tree branch, namely the tree branch which defines the cut set. Every tree branch defines a unique Fundamental cut set.



Cut sets of the tree of  $G_T = \{2, 3, 5\}$  are  $G_{C2} = \{2, 1, 6\}$   
 $G_{C3} = \{3, 1, 4, 5\}$   $G_{C5} = \{5, 4, 6\}$ .



# Fundamental Cut-set

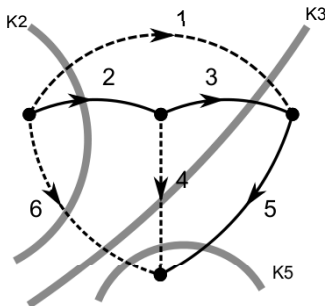

If we apply KCL to the three cut sets, we obtain

$$i_2 + i_1 + i_6 = 0$$

$$i_3 + i_1 + i_4 + i_6 = 0$$

$$i_4 + i_5 + i_6 = 0$$

which are called Fundamental cut-set equations. Reference direction for the cut set which agrees with that of the tree branch defining the cut set.



# Fundamental Cut-set

$$i = \begin{bmatrix} i_l \\ \text{---} \\ i_b \end{bmatrix} = \begin{bmatrix} i_1 \\ i_4 \\ i_6 \\ \text{---} \\ i_2 \\ i_3 \\ i_5 \end{bmatrix}$$

where  $i_l$  is link current vector and  $i_b$  is tree branch current vector. In matrix form:

$$\begin{bmatrix} 1 & 0 & 1 & | & 1 & 0 & 0 \\ 1 & 1 & 1 & | & 0 & 1 & 0 \\ 0 & 1 & 1 & | & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_4 \\ i_6 \\ \text{---} \\ i_2 \\ i_3 \\ i_5 \end{bmatrix} = 0$$



# Fundamental Cut-set

$$Qi = [ E|I ] \begin{bmatrix} i_l \\ \text{---} \\ i_b \end{bmatrix} = 0$$

$Q$  is called the Fundamental cut-set matrix.  $Q$  is an  $n_b - n_n + 1 \times n_n - 1$

$$i_b = -Ei_l$$

$Q$  has a rank  $n_n - 1$  it includes the unit matrix. Hence the linear algebraic equations obtained by applying KCL to each Fundamental cut set constitute a set of  $n_n - 1$  linearly independent equations.



## Relation Between $B$ and $Q$

$$F = -E^T$$

**Proof :** Since they are the tree-branch voltages of the tree, the branch voltages are given by

$$V = Q^T V_n$$

$$BV = BQ^T V_n = 0$$

$$BQ^T V_n = 0$$

$$BQ^T = 0$$



$$IE^T + FI = 0$$

$$E^T + F = 0$$



$$E^T = -F$$



# Example

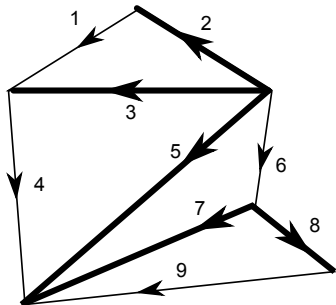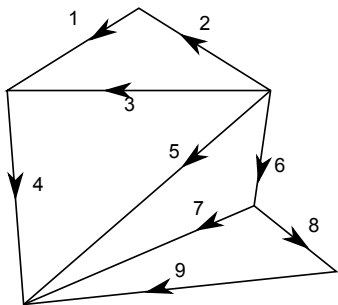

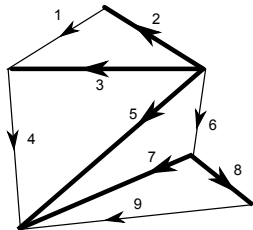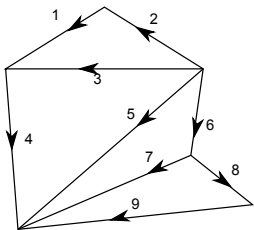Fundamental cut sets of the tree  $G_T = \{2, 3, 5, 7, 8\}$  are  $G_{C2} = \{2, 1\}$ ,  
 $G_{C3} = \{3, 1, 4\}$ ,  $G_{C5} = \{5, 4, 6\}$ ,  $G_{C7} = \{7, 6, 9\}$ ,  $G_{C8} = \{8, 9\}$ .





KCL equations based on Fundamental cut sets

$$\left[ \begin{array}{cccc|cccccc}
 -1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\
 1 & -1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\
 0 & 1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\
 0 & 0 & -1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 \\
 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 & 0 & 1
 \end{array} \right] \begin{array}{c} i_1 \\ i_4 \\ i_6 \\ i_9 \\ \hline i_2 \\ i_3 \\ i_5 \\ i_7 \\ i_8 \end{array} = 0$$





# Example

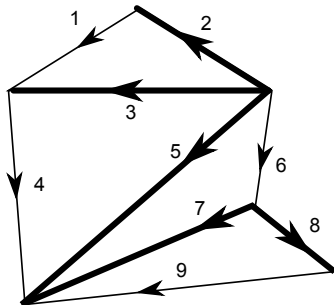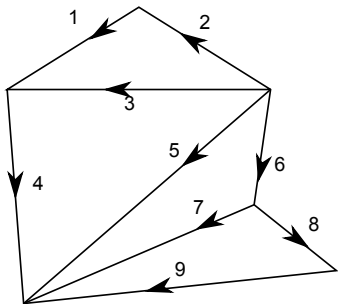

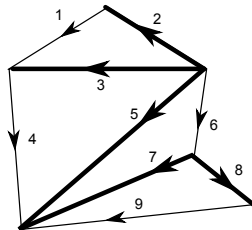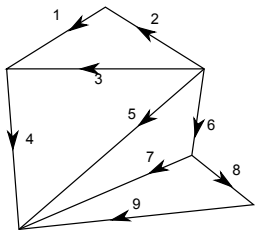
Fundamental Loop sets of the tree  $G_T = \{2, 3, 5, 7, 8\}$  are  $G_{L1} = \{1, 2, 3\}$ ,  
 $G_{L4} = \{4, 3, 4\}$ ,  $G_{L6} = \{6, 5, 6\}$ ,  $G_{L9} = \{9, 7, 8\}$ .






KVL equations based on the Fundamental loops

$$\left[ \begin{array}{cccc|cccc}
 1 & 0 & 0 & 0 & 1 & -1 & 0 & 0 & 0 \\
 0 & 1 & 0 & 0 & 0 & 1 & -1 & 0 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 & -1 & 1 & 0 \\
 0 & 0 & 0 & 1 & 0 & 0 & 0 & -1 & 1
 \end{array} \right]
 \begin{bmatrix}
 V_1 \\
 V_4 \\
 V_6 \\
 V_9 \\
 \text{---} \\
 V_2 \\
 V_3 \\
 V_5 \\
 V_7 \\
 V_8
 \end{bmatrix}
 = 0$$

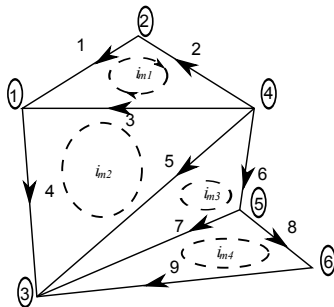

KVL equations for the nodes


$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \\ V_9 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & -1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & -1 \\ 0 & 0 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_{n1} \\ V_{n2} \\ V_{n3} \\ V_{n4} \\ V_{n5} \\ V_{n6} \end{bmatrix}$$

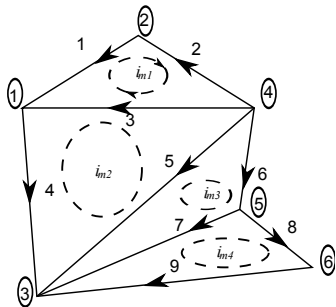

KCL equations for the nodes

$$\begin{bmatrix}
 -1 & 0 & -1 & 1 & 0 & 0 & 0 & 0 & 0 \\
 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & -1 & -1 & 0 & -1 & 0 & -1 \\
 0 & 1 & 1 & 0 & 1 & 1 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & -1 & 1 & 1 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1
 \end{bmatrix}
 \begin{bmatrix}
 i_1 \\
 i_2 \\
 i_3 \\
 i_4 \\
 i_5 \\
 i_6 \\
 i_7 \\
 i_8 \\
 i_9
 \end{bmatrix}
 = 0$$

Mesh equations

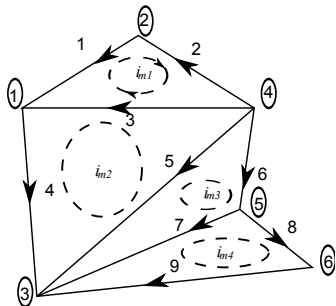

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \\ i_8 \\ i_9 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 0 & 0 \\ -1 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{m1} \\ i_{m2} \\ i_{m3} \\ i_{m4} \end{bmatrix}$$