

Obtain the terminal equ. of the circuit given in Fig. 1 for the terminal graph given in Fig. 2

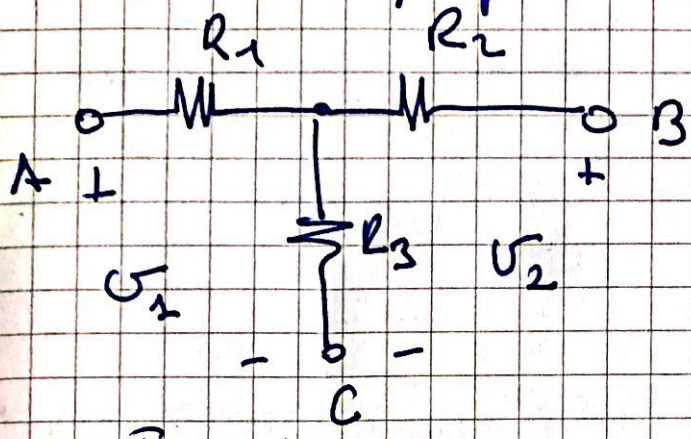


Figure 1.

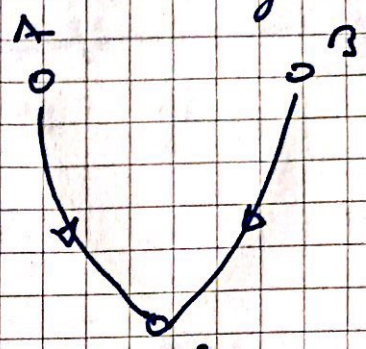


Figure 2.

Terminal Equ. →


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} ? \\ ? \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$a_{11} = \frac{V_1}{i_1} \Big|_{i_2=0}$$


$$a_{12} = \frac{V_1}{i_2} \Big|_{i_1=0}$$

$$a_{21} = \frac{V_2}{i_1} \Big|_{i_2=0}$$

$$a_{22} = \frac{V_2}{i_2} \Big|_{i_1=0}$$

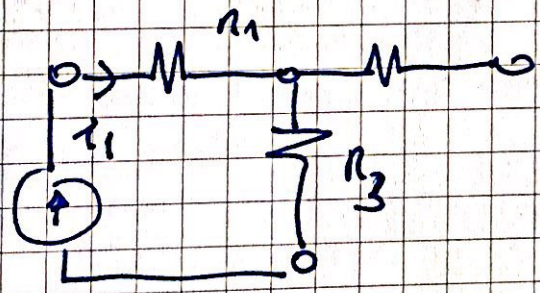
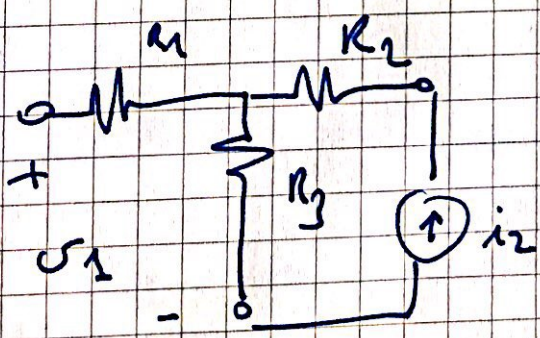
$$\begin{aligned} V_1 &= i_1 (R_1 + R_3) & V_2 &= R_3 i_1 \\ a_{11} &= R_1 + R_3 & & \end{aligned}$$



$$\begin{aligned} V_1 &= R_3 i_2 & V_2 &= (R_3 + R_2) i_2 \\ a_{21} &= R_3 & & \end{aligned}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_3 + R_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



Obtain the terminal eqn. of the circuit given in Fig 1 for the terminal given in Fig. 2.

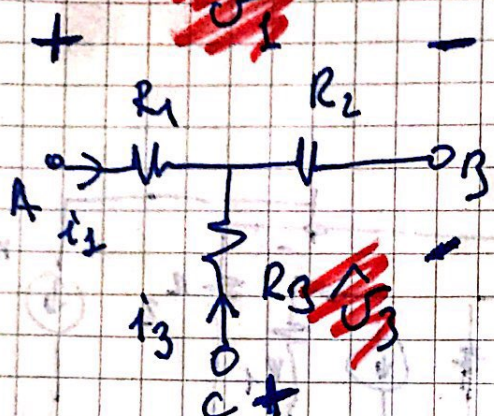


Figure 1.


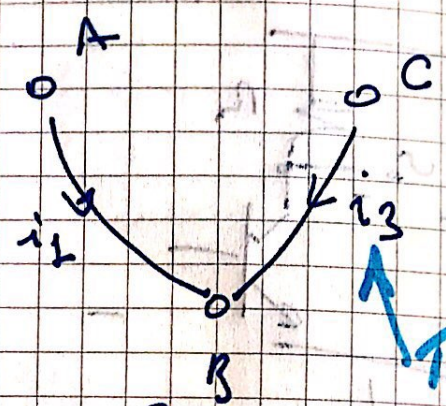


Figure 2.

Terminal Equ.

$$\begin{bmatrix} \hat{U}_1 \\ \hat{U}_3 \end{bmatrix} = \begin{bmatrix} ? \\ ? \end{bmatrix} \begin{bmatrix} i_1 \\ i_3 \end{bmatrix}$$


$$D_{11} = \frac{\hat{U}_1}{i_1} \Big|_{i_3=0}, \quad D_{12} = \frac{\hat{U}_1}{i_3} \Big|_{i_1=0}, \quad D_{21} = \frac{\hat{U}_3}{i_1} \Big|_{i_3=0}, \quad D_{22} = \frac{\hat{U}_3}{i_3} \Big|_{i_1=0}$$

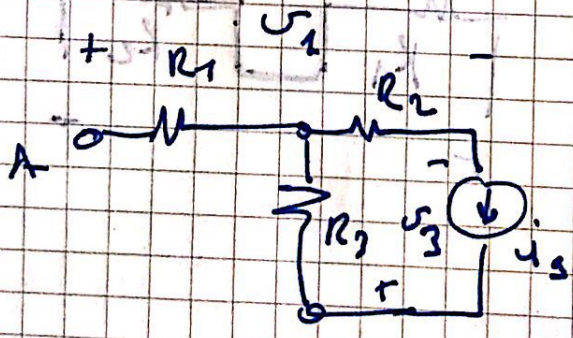

$$\hat{U}_3 = (R_3 + R_2) i_3$$

$$\hat{U}_2 = R_2 i_3$$

$$\hat{U}_1 = U_2 = R_2 i_3$$

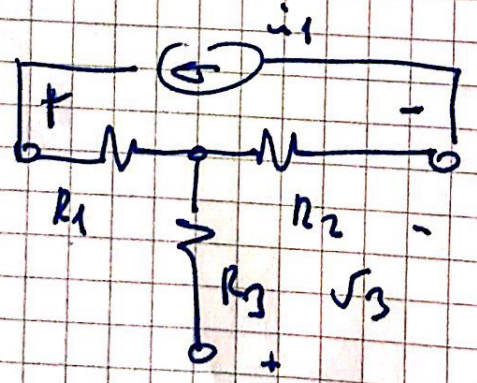

$$\hat{U}_1 = (R_1 + R_2) i_1 \quad ; \quad \hat{U}_3 = R_2 i_1$$

$$\begin{bmatrix} \hat{U}_1 \\ \hat{U}_3 \end{bmatrix} = \begin{bmatrix} R_1 + R_2 & R_2 \\ R_2 & R_3 + R_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_3 \end{bmatrix}$$



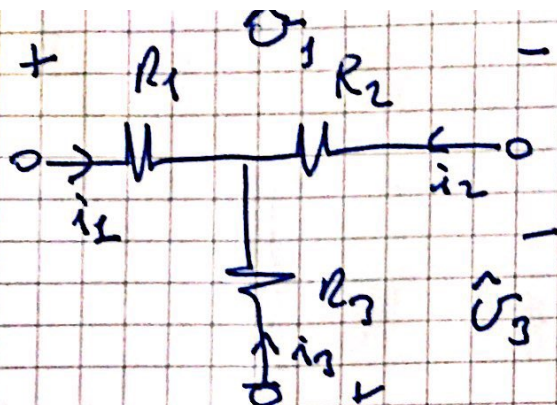


Figure 1

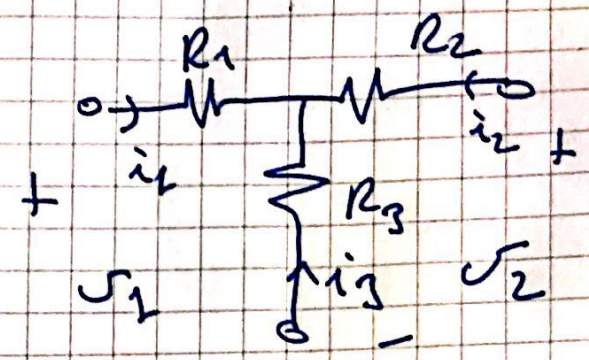


Figure 2

Obtain the terminal Equ₁ of Figure 1 from the terminal equations of Figure 2.

$$\hat{U}_1 = U_1 - U_2$$

$$i_1 + i_2 + i_3 = 0$$

$$\hat{U}_3 = -U_2$$

$$\begin{vmatrix} \hat{U}_1 \\ \hat{U}_3 \end{vmatrix} = \begin{vmatrix} 1 & -1 \\ 0 & -1 \end{vmatrix} \begin{vmatrix} U_1 \\ U_2 \end{vmatrix}$$

KVL

$$\begin{vmatrix} i_1 \\ i_2 \end{vmatrix} = \begin{vmatrix} 1 & 0 \\ -1 & -1 \end{vmatrix} \begin{vmatrix} i_1 \\ i_3 \end{vmatrix}$$

KCL

$$\begin{vmatrix} \hat{U}_1 \\ \hat{U}_3 \end{vmatrix} = \begin{vmatrix} 1 & -1 \\ 0 & -1 \end{vmatrix} \begin{vmatrix} U_1 \\ U_2 \end{vmatrix}$$

$$= \begin{vmatrix} 1 & -1 \\ 0 & -1 \end{vmatrix} \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_3 + R_2 \end{bmatrix} \begin{vmatrix} i_1 \\ i_3 \end{vmatrix}$$

$$= \begin{vmatrix} 1 & -1 \\ 0 & -1 \end{vmatrix} \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_3 + R_2 \end{bmatrix} \begin{vmatrix} 1 & 0 \\ -1 & -1 \end{vmatrix} \begin{vmatrix} i_1 \\ i_3 \end{vmatrix}$$

$$= \begin{vmatrix} R_1 + R_2 & R_2 \\ R_2 & R_3 + R_2 \end{vmatrix} \begin{vmatrix} i_1 \\ i_3 \end{vmatrix}$$

~~Equation~~