

Circuit and System Analysis

EHB 232E

Prof. Dr. Müştak E. Yalçın

Istanbul Technical University
Faculty of Electrical and Electronic Engineering

mustak.yalcin@itu.edu.tr

Outline I

1 Sinusoidal Steady-State Analysis

- Phasor analysis
- Properties of phasors
- Representation of state-space equations
- Transfer function
- Kirchhoff's Laws in the Frequency Domain

Sinusoidal Steady-State Analysis

If a system is exponentially stable

$$\lim_{t \rightarrow \infty} \Phi(t) = 0$$

Forced response is the complete response.

$$x(t) = \Phi(t)x_0 - \Phi(t)x_p(t_0) + x_p(t)$$

Sinusoidal steady-state behavior

Sinusoidal steady-state behavior of linear time-invariant circuits when the circuits are driven by one or more sinusoidal sources at some frequency w and when, after all "transients" have died down, all currents and voltages are sinusoidal at frequency w .

Electric Circuits, James W. Nilsson and Susan A. Riedel, Ch.9 and 10

Phasor

The idea is to associate with each sine wave (of voltage or current) a complex number called the phasor.

$x(t)$ is a complex variable and in polar coordinate

$$x(t) = X_m e^{j(\omega t + \theta)}$$

where $j = \sqrt{-1}$, X_m ($|X|$) is called the magnitude of $x(t)$ and θ (\angle) is called the phase of $x(t)$.

Rectangular representation of complex $x(t)$ is

$$x(t) = X_m \cos(\omega t + \theta) + jX_m \sin(\omega t + \theta)$$

Real part

$$X_m \cos(\omega t + \theta) = \operatorname{Re}\{x(t)\}$$

Imaginary part

$$X_m \sin(\omega t + \theta) = \operatorname{Im}\{x(t)\}$$

from Euler's identity.

The quantity (**phasor**)

$$X = X_m e^{j\theta}$$

is a complex number that carries the amplitude and phase angle of the given sinusoidal function. This complex number is by definition the **phasor** representation of the given sinusoidal function.

Using phasor representation, a complex variable is given

$$x(t) = X e^{wtj}$$

Examples: Electric Circuits, James W. Nilsson and Susan A. Riedel, pp. 334

Example

Phasor of the sinusoidal function

$$x(t) = 110\sqrt{2} \cos(wt + \frac{\pi}{2})$$

using

$$x(t) = \operatorname{Re}\left\{\underbrace{110\sqrt{2}e^{j\frac{\pi}{2}}}_{\text{phasor}} e^{j\omega t}\right\}$$

is obtain

$$X = 110\sqrt{2}e^{j\frac{\pi}{2}}$$

$X_m = 100\sqrt{2}$ (or $|X| = 100\sqrt{2}$), $\theta = \frac{\pi}{2}$ (or $\angle \frac{\pi}{2}$). $|X|_{\text{rms}} = 100$

A complex number (phasor) in rectangular coordinate

$Z = a + bj = Z_m e^{j\theta}$, magnitude

$$Z_m = \sqrt{a^2 + b^2}$$

phase

$$\theta = \arctan\left(\frac{b}{a}\right)$$

$$3 + 4j = 5e^{j0.927} \quad 3 = 5 \cos(0.927) \quad 4 = 5 \sin(0.927)$$
$$5 = \sqrt{3^2 + 4^2} \quad 0.927 = \arctan \frac{4}{3}$$

$$1 + j = \sqrt{2}e^{j0.785} \quad 1 = \sqrt{2} \cos(0.785) \quad 1 = \sqrt{2} \sin(0.785))$$
$$\sqrt{2} = \sqrt{1^2 + 1^2} \quad 0.785 = \arctan \frac{1}{1}$$

$$5e^{j0.927} + \sqrt{2}e^{j0.785} = ?$$
$$3 + 4j + 1 + j = 4 + 5j = 6.403e^{j0.896}$$

$$(3 + 4j) \times (1 + j) = ?$$

$$5e^{j0.927} \times \sqrt{2}e^{j0.785} = 5\sqrt{2}e^{j1.71}$$

Properties of phasors



$$y(t) = \alpha_1 x_1(t) + \alpha_2 x_2(t)$$

$$Y = \alpha_1 X_1 + \alpha_2 X_2$$



$$\frac{d}{dt} \{ X_m e^{\theta j} e^{j w t} \} = \left\{ \frac{d}{dt} X_m e^{\theta j} e^{j w t} \right\} = \underbrace{\{ j w A X_m e^{\theta j} e^{j w t} \}}_{\text{phasor}}$$

- X is phasor of $x(t)$

$$y(t) = \frac{d^n x(t)}{dt^n}$$

then phasor of $y(t)$

$$Y = (j w)^n X.$$

- A are B phasor

- If $\operatorname{Re}\{A e^{j w t}\} = \operatorname{Re}\{B e^{j w t}\}$ then $A = B$.
- If $A = B$ then $\operatorname{Re}\{A e^{j w t}\} = \operatorname{Re}\{B e^{j w t}\}$.

Phasor & State-space equation

Lets find the sinusoidal particular solution ($Xe^{j\omega t}$) of linear time invariant state equation

$$\dot{x} = Ax + Be$$

for a sinusoidal input $Ee^{j\omega t}$. Substituting the solution and input

$$j(\omega)X = AX + BE$$

The sinusoidal solution is then

$$X = (j\omega I - A)^{-1}BE$$


The solution is defined for $\det(j\omega I - A) \neq 0$ which means $j\omega \neq \lambda$. Input frequency is equal the natural frequency.

Transfer function

A linear time invariant single input single output system ($e, y \in R$) is defined by

$$\begin{aligned}\dot{x} &= Ax + Be \\ y &= Cx + De\end{aligned}$$

what if $e \in R^m$, $y \in R^l$...

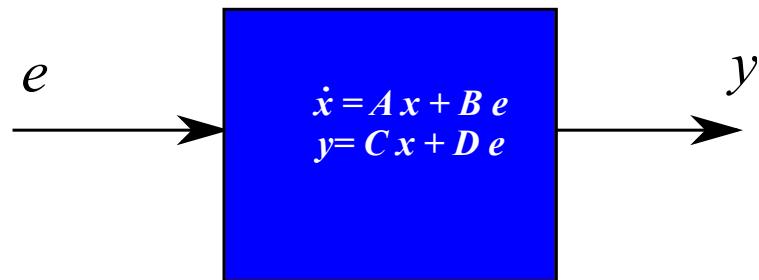

Using phasors, the output of the system

$$Y = \underbrace{(C(jwI - A)^{-1}B + D)}_{\text{transfer function}} E$$

Transfer function

$$H(jw) = (C(jwI - A)^{-1}B + D)$$

from input E to output Y

Example

$$\frac{dx}{dt} = \begin{bmatrix} -\sqrt{2} & -1 \\ 1 & 0 \end{bmatrix} x + \begin{bmatrix} 1 \\ 0 \end{bmatrix} e(t); y = [0 \ 1]x$$

Transfer function (which is a function of w !)



$$H(jw) = \frac{1}{1 - w^2 + j\sqrt{2}w}$$



For the input $e(t) = \sin(wt)$ (phasor of input signal $E = 1$) phasor of the output is

$$Y = H(j1)E = \frac{-j}{\sqrt{2}} = \frac{1}{\sqrt{2}}e^{-j\pi/2}$$

Hence output signal is
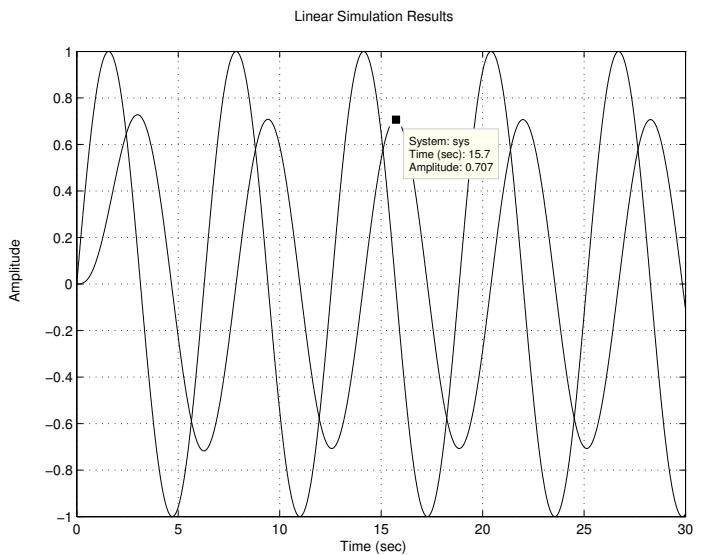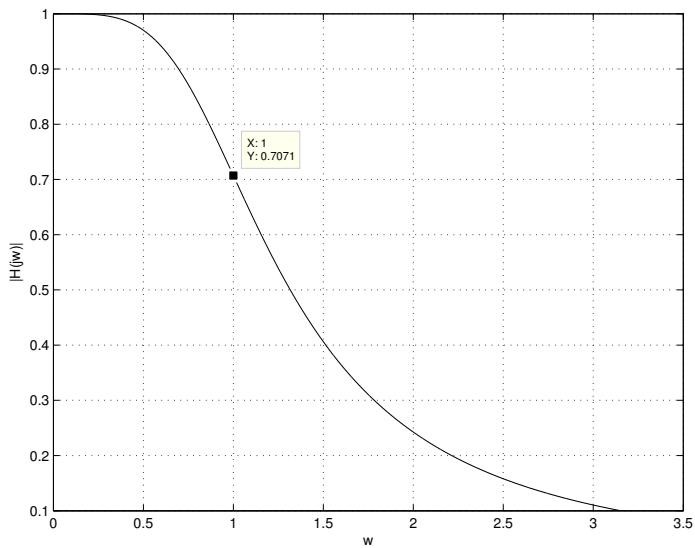
$$y(t) = \frac{1}{\sqrt{2}} \sin(t - \pi/2)$$



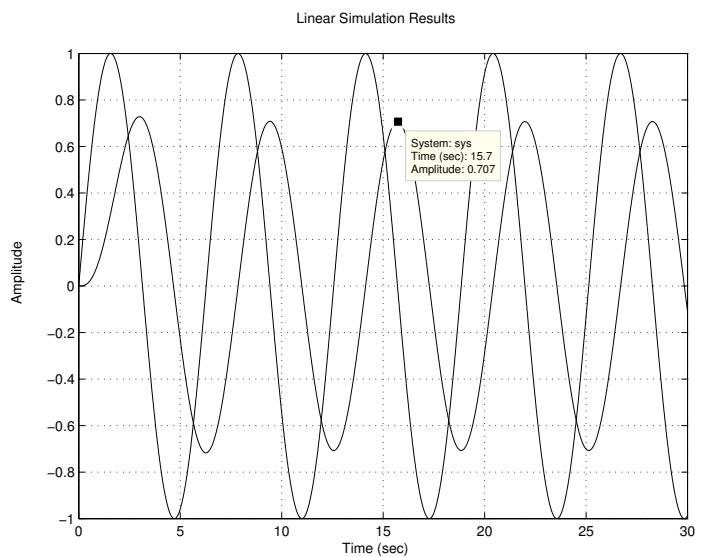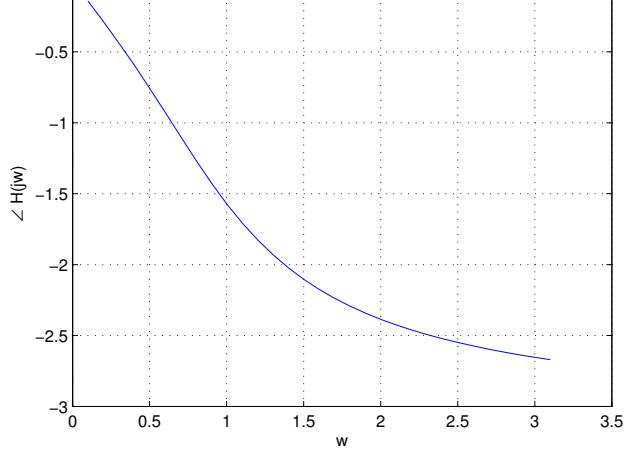

Kirchhoff's Laws in the Frequency Domain

Lets assuming that $v_1, v_2 \dots v_{n_e}$, represent voltages around a closed path in a circuit.

KVL requires that

$$\sum_{k=1}^{n_e} v_k(t) = 0$$

We assume that the circuit is operating in a sinusoidal steady state therefore

$$\sum_{k=1}^{n_e} \operatorname{Re} \{ V_k e^{j\omega t} \} = 0$$

Factoring the term $e^{j\omega t}$ from each term yields

$$\sum_{k=1}^{n_e} V_k = 0.$$

A similar derivation applies to a set of sinusoidal currents (KCL). Thus if

$$\sum_{k=1}^{n_e} i_k(t) = 0$$

We assume that the circuit is operating in a sinusoidal steady state therefore

$$\sum_{k=1}^{n_e} \operatorname{Re}\{I_k e^{\theta_k}\} = 0$$

Factoring the term $e^{j\omega t}$ from each term yields

$$\sum_{k=1}^{n_e} I_k = 0.$$

Question: Four branches terminates at a common node. The reference direction of each branch current (i_1, i_2, i_3, i_4 , is toward the node if
 $i_1 = 100 \cos(\omega t + 25^\circ)$ A $i_2 = 100 \cos(\omega t + 145^\circ)$ A
 $i_3 = 100 \cos(\omega t - 95^\circ)$ A, find i_4