

# Circuit and System Analysis

## EHB 232E

Prof. Dr. Müştak E. Yalçın

Istanbul Technical University  
Faculty of Electrical and Electronic Engineering

[mustak.yalcin@itu.edu.tr](mailto:mustak.yalcin@itu.edu.tr)

# Outline I

## 1 Sinusoidal Steady-State Analysis

- Mesh-Current Method in Frequency Domain
- Node-voltage Method in Frequency Domain
- Network functions
- Superposition of Sinusoidal Steady States
- Thevenin - Norton Equivalent Circuits

## Mesh-Current Method in Frequency Domain

The number of equations to be solved are equal to the number of independent loops ( $n_e - n_d + 1$ ). There exists a tree such that the meshes are Fundamental loops\*.

$$B_1 \mathbf{R} B_1^T i_c + B_2 v_k = 0$$

where  $v_k$  and  $v_R$  voltages of independent voltage sources and resistors. Instead of  $V_e = \mathbf{R}I_e$  using

$$V_e = \mathbf{Z}I_e$$


we have

$$B_1 \mathbf{Z} B_1^T I_c + B_2 V_k = 0$$

where  $B_1 \mathbf{Z} B_1^T$  mesh impedance matrix.

▶ See :EHB211 E

## Example

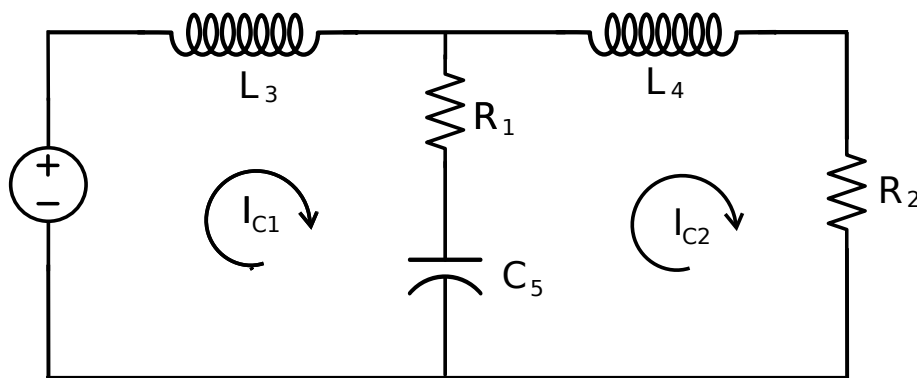

$$\begin{aligned} M1 \quad & L_3 j\omega I_{c1} + \left( \frac{1}{C_5 j\omega} + R \right) (I_{c1} - I_{c2}) - V_G = 0 \\ M2 \quad & L_4 j\omega I_{c2} + R_2 I_{c2} + \left( \frac{1}{C_5 j\omega} + R \right) (I_{c2} - I_{c1}) = 0 \end{aligned}$$


In matrix form

$$\begin{bmatrix} R_1 + \frac{1}{C_5 j\omega} + L_3 j\omega & -\frac{1}{C_5 j\omega} - R_1 \\ -\frac{1}{C_5 j\omega} - R_1 & L_4 j\omega + R_2 + R_1 + \frac{1}{C_5 j\omega} \end{bmatrix} \begin{bmatrix} I_{c1} \\ I_{c2} \end{bmatrix} = \begin{bmatrix} V_G \\ 0 \end{bmatrix}$$

$$V_{L_3} = L_3 j\omega [1 \ 0] \begin{bmatrix} \cdot & -\frac{1}{Cj\omega} - R_1 \\ -\frac{1}{Cj\omega} - R_1 & \cdot \end{bmatrix}^{-1} \begin{bmatrix} V_G \\ 0 \end{bmatrix}$$

$$v_G(t) = 4 \cos(2\pi 60t + \frac{\pi}{3}), \quad L_3 = L_4 = 3mH, \quad C = 4\mu F, \quad R_1 = R_2 = 2k\Omega$$
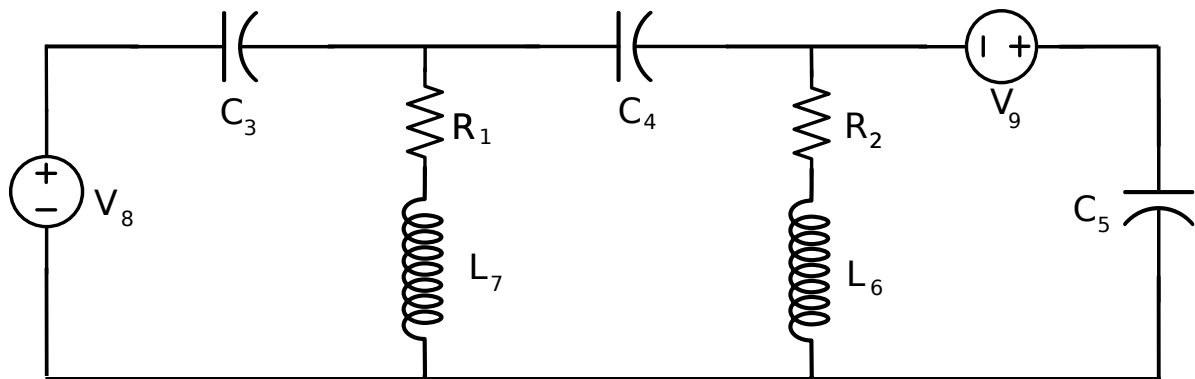
$$V_{L_3} = 310^{-3} j2\pi 60 [1 \ 0] \begin{bmatrix} \cdot & -\frac{10^6}{4j2\pi 60} - 2k \\ -\frac{10^6}{4j2\pi 60} - 2k & \cdot \end{bmatrix}^{-1} \begin{bmatrix} 4e^{\frac{\pi}{3}j} \\ 0 \end{bmatrix}$$




$$Z \begin{bmatrix} I_{c1} \\ I_{c2} \\ I_{c3} \end{bmatrix} = \begin{bmatrix} V_8 \\ 0 \\ V_9 \end{bmatrix}$$

where

$$Z = \begin{bmatrix} \frac{1}{C_3 j\omega} + R_1 + L_7 j\omega & -R_1 - L_7 j\omega & 0 \\ -R_1 - L_7 j\omega & R_1 + (L_7 + L_6)j\omega + \frac{1}{C_4 j\omega} + R_2 & -R_2 - L_6 j\omega \\ 0 & -R_2 - L_6 j\omega & R_2 + L_6 j\omega + \frac{1}{C_5 j\omega} \end{bmatrix}$$

$$I_4 = 2V_2$$

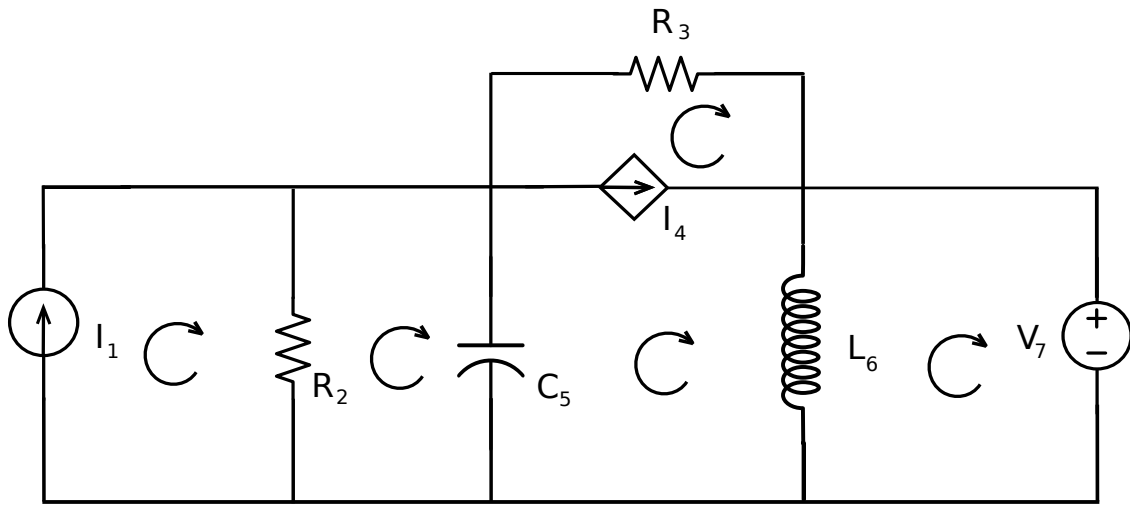

$$\begin{bmatrix} R_2 & -R_2 & 0 & 0 & 0 \\ -R_2 & R_2 + \frac{1}{C_5 j\omega} & -\frac{1}{C_5 j\omega} & 0 & 0 \\ 0 & -\frac{1}{C_5 j\omega} & \frac{1}{C_5 j\omega} + L_6 j\omega & 0 & -L_6 j\omega \\ 0 & 0 & 0 & R_3 & 0 \\ 0 & 0 & 0 & -L_6 j\omega & L_6 j\omega \end{bmatrix} \begin{bmatrix} I_{c1} \\ I_{c2} \\ I_{c3} \\ I_{c4} \\ I_{c5} \end{bmatrix} = \begin{bmatrix} -V_1 \\ 0 \\ -V_4 \\ V_4 \\ -V_7 \end{bmatrix}$$

$$\begin{aligned}
 I_1 &= I_{c1} \\
 I_4 &= 2V_2 \\
 I_{c3} - I_{c4} &= -2V_1
 \end{aligned}$$

with above equ.s

$$\begin{bmatrix}
 R_2 & -R_2 & 0 & 0 & 0 & 1 & 0 \\
 -R_2 & R_2 + \frac{1}{C_5 j\omega} & -\frac{1}{C_5 j\omega} & 0 & 0 & 0 & 0 \\
 0 & -\frac{1}{C_5 j\omega} & \frac{1}{C_5 j\omega} + L_6 j\omega & 0 & -L_6 j\omega & 0 & 1 \\
 0 & 0 & 0 & R_3 & 0 & 0 & -1 \\
 0 & 0 & -L_6 j\omega & 0 & L_6 j\omega & 0 & 0 \\
 1 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 1 & -1 & 0 & 2 & 0
 \end{bmatrix}
 \begin{bmatrix}
 I_{c1} \\
 I_{c2} \\
 I_{c3} \\
 I_{c4} \\
 I_{c5} \\
 V_1 \\
 V_4
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 0 \\
 0 \\
 -V_2 \\
 I_1 \\
 0
 \end{bmatrix}$$



## Node-voltage Method

The fundamental cut-set equations for the nodes (which do not correspond to node of a voltage sources)

$$A_i = 0$$

current sources  $i_k$  and currents of one ports  $i_e$

$$A_1 i_e + A_2 i_k = 0$$

in Sinusoidal steady-state  $i_e = YV_e$

$$A_1 YV_e + A_2 i_k = 0$$


using  $V_e = A_1^T V_d$  we have

$$A_1 Y A_1^T V_d + A_2 i_k = 0$$

where  $V_d$  is phasor of the node voltage.


► See :EHB211 E

## Example

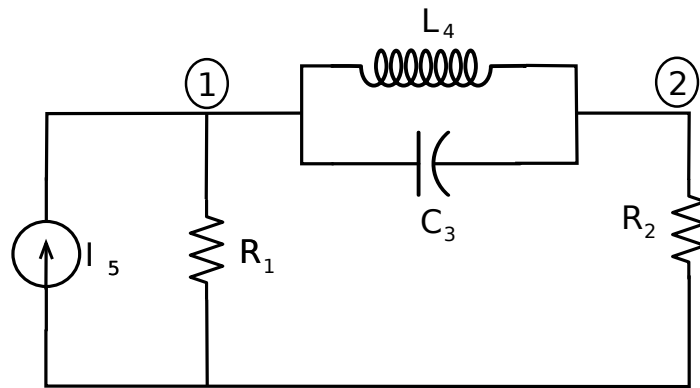

$$\begin{bmatrix} G_1 + C_3 j\omega + \frac{1}{L_3 j\omega} & -C_3 j\omega - \frac{1}{L_3 j\omega} \\ -C_3 j\omega - \frac{1}{L_3 j\omega} & G_2 + C_3 j\omega + \frac{1}{L_3 j\omega} \end{bmatrix} \begin{bmatrix} V_{d1} \\ V_{d2} \end{bmatrix} = \begin{bmatrix} I_1 \\ 0 \end{bmatrix}$$

## Example

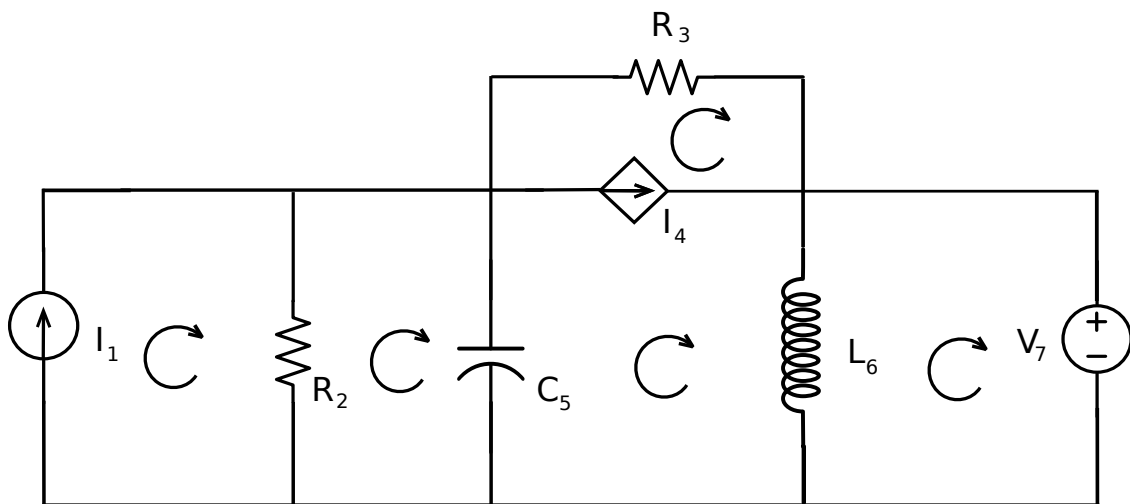

$$\begin{bmatrix} G_2 + G_3 + C_5 j\omega & -G_3 \\ -G_3 & G_3 + \frac{1}{L_6 j\omega} \end{bmatrix} \begin{bmatrix} V_{d1} \\ V_{d2} \end{bmatrix} = \begin{bmatrix} I_1 - I_4 \\ I_4 - I_7 \end{bmatrix}$$

## Example

$$V_7 = V_{d1}$$

$$I_4 = 2V_2 = 2V_{d1}$$

$$\begin{bmatrix} G_2 + G_3 + C_5j\omega & -G_3 & 0 \\ -G_3 & G_3 + \frac{1}{L_6j\omega} & 1 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_{d1} \\ V_{d2} \\ I_7 \end{bmatrix} = \begin{bmatrix} I_1 \\ 0 \\ V_7 \end{bmatrix}$$

$$v_7(t) = 2 \cos(2\pi 60t + \frac{2\pi}{3}), \quad i_1(t) = 3 \cos(2\pi 60t + \frac{7\pi}{3}), \quad L_6 = 2H, \quad C = 2F, \\ R_2 = R_3 = 1\Omega$$

$$\begin{bmatrix} 1 + 1 + 2j2\pi 60 & -1 & 0 \\ -1 & 1 + \frac{1}{2j2\pi 60} & 1 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_{d1} \\ V_{d2} \\ I_7 \end{bmatrix} = \begin{bmatrix} 3e^{\frac{7\pi}{3}j} \\ 0 \\ 2e^{\frac{2\pi}{3}j} \end{bmatrix}$$

## Network functions

Consider a general linear time-invariant circuit  $N$ . Assume that  $N$  is driven by one independent source, say, the sinusoidal current source  $I_s$  represented by the phasor.


Suppose we want to calculate the node voltage  $E$ , and consider the dependence of the phasor  $E$  on  $\omega$ .

$$\frac{E(j\omega)}{I_s}$$

is a function of  $j\omega$  which depends only on the circuit  $N$  and not on  $I_s$ . it is called the transfer impedance from  $I_s$  to  $E$ .

Network functions : (a) Voltage transfer functions, (b) Transfer admittances, (c) Current transfer function, (d) Transfer impedance.

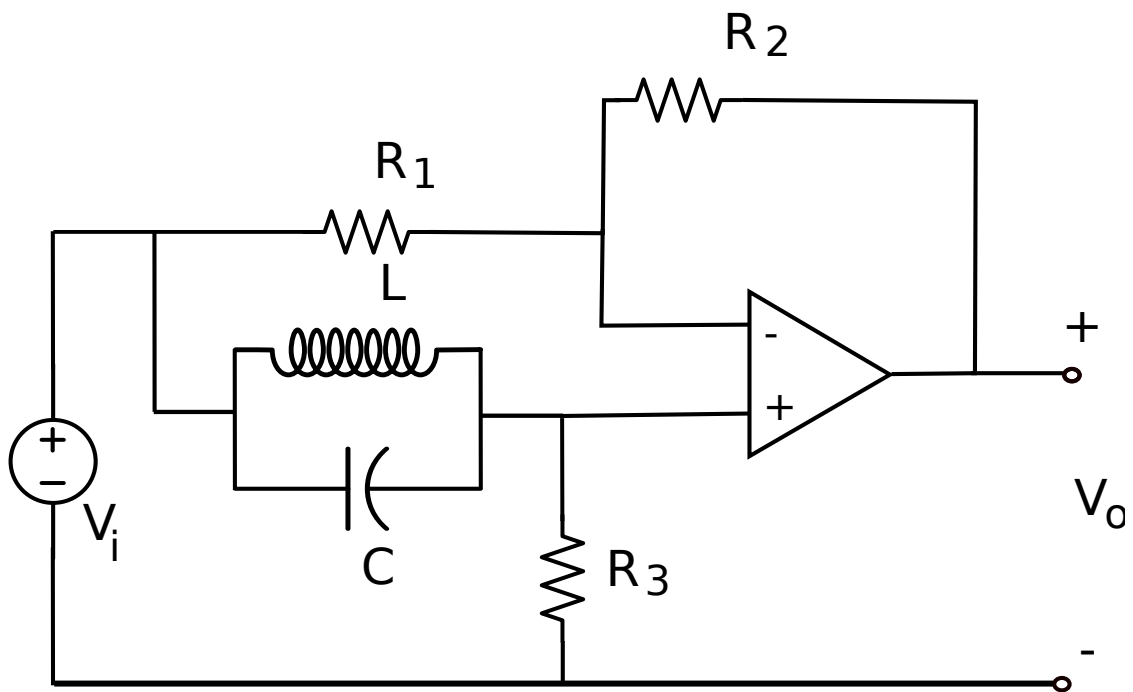Find voltage transfer functions from  $V_i$  to  $V_o$ .





Example : Chua's book, Page 526, Examples 2 and 3.

# Network functions and Sinusoidal Waveforms

A linear time-invariant circuit  $N$  in the sinusoidal steady state of frequency  $\omega$ .  $H(j\omega) = |H(j\omega)|e^{j\angle H(j\omega)}$  is the voltage transfer function from  $V_s = |V_s|e^{j\angle V_s}$  to  $V_k = |V_k|e^{j\angle V_k}$ .


$$\begin{aligned}V_k &= |V_k|e^{j\angle V_k} = |H(j\omega)|e^{j\angle H(j\omega)}|V_s|e^{j\angle V_s} \\ &= |H(j\omega)||V_s|e^{j(\angle H(j\omega)+\angle V_s)}\end{aligned}$$

$$v_k(t) = |H(j\omega)||V_s|\cos(\omega t + \angle H(j\omega) + \angle V_s)$$

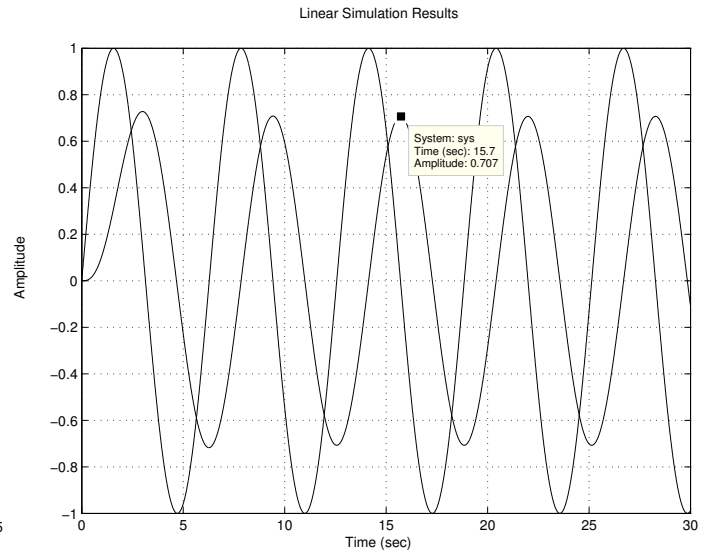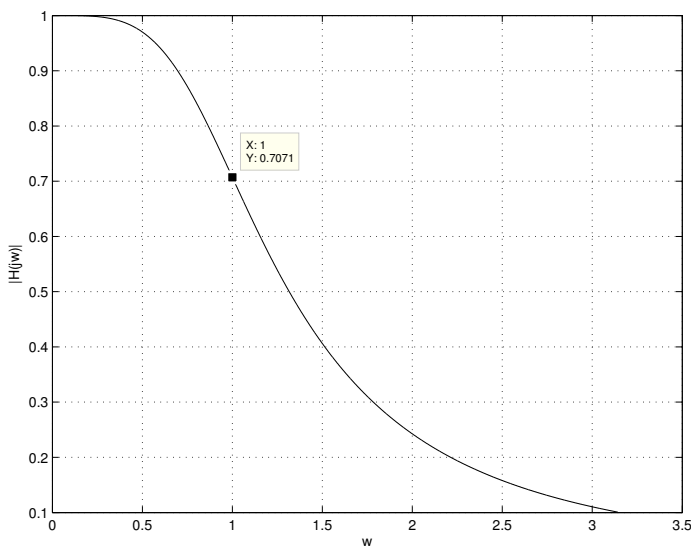

## Example: Low Pass Filter

▶ YouTube Video: RC Filter

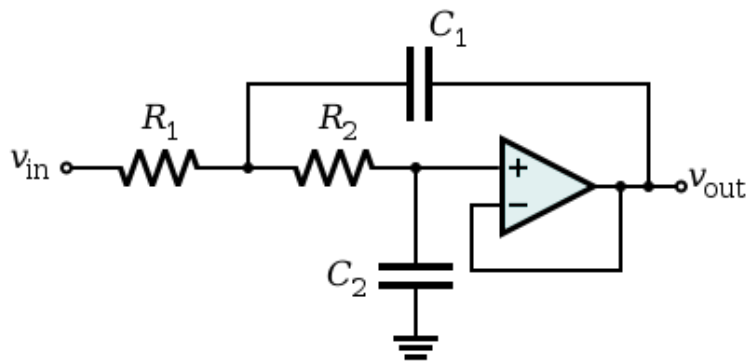

Verify



$$H(j\omega) = \frac{V_o}{V_i} = \frac{\omega_0^2}{\omega_0^2 - \omega + 2\alpha j\omega}$$

where  $\omega_0^2 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$  and  $2\alpha = \frac{(R_1 + R_2)}{(R_1 R_2)} \frac{1}{C_1}$  (Note that  $Q = \frac{\omega_0}{2\alpha}$ )


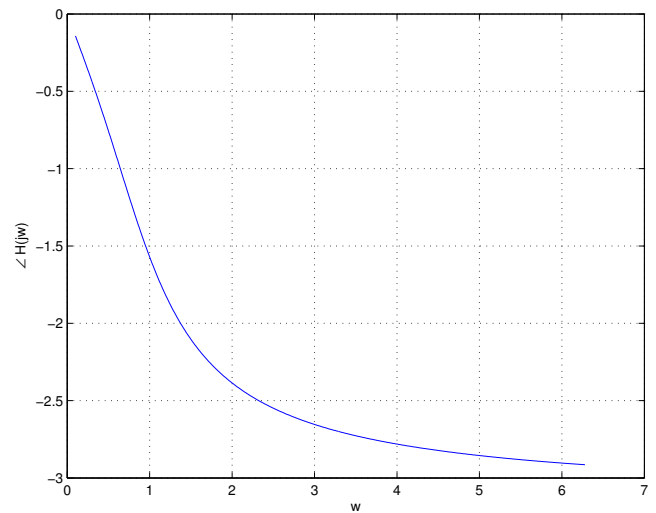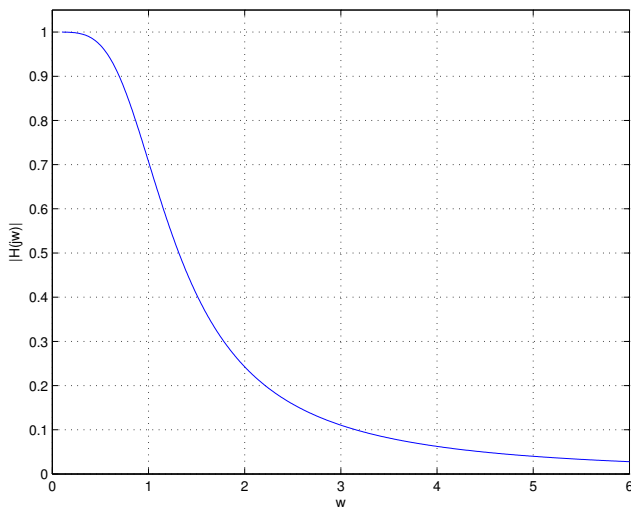
## Example: Low Pass Filter

$$\omega_o = 1 \text{ and } 2\alpha = \sqrt{2}$$




$$H(j1) = \frac{1}{\sqrt{2}j} = \frac{1}{\sqrt{2}} e^{-\frac{\pi}{2}}$$

$$|H(j\omega)| \text{ in decibels} = 20 \log(|H(j\omega)|)$$


$$|H(j0)| = 0dB, |H(j1)| = \frac{1}{\sqrt{2}} = -3dB$$

## Second Order Low Pass Filter

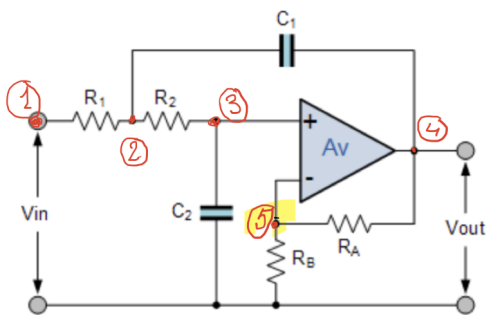

Transfer function:  $\frac{V_o}{V_i} = ?$

NODE 5

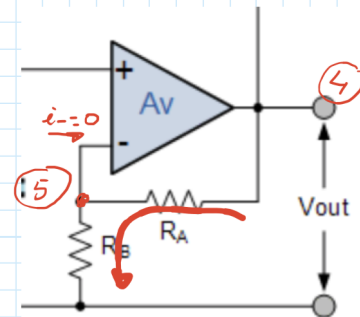


for OPAMP  $V_{n3} = V_{n5}$

$$V_{n5} = \frac{R_B}{R_A + R_B} \cdot V_{n4} \quad \text{Note } V_{n4} = V_o$$

$$= k V_{n4}$$

NODE 2

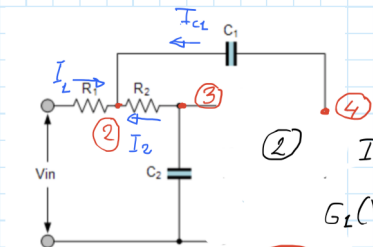



$$I_1 + I_2 + I_{C1} = 0$$

$$G_1(V_{n1} - V_{n2}) + G_2(V_{n3} - V_{n2}) + C_2 j\omega(V_{n4} - V_{n2}) = 0$$

$$\text{Eqn 2} \quad G_1 V_{n1} - (G_1 + G_2 + C_2 j\omega)V_{n2} + G_2 V_{n3} + C_2 j\omega V_{n4} = 0 \quad \text{Note } V_{n2} = V_i$$

$$V_{n3} = V_{n5} = k V_{n4}$$



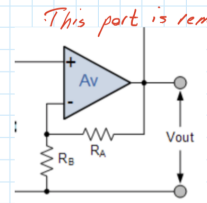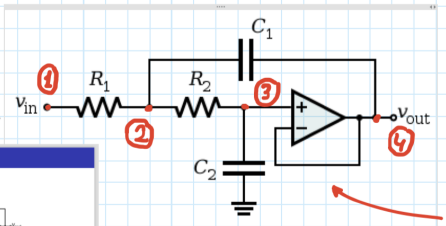

Example: Low Pass Filter

Verify

$$H(j\omega) = \frac{V_o}{V_i} = \frac{-\omega_c^2}{-\omega^2 + j\omega + 1}$$

where  $\omega_c^2 = \frac{1}{R_1 R_2 C_1 C_2}$  and  $2\alpha = \frac{(R_1 + R_2)}{R_1 R_2 C_1 C_2}$  (Note that  $Q = \frac{1}{2\alpha}$ )

$$H(j\omega) = \frac{V_o}{V_i} = \frac{1}{-C_1 C_2 R_1 R_2 \omega^2 + (R_1 + R_2) C_2 j\omega + 1}$$

without  $\epsilon$   $k$

$$H(j\omega) = \frac{V_o}{V_i} = \frac{1}{-\omega^2 + \frac{(R_1 + R_2) C_2}{R_1 R_2 C_1 C_2} j\omega + \frac{1}{R_1 R_2 C_1 C_2}}$$

$\omega = 0 \quad H(j0) = 1$

$$\omega_c^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$H(j\omega) = \frac{1}{-\frac{1}{R_1 R_2 C_1 C_2} + \frac{(R_1 + R_2) C_2}{R_1 R_2 C_1 C_2} \cdot \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} j + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$= -j \frac{\sqrt{R_1 R_2 C_1 C_2}}{(R_1 + R_2) C_2}$$

Let's  $R_1 = R_2 = R$  and  $C_1 = 2C_2$

$$= -j \frac{R}{2R} \sqrt{\frac{C_1 C_2}{C_2^2}}$$

$$= -j \frac{1}{2} \sqrt{2}$$

$$= -j \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{2}} e^{-j\frac{\pi}{4}}$$

$$\omega = \hat{\omega} = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$H(j\hat{\omega}) = \frac{1}{\sqrt{2}} e^{-j\frac{\pi}{4}}$$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{2}}$$

$$\omega = \omega_c \quad H(j\omega) = 0$$

SPICE PRO6.

OPAMP  
OPAMP MODEL

```

R1 1 2 1k
R2 2 3 1k
C2 3 0 2u
C1 2 4 4u
XOP 3 4 4 OPAMP1 1 2 6
SUBCKT OPAMP1 1 2 6
* INPUT IMPEDANCE
RIN 1 2 10MEG
* DC GAIN (100K) AND POLE 1 (10HZ)
EGAIN 3 0 1 2 100K
RFP1 3 4 1k
CPI 4 0 15.915uF
* OUTPUT BUFFER AND RESISTANCE*
EBUFFER 5 0 4 0 1
ROUT 5 6 10
.ENDS
Vin 1 0 DC 0.0 AC 1.0 0.0
.ac dec 100 1Hz 1000Hz
.END

```




plot  $\text{mag}(V(4))$

$$\omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\omega = 353.55$$

$$f = 56.2 \text{ Hz}$$

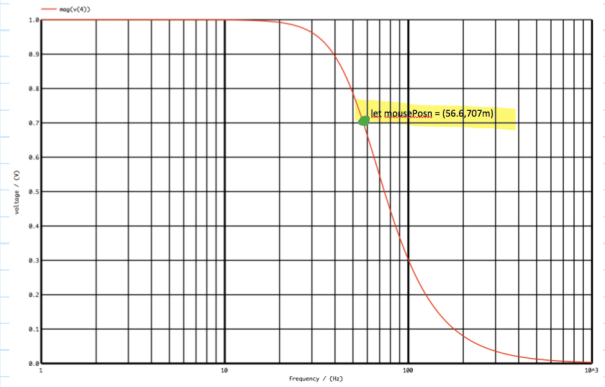

## Superposition of Sinusoidal Steady States

Let  $N$  be a linear time-invariant circuit which is driven by two sinusoidal independent sources operating at two different frequencies.

Voltage source is specified by phasor  $E$ , and operates at frequency  $\omega_1$ . The current source is specified by phasor  $I$ , and operates at frequency  $\omega_2$ .


$H_1(j\omega)$  be the voltage transfer function of from  $E$  to  $V_k$  and  $H_2(j\omega)$  be the transfer impedance from  $I$  to  $V_k$ .

By the superposition theorem, the resulting steady state is the superposition of two sinusoids

$$v_k(t) = |H_1(j\omega)| |E| \cos(\omega_1 t + \angle H_1(j\omega) + \angle E) + |H_2(j\omega)| |I| \cos \omega_2 t + \dots$$

$\omega_1 = r\omega_2$  if  $r$  is a rational number then periodic if  $r$  is an irrational number then almost periodic

## Thevenin - Norton Equivalent Circuits

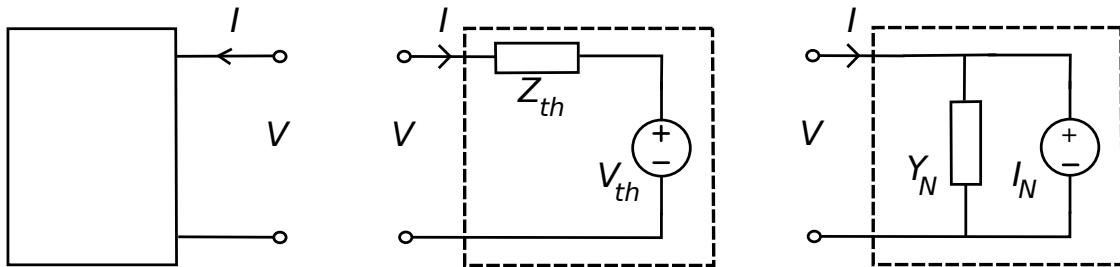


The techniques for finding the Thevenin equivalent voltage ( $V_{th}$ ) and impedance ( $Z_{th}(j\omega)$ ) are identical to those used for resistive circuits, except that the frequency domain equivalent circuit involves the manipulation of complex quantities.


Driving-point characteristic of Thevenin equivalent circuit is defined by

$$V = Z_{th}(j\omega)I + V_{th}$$

► More detail EHB211 E: Slayt 192

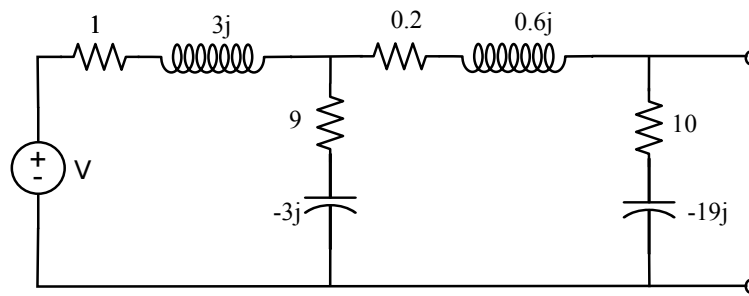



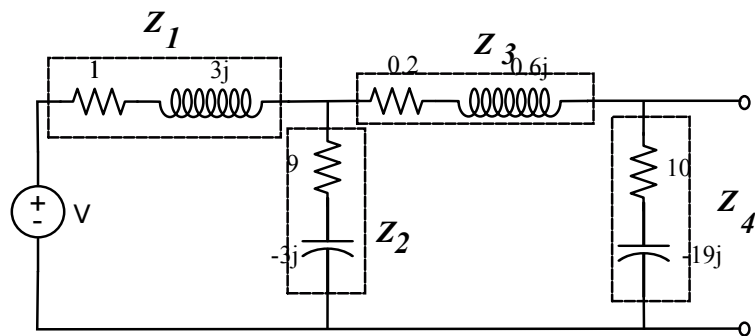


$$Z_{th} = (((Z_1 // Z_2) + Z_3) // Z_4)$$

$$V_1 = \frac{(Z_3 + Z_4) // Z_2}{(Z_3 + Z_4) // Z_2 + Z_1} V$$

$$V_{th} = \frac{Z_4}{Z_3 + Z_4} V_1$$

## Example

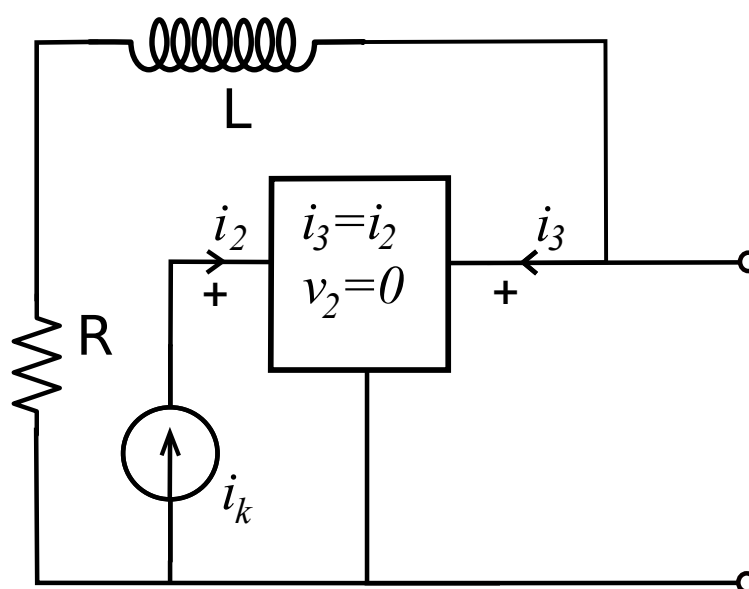

## Example

$Y = j$ ,  $i_1 = 2v_2$  and  $i_2 = -2v_1$  In steady state  $I_{c1} = 1 - j$ . Find complex power of two-port.

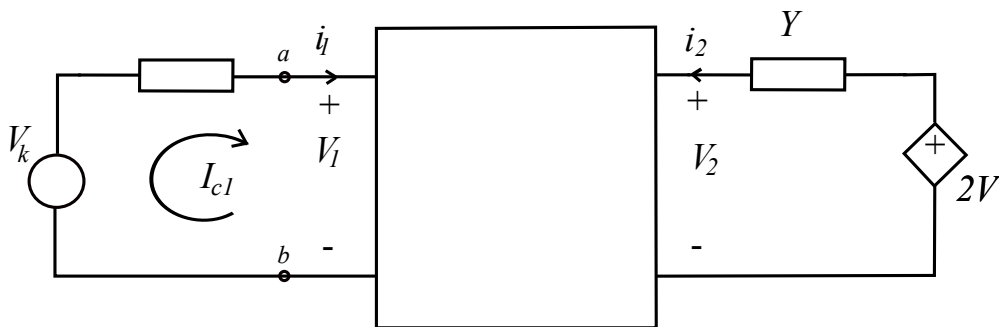


Figure: ( $i_1 = 2v_2$ ,  $i_2 = -2v_1$  ve  $Y = j$  and  $I_{c1} = 1 - j$ ).