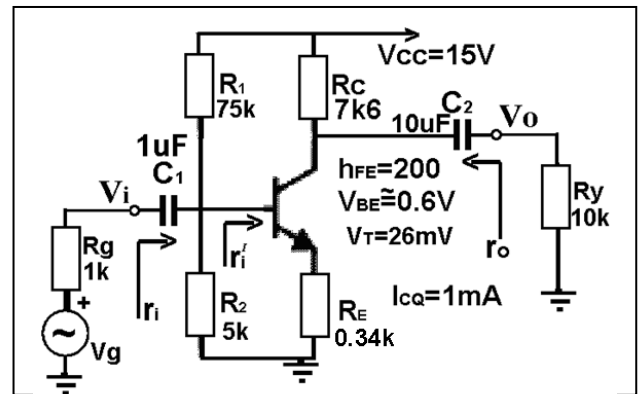


P1- For the transistor in the figure, $I_{CQ}=1\text{mA}$, $\beta_F=h_{FE}=200$, $V_{BE}\approx 0.6\text{V}$, $V_T\approx 26\text{mV}$, $C_{cb}=10\text{pF}$ and $F_T=100\text{MHz}$ are given.

Signature:

a) Find the cut-off frequencies for the low and high frequency regions.



b) V_g is a sinusoidal signal the amplitude of which is 5mV and the frequency of which is the cut-off frequency at the high frequency region. Draw $v_g(t)$ and $v_o(t)$ for the same time-axis.

c) Calculate the tilt and the rising-time of the circuit for a square-wave source of 10kHz . Draw the output signal $V_o(t)$ (the amplitude of the square-wave source is 10mV).

A-1-

$$a) r_{i'} = r_b = R_F \left(\frac{1}{g_m} + R_E \right)$$

$$\downarrow$$

$$= 200 (26 + 340)$$

$$\downarrow$$

$$\approx 73k$$

$$r_i = R_2 \parallel R_1 \parallel r_{i'} \approx 4,4k$$

Low frequency region

$$C_1 \rightarrow \tau_1 = C_1 \cdot (r_i + R_g) = 1\mu F \cdot 5,4k$$

$$\downarrow$$

$$= 5,4ms$$

$$f_{L1} = \frac{1}{2\pi\tau_1} = 29,5Hz$$

$$C_2 \rightarrow \tau_2 = C_2 (R_C + R_L) = 10\mu F \cdot 17,6k$$

$$\downarrow$$

$$= 176ms$$

$$f_{L2} = \frac{1}{2\pi\tau_2} \approx 1Hz$$


$$f_{LC} \approx f_{L1} \approx 30Hz$$

a)

High frequency $\frac{v_c}{v_b} = \frac{-\beta_m (R_c // R_L)}{1 + \beta_m R_E} \approx -12$

$F_T = \frac{\beta_m}{2\pi (C_{be} + C_b)} \rightarrow C_{be} = \frac{\beta_m}{2\pi f_T} - C_b$

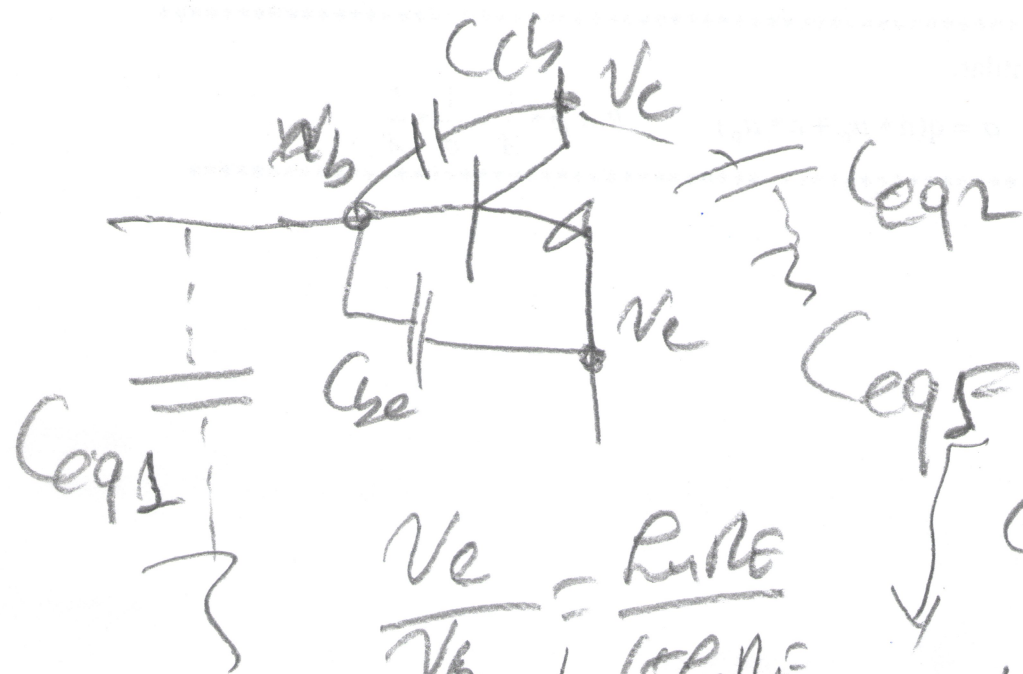$f_T = 61,2p - 10p$
 $\downarrow = 51,2pF$



$\frac{v_e}{v_b} = \frac{\beta_m R_E}{1 + \beta_m R_E} \approx 0,93$

$C_{eq1} = C_b (1 - (-12)) + C_{be} (1 - \frac{v_e}{v_b})$
 $= 130pF + 3,6pF$
 $\downarrow = 134pF$

$C_{eq2} \approx C_{cb} = 10pF$

$F_{HL} = \frac{1}{2\pi C_{eq1} (R' // M // N // P)} \approx 1,5MHz$
 $\approx 0,8h$ $\rightarrow F_{Hc} \approx 1MHz$

$F_{HL} = \frac{1}{2\pi C_{eq2} (R_c // R_L)} = 7MHz$

$$b) A_v = \frac{v_c}{v_b} \cdot \frac{v_b}{v_e}$$

$$\frac{v_c}{v_b} = \frac{-g_m \cdot (R_c \parallel R_L)}{1 + g_m R_E} \approx \frac{-\frac{1}{26} \cdot 4,3k}{1 + g_m \cdot 0,34k}$$

$$\approx -12$$


$$\frac{v_b}{v_e} = \frac{r_i}{r_i + R_L} = \frac{4,4}{5,4}$$

$$A_v = \frac{4,4}{5,4} \cdot (-12) \approx -10$$

$F_{Hc} \approx 1 \text{ MHz}$
 $v_i(t)$

Phase difference = $180 - 45$
 $\approx 135^\circ$

$$|G_{AM}| = \frac{10}{\sqrt{2}} \approx 7$$

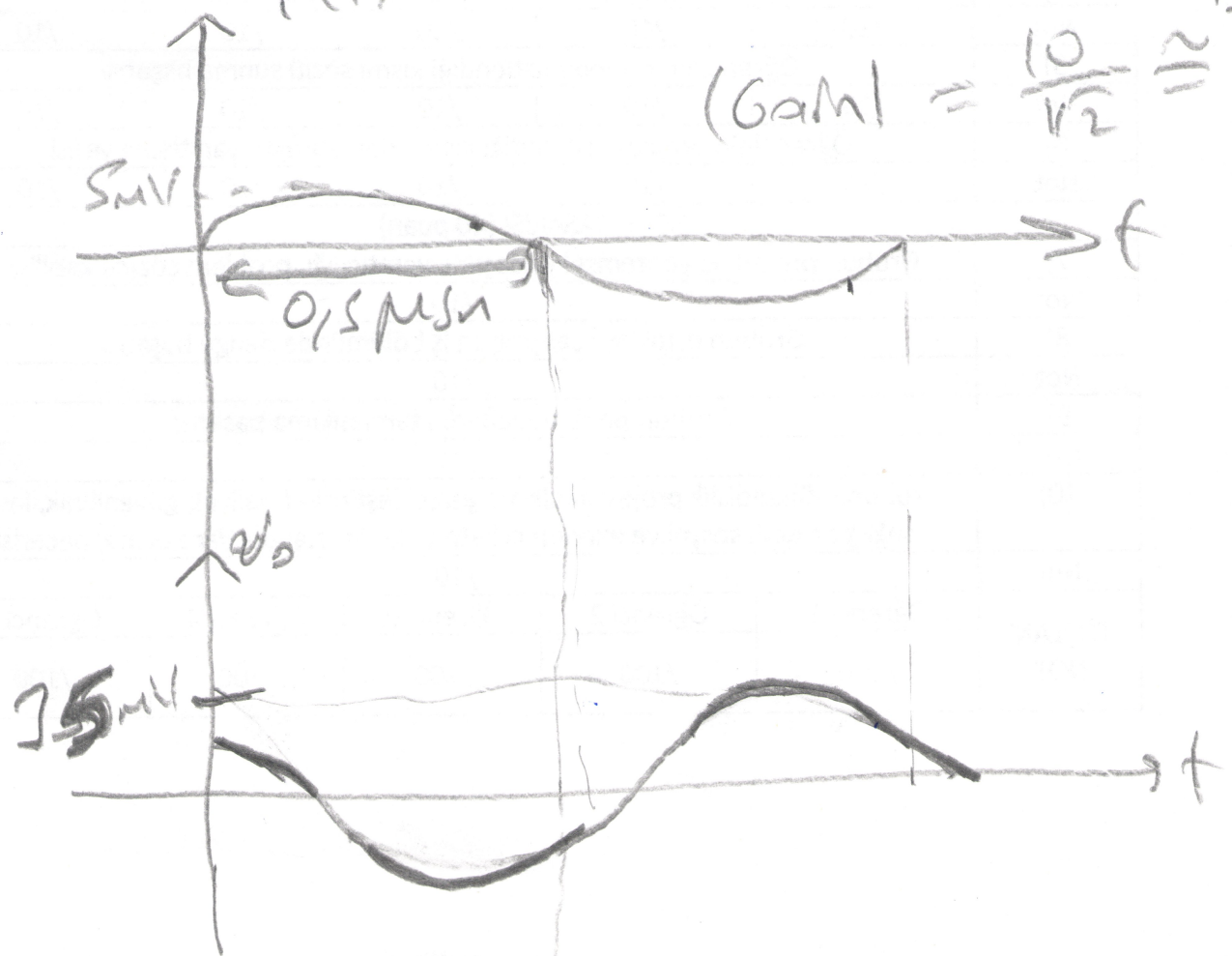

c)

$$t_r = \frac{0,55}{f_{HC}} = \frac{0,55}{1 \text{ MHz}} = 0,55 \mu\text{s}$$

$$A_v(f) = \frac{T_D}{2} = \frac{50 \mu\text{s}}{2} = \frac{1}{100} \frac{\text{V}}{\text{V}}$$

