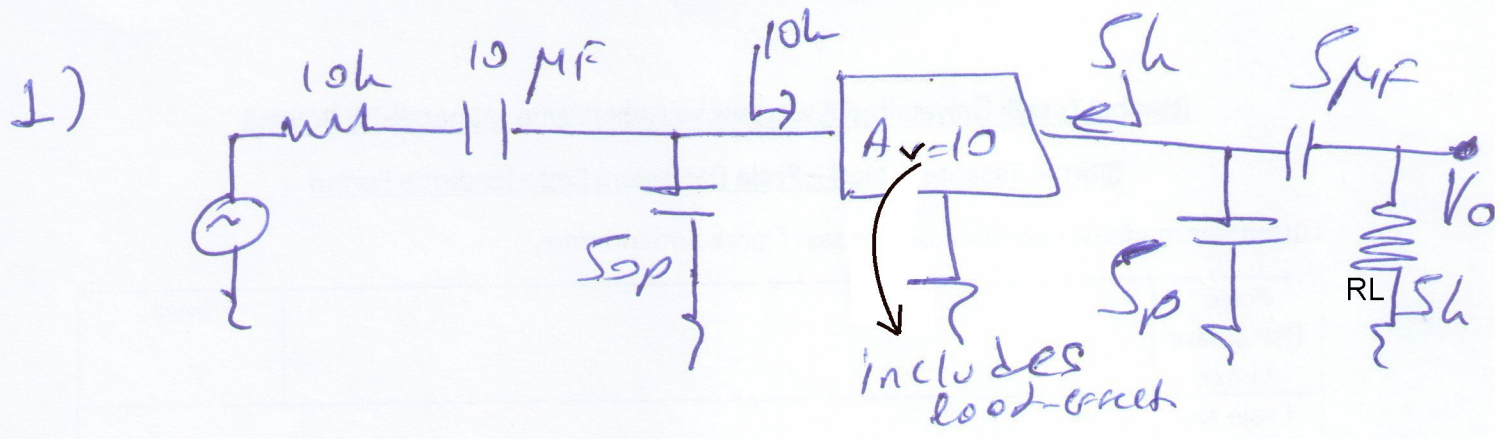


Summer 19 - MTL - Solution



a) cutoff frequencies

Low frequency region

$$\omega_{L1} = \frac{1}{10\mu F \cdot (10k + 10k)} = 5 \text{ rad/s}$$

$$\omega_{L2} = \frac{1}{5\mu F \cdot (5k + 5k)} = 20 \text{ rad/s}$$

$$f_{LC} \approx 4 \text{ Hz}$$

High frequency region

$$\omega_{H1} = \frac{1}{5s_p \cdot (10k // 10k)} = 4 \text{ Mrad/s}$$

$$\omega_{H2} = \frac{1}{5s_p \cdot (5k // 5k)} = 80 \text{ Mrad/s}$$

$$\omega_{HC} \approx 4 \text{ Mrad/s}$$

$$f_{HC} \approx 637 \text{ kHz}$$


b) Pulse response ($V_{Pam} = 20\text{mV}$, $t_d = 10\text{ms}$)

$$t_r = \frac{0.35}{637k} \approx 0.6 \mu\text{s}$$

$$f_s = \frac{1}{T_s} \rightarrow \frac{1}{\omega_{L1}} = \frac{1}{5}$$

$$d_r = \frac{t_d}{T_s} = \frac{1}{2000}$$


$$d = d_1 + d_2 = \frac{1}{2000}$$

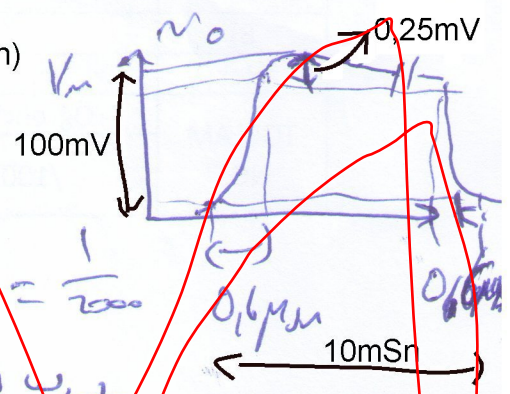

$$V_m = A_v \cdot V_{Pam} = 10 \cdot 20\text{mV} = 0.2\text{V}$$

$$V_m = 5 \times 10^{-2} \times 0.2 = 0.1\text{V}$$

27

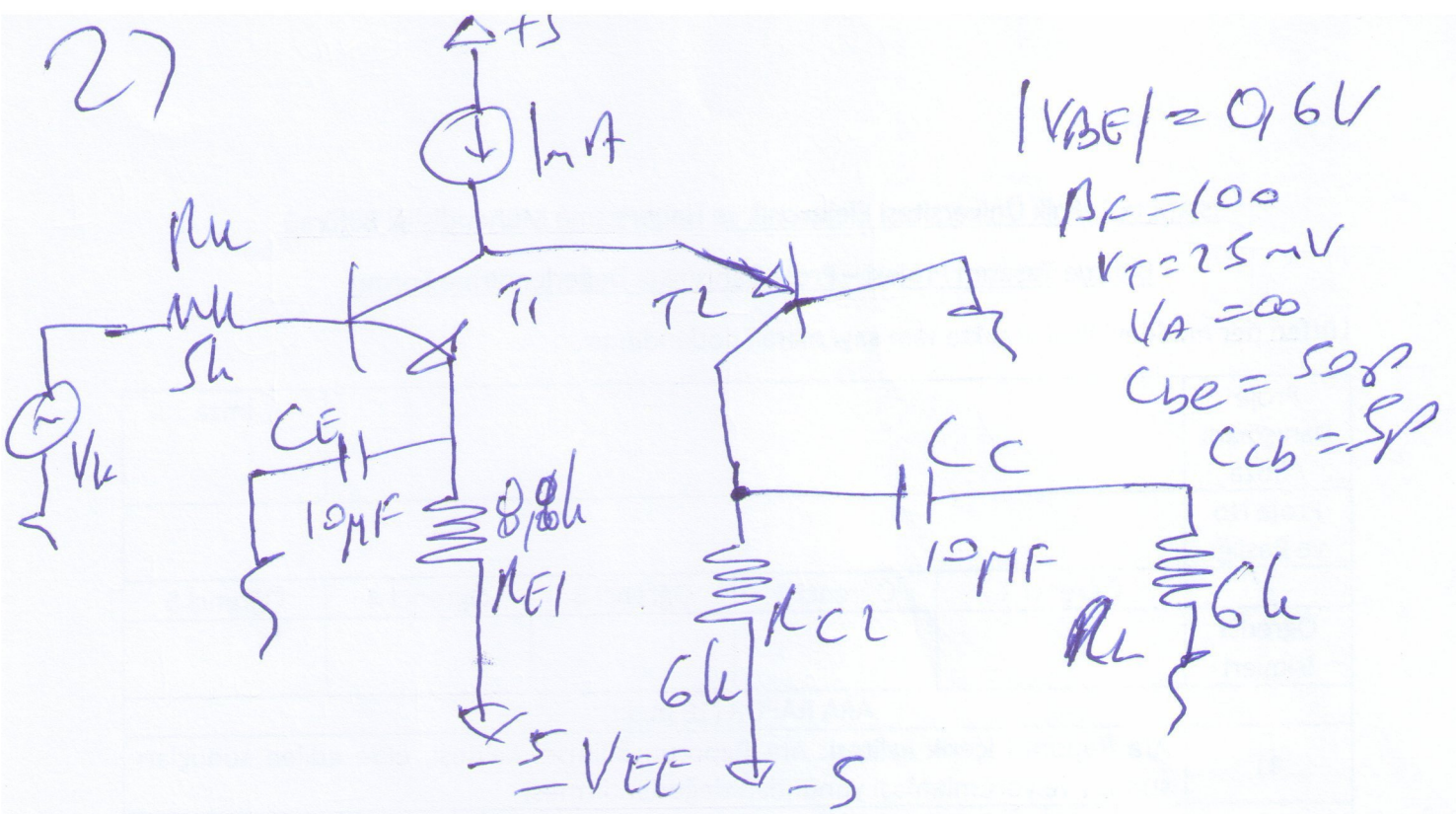

a) Find the poles and the zero.

$$f_{LEP} = \frac{1}{\left[8,8k \parallel \left(\frac{1}{g_{m1}} + \frac{R_k}{\beta_F} \right) \right] \cdot C_E \cdot 2\pi}$$

-1000Ω

can be ignored

$$g_{m1} = \frac{I_{C1}}{V_T} \quad I_{C1} = \beta_F \cdot I_{B1} = \frac{0 - V_{BE} - V_{EE} + V_{CC}}{R_{E1}}$$

$$\downarrow \quad \downarrow$$


$$= \frac{0,5mA}{25mV} = 20mA/V \quad = \frac{4,4k}{8,8k} = 0,5mA$$

$$f_{LEP} \approx \frac{1}{2\pi \cdot 100 \cdot 10\mu F} \approx 1k / 2\pi = 160Hz$$

$$f_{LEO} = \frac{1}{2\pi \cdot 8,8k \cdot 10\mu} \approx 2Hz$$

f_{LC}
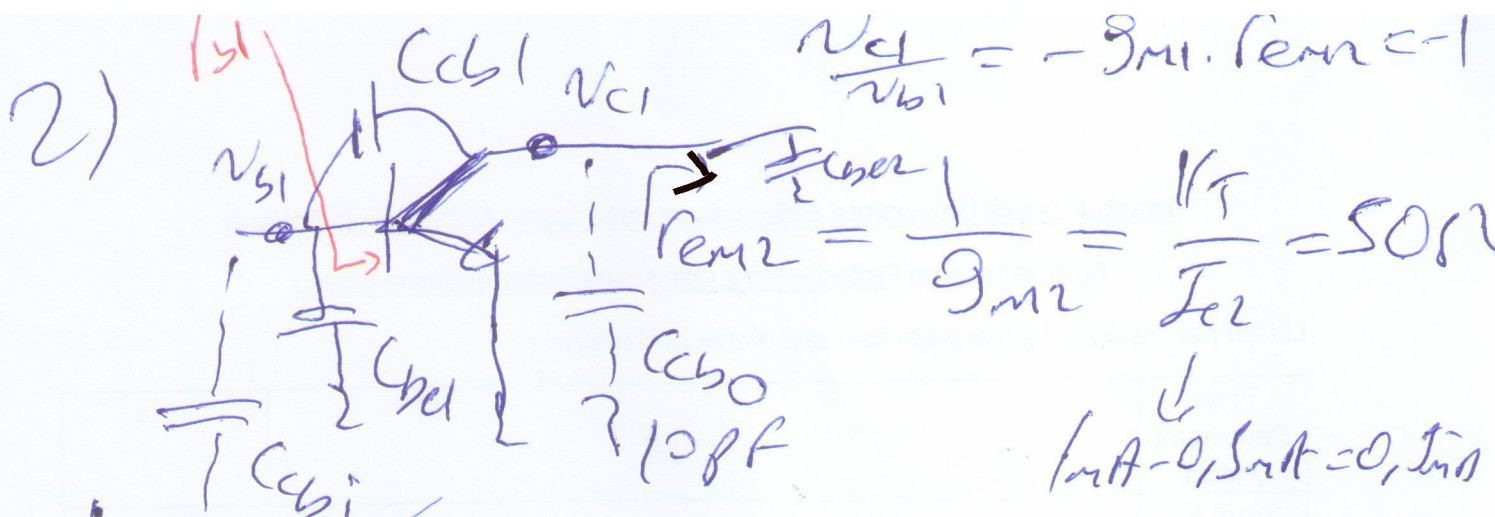
$$f_{LCc} = \frac{1}{2\pi \cdot (6k + 6k) \cdot 10\mu} = 1,2Hz$$




$$C_{cbi} = C_{cb1} (1 - (-1)) = 10 \text{ pF}$$

$$C_{cb0} = C_{cb1} (1 - \frac{1}{-1}) = 10 \text{ pF}$$

$$f_{u1} = \frac{1}{2\pi \cdot 60 \text{ pF} \cdot (R_{in} || r_{b1})} \approx 1 \text{ MHz}$$

$$r_{b1} = \rho_F \cdot \frac{1}{g_{m1}} = 5 \Omega$$
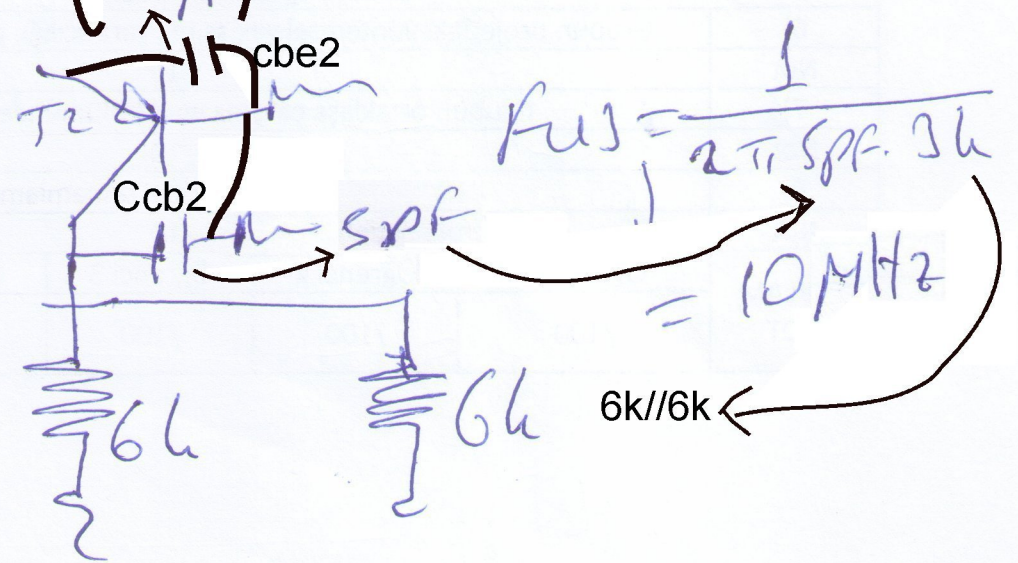
$$f_{u2} = \frac{1}{2\pi (10 \text{ pF} + 50 \text{ pF}) \cdot r_{em2}} \approx 5.3 \text{ MHz}$$



$$f_{uc} \approx f_{u1} = 1 \text{ MHz}$$

