

$$\text{For BJT: } g_m = \frac{I_{CQ}}{V_T} \quad r_{be} = r_\pi = \frac{\beta_F}{g_m}$$

$$\frac{V_C}{V_b} = -g_m \frac{r_{ce}^2}{g_m r_{eo} r_{ce}^2 + r_{ce}^2 + r_{eo} r_{ce}} (r_{cN}/r_{co})$$

$$r_{cN} = r_{ce} + r_{be}/r_{eo} + g_m (r_{be}/r_{eo}) r_{ce} \quad (r_{cN} \neq r_{ci}) \quad (r_{bo} = 0 \rightarrow r_{cN} = r_{ci})$$

$$r_{co} \ll r_{cN} \text{ and } r_{eo} \ll r_{ce} \rightarrow \frac{v_c}{v_b} \cong -\frac{g_m r_{co}}{1 + g_m r_{eo}}$$

$$\frac{v_e}{v_b} = g_m \frac{\frac{r_{eo}}{1 + g_m r_{eo}} \frac{r_{cN}}{r_{cN} + r_{co}} + \frac{r_{eo}}{\beta_F}}{1 + g_m \frac{r_{eo}}{\beta_F}}$$

$$r_{co} \ll r_{cN} \text{ and } g_m r_{eo} \ll \beta_F \rightarrow \frac{v_e}{v_b} \cong \frac{g_m r_{eo}}{1 + g_m r_{eo}}$$

$$\frac{v_c}{v_e} = \left(\frac{g_m}{1 + g_m \frac{r_{bo}}{\beta_F}} + \frac{1}{r_{ce}} \right) (r_{ce}/r_{co})$$

$$r_{co} \ll r_{ce} \text{ and } \frac{1}{r_{ce}} \ll \frac{g_m}{1 + g_m \frac{r_{bo}}{\beta_F}} \rightarrow \frac{v_c}{v_e} \cong \frac{g_m r_{co}}{1 + g_m \frac{r_{bo}}{\beta_F}}$$

$$r_{ei} = \left[\frac{1}{g_m} \frac{\left(1 + g_m \frac{r_{bo}}{\beta_F} \right) (r_{ce} + r_{co})}{\frac{1}{g_m} + \frac{r_{bo}}{\beta_F} + r_{ce}} \right] // [r_{be} + r_{bo}]$$

$$r_{co} \ll r_{ce} \text{ and } \frac{\beta_F + g_m r_{bo}}{\beta_F} \ll g_m r_{ce} \rightarrow r_{ei} \cong \frac{1}{g_m} + \frac{r_{bo}}{\beta_F}$$


$$r_{bi} = r_{be} \frac{r_{be} + r_{eo} + \beta_F r_{eo} + g_m r_{ce}^2}{r_{be} + g_m r_{eo} r_{be} - g_m r_{eo} r_{be} \frac{r_{cN}}{r_{cN} + r_{co}}}$$

$$r_{co} \ll r_{cN} \text{ and } g_m r_{eo} \ll \beta_F \rightarrow r_{bi} \cong \beta_F \left(\frac{1}{g_m} + r_{eo} \right)$$

$$r_{ci} = r_{ce} + \frac{g_m r_{ce} r_{be} r_{eo}}{r_{eo} + r_{be} + r_{bo}} + \frac{r_{eo} (r_{be} + r_{bo})}{r_{eo} + r_{be} + r_{bo}}$$

$$r_{eo} \ll (r_{be} + r_{bo}) \rightarrow r_{ci} \cong r_{ce} + \frac{g_m r_{ce} r_{be} r_{eo}}{r_{be} + r_{bo}} + r_{eo}$$

%%%%%%%%%%%%%

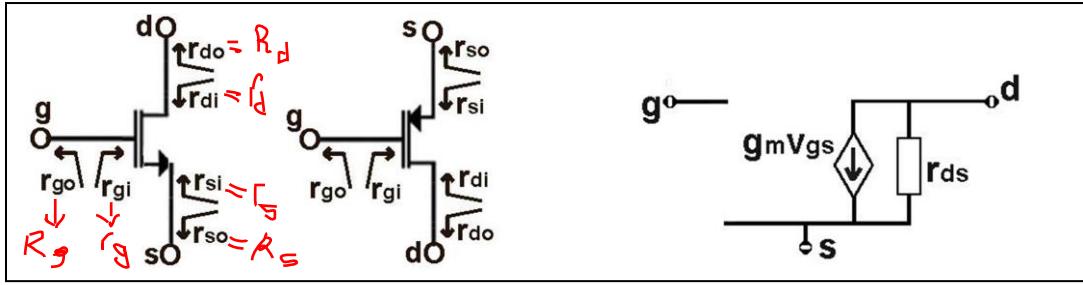

$$\text{For MOSFET: } g_m = \sqrt{2\beta I_{DQ}} \quad r_{gs} = \infty$$

$$d \leftrightarrow c, s \leftrightarrow e, b \leftrightarrow g$$

$$(\beta_F = \infty), (r_{gs} \equiv r_{be}), (r_{ds} \equiv r_{ce}), (r_{gi} \equiv r_{bi}), (r_{go} \equiv r_{bo}), (r_{si} \equiv r_{ei}), (r_{so} \equiv r_{eo}), (r_{di} \equiv r_{ci}), (r_{do} \equiv r_{co})$$

$$\frac{V_d}{V_g} = -g_m \frac{r_{ds}^2}{g_m r_{so} r_{ds}^2 + r_{ds}^2 + r_{so} r_{ds}} \quad (r_{di} // r_{do})$$

$$r_{di} = r_{ds} + r_{so} + g_m r_{so} r_{ds}$$

$$r_{do} \ll r_{di} \text{ and } r_{so} \ll r_{ds} \rightarrow \frac{v_d}{v_g} \cong -\frac{g_m r_{do}}{1 + g_m r_{so}}$$

$$\frac{v_s}{v_g} = \frac{g_m r_{so}}{1 + g_m r_{so}} \frac{r_{di}}{r_{di} + r_{do}}$$

$$r_{do} \ll r_{di} \rightarrow \frac{v_s}{v_g} \cong \frac{g_m r_{so}}{1 + g_m r_{so}}$$

$$\frac{v_d}{v_s} = \left(g_m + \frac{1}{r_{ds}} \right) (r_{ds} // r_{do})$$

$$r_{do} \ll r_{ds} \text{ and } \frac{1}{r_{ds}} \ll g_m \rightarrow \frac{v_c}{v_e} \cong g_m r_{do}$$

$$r_{si} = \left[\frac{1}{g_m} \frac{(r_{ds} + r_{do})}{\frac{1}{g_m} + r_{ds}} \right]$$

$$r_{do} \ll r_{ds} \text{ and } \frac{1}{g_m} \ll r_{ds} \rightarrow r_{si} \cong \frac{1}{g_m}$$

$$r_{gi} = \infty$$

$$r_{di} = r_{ds} + g_m r_{so} r_{ds} + r_{so}$$
