

New current-mode special function continuous-time active filters employing only OTAs and OPAMPs

ERDEM SERKAN ERDOGAN, RASIT ONUR TOPALOGLU,
HAKAN KUNTMAN and OGUZHAN CICEKOGLU

INT. J. ELECTRONICS, VOL. 91, NO. 6, JUNE 2004, 345–359

Active-Only Filters

- Active filters utilizing an operational amplifier (OPAMP) pole and the transconductance control property of the operational transconductance amplifier (OTA) have received considerable attention recently.

These filters do not need to employ additional passive elements, and are therefore sometimes called active-only filters.

Active-Only Filters

- The major advantage of these circuits is the elimination of passive elements that may result in a reduction of chip area for integrated circuit implementations.
- A growing number of publications exists in the literature on OPAMP and OTA-only filters

Active-Only Filters

- This study offers new topologies in current-mode active-only multifunction filter implementation.
- Three new current mode active-only filters are proposed.
- By cascading the proposed filters, which implement LPN and HPN functions, higher order band-pass and band-stop filter functions can be obtained.

Active-Only Filters

- OTA is assumed as an ideal voltage-controlled current source.
- The g_m (transconductance gain), which is used to relate output current to input voltage, is
- a function of the bias current, I_A .
- For the case of OTAs using MOS transistors in the saturation region, the g_m s are proportional to $\sqrt{I_A}$

Active-Only Filters

- The OPAMP, can be modelled by a single pole model, which can be written as B/s for the operating range of frequencies,
- This model of the OPAMP is valid between the first and second poles in the frequency domain.
- valid from a few kilohertz to a few megahertz.

Active-Only Filters

Figure 1 (high-pass notch function, circuit 1):

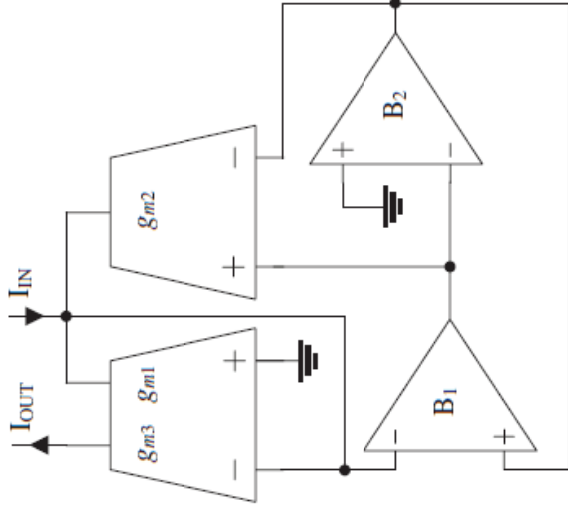


Figure 1. Circuit 1, high-pass notch.

$$\begin{aligned}
 T_{\text{HPN}}(s) &= \frac{I_{\text{out}}}{I_{\text{in}}} = \frac{A_{\text{HPN}}(s^2 + \omega_0^2)}{s^2 + (\omega_p/Q)s + \omega_p^2} \\
 &= -\frac{g_{m3}(s^2 + B_1B_2)}{g_{m1}s^2 + g_{m2}B_1s + B_1B_2(g_{m1} + g_{m2})}
 \end{aligned}
 \tag{1a}$$

The angular resonant frequency, quality factor and pass-band gain, denoted by A_{HPN} , are given by

$$\omega_p = \sqrt{\frac{(g_{m1} + g_{m2})B_1B_2}{g_{m1}}} \quad \omega_0 = \sqrt{B_1B_2}
 \tag{1b}$$

$$Q = \frac{1}{g_{m2}} \sqrt{\frac{g_{m1}(g_{m1} + g_{m2})B_2}{B_1}} \quad A_{\text{HPN}} = -\frac{g_{m3}}{g_{m1}}
 \tag{1c}$$

The active sensitivities of the circuit are expressed as

$$S_{B_1}^{\omega_p} = S_{B_2}^{\omega_p} = S_{B_1}^{\omega_0} = S_{B_2}^{\omega_0} = -S_{B_1}^Q = S_{B_2}^Q = \frac{1}{2}
 \tag{1d}$$

$$S_{g_{m1}}^{\omega_p} = -S_{g_{m2}}^{\omega_p} = \frac{-g_{m2}}{2(g_{m1} + g_{m2})}
 \tag{1e}$$

$$S_{g_{m1}}^Q = -S_{g_{m2}}^Q = \frac{2g_{m1} + g_{m2}}{2(g_{m1} + g_{m2})}
 \tag{1f}$$

Active-Only Filters

Figure 2 (low-pass notch function, circuit 2):

$$T_{\text{LPN}}(s) = \frac{I_{\text{out}}}{I_{\text{in}}} = \frac{A_{\text{LPN}}(s^2 + \omega_0^2)}{s^2 + (\omega_p/Q)s + \omega_p^2} = -\frac{g_{m3}(s^2 + B_1B_2)}{(g_{m1} + g_{m2})s^2 + g_{m2}B_2s + B_1B_2g_{m1}} \quad (2a)$$

The angular resonant frequency, quality factor and pass-band gain, denoted by A_{LPN} , are given by

$$\omega_p = \sqrt{\frac{g_{m1}B_1B_2}{(g_{m1} + g_{m2})}} \quad \omega_0 = \sqrt{B_1B_2} \quad (2b)$$

$$Q = \frac{1}{g_{m2}} \sqrt{\frac{g_{m1}(g_{m1} + g_{m2})B_1}{B_2}} \quad A_{\text{LPN}} = -\frac{g_{m3}}{g_{m1} + g_{m2}} \quad (2c)$$

The active sensitivities of the circuit are expressed as

$$S_{B_1}^{\omega_p} = S_{B_2}^{\omega_p} = S_{B_1}^{\omega_0} = S_{B_2}^{\omega_0} = S_{B_1}^Q = S_{B_2}^Q = -S_{B_2}^Q = \frac{1}{2} \quad (2d)$$

$$S_{g_{m1}}^{\omega_p} = -S_{g_{m2}}^{\omega_p} = \frac{g_{m2}}{2(g_{m1} + g_{m2})} \quad (2e)$$

$$S_{g_{m1}}^Q = -S_{g_{m2}}^Q = \frac{2g_{m1} + g_{m2}}{2(g_{m1} + g_{m2})} \quad (2f)$$

$$S_{g_{m3}}^{A_{\text{LPN}}} = 1 \quad S_{g_{m1}}^{A_{\text{LPN}}} = -\frac{g_{m1}}{g_{m1} + g_{m2}} \quad S_{g_{m2}}^{A_{\text{LPN}}} = -\frac{g_{m2}}{g_{m1} + g_{m2}} \quad (2g)$$

Thus, all sensitivities are no more than unity or can be made smaller than unity.

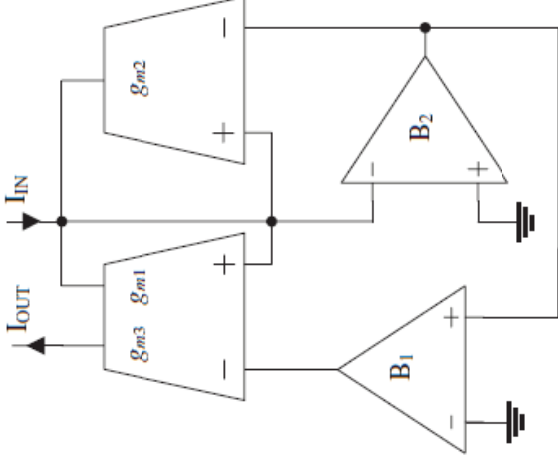


Figure 2. Circuit 2, low-pass notch.

Active-Only Filters

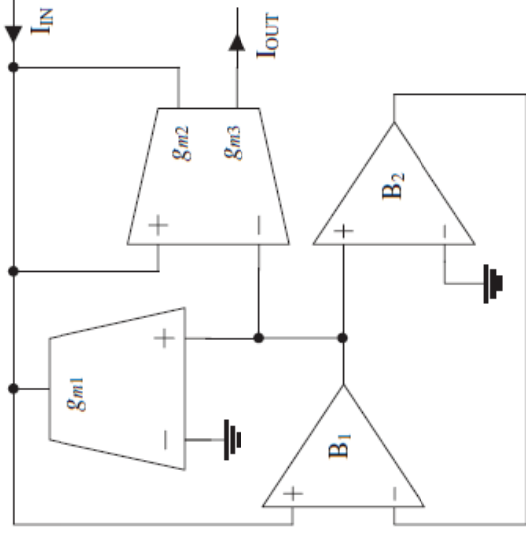


Figure 3. Circuit 3, AP function.

Figure 3 (all-pass function, circuit 3):

$$T_{AP}(s) = \frac{I_{out}}{I_{in}} = \frac{A_{AP}(s^2 - (\omega_p/Q)s + \omega_p^2)}{s^2 + (\omega_p/Q)s + \omega_p^2} \quad (3a)$$

$$= -\frac{g_{m3}(s^2 - B_1s + B_1B_2)}{g_{m2}s^2 + (g_{m1}B_1 - g_{m2}B_1)s + B_1B_2g_{m2}}$$

The delay is given by

$$\tau_{AP}(\omega) = \frac{2(\omega_p^2 + \omega^2)}{Q\omega_p((\omega_p^2 - \omega^2)^2/\omega_p^2 + \omega^2/Q^2)} \quad (3b)$$

$$= \frac{2B_1g_{m2}(g_{m1} - g_{m2})(\omega^2 + B_1B_2)}{(g_{m2}^2\omega^2(\omega^2 - 2B_1B_2) + B_1^2(B_2^2g_{m2}^2 + (g_{m1} - g_{m2})^2\omega^2))}$$

The angular resonant frequency, quality factor and pass-band gain, denoted by A_{AP} , are given by

$$\omega_p = \sqrt{B_1B_2} \quad (3c)$$

$$Q = \frac{g_{m2}}{(g_{m1} - g_{m2})} \sqrt{\frac{B_2}{B_1}} \quad A_{AP} = -\frac{g_{m3}}{g_{m2}} \quad (3d)$$

Active-Only Filters

The active sensitivities of the circuit are expressed as

$$S_{B_1}^{\omega_p} = S_{B_2}^{\omega_p} = S_{B_2}^Q = -S_{B_1}^Q = \frac{1}{2} \quad (3e)$$

$$-S_{g_{m1}}^Q = S_{g_{m2}}^Q = \frac{g_{m1}}{(g_{m1} - g_{m2})} \quad (3f)$$

$$S_{g_{m3}}^{A_{AP}} = -S_{g_{m2}}^{A_{AP}} = 1 \quad (3g)$$

Thus, all sensitivities except the sensitivities of Q on g_{m1} and g_{m2} are no more than unity. However, this drawback can be tolerated for particular phase responses and g_m values. g_{m3} should be chosen equal to $(g_{m1} - g_{m2})$ for proper operation.

Active-Only Filters

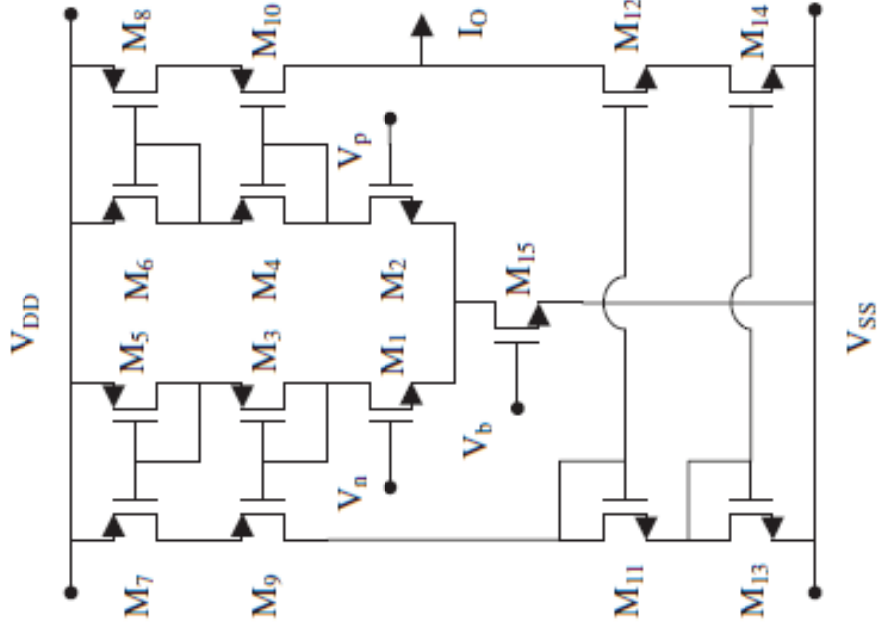


Figure 4. CMOS OTA circuit.

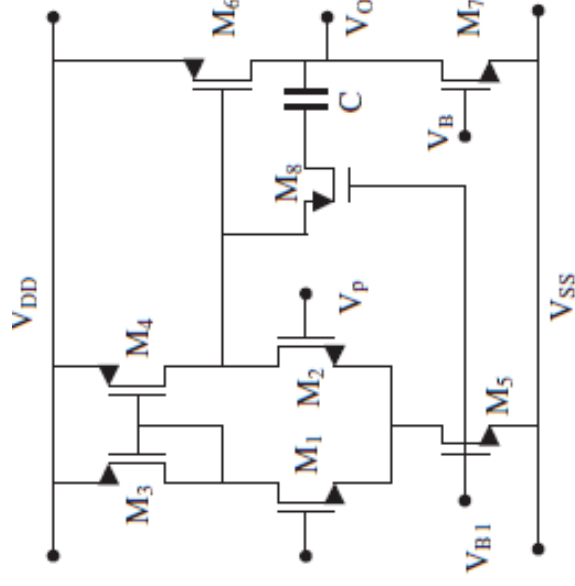


Figure 5. CMOS OPAMP circuit.

Active-Only Filters

- **Simulation results, discussion and design example**
- The filters are designed to realize a filter response with a resonant frequency f_0 of 417 kHz.
- The compensation capacitors of the OPAMPs are taken as 50 pF.
- A GBW of 417 kHz is obtained for both OPAMPs with these capacitances.

Active-Only Filters

Transistor	L (μm)	W (μm)	Transistor	L (μm)	W (μm)
M1	3	60	M8	3	12
M2	3	60	M9	3	12
M3	3	12	M10	3	12
M4	3	12	M11	3	5
M5	3	12	M12	3	5
M6	3	12	M13	3	5
M7	3	12	M14	3	5
			M15	3	25

Table 1. Dimensions of transistors used in CMOS OTA.

Transistor	L (μm)	W (μm)	Transistor	L (μm)	W (μm)
M1	10	180	M5	32	12
M2	10	180	M6	10	392
M3	10	280	M7	10	232
M4	10	280	M8	10	39

Table 2. Dimensions of transistors used in CMOS OPAMP.

Active-Only Filters

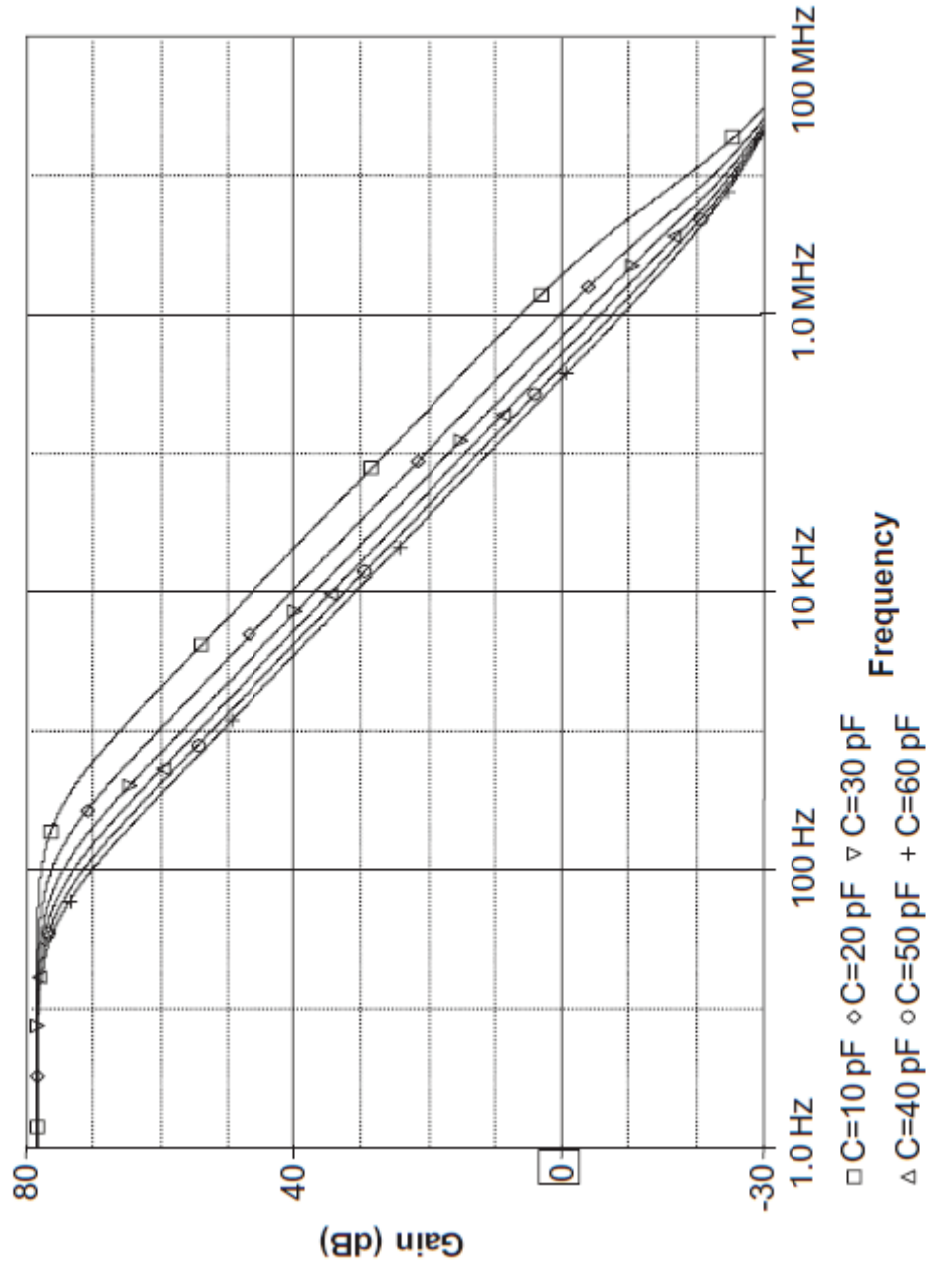


Figure 6. Gain-bandwidth product dependence of CMOS OPAMP on the compensation capacitor.

Active-Only Filters

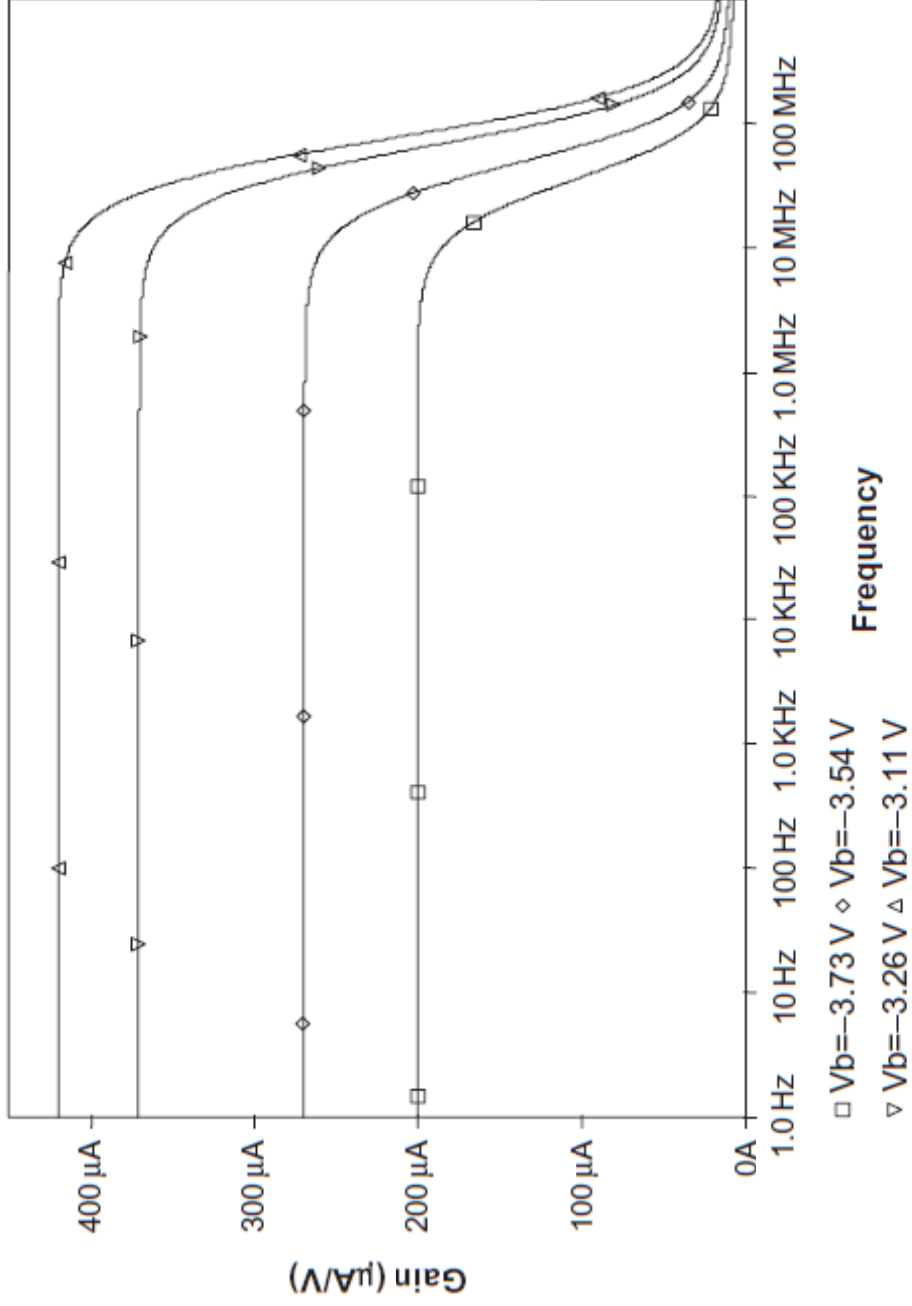


Figure 7. Frequency response dependence of CMOS OTA on bias voltage.

Active-Only Filters

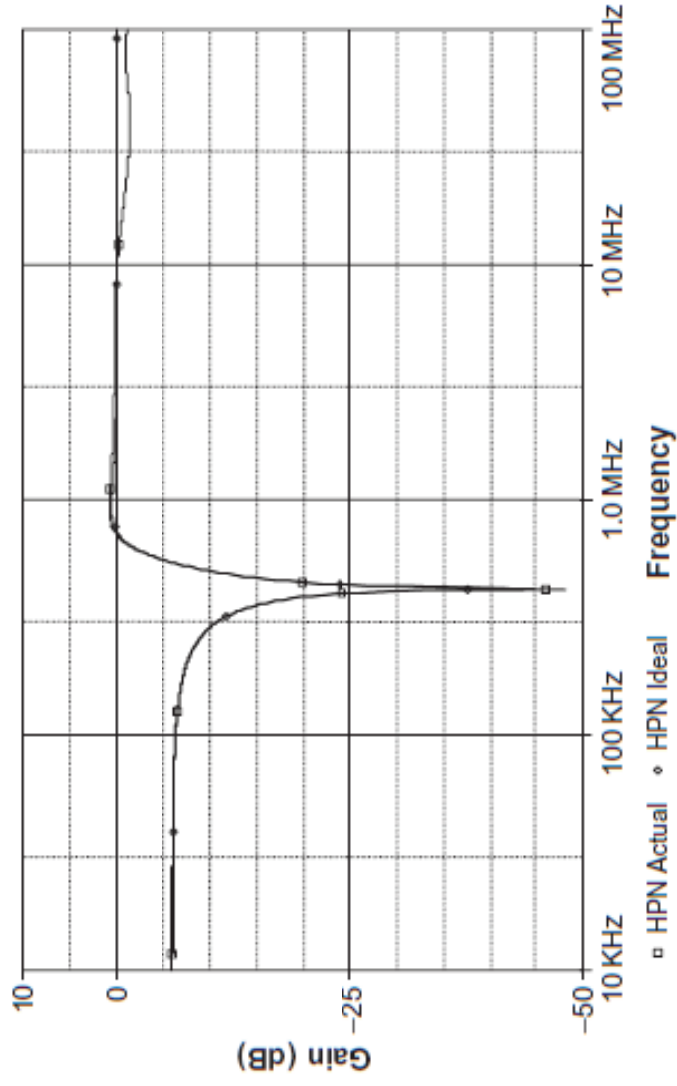


Figure 8(a). Frequency response of proposed HPN circuit, simulated with CMOS macro models of OPAMPs and OTAs.

Active-Only Filters

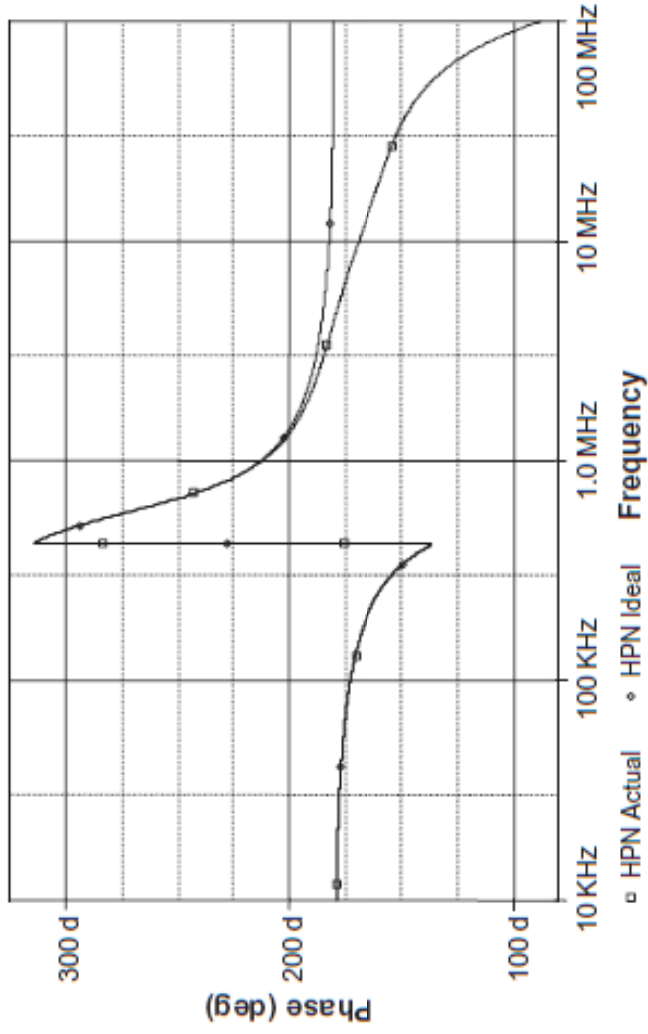


Figure 8(b). Phase response of proposed HPN circuit, simulated with CMOS macro models of OPAMPs and OTAs.

Active-Only Filters

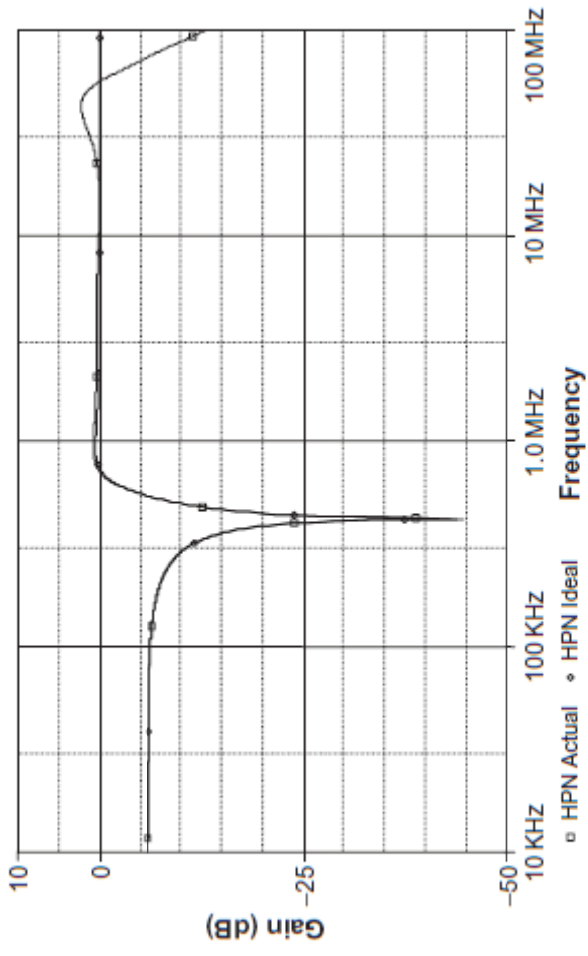


Figure 9(a). Frequency response of proposed HPN circuit, simulated with parasitics extracted from chip layout.

Active-Only Filters

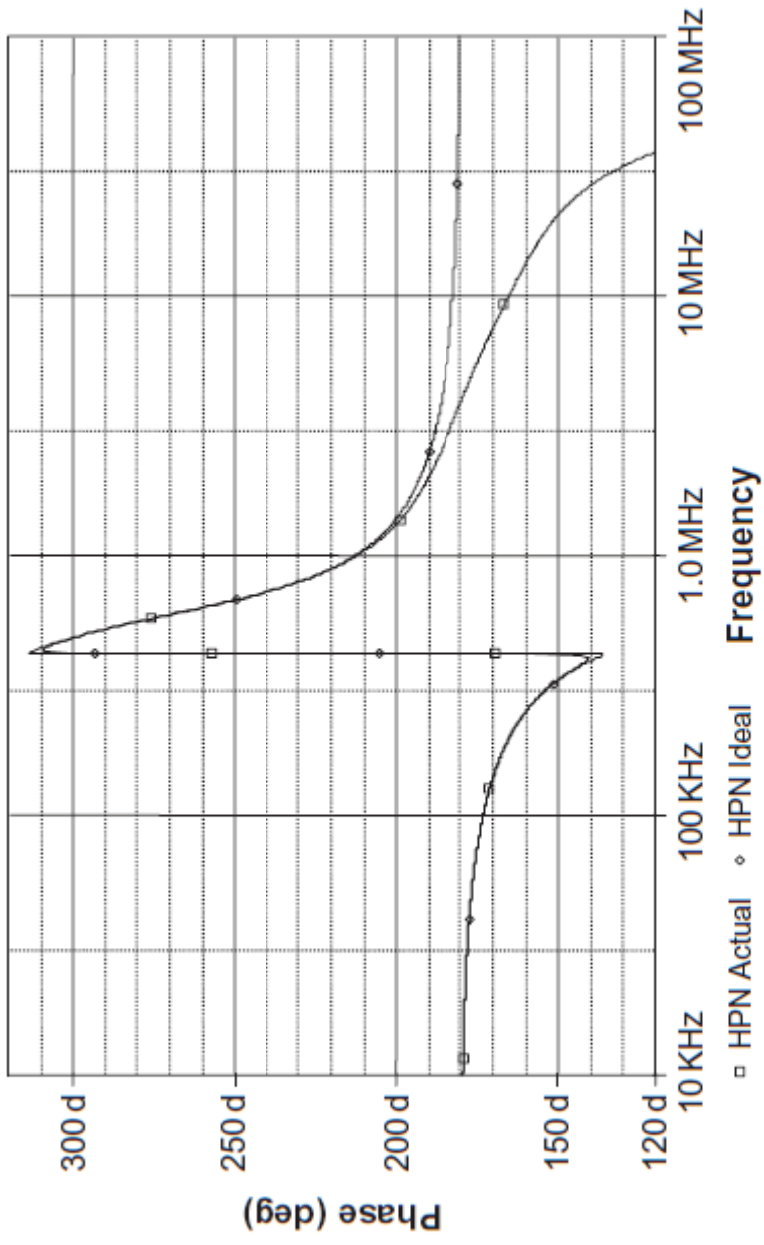


Figure 9(b). Phase response of proposed HPN circuit, simulated with parasitics extracted from chip layout.

Active-Only Filters

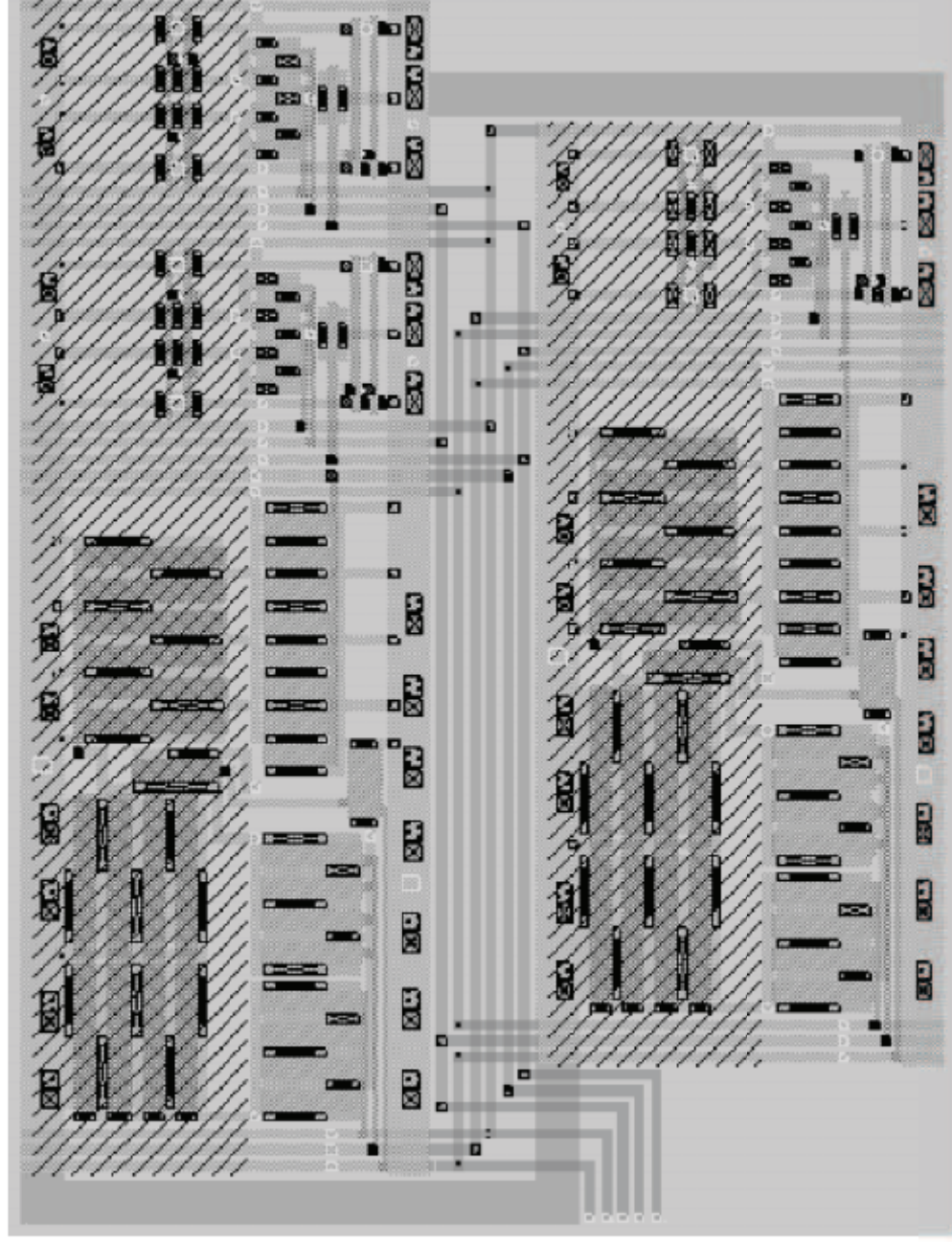


Figure 9(c). Layout of the filter chip implemented with SCMOS 2 μm technology.

Active-Only Filters

- the parameters can each be independently adjusted to any desired value without disturbing the others.
- Figure 10 shows the simulated HPN responses for $Q=1.41$ and for $Q=2.55$, both with the same zero frequency and pass-band gain.
- The Q parameter is changed by tuning the gms of OTAs

$$(g_{m1} = g_{m3} = 420 \mu\text{A/V}, g_{m2} = 200 \mu\text{A/V})$$

Active-Only Filters

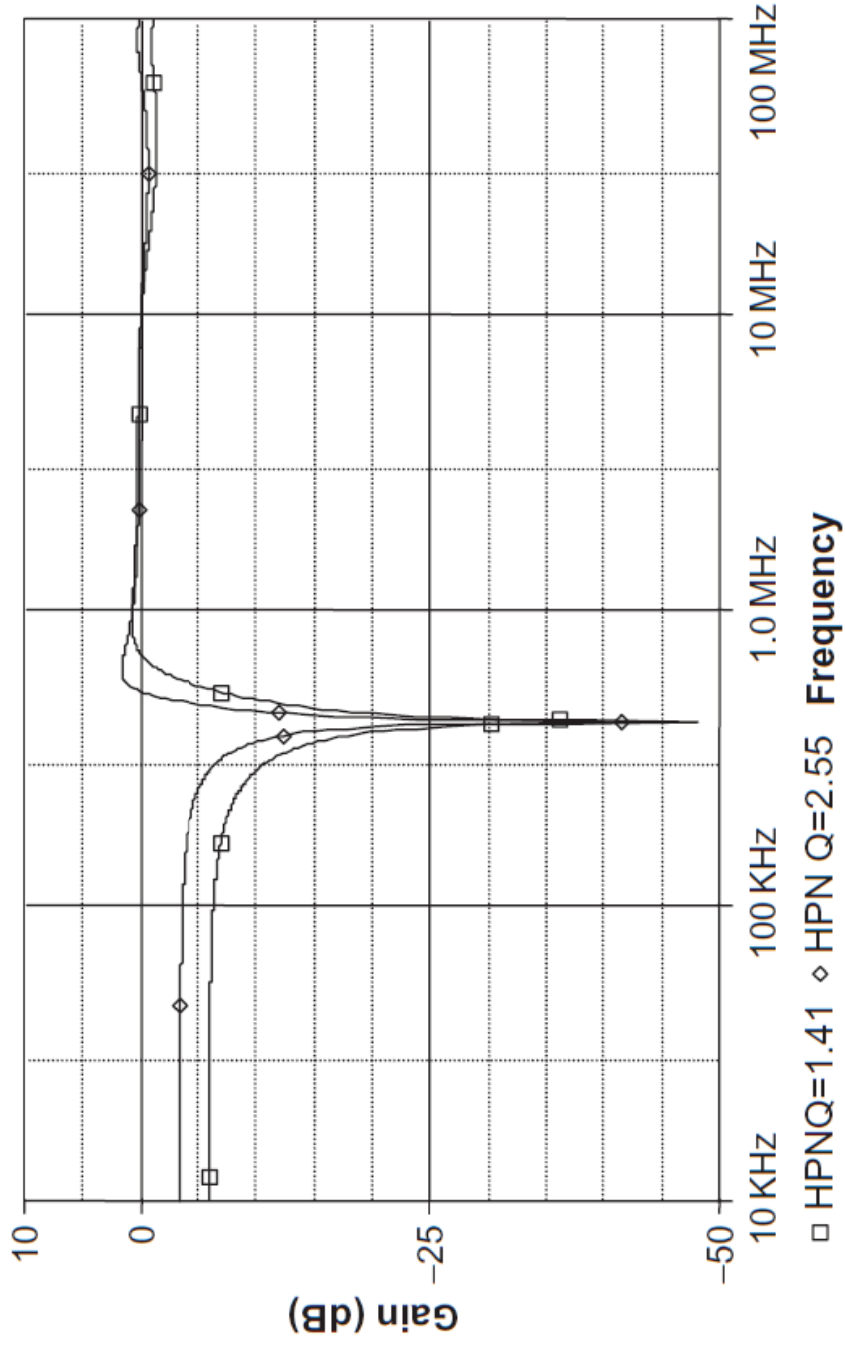


Figure 10. Frequency response of proposed HPN circuit for $Q = 1.41$ together with the response for $Q = 2.55$.

Active-Only Filters

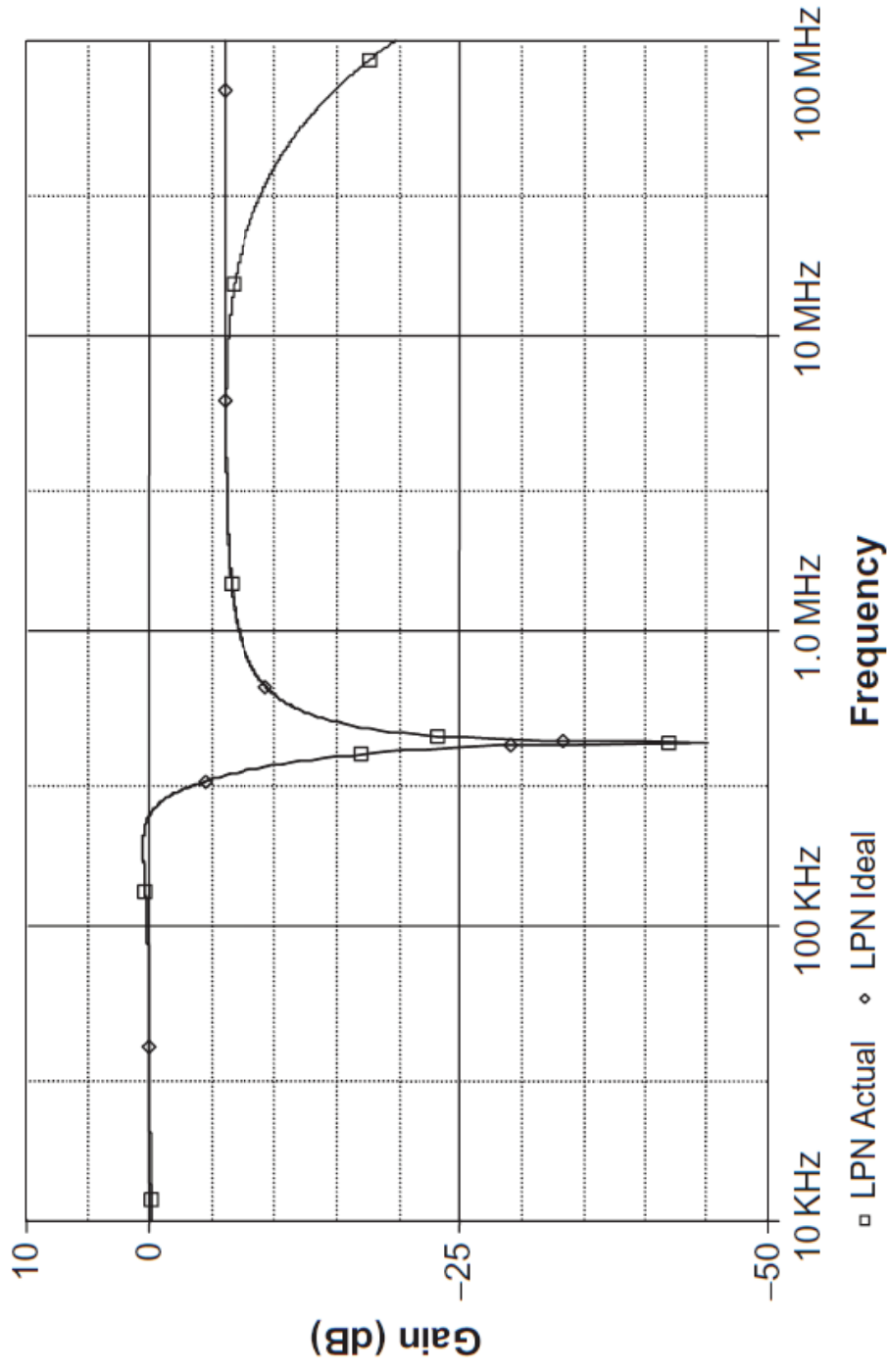


Figure 11(a). Frequency response of proposed LPN circuit, simulated with parasitics extracted from chip layout.

Active-Only Filters

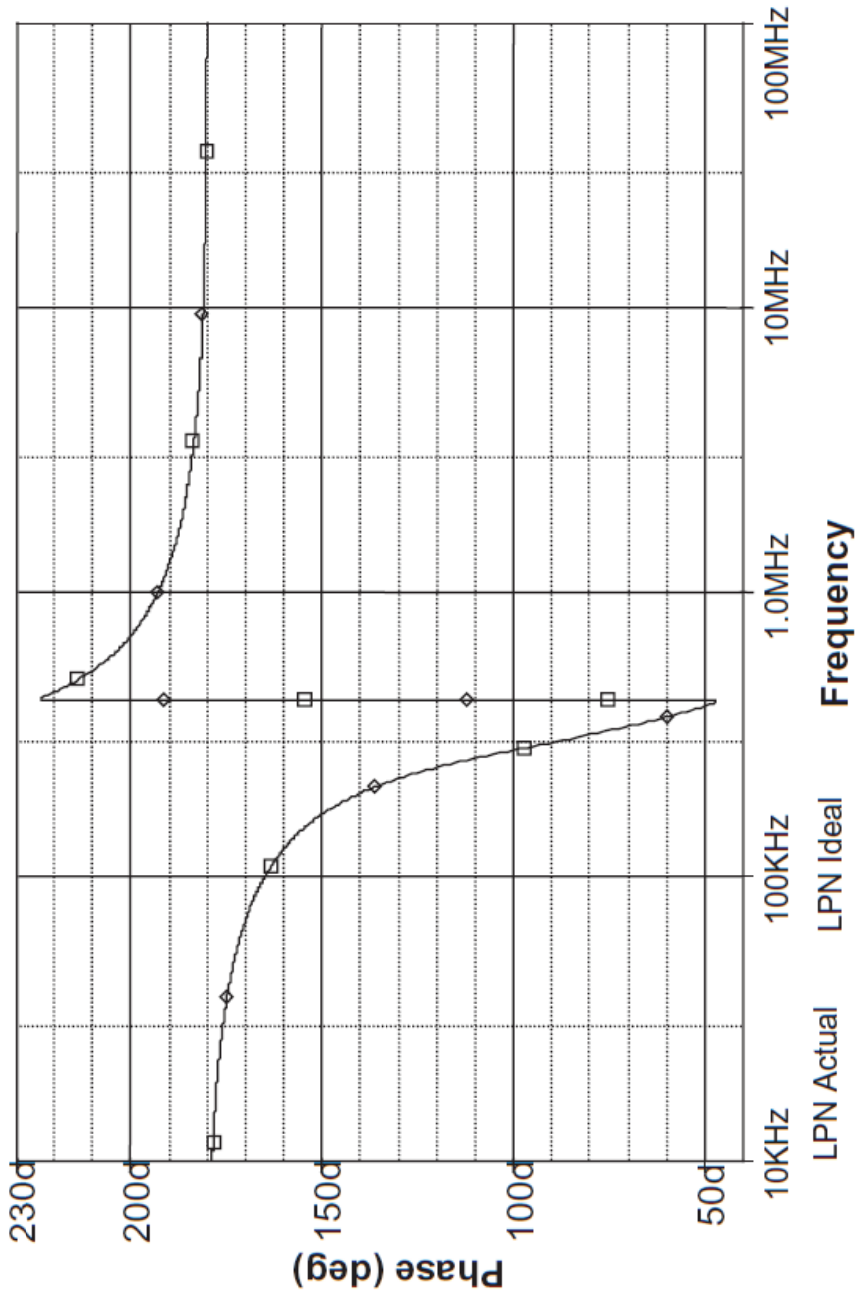


Figure 11(b). Phase response of proposed LPN circuit, simulated with parasitics extracted from chip layout.

Active-Only Filters

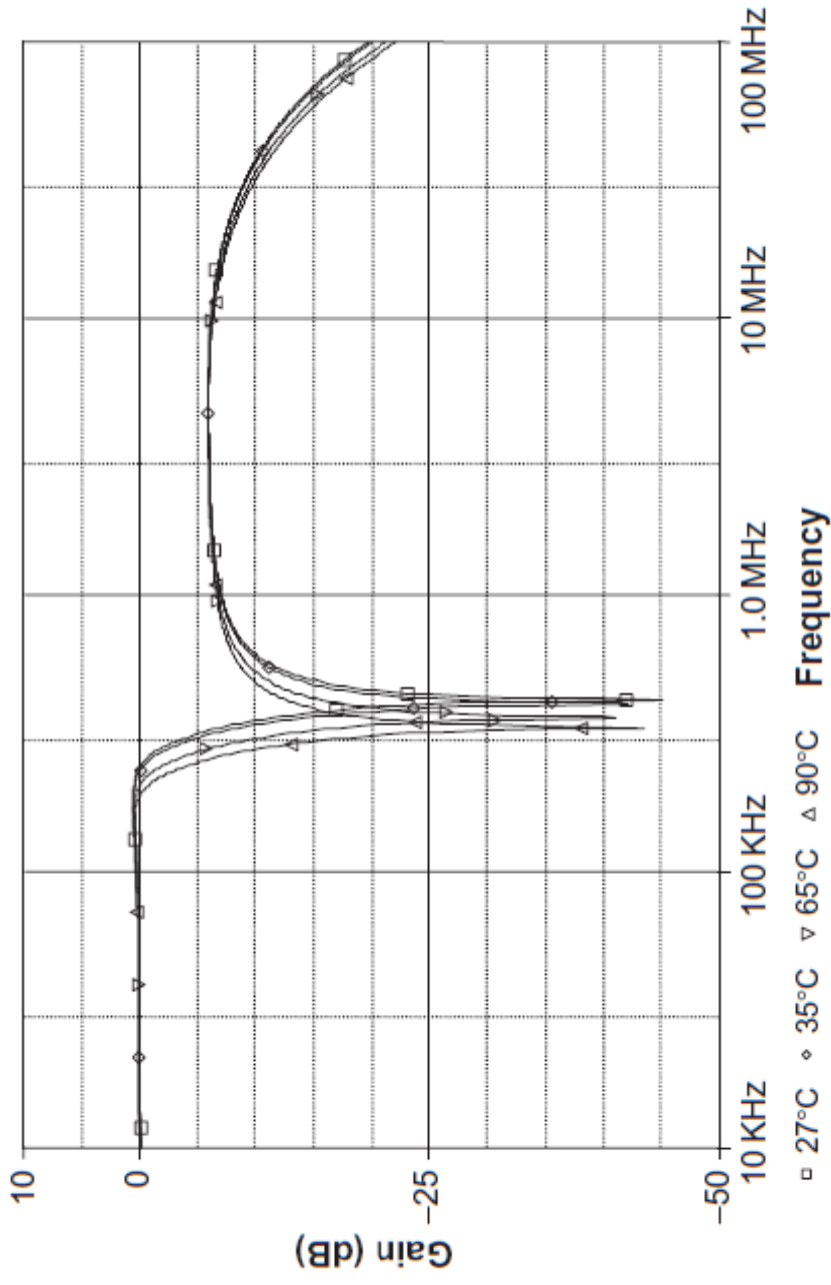


Figure 11(c). Temperature dependence of proposed LPN circuit, simulated with parasitics extracted from chip layout.

Active-Only Filters

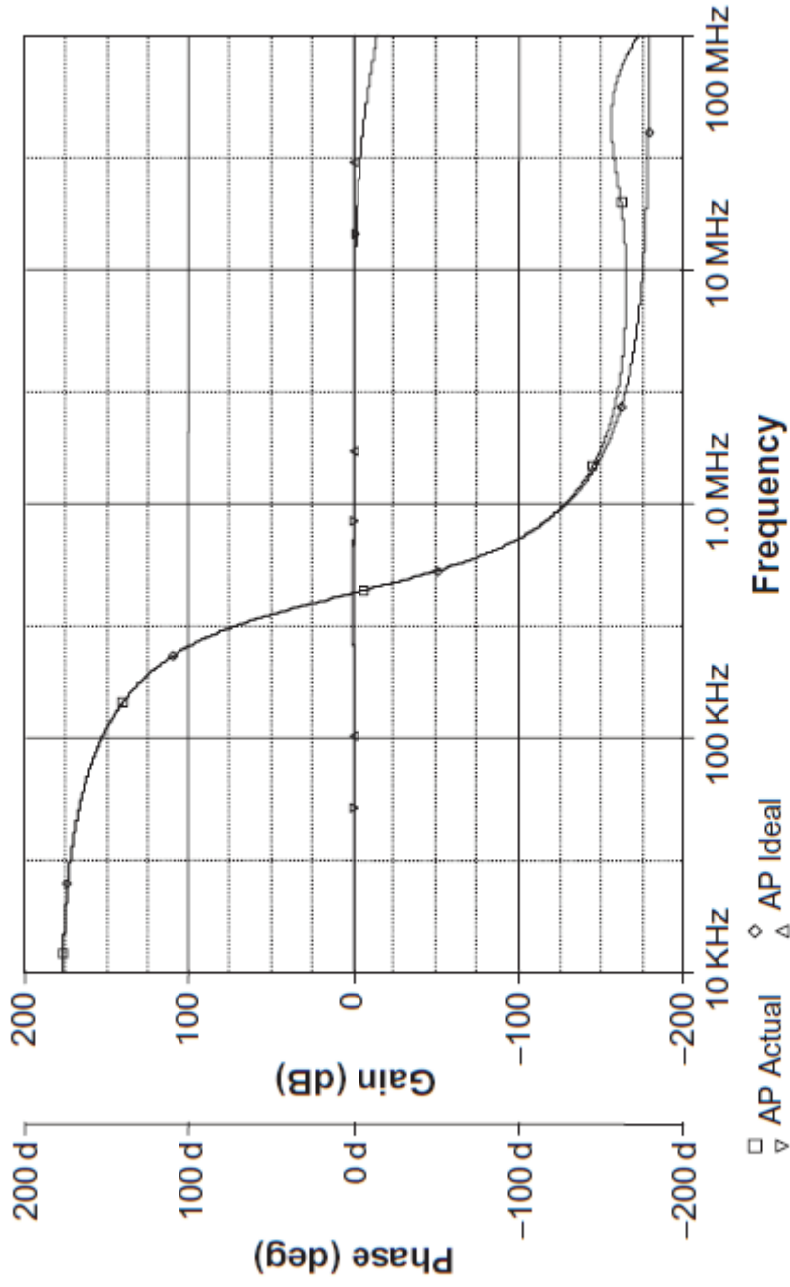


Figure 12. Frequency response of proposed AP circuit, simulated with CMOS macro models of OPAMPs and OTAs.

Active-Only Filters

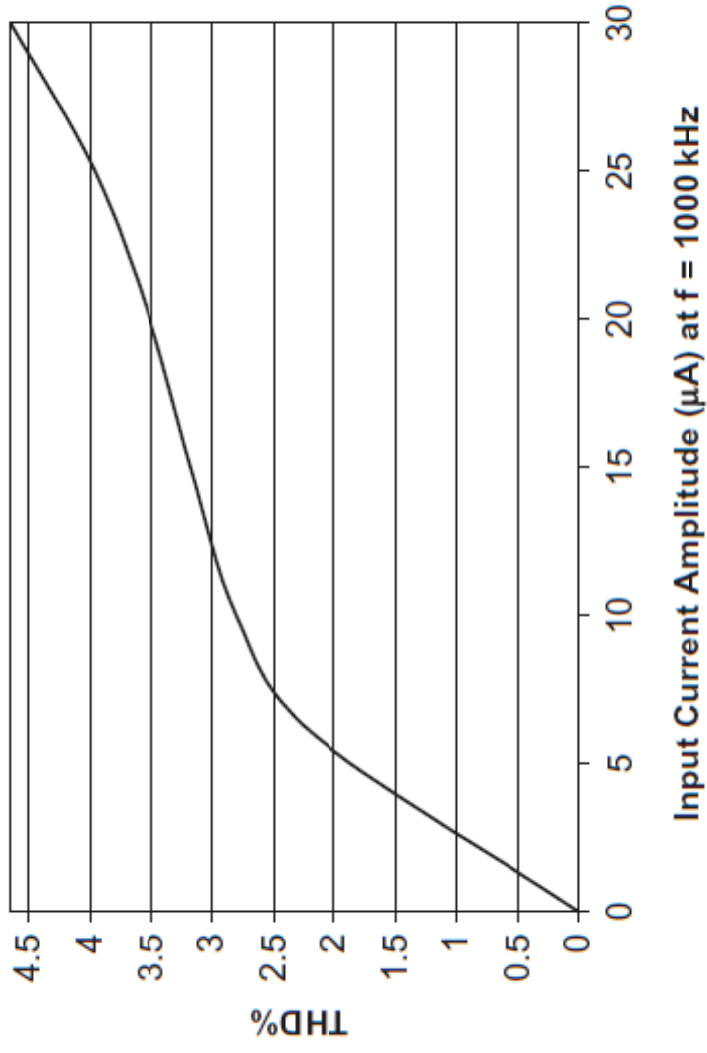


Figure 13. Dependence of total harmonic distortion at output of circuit 1 on input signal amplitude; input is a 1000 kHz sinusoidal current signal.

Active-Only Filters

• **References**

- ERDOGAN, E. S., TOPALOGLU, R. O., KUNTMAN, H. and CICEKOGLU, O., 2004, New current-mode special function continuous-time active filters employing only OTAs and OPAMPs, *International Journal of Electronics*, VOL. 91, NO. 6, 345–359
- ABUELMA'ATTI, M. T., and ALZAHHER, H. A., 1997, Universal three inputs and one output current-mode filter without external passive elements. *Electronics Letters*, 33, 281–283.
- LAKER, K. R., and SANSEN, W. M. C., 1994, *Design of Analog Integrated Circuits and Systems* (New York: McGraw Hill), }6, pp. 475–627.
- SINGH, A. K., and SENANI, R., 1998, Low-component count active-only immittances and their application in realizing simple multifunction biquads. *Electronics Letters*, 34, 718–719.
- TSUKUTANI, T., HIGASHIMURA, M., KINUGASA, Y., SUMI, Y., and FUKUI, Y., 1999, A general class of current-mode active-only filters. *Proceedings of the International Technical Conference on Circuits/Systems, Computers and Communications, ITC-CSCC'99*, Niigata, Japan, 297–300.
- TSUKUTANI, T., HIGASHIMURA, M., KINUGASA, Y., SUMI, Y., and FUKUI, Y., 2000a, Novel voltage-mode active-only biquad with two integrator loops. *Proceedings of the International Technical Conference on Circuits/Systems Computers and Communications ITC-CSCC'2000*, Pusan, Korea, pp. 207–210.

Active-Only Filters

- TSUKUTANI, T., HIGASHIMURA, M., SUMI, Y., and FUKUI, Y., 2000b, Electronically tunable current-mode active-only biquadratic filter. *International Journal of Electronics*, 87, 307–314.
- TSUKUTANI, T., HIGASHIMURA, M., SUMI, Y., and FUKUI, Y., 2000c, Voltage-mode active-only biquad. *International Journal of Electronics*, 87, 1435–1442.
- TSUKUTANI, T., HIGASHIMURA, M., TAKAHASHI, N., SUMI, Y., and FUKUI, Y., 2001a, Novel voltage-mode biquad without external passive elements. *International Journal of Electronics*, 88, 13–22.
- TSUKUTANI, T., HIGASHIMURA, M., TAKAHASHI, N., SUMI, Y., and FUKUI, Y., 2001b, Novel voltage-mode biquad using only active devices. *International Journal of Electronics*, 88, 339–346.
- TSUKUTANI, T., ISHIDA, M., TSUIKI, S., and FUKUI, Y., 1996, Current mode biquad without external passive elements. *Electronics Letters*, 23, 197–198.