

Soru 1.

$$a) I_2 \cdot R_3 = V_{R1} \frac{R_3}{R_1} \quad V_{R1} = V_T \cdot \ln\left(\frac{I_2 \cdot A_{E1}}{I_1 \cdot A_{E2}}\right) \quad I_1 \cdot R_2 = I_2 \cdot R_3$$

$$V_{ref} = V_{EB2} + I_2 \cdot R_3 = V_{EB2} + \frac{R_2}{R_1} \cdot V_T \cdot \ln\left(\frac{R_2 \cdot A_{E1}}{R_3 \cdot A_{E2}}\right) = V_{EB2} + \frac{R_2}{R_1} \cdot V_T \cdot \ln\left(\frac{R_2}{R_3} \cdot m\right)$$

$$b) m = 10, V_{BEon} = 0.7V, V_T = 26mV, R_2 = R_3$$

$$V_{ref} = V_{EB2} + \frac{R_2}{R_1} \cdot V_T \cdot \ln(m)$$

$$\frac{\partial V_{ref}}{\partial T} = \frac{\partial V_{BE}}{\partial T} + \frac{R_2}{R_1} \cdot \frac{\partial V_T}{\partial T} \cdot \ln(m) = 0$$

$$\frac{R_2}{R_1} = \frac{-\frac{\partial V_{BE}}{\partial T}}{\frac{\partial V_T}{\partial T} \cdot \ln(m)} = \frac{-2.5mV / ^\circ C}{0.05mV / ^\circ C \times \ln(10)} = 12.78$$

$$V_{ref} = 0.7V + 12.78 \times 26mV \times \ln(10) = 1.464V$$

Soru 2.

a)

$$SR = \frac{I_o \cdot \omega_l}{g_{mi}} = \omega_l \cdot \sqrt{\frac{I_o}{\mu \cdot C_{OX} \cdot \left(\frac{W}{L}\right)_1}}$$

$$I_5 = I_o = \frac{SR^2}{\omega_l^2} \cdot \mu \cdot C_{OX} \cdot \left(\frac{W}{L}\right)_1 = \frac{(10 \times 10^6)^2}{(2 \times \pi \times 5 \times 10^6)^2} \cdot 20 \times 10^{-6} \times 9 = 18.25 \mu A$$

$$C_c = \frac{I_o}{SR} = \frac{18.25 \mu A}{10V / \mu sn} = 1.825 pF$$

b)

$$\frac{(W/L)_3}{(W/L)_6} = \frac{(W/L)_4}{(W/L)_6} = \frac{1}{2} \frac{(W/L)_5}{(W/L)_7} = \frac{I_o}{2 \cdot I_7}$$

$$\frac{1}{2} \cdot \frac{(W/L)_5}{(W/L)_7} = \frac{(W/L)_3}{(W/L)_6} = \frac{15}{45} \rightarrow I_7 = \frac{I_0}{2} \cdot \frac{(W/L)_6}{(W/L)_3} = \frac{1}{2} \times 18.25 \mu A \times 3 = 27.37 \mu A$$

$$(W/L)_7 = \frac{1}{2} \cdot (W/L)_5 \cdot \frac{(W/L)_6}{(W/L)_3} = \frac{1}{2} \cdot 5.3 = 7.5$$

c)

$$K_{V1} = \frac{g_{m1}}{g_{o2} + g_{o4}}, K_{V2} = -\frac{g_{m6}}{g_{o6} + g_{o7}}$$

$$g_{m1} = g_{m2} = \sqrt{I_5 \cdot k_N' \cdot \left[\frac{W}{L} \right]_1} = \sqrt{18.25 \mu A \times 20 \mu A / V^2 \times 9} = 57 \mu A / V$$

$$g_{m6} = \sqrt{2 \cdot I_7 \cdot k_P' \cdot \left[\frac{W}{L} \right]_6} = \sqrt{2 \times 27.37 \mu A \times 10 \mu A / V^2 \times 45} = 156 \mu A / V$$

$$g_{o2} + g_{o4} = \frac{1}{2} \cdot I_0 \cdot (\lambda_N + \lambda_p) = \frac{1}{2} \cdot 18.25 \mu A \cdot (0.03 V^{-1}) = 0.273 \mu A / V$$

$$g_{o6} + g_{o7} = I_7 \cdot (\lambda_N + \lambda_p) = 27.37 \mu A \times (0.03 V^{-1}) = 0.82 \mu A / V$$

$$K_{V1} = 209, K_{V2} = -190, K_d = 39710$$

Soru 3.

$$K_{V1} = \frac{g_{m1}}{g_{m4}} = \frac{\sqrt{k_N' \cdot (W/L)_1}}{\sqrt{k_P' \cdot (W/L)_3}} \rightarrow (W/L)_3 = (W/L)_4 = \frac{k_N' \cdot (W/L)_1}{k_P' \cdot K_{V1}^2} = \frac{20 \mu A / V^2 \cdot 3}{10 \mu A / V^2 \cdot 9} = \frac{2}{3}$$

$$SR = B \cdot \frac{I_A}{C_L + C_{ni}} \rightarrow B \cdot I_A = SR \cdot (C_L + C_{ni}) = 5V / \mu sn \times 50.3 pF = 251 \mu A$$

$$B = \frac{B \cdot I_A}{I_A} = \frac{251 \mu A}{100 \mu A} = 2.51$$

$$(W/L)_5 = B \cdot (W/L)_3 = 2.5 \times \frac{2}{3} = 1.66$$

$$G_m = B \cdot \sqrt{k_n' \cdot I_A \cdot \left(\frac{W}{L}\right)_1} = 2.5 \times \sqrt{20 \mu A / V^2 \times 100 \mu A \times 3} = 194 \mu A / V$$

b- baskın olmayan kutba kadar -20dB/dek ile düşmeli. Bunun için

$$f_{nd5} = GBW = \frac{g_{m4}}{2\pi C_{n5}}$$

$$g_{m4} = \sqrt{k_p' \cdot I_A \cdot \left(\frac{W}{L}\right)_4} = \sqrt{10 \mu A / V^2 \times 100 \mu A \times \left(\frac{2}{3}\right)} = 25.81 \mu A / V$$

$$f_{nd5} = GBW = \frac{25.81 \mu A / V}{2\pi \times 0.3 pF} = 13.7 MHz$$

$$R_o = \frac{2}{(\lambda_N + \lambda_P) \cdot B \cdot I_A} = \frac{2}{0.03 V^{-1} \times 251 \mu A} = 265 k\Omega$$

$$K_V = G_m \cdot R_o = 194 \mu A / V \times 265 k = 51$$


$$f_d = \frac{1}{2\pi R_o (C_{Lmin} + C_{n7})} = \frac{GBW}{K_V} = \frac{13.7 MHz}{51} = 268 kHz$$

$$(C_{Lmin} + C_{n7}) = \frac{1}{2\pi R_o \cdot f_d} = \frac{1}{2\pi \times 265 k \times 268 k} = 2.24 pF$$

$$C_{Lmin} = 2.24 pF$$

Soru 4.

a-

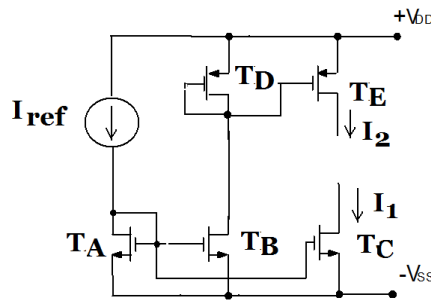

$$(W/L)_A = (W/L)_B = (W/L)_C, (W/L)_D = (W/L)_E, I_{ref} = 100 \mu A$$

$$b- r_z = \frac{I}{g_{d10} + g_{d12}} = \frac{I}{g_{d10} + g_{dE}} = \frac{1}{I_2 \cdot (\lambda_N + \lambda_P)} = \frac{1}{100 \mu A \times (0.03)} = 333 k\Omega$$