

belirleyiniz.

(10)

(10)

$$a) K_V = \frac{-R_2}{R_1} = -1 \Rightarrow R_1 = R_2 \rightarrow R_1 = R_2 = 10 \text{ k}\Omega$$

$$b) h_1 = \frac{\pi}{2} \cdot \frac{R_1}{R_2} \cdot \frac{V_X}{\beta \cdot K_{VO} \cdot V_{IP}}, V_X = 0,7 \text{ V}, \beta = \frac{R_1}{R_1 + R_2} = \frac{1}{2}, V_{sat} = 2 \text{ V} \Rightarrow |V_{IP}| = \frac{|V_{CC} - V_{sat} - V_{OL}|}{1 \text{ k}\Omega} = 7,3 \text{ V}$$

$$\Rightarrow h_1 = \frac{\pi}{2} \cdot 1 \cdot \frac{0,7}{\frac{1}{2} \cdot K_{VO} \cdot 7,3} \leq 10^{-4} \Rightarrow K_{VO} \geq \frac{\pi \cdot 0,7 \cdot 10^4}{7,3} \approx 3012,5$$

$$h_2 = -\frac{\pi}{2} \left(1 - \frac{R_1}{R_2} \cdot \frac{V_X}{V_{IP}}\right)^2 \left(\frac{\omega}{\beta K_{VO} \omega_0}\right)^2 \Rightarrow h_2 = -\frac{\pi}{2} \cdot \left(1 + \frac{1}{1} \cdot \frac{0,7}{7,3}\right)^2 \left(\frac{2\pi \cdot 20 \cdot 10^3}{\frac{1}{2} \cdot K_{VO} \cdot \omega_0}\right)^2 \leq 10^{-2}$$

$$K_{VO} \cdot \omega_0 \geq \sqrt{\frac{\pi}{2 \cdot 10^{-2}} \cdot \left(1 + \frac{0,7}{7,3}\right) \cdot (4\pi \cdot 20 \cdot 10^3)} \approx 3,15 \cdot 10^6 \Rightarrow K_{VO} \cdot f_0 \geq 519 \text{ kHz}$$

$$\omega_H = \frac{\pi \cdot \gamma E}{2V_X \left(2 - \frac{R_2}{R_1} \cdot \frac{V_{IP}}{V_X}\right)} \Rightarrow f_H = \frac{\gamma E}{4V_X \left(2 - \frac{R_2}{R_1} \cdot \frac{V_{IP}}{V_X}\right)} = \frac{\gamma E}{4 \cdot 0,7 \cdot \left(2 + 1 \cdot \frac{7,3}{0,7}\right)} \geq 10 \text{ kHz}$$

$$\gamma E \geq 10^4 \cdot 4 \cdot 0,7 \left(2 + \frac{7,3}{0,7}\right) = 348 \text{ V/ms}$$