

LT.Ü.  
ELEKTRİK ELEKTRONİK FAKÜLTESİ

Soru	1	2	3	4	5	6	7	8	Topl
Not									

Tarih

Bölüm


İsri

No

Adı Soyadı

İmzası

1

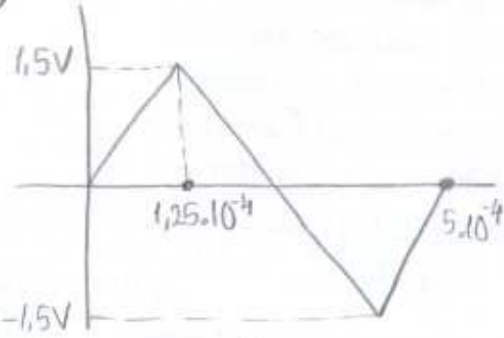

$$k = \frac{\Delta V}{\Delta t} = \frac{1,5V}{1,25 \cdot 10^{-4}} = 12000$$

$$\bullet V_I = V_R + k t_s \Rightarrow k t_s = V_I - V_R = 5,05 - 5 = 0,05$$

$$k t_s = 0,05 \Rightarrow t_s = \frac{0,05}{12000} \approx 4,17 \cdot 10^{-6} \text{ sn}$$

$$t_s \leq 4,17 \mu\text{sn}$$

$$\bullet V_I = V_R + \sqrt{k^2 t_s^2 + 2k \frac{V_{\text{omax}} - V_{\text{omin}}}{K_{\text{vo}} \cdot \omega_0}} \Rightarrow 0,15 = \sqrt{(0,05)^2 + 2 \cdot 12000 \cdot \frac{12 - (-10)}{K_{\text{vo}} \cdot 2\pi \cdot f_0}}$$

$$0,0225 = 2,5 \cdot 10^{-3} + \frac{24000 \cdot 22}{K_{\text{vo}} \cdot f_0 \cdot 2\pi} \Rightarrow 0,02 = \frac{24000 \cdot 22}{K_{\text{vo}} \cdot f_0 \cdot 2\pi} \Rightarrow K_{\text{vo}} \cdot f_0 \geq 4,2 \text{ MHz} \Rightarrow K_{\text{vo}} \cdot f_0 \geq 4,2 \text{ MHz}$$

$$\bullet V_I = V_R + k t_s + k \cdot \frac{V_{\text{omax}} - V_{\text{omin}}}{\gamma E} \Rightarrow 0,15 = 0,05 + 12000 \cdot \frac{12 - (-10)}{\gamma E} \Rightarrow 0,1 = \frac{12000 \cdot 22}{\gamma E}$$

$$\Rightarrow \gamma E = 2,64 \text{ V}/\mu\text{sn} \Rightarrow \gamma E \geq 2,64 \text{ V}/\mu\text{sn}$$

$$\text{c) } I_2 = \frac{V_{\text{ref}}}{R_1} \Rightarrow R_1 = \frac{V_{\text{ref}}}{I_2} = \frac{1,5V}{500\text{mA}} = 3 \Omega \rightarrow R_1 = 3 \Omega$$

$$R_{L\text{max}} = \frac{V_{\text{CC}} - V_{\text{DSmin}} - V_{\text{ref}}}{I_2}, \quad V_{\text{DSmin}} = V_{\text{GS}} - V_{\text{T}}, \quad I_{\text{D}} = \frac{k}{2} (V_{\text{GS}} - V_{\text{T}})^2 (1 + \lambda V_{\text{DS}})$$

$$\lambda V_{\text{DS}} \ll 1 \text{ kabulü ile } \rightarrow V_{\text{GS}} - V_{\text{T}} = \sqrt{\frac{2 I_{\text{D}}}{k}} = \sqrt{\frac{2 \cdot 500 \cdot 10^{-3}}{2}} \approx 0,71 \text{ V} \rightarrow V_{\text{DSmin}} = 0,71 \text{ V}$$

$$R_{L\text{max}} = \frac{25V - 0,71V - 1,5V}{500\text{mA}} = 45,58 \Omega \rightarrow R_{L\text{max}} = 45,58 \Omega$$

$$R_0 = \mu K_{\text{vo}} R_1, \quad \mu = g_m \cdot r_{\text{ds}} \Rightarrow g_m = \sqrt{2 I_{\text{D}} k} = \sqrt{2 \cdot 500 \cdot 10^{-3} \cdot 2} \approx 1,41 \text{ A/V}, \quad r_{\text{ds}} = \frac{1}{\lambda I_{\text{D}}} = \frac{1}{0,01 \cdot 500 \cdot 10^{-3}} = 200 \Omega$$

$$\mu = g_m \cdot r_{ds} = 1,41 \cdot 200 = 282 \Rightarrow R_{10} = 282 \cdot K_{V0} \cdot 3 \geq 10^9 \Rightarrow K_{V0} \geq \frac{10^9}{282 \cdot 3} \approx 1,18 \cdot 10^6$$

$$K_{V0} \geq 1,18 \cdot 10^6 \approx 121,4 \text{ HdB}$$

$$3) a) I_D = I_b = \frac{V_I}{R_I} \Rightarrow t_d = t_b = C \cdot \frac{V_H}{I_D} = \frac{C \cdot V_H \cdot R_I}{V_I}$$

$$t_d + t_b = \frac{2C V_H R_I}{V_I} \Rightarrow f = \frac{V_I}{2C V_H R_I}$$

$$V_H = 2 \cdot \frac{R_1}{R_2} \cdot V_{0\text{max}} \Rightarrow f = \frac{V_I}{4R_1 C V_{0\text{max}}} \cdot \frac{R_2}{R_1}$$

$$b) \frac{\partial f}{\partial V_I} = 2 \text{ kHz/V} \Rightarrow \frac{\partial f}{\partial V_I} = \frac{1}{2C V_H R_I} = 2 \text{ kHz/V} \Rightarrow R_I = \frac{1}{2 \cdot 1,47 \cdot 10^{-9} \cdot 2 \cdot 2 \cdot 10^3} \approx 2,66 \text{ k}\Omega$$

$$V_H = 2 \cdot \frac{R_1}{R_2} \cdot (V_2 + V_0) \Rightarrow 2 = 2 \cdot \frac{R_1}{R_2} \cdot (1,7 + 0,6) \Rightarrow \frac{R_2}{R_1} = 5,3 \Rightarrow \begin{matrix} R_1 = 1 \text{ k}\Omega \\ R_2 = 5,3 \text{ k}\Omega \end{matrix}$$

$$R_6 = R_1 // R_2 = 1 \text{ k} // 5,3 \text{ k} \Rightarrow R_6 = 0,84 \text{ k}\Omega$$

$$R_5 = R_I \Rightarrow R_5 = 2,66 \text{ k}\Omega$$

$$R_8 = R_3 // R_3 = \frac{R_3}{2} \Rightarrow R_8 = 5 \text{ k}\Omega$$

R1	1kΩ
R2	5,3kΩ
R3	10kΩ
R5	2,66kΩ
R6	0,84kΩ
R8	5kΩ