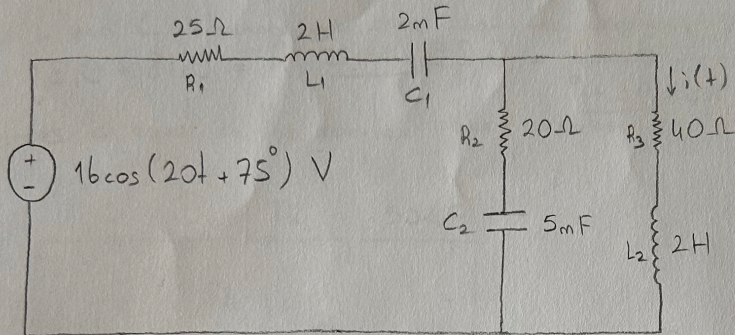



P 10.5-23

Determine the steady-state current $i(t)$ for the circuit in Figure P 10.5-23.



$$Z_{L1} = j\omega L = j \cdot 20 \cdot 2 = 40j \Omega \quad Z_{C1} = \frac{1}{j\omega C} = \frac{10^3}{j \cdot 20 \cdot 2} = -25j \Omega$$
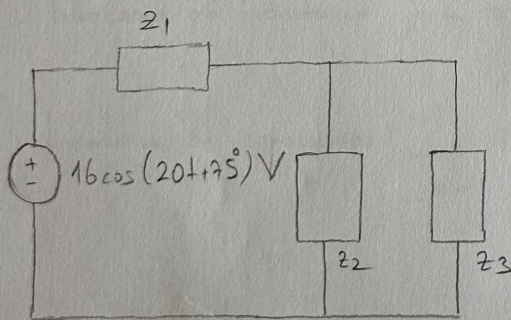
$$Z_{L2} = j\omega L = j \cdot 20 \cdot 2 = 40j \Omega \quad Z_{C2} = \frac{1}{j\omega C} = \frac{10^3}{j \cdot 20 \cdot 5} = -10j \Omega$$



$$Z_1 = 25 + 15j \Omega$$

$$Z_2 = 20 - 10j \Omega$$


$$Z_3 = 40 + 40j \Omega$$

$$Y_2 = \frac{1}{20 - 10j} S, \quad Y_3 = \frac{1}{40 + 40j} S \implies Y_2 + Y_3 = 0,525 + 7,5 \times 10^{-3} j S$$

$$\frac{1}{Y_2 + Y_3} = Z_{23} = 18,67 - 2,67j$$


P 10.5-23

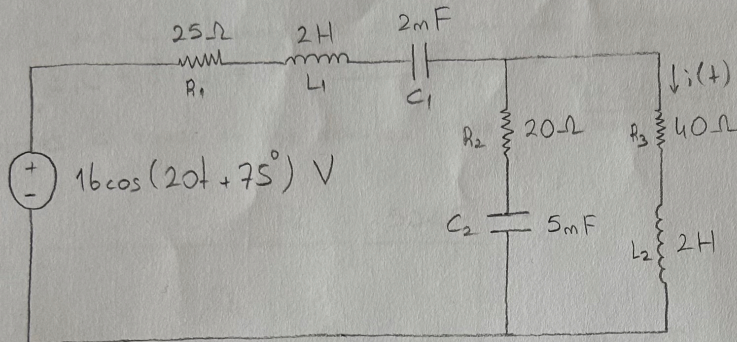Determine the steady-state current $i(t)$ for the circuit in Figure P 10.5-23.



$$Z_{L1} = j\omega L = j \cdot 20 \cdot 2 = 40j \Omega \quad Z_{C1} = \frac{1}{j\omega C} = \frac{10^3}{j \cdot 20 \cdot 2} = -25j \Omega$$
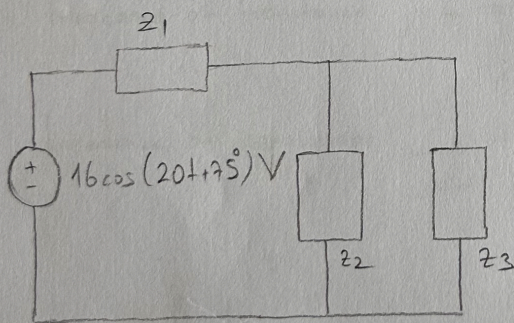
$$Z_{L2} = j\omega L = j \cdot 20 \cdot 2 = 40j \Omega \quad Z_{C2} = \frac{1}{j\omega C} = \frac{10^3}{j \cdot 20 \cdot 5} = -10j \Omega$$



$$Z_1 = 25 + 15j \Omega$$

$$Z_2 = 20 - 10j \Omega$$

$$Z_3 = 40 + 40j \Omega$$

$$Y_2 = \frac{1}{20 - 10j} \text{ S}, \quad Y_3 = \frac{1}{40 + 40j} \text{ S} \Rightarrow Y_2 + Y_3 = 0,525 + 7,5 \times 10^{-3} j \text{ S}$$

$$\frac{1}{Y_2 + Y_3} = Z_{23} = 18,67 - 2,67j$$

$$Z_{eq} = 25 + 15j + 18,67 - 2,67j = 43,67 + 12,33j \Omega$$

$$Z_{eq} = 45,38 \angle 15,77^\circ$$

$$I = \frac{V}{Z_{eq}} = \frac{16 \angle 45^\circ}{45,38 \angle 15,77^\circ} = 0,35 \angle 29,23^\circ \text{ A} = 0,18 + 0,3j$$


From current divider:

$$(0,18 + 0,3j) \cdot \frac{20 - 10j}{(20 - 10j) + (40 + 40j)} = 0,116 + 0,012j = i(t)$$

$$i(t) \cong 0,12 \angle 6,10^\circ \text{ A} = 0,12 \cos(20t + 6,10^\circ) \text{ A}$$

P 11.5-6

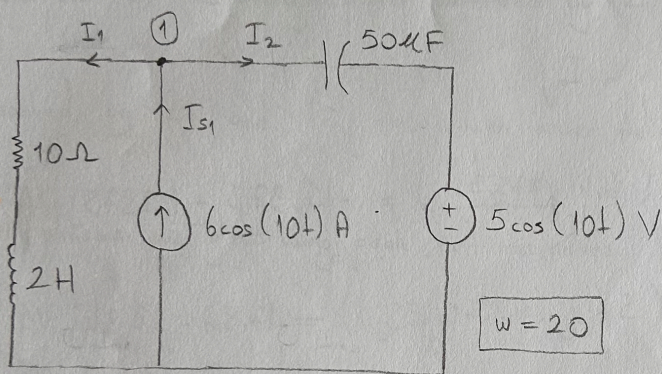For the circuit of Figure P 11.5-6, determine the complex power of the R, L and C elements and show that the complex power delivered by the sources is equal to the complex power absorbed by the R, L and C elements.



$$I_{s1} = 6 \cos(10t) \text{ A}$$

$$V_{s2} = 5 \cos(10t) \text{ V}$$

$$\text{Impedance of inductance: } j\omega L \Rightarrow 20j \quad \checkmark$$

$$\text{Impedance of capacitance: } \frac{1}{j\omega C} \Rightarrow -2j \quad \checkmark$$

From node 1:

$$I_{s1} = I_1 + I_2 \Rightarrow 6 \angle 0^\circ = I_1 + I_2 \Rightarrow I_1 = 6 \angle 0^\circ - I_2$$

From KVL:

$$(10 + 20j) I_1 - 5 \angle 0^\circ + (2j) I_2 = 0$$

$$\Rightarrow (10+20j)(6-I_2) - 5 + (2j)I_2 = 0$$

$$\Rightarrow 60 - 10I_2 + 120j - 20jI_2 - 5 + 2jI_2 = 0$$

$$\Rightarrow I_2(-10-20j+2j) = -55-120j \Rightarrow I_2 = 6,39 + 0,495j \text{ A}$$

$$I_1 = -0,39 - 0,5j \text{ A} \Rightarrow I_1 = 0,63 \angle 232^\circ \text{ A}$$

$$I_2 = 6,41 \angle 175,53^\circ \text{ A}$$

The delivered powers: $(\frac{1}{2} \cdot V_o \cdot I_m)$

$$S_{5\angle 0^\circ} = \frac{1}{2} \cdot (5 \angle 0^\circ) (6,41 \angle 175,53^\circ) = -15,975 + 1,2375j \text{ VA}$$

$$S_{6\angle 0^\circ} = \frac{1}{2} (6 \angle 0^\circ) (5 - 2j(6,39 + 0,495j)) = 17,97 - 38,34j \text{ VA}$$

$$\text{Total delivered power} \rightarrow (-16 + 1,1j) + (18 - 38,3j) = 2 - 37,1j \text{ VA}$$

The absorbed powers:

$$S_{20j\Omega} = \underbrace{(-0,39 - 0,5j)}_{I_1}^2 \cdot \left(\frac{20j}{2}\right) = 4j \text{ VA}$$

$$S_{10\Omega} = \underbrace{(-0,39 - 0,5j)}_{I_1}^2 \cdot \left(\frac{10}{2}\right) = 2 \text{ VA}$$

$$S_{-2j\Omega} = \underbrace{(6,39 + 0,495j)}_{I_2}^2 \cdot \left(\frac{-2j}{2}\right) = -41,1j \text{ VA}$$

$$\text{Total absorbed power} \rightarrow 2 - 37,1j \text{ VA}$$

12,5

total absorbed power = total delivered power


P 11.5 - 14

The source voltage in the circuit shown in Figure P 11.5 - 14 is $V_s = 24 \angle 30^\circ$ V.

Consequently, $I_1 = 3,13 \angle 25,4^\circ$ A, $I_2 = 1,99 \angle 52,9^\circ$ A and $V_4 = 8,88 \angle -10,6^\circ$ V.

Determine (a) the average power absorbed by Z_4 , (b) the average power absorbed by Z_1 , and (c) the complex power delivered by the voltage source.

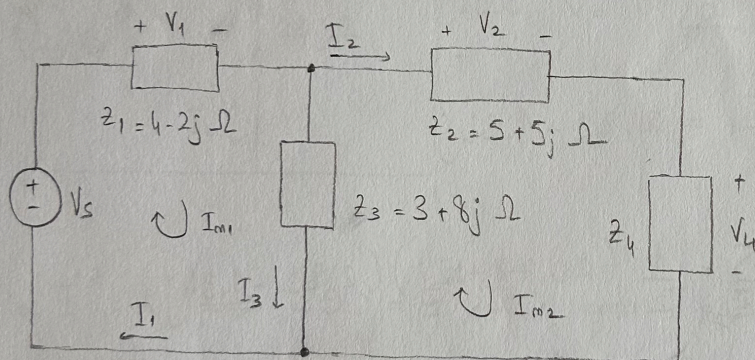(All phasors are given using peak, not rms values.)



$$I_{m1} = I_1 = 2,82 + 1,34j$$

$$I_{m2} = I_2 = 1,2 + 1,58j$$

$$V_s = 20,78 + 12j$$

Mesh 1

$$(4 - 2j) I_{m1} + (3 + 8j) (I_{m1} - I_{m2}) - \underbrace{(20,78 + 12j)}_{V_s} = 0$$

Mesh 2

$$(5+5j) I_{m2} + Z_4 \cdot I_{m2} - (3+8j)(I_{m1} - I_{m2}) = 0$$

$$\Rightarrow (5+5j)(1,2+1,58j) + Z_4(1,2+1,58j) = (3+8j)(1,62-0,24j)$$

$$Z_4(1,2+1,58j) = 8,68 - 1,66j \Rightarrow Z_4 = 2 - 4j \Omega$$

$$S_{Z_4} = \frac{1}{2} \cdot (1,2+1,58j)^2 \cdot (2-4j) = 6,52 + 5,9j \text{ VA} \rightarrow \text{the average power absorbed by } Z_4$$

$$S_{Z_1} = \frac{1}{2} \cdot (2,82+1,34j)^2 \cdot (4-2j) = 0,23 + 1,06j \text{ VA} \rightarrow \text{the average power absorbed by } Z_1$$

$$V_s = 20,78 + 12j, \quad I_1 = 2,82 + 1,34j$$

$$S = \frac{1}{2} \cdot V \cdot \dot{I}^* \Rightarrow S = \frac{1}{2} (20,78 + 12j)(2,82 - 1,34j)$$

$$S = 37,33 + 3j \text{ VA} \rightarrow \text{the complex power delivered by the voltage source}$$


P 11.6-4

Consider the model of one communication circuit, shown in Figure P 11.6-4.

If an average power of 500 W is dissipated in the $20\text{-}\Omega$ resistor,

find (a) V_{rms} , (b) I_{rms} , (c) the power factor seen by the source, and

(d) $|V_s|$.

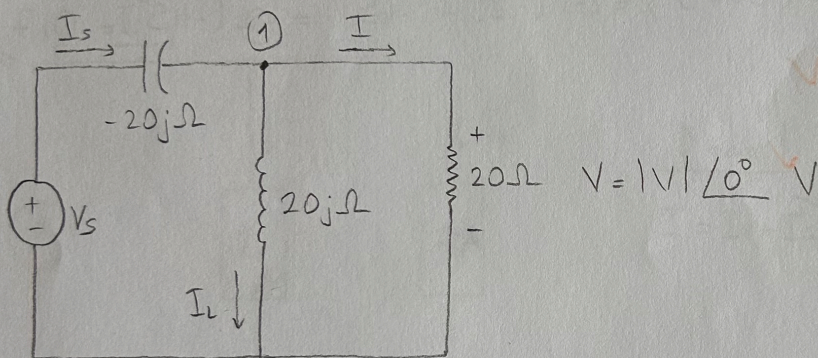

$$P = I^2 \cdot R \Rightarrow 500 = I^2 \cdot 20 \Rightarrow I = 5\text{ A}$$

$$V = I \cdot R \Rightarrow 5 \angle 0^\circ \times 20 \angle 0^\circ = 100 \angle 0^\circ \text{ V} \checkmark$$

$$I_L = \frac{100 \angle 0^\circ}{20j} = 5 \angle -90^\circ \text{ A}$$

$$\text{From node 1} \rightarrow I_s = I + I_L = 5\sqrt{2} \angle -45^\circ \text{ A} \checkmark$$

We can find V_s with: $V_s = V + I_s \cdot (-20j)$

$$V_s = 100 \angle 0^\circ + (5\sqrt{2} \angle -45^\circ \cdot (-20j)) \text{ V}$$

$$V_s = 100 \angle -90^\circ \text{ V}$$

$$\Rightarrow V_{\text{rms}} = 100 \text{ V} \quad \checkmark$$

$$\Rightarrow I_{\text{rms}} = 7,07 \text{ V} \quad \checkmark$$

$$\Rightarrow \text{power factor} = \cos(\theta_v - \theta_i) = \cos(-90^\circ - (-45^\circ)) = \cos(-45^\circ) = 0,7$$

\hookrightarrow lagging \checkmark

$$\Rightarrow |V_s| = 100 \text{ V} \quad \checkmark$$


+12,5

P 11.6 - 5

Two impedances are supplied by $V = 100 \angle 160^\circ$ V_{rms}, as shown in Figure P 11.6-5,

where $I = 2 \angle 130^\circ$ A_{rms}. The first load draws $P_1 = 23,2$ W, and

$Q_1 = 50$ VAR. Calculate I_1, I_2 , the power factor of each impedance, and the total power factor of the circuit.

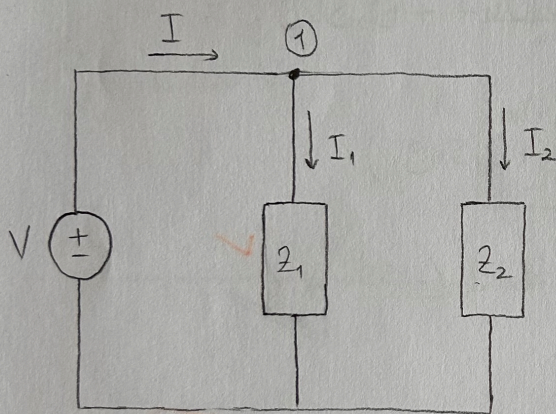

Node 1
 $I = I_1 + I_2$

$S = P + j \cdot Q$
↓
visual power

$\checkmark \implies S_1 = P_1 + j \cdot Q_1$

$P_1 = 23,2 \text{ W} \quad Q_1 = 50 \text{ VAR}$

$S_1 = 23,2 + 50j \implies (23,2)^2 + (50)^2 = (55,12)^2$

$\checkmark S_1 = 55,12 \angle 65,1^\circ \text{ VA} \implies \text{pf}_1 = \cos 65,1^\circ = 0,422 \rightarrow \text{lagging} \checkmark$

$$S_1 = I_1^* \cdot V \Rightarrow I_1^* = \frac{S_1}{V} = \frac{55,12 \angle 65,1^\circ}{100 \angle 160^\circ} = 0,551 \angle -94,9^\circ$$

$$I_1 = 0,551 \angle 94,9^\circ \text{ A} \checkmark$$

I is given as $2 \angle 190^\circ \text{ A}$. From Node 1, $I = I_1 + I_2$.

$I_2 = I - I_1 \rightarrow$ We have to write components of I and I_1 .

$$I = -1,97 - 0,348j \text{ A} \quad , \quad I_1 = -0,047 + 0,549j \text{ A}$$

$$I_2 = (-1,97 - 0,348j) - (-0,047 + 0,549j)$$

$$I_2 = -1,923 - 0,897j \Rightarrow I_2 = 2,12 \angle -155^\circ \text{ A} \checkmark$$

$$S_2 = \overset{*}{I}_2 \cdot V = (2,12 \angle 155^\circ)(100 \angle 160^\circ) = 212 \angle -45^\circ \quad (125)$$

$$\Rightarrow pf_2 = \cos(-45^\circ) = 0,707 \rightarrow \text{leading} \checkmark$$

Total power of the circuit:

$$S = S_1 + S_2 \Rightarrow (23,2 + 50j) + (150 - 150j) = 173,2 - 100j$$

$$S = 200 \angle -30^\circ \text{ VA} \Rightarrow pf = \cos(-30^\circ) = 0,866 \rightarrow \text{leading} \checkmark$$

$$Z_2 = 14,4 \angle 53,1^\circ \Omega \implies Z_2 = 8,64 + 11,51j$$

$$Y_2 = \frac{1}{8,64 + 11,51j} = 0,041 - 0,055j \text{ S}$$

$$0,041 - 0,055j = \frac{1}{R_2} + \frac{1}{j\omega L}$$

$$0,041 - 0,055j = \underbrace{\frac{j\omega L}{R_2 j\omega L}}_{\text{real}} + \underbrace{\frac{R_2}{R_2 j\omega L}}_{\text{complex}}$$

$$\frac{1}{R_2} = 0,041 \implies R_2 \approx 24,03 \Omega$$

$$-0,055j = \frac{j}{-\omega L} \implies 0,055 \cdot 20 \cdot L = 1$$

$$\implies L \approx 0,90 \text{ H}$$


$$i(t) = \frac{V}{Z_1 + Z_2} = \frac{15 + 0j}{22,61 + 5,26j} = 0,62 - 0,14j = 0,6356 \angle 12,72^\circ$$

$$v(t) = (0,62 - 0,14j)(8,64 + 11,51j) = 6,9682 + 5,9266j$$

$$\implies v(t) \approx 9,3 \cdot \cos(20t + 40^\circ) \text{ V}$$

P 10.5-13

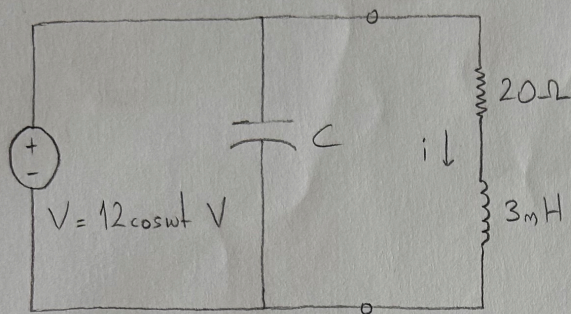Determine the current $i(t)$ for a tone at 796 Hz when $C = 10 \mu\text{F}$.



$$f = 796 \text{ Hz} \implies \omega = 2\pi \cdot 796 = 5001,41 \text{ rad/s}$$

$$Z_L = j\omega L = j \cdot 5000,41 \cdot 3 \cdot 10^{-3} = 15j$$

$$Z = 20 + 15j$$

$$i(t) = \frac{V}{Z} = \frac{12 + 0j}{20 + 15j} = \frac{12 \angle 0^\circ}{25 \angle 36,87^\circ} = 0,48 \angle -36,87^\circ$$

$$i(t) = 0,48 \cdot \cos(5001,41t - 36,87^\circ)$$

$+12j^5$