
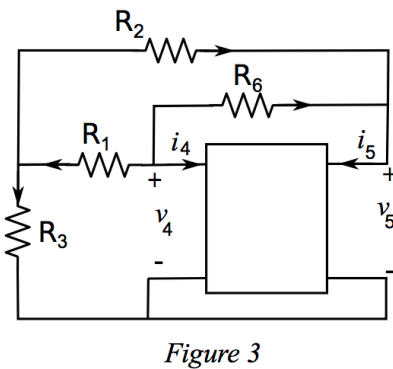


## Homework-1

1. For the circuit given in Figure 1, obtain the equations to analysis the circuit using Chord (Line) current method such that unknown variables are  $i_6, i_7$  and  $i_8$  ( $V_3 = \alpha i_4, V_4 = \beta V_8, V_5 = \beta i_7$ ).

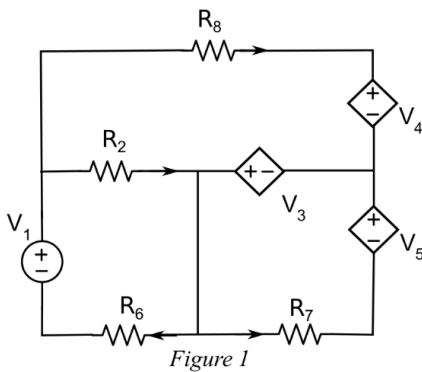2. For the circuit given in Figure 3, obtain the equations to analysis the circuit using Generalized Branch Voltages method such that unknown variables are  $v_1, v_2$  and  $v_3$  ( $i_4 = \beta i_5, i_5 = v_5$ ).



**P 6.4-23**  $\oplus$  The input to the circuit shown in Figure P 6.4-23 is the voltage source voltage  $v_s$ . The output is the node voltage  $v_o$ . The output is related to the input by the equation  $v_o = kv_s$  where  $k = \frac{v_o}{v_s}$  is called the gain of the circuit. Determine the value of the gain  $k$ .

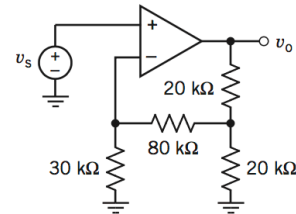


Figure P 6.4-23

**P 6.5-11**  $\oplus$  The circuit shown in Figure P 6.5-11 is called a Howland current source. It has one input,  $v_{in}$ , and one output,  $i_{out}$ . Show that when the resistances are chosen so that  $R_2R_3 = R_1R_4$ , the output is related to the input by the equation

$$i_{out} = \frac{v_{in}}{R_1}$$

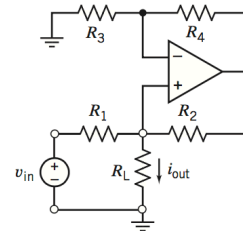


Figure P 6.5-11

**P 6.4-19** The circuit shown in Figure P 6.4-19 has one input,  $v_s$ , and one output,  $v_o$ . The circuit contains one unspecified resistance,  $R$ .

- Express the gain of the circuit  $v_o/v_s$  in terms of the resistance  $R$ .
- Determine the range of values of the gain that can be obtained by specifying a value for the resistance  $R$ .
- Design the circuit so that  $v_o = -3v_s$ .

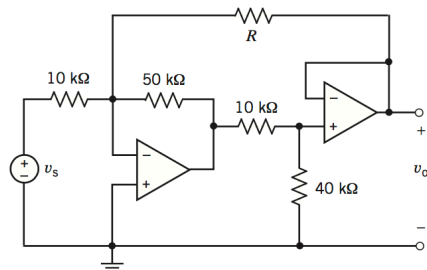


Figure P 6.4-19