

Basic of Electrical Circuits

EHB 211E

Prof. Dr. Müştak E. Yalçın

Istanbul Technical University
Faculty of Electrical and Electronic Engineering


mustak.yalcin@itu.edu.tr

Lecture 4.

- 1 Independent KCL and KVL Equations
 - Independent KCL Equations
 - Independent KVL Equations

Independent KCL Equations

Cut sets for the nodes are

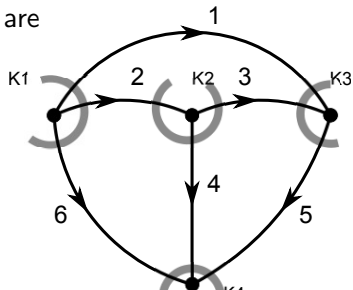

$$G_{K1} = \{1, 2, 6\}, G_{K2} = \{2, 3, 4\}, G_{K3} = \{1, 3, 5\}, G_{K4} = \{4, 5, 6\}.$$

If we apply KCL to the cut sets, we obtain

$$i_1 + i_2 + i_6 = 0$$

$$i_4 + i_3 - i_2 = 0$$

$$i_5 - i_1 - i_3 = 0$$

$$-i_5 - i_4 - i_6 = 0$$

which are node equations. **current reference direction [+ if branch leaves the node]**

Independent KCL Equations

In matrix form

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & 1 & 0 & 0 \\ -1 & 0 & -1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = 0$$

For an n_n -node n_b -branch connected graph G , node equations are given by

$$A_a i = 0$$

where $i = [i_1 \ i_2 \ \dots \ i_{n_b}]^T$ is called the branch current vector. A_a is called incidence matrix of the graph G and $A_a \in \{-1, 0, 1\}^{n_n \times n_b}$.

Independent KCL Equations

$$\begin{aligned} -i_1 - i_2 - i_6 &= 0 \\ -i_4 - i_3 + i_2 &= 0 \\ -i_5 + i_1 + i_3 &= 0 \\ + - - - - & \\ -i_5 - i_4 - i_6 &= 0 \end{aligned}$$

The four equations are linearly dependent. Any three of the four equations are linearly independent.

Independence property of KCL equations


For any connected graph with n_n nodes, the KCL equations for any $n_n - 1$ of these nodes form a set of $n_n - 1$ linearly independent equations.

Independent KCL Equations

If in A_a , we delete the row corresponding to the datum node (reference node), we obtain the *reduced incidence matrix* A which is of dimension $n_n - 1 \times n_e$. The KCL equations is given by

$$A i = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & 1 & 0 & 0 \\ -1 & 0 & -1 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = 0$$

Independent KCL Equations

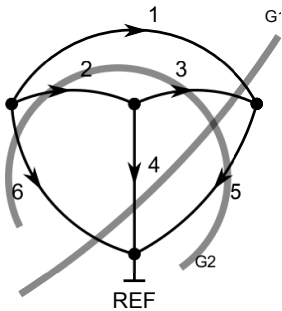

$$i_1 + i_3 + i_4 + i_6 = 0$$

The first one is obtained by first and second node equations


$$i_1 + i_2 + i_6 = 0$$

$$i_4 + i_3 - i_2 = 0$$

$$+ \quad - \quad - \quad - \quad -$$

$$i_1 + i_3 + i_4 + i_6 = 0$$

Independent KVL Equations

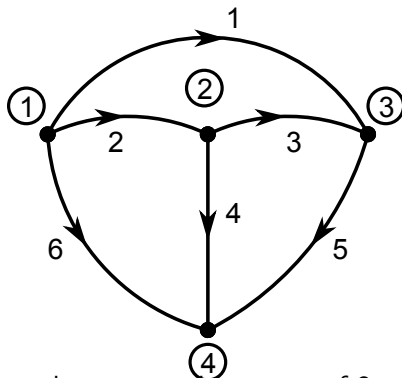

All 6 edges voltages can be expressed in terms of 3 node-to-datum voltages as follows:

$$V_1 = V_{n1} - V_{n3}$$

$$V_2 = V_{n1} - V_{n2}$$

$$V_3 = V_{n2} - V_{n3}$$

$$V_4 = V_{n2}$$

$$V_5 = V_{n3}$$

$$V_6 = V_{n1}$$

Independent KVL Equations

$$V_1 = V_{n1} - V_{n3}$$

$$V_2 = V_{n1} - V_{n2}$$

$$V_3 = V_{n2} - V_{n3}$$

$$V_4 = V_{n2}$$

$$V_5 = V_{n3}$$

$$V_6 = V_{n1}$$

$$V = \begin{bmatrix} 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix} V_n$$


Independent KVL Equations

For an n_n -node n_b -branch connected graph G , independent KVL equations are given by

$$V = MV_n$$

where $V = [V_1 \ V_2 \ \dots \ V_{n_e}]^T$ and $V_n = [V_{n1} \ V_{n2} \ \dots \ V_{nn_n-1}]^T$ are called the branch voltage vector and node-to-datum voltage vector, respectively. M is a $n_e \times n_n - 1$ matrix.

Independent KVL Equations

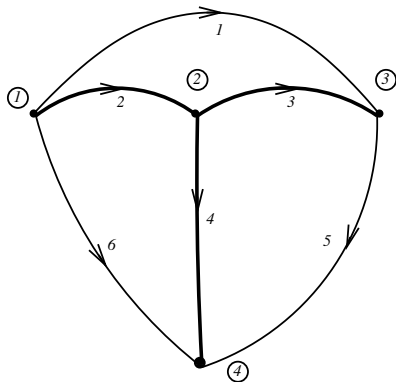

KVL equation for the closed node sequence 1-2-3-1

$$V_2 + V_3 - V_1 = 0$$

This equation can be obtained from the first three equations.

Independent KVL and KCL Equations

Comparing the independent KVL and KCL equations, we conclude that

$$M = A^T$$

- current reference directions is chosen,
- a datum node is chosen and the reduced incidence matrix A is defined,
- KCL is written as $Ai = 0$
- then we use associated reference directions to find that KVL ($V = A^T V_n$).

Tellegen's Theorem

Consider an arbitrary circuit. Let the graph have n_b branches. Let us use associated reference directions. Let $i = [i_1 \ i_2 \ \dots \ i_{n_b}]^T$ be any set of branch currents satisfying KCL for G and let $V = [V_1 \ V_2 \ \dots \ V_{n_b}]^T$ be any set of branch voltages satisfying KVL for G , then

$$\sum_{k=1}^{n_b} v_k i_k = 0.$$

Proof Since i satisfies KCL, we have

$$A i = 0$$

and since V satisfies KVL, we have

$$V = A^T V_n.$$

Using these two equations, we obtain

$$V^T i = V_n^T A i = V_n^T (A i) = 0.$$