

BASICS OF ELECTRICAL CIRCUITS

Homework -IV

1. (a) The 3-terminal circuit element in Figure 1 ($v_b = \beta v_2$) is given with the terminal graph shown in Figure 2. For this terminal graph, obtain terminal equations in the following form

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \cdot & \cdot \\ \cdot & \cdot \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

- (b) Using the result in (a), obtain terminal equations for the terminal graph given in Figure 3 in the following form

$$\begin{bmatrix} \hat{v}_1 \\ i_3 \end{bmatrix} = \begin{bmatrix} \cdot & \cdot \\ \cdot & \cdot \end{bmatrix} \begin{bmatrix} i_1 \\ \hat{v}_3 \end{bmatrix}$$

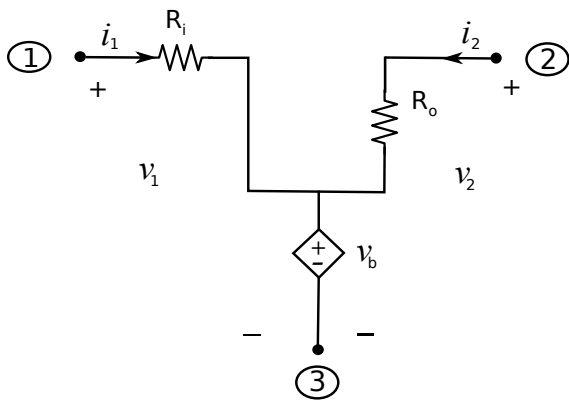


Figure 1

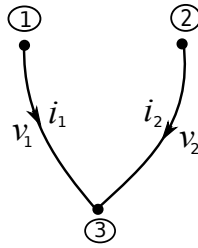


Figure 2

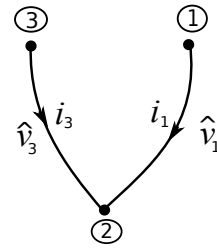


Figure 3