

## Homework-II

Due: 29.04.2019

**P 12.5-1** Consider a three-wire Y-to- $\Delta$  circuit. The voltages of the Y-connected source are  $V_a = (208/\sqrt{3})\angle -30^\circ$  V rms,  $V_b = (208/\sqrt{3})\angle -150^\circ$  V rms, and  $V_c = (208/\sqrt{3})\angle 90^\circ$  V rms. The  $\Delta$ -connected load is balanced. The impedance of each phase is  $Z = 12\angle 30^\circ \Omega$ . Determine the line currents and calculate the power dissipated in the load.

**P 12.5-3** The balanced circuit shown in Figure P 12.5-3 has  $V_{ab} = 380\angle 30^\circ$  V rms. Determine the phase currents in the load when  $Z = 3 + j4 \Omega$ . Sketch a phasor diagram.

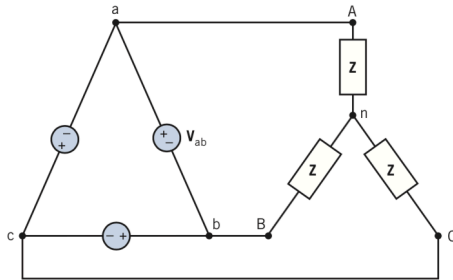


Figure P 12.5-3 A  $\Delta$ -Y circuit.

**P 12.7-2** A three-phase motor delivers 20 hp operating from a 480-V rms line voltage. The motor operates at 85 percent efficiency with a power factor equal to 0.8 lagging. Find the magnitude and angle of the line current for phase A.

*Hint:* 1 hp = 745.7 W

**P 12.7-6** A building is supplied by a public utility at 4.16 kV rms. The building contains three balanced loads connected to the three-phase lines:

- $\Delta$  connected, 500 kVA at 0.85 lagging
- Y connected, 75 kVA at 0.0 leading
- Y connected; each phase with a  $150\text{-}\Omega$  resistor parallel to a  $225\text{-}\Omega$  inductive reactance

The utility feeder is five miles long with an impedance per phase of  $1.69 + j0.78 \Omega/\text{mile}$ . At what voltage must the utility supply its feeder so that the building is operating at 4.16 kV rms?

*Hint:* 4.16 kV is the line-to-line voltage of the balanced Y-connected source.

**P 12.7-8** The balanced three-phase load of a large commercial building requires 480 kW at a lagging power factor of 0.8. The load is supplied by a connecting line with an impedance of  $5 + j25 \text{ m}\Omega$  for each phase. Each phase of the load has a line-to-line voltage of 600 V rms. Determine the line current and the line voltage at the source. Also, determine the power factor at the source. Use the line-to-neutral voltage as the reference with an angle of  $0^\circ$ .

**P 11.9-17** Determine the complex power supplied by the source in the circuit shown in Figure P 11.9-17.

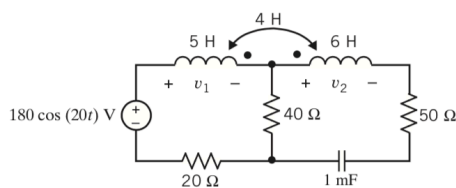


Figure P 11.9-17

**P 11.11-3** Computer analysis of the circuit shown in Figure P 11.11-3 indicates that when

$$v_s(t) = 12 \cos(4t + 30^\circ) \text{ V}$$

the mesh currents are given by

$$i_1(t) = 1.001 \cos(4t - 47.01^\circ) \text{ A}$$

and

$$i_2(t) = 0.4243 \cos(4t - 15.00^\circ) \text{ A}$$

Check the results of this analysis by checking that the equations describing currents and voltages of coupled coils are satisfied.

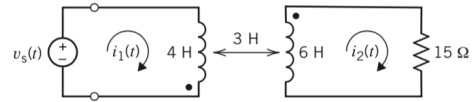


Figure P 11.11-3

**P 14.8-15** A circuit is described by the transfer function

$$\frac{V_o}{V_1} = H(s) = \frac{9s + 18}{3s^3 + 18s^2 + 39s}$$

Find the step response and impulse response of the circuit.

**P 14.8-23** The input to the circuit shown in Figure P 14.8-23 is the voltage of the voltage source  $v_1(t)$ , and the output is the voltage  $v_o(t)$ . Determine the step response of the circuit.

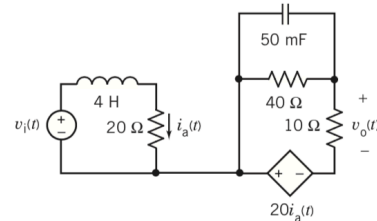


Figure P 14.8-23