

# Circuit and System Analysis

## EHB 232E

Prof. Dr. Müştak E. Yalçın


Istanbul Technical University  
Faculty of Electrical and Electronic Engineering

[mustak.yalcin@itu.edu.tr](mailto:mustak.yalcin@itu.edu.tr)

# Outline I

- 1 Laplace Transform in Circuit Analysis-Cont.
  - Network Parameters
  - Combinations of two-port networks
  - Reciprocal Network
  - Thevenin - Norton Equivalent Circuits

## Network Parameters

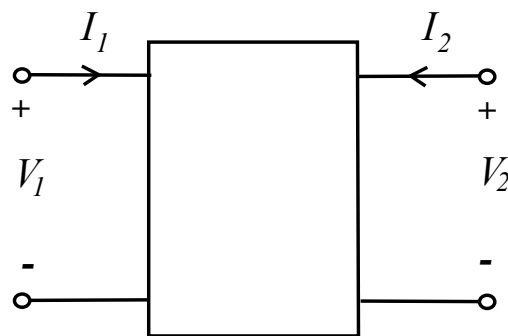

**Impedance matrix (z-parameter)** The two currents  $I_1$  and  $I_2$  are assumed to be known, and the voltages  $V_1$  and  $V_2$  can be found by:

$$\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}$$

where

$$\begin{aligned} z_{11} &= \left. \frac{V_1(s)}{I_1(s)} \right|_{I_2=0} & z_{12} &= \left. \frac{V_1(s)}{I_2(s)} \right|_{I_1=0} \\ z_{21} &= \left. \frac{V_2(s)}{I_1(s)} \right|_{I_2=0} & z_{22} &= \left. \frac{V_2(s)}{I_2(s)} \right|_{I_1=0} \end{aligned}$$

## Network Parameters

**Admittance matrix (y-parameters)** The two voltages  $V_1$  and  $V_2$  are assumed to be known, and the currents  $I_1$  and  $I_2$  can be found by:

$$\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}$$

where

$$y_{11} = \left. \frac{I_1(s)}{V_1(s)} \right|_{V_2=0} \quad y_{12} = \left. \frac{I_1(s)}{V_2(s)} \right|_{V_1=0}$$
$$y_{21} = \left. \frac{I_2(s)}{V_1(s)} \right|_{V_2=0} \quad y_{22} = \left. \frac{I_2(s)}{V_2(s)} \right|_{V_1=0}$$

$y_{21}$  and  $y_{12}$  are transfer admittances

## g-parameters

Inverse hybrid model, we assume  $V_1$  and  $I_2$  are known, and find  $V_2$  and  $I_1$  by :

$$\begin{bmatrix} I_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1(s) \\ I_2(s) \end{bmatrix}$$

where

$$g_{11} = \left. \frac{I_1(s)}{V_1(s)} \right|_{I_2=0} \quad g_{12} = \left. \frac{I_1(s)}{I_2(s)} \right|_{V_1=0}$$
$$g_{21} = \left. \frac{V_2(s)}{V_1(s)} \right|_{I_2=0} \quad g_{22} = \left. \frac{V_2(s)}{I_2(s)} \right|_{V_1=0}$$

## h-parameters

Hybrid model, we assume  $V_2$  and  $I_1$  are known, and find  $V_1$  and  $I_2$  by:

$$\begin{bmatrix} V_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1(s) \\ V_2(s) \end{bmatrix}$$

where

$$\begin{aligned} h_{11} &= \left. \frac{V_1(s)}{I_1(s)} \right|_{V_2=0} & h_{12} &= \left. \frac{V_1(s)}{V_2(s)} \right|_{I_1=0} \\ h_{21} &= \left. \frac{I_2(s)}{I_1(s)} \right|_{V_2=0} & h_{22} &= \left. \frac{I_2(s)}{V_2(s)} \right|_{I_1=0} \end{aligned}$$

## ABCD-parameters


Transmission model, we assume  $V_1$  and  $I_1$  are known, and find  $V_2$  and  $I_2$  by:

$$\begin{bmatrix} V_1(s) \\ I_1(s) \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2(s) \\ -I_2(s) \end{bmatrix}$$

where


$$A = \left. \frac{V_1(s)}{V_2(s)} \right|_{I_2=0} \quad B = \left. \frac{V_1(s)}{-I_2(s)} \right|_{V_2=0}$$
$$C = \left. \frac{I_1(s)}{V_2(s)} \right|_{I_2=0} \quad D = \left. \frac{-I_1(s)}{I_2(s)} \right|_{V_2=0}$$

## Example

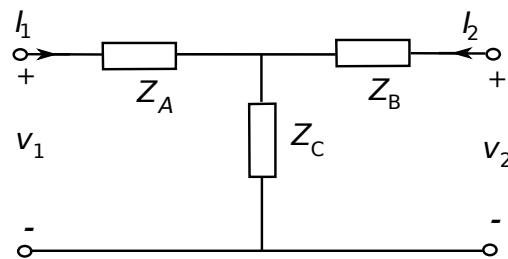

$$\begin{aligned} z_{11} &= \left. \frac{V_1(s)}{I_1(s)} \right|_{I_2=0} = Z_A + Z_C & z_{12} &= \left. \frac{V_1(s)}{I_2(s)} \right|_{I_1=0} = Z_C \\ z_{21} &= \left. \frac{V_2(s)}{I_1(s)} \right|_{I_2=0} = Z_C & z_{22} &= \left. \frac{V_2(s)}{I_2(s)} \right|_{I_1=0} = Z_B + Z_C \end{aligned}$$




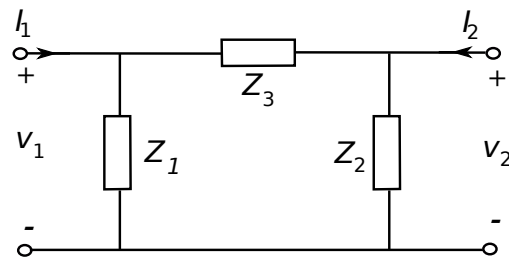

ABCD

$$1 + \frac{Z_3}{Z_2} \quad Z_3 \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{Z_3}{Z_1 Z_2} \quad 1 + \frac{Z_3}{Z_1}$$

## Example


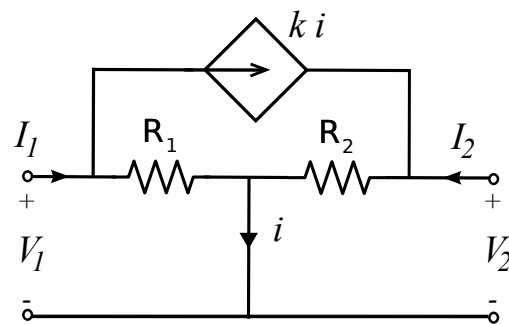


For h-parameters

$$h_{11} = \left. \frac{V_1(s)}{I_1(s)} \right|_{V_2=0} \quad \text{Port 2 short circuit}$$

$$h_{21} = \left. \frac{I_2(s)}{I_1(s)} \right|_{V_2=0} \quad \text{Port 2 short circuit}$$

$$h_{11} = \left. \frac{V_1(s)}{I_1(s)} \right|_{V_2=0} \quad h_{21} = \left. \frac{I_2(s)}{I_1(s)} \right|_{V_2=0}$$

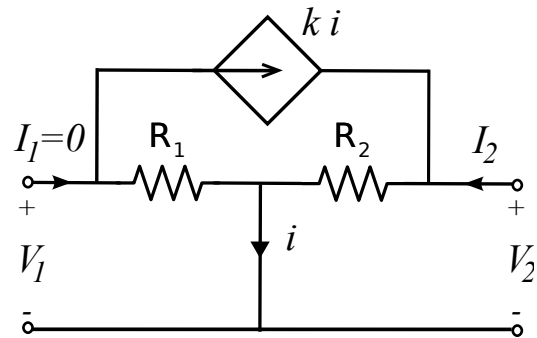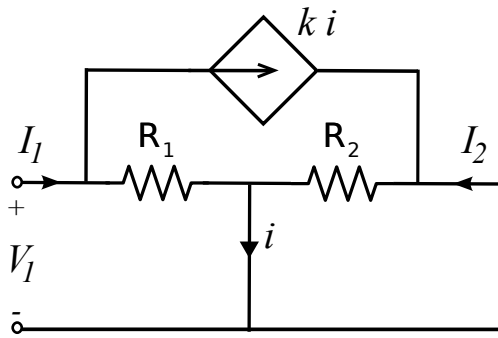

Input current ( $i = I_1$ )

$$I_1 = k \frac{V_1}{R_1} + \frac{V_1}{R_1}$$

then

$$h_{11} = \frac{R_1}{1 + k}$$

for  $h_{21}$

$$I_2 = -ki$$

Substituting  $I_1 = (k + 1)i$  into the above equ

$$h_{21} = -\frac{k}{1 + k}$$

Problems: Richard C. Dorf, James A. Svoboda-Introduction to Electric Circuits, Wiley (2013) pp. 850

The rest of the parameters


$$h_{12} = \left. \frac{V_1(s)}{V_2(s)} \right|_{I_1=0} \quad h_{22} = \left. \frac{I_2(s)}{V_2(s)} \right|_{I_1=0}$$

For  $I_1 = 0$ , the circuit is given

$$h_{12} = -\frac{R_1 k}{(1+k)R_2} \quad h_{22} = \frac{1}{(1+k)R_2}$$

# Combinations of two-port networks

## Series-series connection

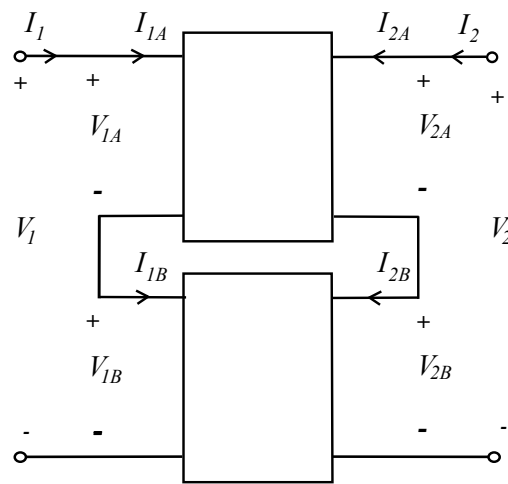

From KCL and KVL

$$I_1 = I_{1A} = I_{1B} \quad I_2 = I_{2A} = I_{2B}$$


and

$$V_1 = V_{1A} + V_{1B} \quad V_2 = V_{2A} + V_{2B}$$

$$\begin{aligned}
\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} &= \begin{bmatrix} V_{1A}(s) \\ V_{2A}(s) \end{bmatrix} + \begin{bmatrix} V_{1B}(s) \\ V_{2B}(s) \end{bmatrix} = \begin{bmatrix} z_{11A} & z_{12A} \\ z_{21A} & z_{22A} \end{bmatrix} \begin{bmatrix} I_{1A}(s) \\ I_{2A}(s) \end{bmatrix} \\
&\quad + \begin{bmatrix} z_{11B} & z_{12B} \\ z_{21B} & z_{22B} \end{bmatrix} \begin{bmatrix} I_{1B}(s) \\ I_{2B}(s) \end{bmatrix} \\
&= \left\{ \begin{bmatrix} z_{11A} & z_{12A} \\ z_{21A} & z_{22A} \end{bmatrix} + \begin{bmatrix} z_{11B} & z_{12B} \\ z_{21B} & z_{22B} \end{bmatrix} \right\} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}
\end{aligned}$$


$$Z = Z_A + Z_B$$

## Parallel-parallel connection

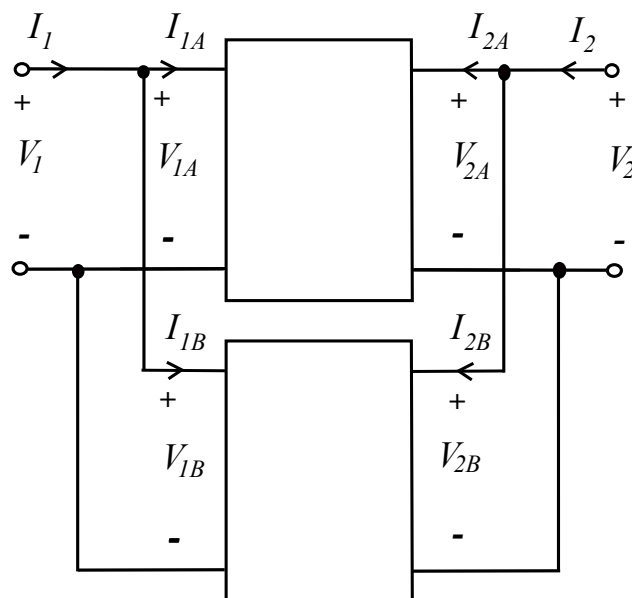

$$Y = Y_A + Y_B$$


## Parallel-series connection

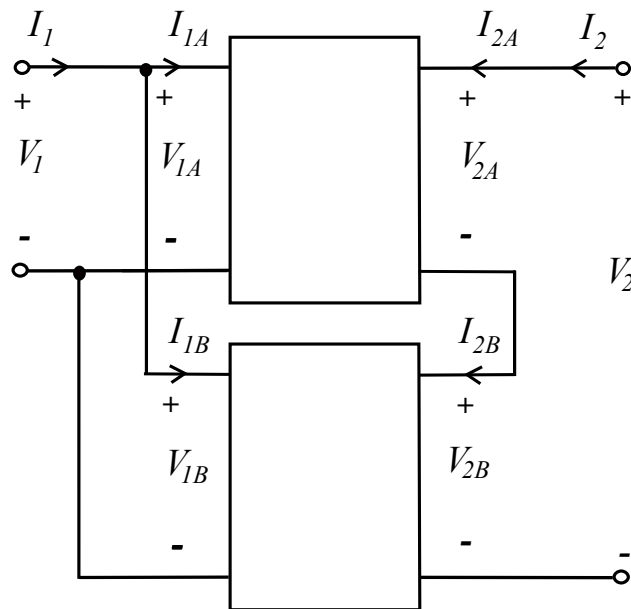

$$g = g_A + g_B$$




## Series-parallel connection

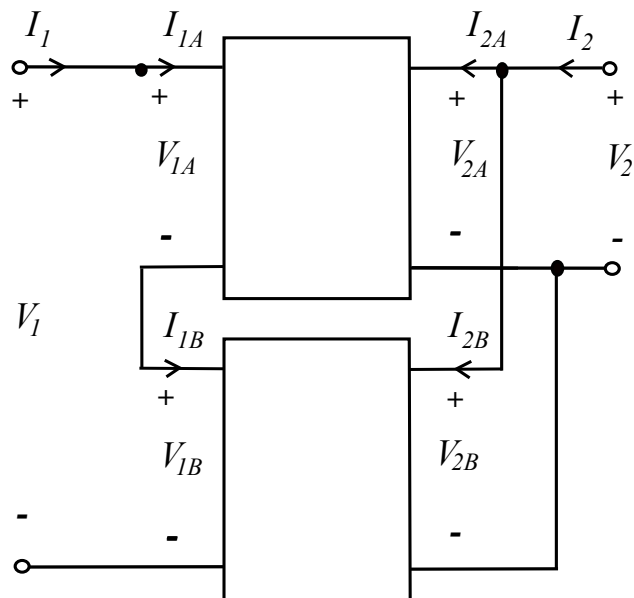

$$h = h_A + h_B$$

## Cascade connection

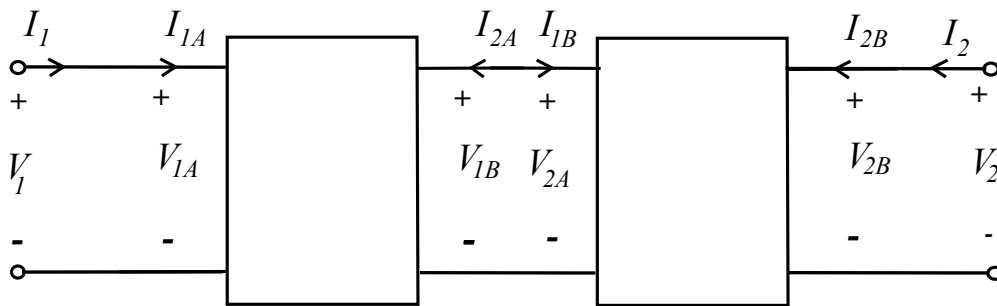

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_A + \begin{bmatrix} A & B \\ C & D \end{bmatrix}_B$$

Good to read : [http://en.wikipedia.org/wiki/Two-port\\_network](http://en.wikipedia.org/wiki/Two-port_network)

## Common emitter

$$v_{be} = f(i_b, v_{ce}) \quad i_c = g(i_b, v_{ce})$$

small signal analysis:

$$v_{be} = \frac{v_{be}}{i_b} i_b + \frac{v_{be}}{v_{ce}} v_{ce} = h_i i_b + h_r v_{ce}$$

$$i_c = \frac{i_c}{i_b} i_b + \frac{i_c}{v_{ce}} v_{ce} = h_f i_b + h_o v_{ce}$$

- $h_i$  input impedance with  $v_{ce} = 0$ . This is AC resistance between base and emitter, the reciprocal of the slope of the current-voltage curve of the input characteristics.
- $h_r$  reverse transfer voltage ratio with  $i_b = 0$ . In general is small and can be ignored.
- $h_f$  forward transfer current ratio or current amplification factor with  $v_{ce} = 0$ .
- $h_o$  output admittance with  $i_b = 0$ . It is slope of the current-voltage curve in the output characteristics. In general is small and can be ignored.

## Reciprocal Network

**Reciprocity theorem** For a reciprocal two-port N, the following relationship holds for each associated two-port representation which exists:

$$z_{12} = z_{21}$$

$$y_{12} = y_{21}$$


$$h_{12} = -h_{21}$$

$$g_{12} = -g_{21}$$

READ : PROOF OF THE RECIPROCITY THEOREM (Chua's book page: 776)

- A gyrator ( $i_1 = Gv_2$  and  $i_2 = -Gv_1$ ) is not reciprocal two-port
- An ideal transformer ( $v_1 = nv_2$  and  $i_2 = ni_1$ ) is a reciprocal two-port.

## Thevenin - Norton Equivalent Circuits

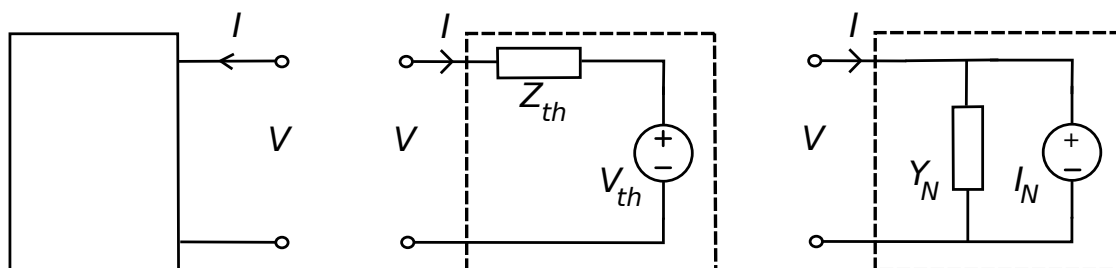

Driving-point characteristic of Thevenin equivalent circuit is defined by

$$V = Z_{th}(s)I + V_{th}(s)$$