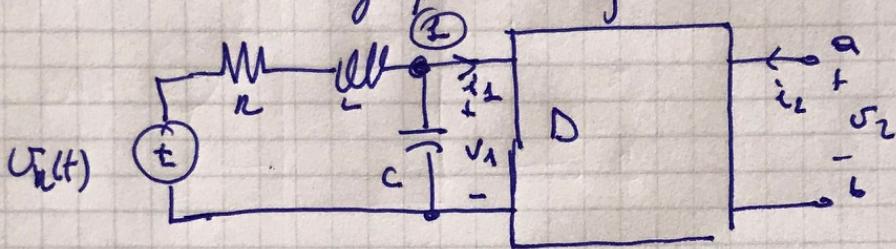


In Figure,  $R=1\Omega$ ,  $L=1H$ ,  $C=1F$  and  $V_{th}(t)=2\cos t$ .

2-port network D is defined by  $i_1 = -2i_2$  and  $v_2 = 2v_1$ .

a) Obtain Thevenin equivalent circuit (in  $\omega$ -domain) with respect to the terminal a and b.

b) What impedance should be connected across the terminal a-b for maximum average power transfer.



a)

$$\textcircled{1} \quad \frac{1}{R+j\omega L} (V_L - V_h) + j\omega C V_1 + I_1 = 0$$


$$I_1 = -2I_2, \quad V_1 = \frac{1}{2}V_2$$

$$\frac{1}{2} \left( j\omega C + \frac{1}{R+j\omega L} \right) V_2 - 2I_2 - \frac{1}{R+j\omega L} V_h = 0$$

$$V_h = 2e^{j0}, \quad \omega = 1$$

$$V_2 = (4-4j) \quad I_2 = 4j$$

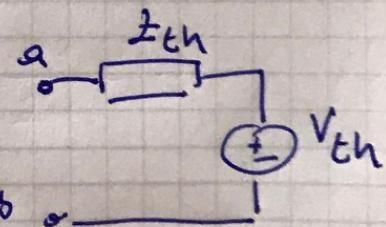$\underbrace{\phantom{0}}_{2\text{th}}$        $\underbrace{\phantom{0}}_{4\text{th}}$



$$\textcircled{2} \quad Z_L = \overline{Z}_{th} = 4+4j = \frac{R_L + j\omega L_L}{4\omega} = \frac{4\Omega}{4H}$$

$$Z_L = \frac{4\Omega}{4H} = 1\Omega$$