 


The common-source (CS) stage is a good alternative since its output swing can be extended from rail to rail. Also body effect does not exist. ☺

A conventional **class-A CS** stage (see the figure on the right) will be sufficient in applications like **switched-capacitor filters**, where the loads are small capacitors (easy-to-drive).

However, when the load is a **low-impedance** one (e.g. an off-chip ohmic load like an **earphone**, or an off-chip large capacitive load), the large-signal driving capability will be limited; particularly because of the fixed bias current I_b (max. value of the current outwards will be I_b). So as to obtain a good driving capability and/or **slew-rate**, I_b must be chosen large enough; yielding a large quiescent current, thus a large quiescent power consumption (the quiescent current I_q is equal to I_b for this case).

☞ The output stage is the most **power consuming** part of an opamp. Therefore, special care must be taken to obtain a power-




65

efficient operation, while keeping other performance characteristics within acceptable limits.


As integration density gets larger, dissipating large power on devices becomes a more critical problem. Trying to keep the power consumption as low as possible is important from this point of view as well.

The **class-B** output stage is a very efficient configuration, but possesses a **dead region** along which both transistors are **OFF**. Unfortunately, this region is usually located around the quiescent (bias) point (That is why the quiescent power is **ZERO**; enhancing the power efficiency ☺). In opamps, we **cannot** tolerate the distortion level caused by such a stage.

 ☞ The output stage must be able to drive the load impedance without degrading the **unloaded** performance and without introducing intolerable distortion.




66

 

By allowing some current flow over the MOSFETs for the quiescent condition, we can avoid the dead region. Then, the quiescent power consumption is **not zero** ☹ but **low enough** ☺; and the output current can be increased for large signal operation (as in class-B). This operation is called the **class-AB** operation. The efficiency is still large enough.


The control of the quiescent current I_Q is important since it must guarantee that both transistors are ON for quiescent condition, besides determining the small-signal behavior of the amplifier.

It is obvious that, as long as the bias voltages V_{Bn} and V_{Bp} are **fixed**, one of the MOSFETs will go **OFF** as v_i travels towards one of the rails. When MOSFETs are employed, it can be shown that when one MOSFET reaches the current level $4I_Q$ the other one goes **OFF** ($\beta_n = \beta_p$ and $V_{thn} = |V_{thp}|$ assumed). (see the curve)

 

67

 Because of the delay caused by **ON-OFF** transitions of the MOSFETs, for the sake of **speed**, both transistors must be kept **ON** for all cases (at least, a small amount of **minimum** current I_{MIN} must flow along, otherwise, a large **crossover distortion** is observed for high-frequency large signals).



The desired curve is given on the right.

Trying to keep both transistors always **ON** requires continuous adjustment (**class-AB control**) of V_{Bn} and V_{Bp} .

example case: When $v_{I,n}$ tends to V_{DD} , $|v_{GS1}|$ will tend to **zero** for a fixed V_{Bp} . However, reducing V_{Bp} accordingly will help keeping M_1 ON).

The **class-AB control** of the current I_Q (and I_{MIN}) can be performed by accordingly controlling one or two voltage sources or current sources, as depicted in the figure below. This control may be performed by using **samples** of the input signal or the output signal.


68

In other words, the **class-AB control** can be performed via

- **feedforward** techniques
- **feedback** techniques

The **feedback** technique is usually better in achieving an accurate **quiescent current control** while enabling operation for lower supply voltages.

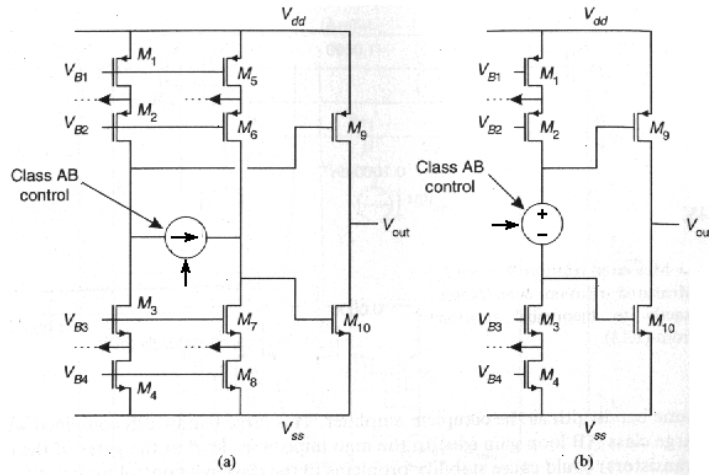The **feedforward** technique, on the other hand, is **faster** (the **feedback** technique slows down the output stage; furthermore some **stability precautions** may be required).



69


A simple **feedforward** structure is shown in the figure on the right (The input voltages V_{IN1} and V_{IN2} are not necessarily voltage sources; they can be formed with aid of input currents). Although resistors are used to obtain a fixed voltage V_{R2} , transistors could also be used (An example for such a circuit will also be supplied shortly).

M_3 - M_5 , M_4 - M_6 and R_1 - R_2 pairs are assumed matched. The quiescent current can be obtained as follows:

$$V_{GS1} + V_{GS2} + V_{R2} = V_{GS5} + V_{GS6} + V_{R1}$$

$$\sqrt{I_1} + \sqrt{I_2} = 2 \cdot \sqrt{I_q}$$
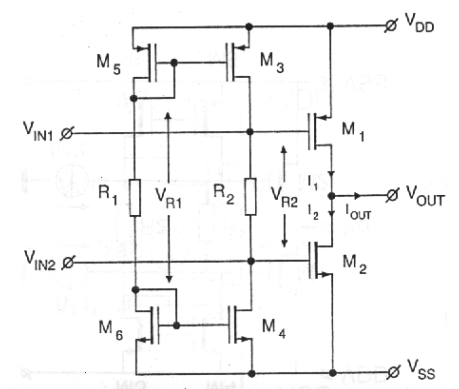
$$I_q = \left(\frac{W}{L}\right)_1 \left(\frac{L}{W}\right)_5 \cdot \frac{V_{R2}}{R_2}$$





Unfortunately, the quiescent current is dependent on V_{DD} via V_{R2} . Furthermore, for large signals, one of the output transistors will be **OFF** ($I_{MIN}=0A$) (see the curve given on the

70

right). This limits the large signal speed.

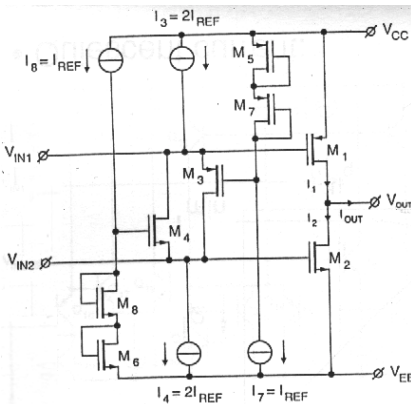 The top and bottom current sources guarantees large input impedances at the input nodes (required to obtain a large voltage gain).



The circuit on the left, wherein current sources and transistors are employed, is more advantageous since the voltage difference $V_{IN1}-V_{IN2}$ can be kept independent of V_{DD} as long as I_{REF} is supply-independent.

The increased number of **series V_{GS} drops** in this **all-MOSFET** version may limit the minimum supply voltage. ☹

The quiescent and minimum currents (I_{MIN} is not zero ☺) for this circuit are obtained below:

71

$$\sqrt{I_1 \frac{L_1}{W_1}} + \sqrt{I_3 \frac{L_3}{W_3}} = \left(\sqrt{\frac{L_5}{W_5}} + \sqrt{\frac{L_7}{W_7}} \right) \sqrt{I_{REF}}$$


$$\sqrt{I_2 \frac{L_2}{W_2}} + \sqrt{I_4 \frac{L_4}{W_4}} = \left(\sqrt{\frac{L_6}{W_6}} + \sqrt{\frac{L_8}{W_8}} \right) \sqrt{I_{REF}}$$

$$I_3 + I_4 = 2I_{REF}$$

$$\left(\sqrt{I_1} - 2\sqrt{I_q} \right)^2 + \left(\sqrt{I_2} - 2\sqrt{I_q} \right)^2 = 2I_q$$


$$I_q = I_{REF}$$
 
$$I_{min} = (2 - \sqrt{2})^2 I_q \approx 0.34 I_q$$




This circuit is widely used as output stage of **LV opamps**.

 The input currents can be the **“summed up”** currents of the **p-** and **n-type** input pairs. Alternatively, if the input signal is in **voltage mode**, a simple **double-output** transconductor (an example given on the right) can be used to obtain these current signals.



72

 

Another output stage example for the *feedforward approach* is shown on the left. Here, the minimum supply voltage is not limited by several V_{GS} drops ☺. This is made possible with help of the V_{AB} voltage difference (such that, $V_X < V_Y$ for LV operation. When large V_{DD} values are used, it is wiser to satisfy $V_X > V_Y$).

The circuit can be operated from a supply voltage slightly greater than the threshold voltage of the transistors.

The quiescent current is well-defined at a value, $I_Q = 2\alpha I_b$. The additional advantage is that, unlike the previous examples, I_{MIN} is also well-controlled via an expression, as simple as that of the quiescent current: $I_{MIN} = \alpha I_b$. ☺

73

So as to avail a proper LV operation, $V_{AB} = V_Y - V_X$ must be chosen such that, the transistors M_{1p} , M_{2p} , M_{3p} , M_{1n} , M_{2n} , M_{3n} all operate in (*but close to the limit of*) saturation. Suitable values for V_X and V_Y can be

$$V_X = V_{DD} - |V_{GS1p,Q}| - |V_{DSsat3p}| - \Delta V, \quad V_Y = V_{GS1n,Q} - V_{DSsat3n} + \Delta V$$

where ΔV is a small margin (e.g. 50mV) to guarantee saturation. Then, the appropriate value for V_{AB} is obtained as

$$V_{AB} = V_{GS1n,Q} + |V_{GS1p,Q}| - 2V_{DSsat} - V_{DD} + 2\Delta V$$

Then, $V_{AB} + V_{DD}$ can be kept less than $2V$ for typical processes (e.g. $V_{TH} = 0.8V$) and large enough transistors.

Since a V_{AB} larger than V_{DD} **cannot** be supplied (unless a **charge pump** is used), $V_{AB} < V_{DD}$ must be satisfied. Then we obtain the limitation for V_{DD} as “ $V_{DD} > 1V$ ”. This is a much better result with respect to previous *feedforward-based* output stages.


The capacitors are used to guarantee a stable feedback since the utilized amplifiers may supply large gain (**important**: this feedback is

74


not using a copy of the current/voltage of the output transistors; it is used *intensively* for proper operation of the feedforward circuitry)

On the right, a conceptual circuit is given which can be utilized to obtain the V_{AB} voltage. The differential amplifier (DA) controlling the matched current I_r , together with the resistor R_r form the voltage $V_{AB} = I_r R_r$ across the nodes Z and W . With aid of the I_r' currents ($I_r' = I_r$) and the resistor R_r' ($R_r' = R_r$), the desired *floating* V_{AB} voltage is achieved across the nodes Y and X . Using currents $I_2 = I_1$ the quiescent voltage values for V_X and V_Y (V_{XQ} and V_{YQ}) are supplied.

 Below is a practical realization of this circuit.



75

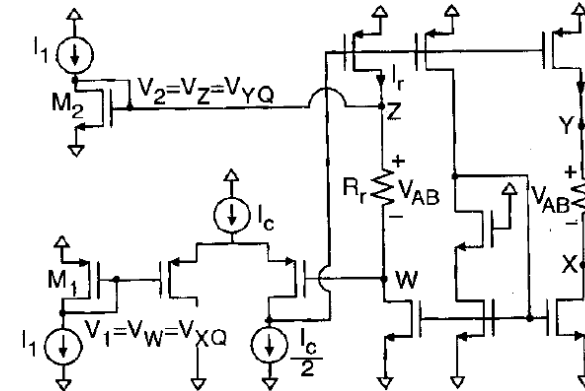


Provided that the bias currents are supply-independent, as long as the V_{AB} voltage is positive, it remains *independent* of the supply voltage V_{DD} .

This is an appreciated feature since it enhances the **PSRR**.

As V_{DD} supply increases above $2V$ (for the above limit example), V_{AB} must be negative (i.e. $V_X > V_Y$ must be satisfied). For such larger V_{DD} values, the above circuit can still be used by just interchanging the X and Y nodes.

Another interesting *feedforward-based* circuit for obtaining a *well-defined* I_Q is shown below. This circuit uses “*dynamic biasing*” with aid of switches and capacitors, so as to achieve the required

76

 

quiescent voltages of the nodes **A** and **B** (respective gate voltages of the **pMOS** and **nMOS** output transistors). ϕ_1 and ϕ_2 are non-overlapping clock phases.

• When ϕ_1 is “1”:

S1, S3 and **S5** are closed (others open); thus the required V_A voltage is obtained across C_{O1} and V_B voltage is obtained over C_{O2} .

• When ϕ_2 is “1”:

S2, S4 and **S6** are closed (others open); thus the

required voltage difference V_{AB} is obtained across C_{O3} and C_{O4} -in series. (**note:** Actually, this equalization process will require several clock periods to settle, since the function is a damped **SC** integration).

77

If we choose $I_{B1}=I_{B2}=I_B$ and achieve a *ratioed* matching among the transistors, such that $\beta_{O1}/\beta_{O3}=\beta_{O2}/\beta_{O4}=\alpha$, then, for the steady-state (quiescent) case for which $I_{D01}=I_{D02}$ (equal to I_Q , by definition), the output transistors are forced to be **ON** with a well-controlled quiescent current: $I_Q=\alpha I_B$.

This design focuses on obtaining a *well-controlled* I_Q but unfortunately does not supply a non-zero I_{MIN} . ☹

C_{O3} and C_{O4} must be chosen large enough compared to C_{GS01} and C_{GS02} , so as to avoid the charge loss during large-signal transients, as far as possible.

Due to a large input drive, V_{G01} and V_{G02} may be pulled beyond V_{SS} and above V_{DD} , respectively. This swing is limited by the forward biasing of the switch bulk junctions (the forward-biased junctions rapidly discharges the capacitances C_{O3} and C_{O4})


Note that the switches **S3** and **S4** -even for steady-state- will have their sources/drains connected to the mid-rail. Assuming that “1”

78

and “0” levels are corresponding to V_{DD} and V_{SS} , and considering a typical threshold of $V_{TH}=0.8V$, we find that, the minimum power supply requirement ($V_{DD}+|V_{SS}|$ for this example) is typically limited by **1.5V**.

If we could have supplied a larger ($>V_{DD}$) gate voltage for the switch transistors, we could have coped with this limitation.

 As a solution, a **clock booster** can be used. An example is given in the figure on the right. Such a circuit can supply “1” levels which are $>V_{DD}$. It is more convenient for such circuits if the driving point impedance is **high** (drawing small currents).



79

In steady-state (**clock LOW**), M_{B1} and M_{B2} operate as an inverter.


When the clock is **HIGH**, capacitor C_{B1} is precharged to V_{DD} through transistor M_{B3} (during this process, the upper terminal behaves like a **source** and the transistor is usually in the triode region). During this process, $V_{GB4}=V_{DD}$ and V_{SB4} travels from V_{SS} to V_{DD} ; M_{B4} is **OFF**, whereas M_{B5} is **ON**, discharging load capacitor C_{BL} .

When the clock goes down, the output of the inverter M_{B1} - M_{B2} goes to V_{DD} . Then, M_{B3} and M_{B5} are **OFF**, whereas M_{B4} is **ON**. If C_{B1} is chosen much larger than C_{BL} , the output voltage is boosted above V_{DD} . Although V_{OUT} tries to reach $2V_{DD}$, during the last part of the transient, the bulk junctions of M_{B3} limit this to approximately $V_{DD}+0.6V$. Nevertheless, this is a sufficiently high voltage to drive the switches **S3** and **S4** in the output stage, when a power supply of $V_{DD}+|V_{SS}|=1.2V$ is used.

So, the **SC** techniques seem to be quite promising for obtaining functional analog circuits operated from low power supplies.

80

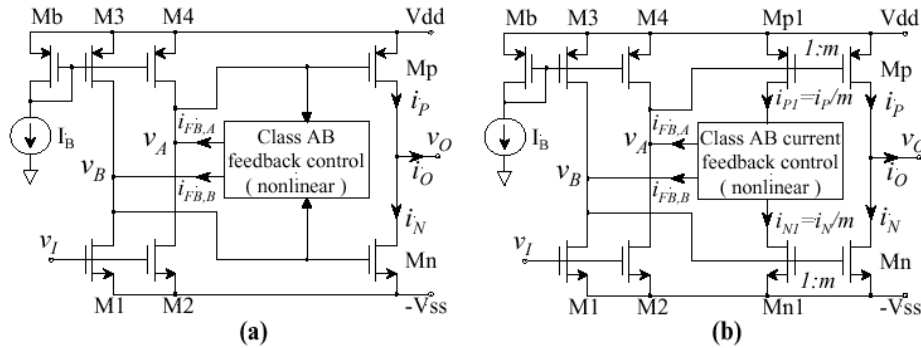The **feedback** approach for **class-AB control** is generally performed by using copies of drain currents or gate voltages of the output transistors, to obtain an information about the output signal.



In the figure above, (a) and (b) shows generalized structures for **feedback-based class-AB control** via using the gate voltages and drain currents of the output transistors, respectively.

81


I_{\min} is kept non-zero with the aid of the feedback loop, as described below.

If M_1 tries to go **OFF** (i.e. reduce its drain current to very low levels), R_{13} will receive a very low current; thus V_{G15} is pulled towards V_{SS} (note that for low currents of M_1 , V_{G14} will be much larger; thus it is practically **OFF**). Then, M_{15} will receive all of the current $2I_{REF}$. Thus, V_{S15} will be controlled by **only** V_{G15} (i.e. by the *small* current of M_1). In this way, The drop in V_{G15} will in turn reduce V_{S15} and that will - via the differential amplifier M_{16} - M_{17} - increase V_{G2} and reduce V_{G1} . These supply an extra I_{\min} current left behind from the net output current. Thus, the minimum current never becomes zero. When M_2 tries to go **OFF** an opposite similar process keeps its drain value equal or above I_{\min} .

The above I_{\min} expression, however, requires additional care to be understood in detail.

Below, another very similar **class-AB** output stage, based on the **feedback** approach, is given. Here, R_{12} and R_{13} receive not only

83

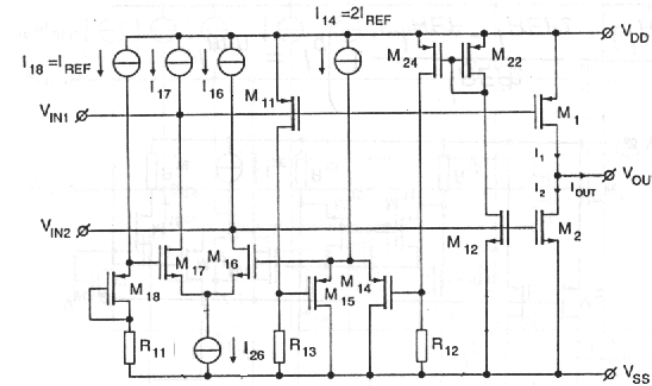

$$I_q = \frac{W_1 L_{11}}{L_1 W_{11}} I_{REF}$$

$$I_{min} = I_q \left(1 - \frac{(\sqrt{2}-1)}{R_{12}} \sqrt{\frac{2L_{14}}{\mu_p C_{ox} W_{14} I_{REF}}} \right)$$

On the left, a good example for **feedback** approach is supplied.


A copy of I_1 flows on R_{13} and a copy of I_2 on R_{12} .

Assuming M_{14} - M_{15} and R_{12} - R_{13} pairs matched, we find $V_{G14}=V_{G15}$ for **quiescent** conditions.

Then, assuming M_{18} matched with M_{14} - M_{15} and R_{11} matched with R_{12} - R_{13} , we obtain $V_{G17}=V_{G16}$, thus $|I_{11}|=I_{REF}$.

In this way, the quiescent and minimum currents are well defined as given on the left.

82

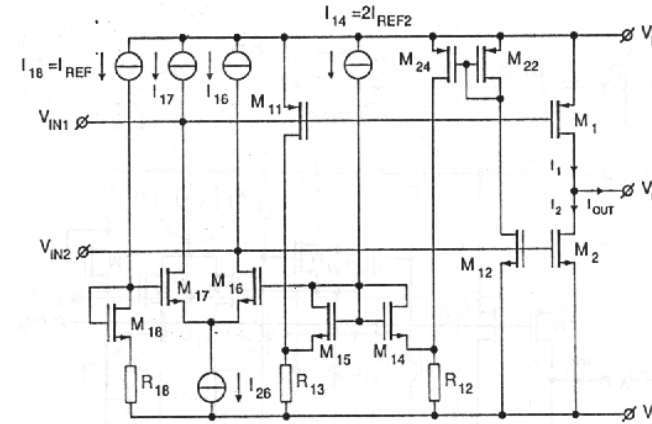

copies of the drain currents of M_2 and M_1 but also those of M_{14} and M_{15} , respectively.

Two different current references are used in this circuit; namely, I_{REF} and I_{REF2} .

The feedback will try to achieve $V_{G16}=V_{G17}$. Assuming R_{12} - R_{13} - R_{18} and M_{14} - M_{15} - M_{18} matched, we find that, for quiescent conditions, (when $I_{OUT}=0A \rightarrow I_1=I_2=I_q$) the equality $I_{R13}=I_{R12}$, thus $V_{S15}=V_{S14}$ will be satisfied. This yields $I_{D15}=I_{D14}=I_{REF2}$ (since $V_{G15}=V_{G14}$ as a result of connection). Assuming M_1 - M_{11} and M_2 - M_{12} matched, we obtain

$$V_{GS18} + I_{REF} R_{18} = V_{GS15} + (I_{REF2} + I_q) R_{13}$$

84

Then we obtain I_q as

$$I_q = I_{REF} - I_{REF2} + (V_{GS18} - V_{GS15})/R_{13}$$

I_{REF} is usually chosen slightly larger than I_{REF2} to supply a small I_q . Therefore, typically $V_{GS18} - V_{GS15}$ is very small. Thus, $I_q = I_{REF} - I_{REF2}$ is obtained. Obtaining I_q as a difference of two currents makes design more flexible.

Usually, β_{11}/β_1 and β_{12}/β_2 are chosen less than 1 to avoid large currents flowing along the control circuitry in large signal conditions. Therefore, more generalized expressions for I_q and I_{MIN} are given below.


$$I_q = \frac{W_1 L_{11}}{L_1 W_{11}} (I_{REF} - I_{REF2})$$

$$I_{min} = I_q \left(1 - \frac{I_{REF2}}{I_{REF} - I_{REF2}} - \frac{\sqrt{2}-1}{(I_{REF} - I_{REF2}) R_{12}} \left(\sqrt{\frac{2I_{REF} L_{14}}{\mu_n C_{ox} W_{14}}} \right) \right)$$

85

Avoiding the drain currents of M_1 and M_2 from being zero for large signal conditions is achieved similarly as the previous circuit. Depending on which output transistor is starting to go **OFF**, the voltage V_{G16} is modulated to supply an opposite move to regulate the drain current of that output transistor at a minimum value.

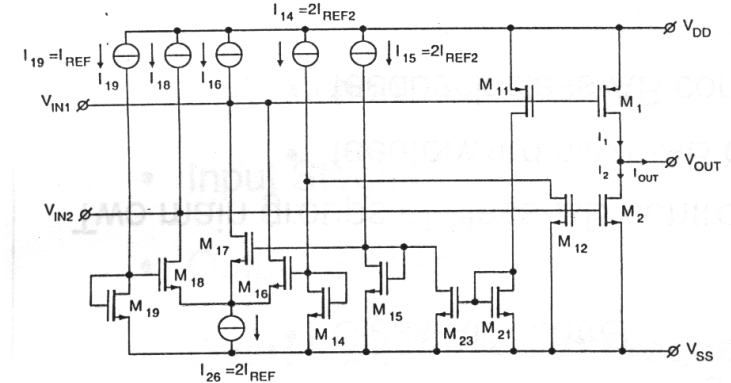The resistors may be a problem, for example in area consumption point of view. Therefore, an **all-MOS** structure like the one on the right would be appreciated. The operation is slightly different but the main principle is same as the two circuits explained above.



86

The quiescent and minimum currents for this output stage are

$$I_q = \frac{W_1 L_{11}}{L_1 W_{11}} (2I_{REF2} - I_{REF})$$

$$I_{min} = I_q \left(1 - \frac{I_{REF}}{2I_{REF2} - I_{REF}} \left(2(\sqrt{2}-1) \sqrt{\frac{W_{19} L_{18}}{L_{19} W_{18}}} + (3-2\sqrt{2}) \frac{W_{19} L_{18}}{L_{19} W_{18}} \right) \right)$$

These examples are enough for the “**class-AB output stages**”

References used for the “**class-AB output stages**” section

- Sakurai S. and Ismail, M., "Low-voltage CMOS operational amplifiers: theory, design, and implementation", Kluwer Academic Publishers, Boston, 1995.
- Yan, S. and Sanchez-Sinencio, E., "Low voltage analog circuit design techniques: A Tutorial," IEICE Trans. Analog Integrated Circuits and Systems, vol.E00 -A, no.2, pp.1-17, 2000.

87

- Sanchez-Sinencio, E. and Andreou, A.G. (Editors), "Low-voltage/low-power integrated circuits and systems: low-voltage mixed-signal circuits," IEEE Press, New York, 1999.
- de Langen, K.J. and Huijsing, J.H. "Compact low-voltage and high-speed CMOS, BiCMOS, and bipolar operational amplifiers", Kluwer Academic Publishers, Boston, 1999.
- Monticelli, D. M., "A quad CMOS single-supply opamp with rail-to-rail output swing," IEEE J. Solid-State Circuits, vol. SC-21, pp. 1026-1034, 1986.
- Hogervost, R., Tero, J.P., Eschauzier, R.G.H. and Huijsing, J.H., "A compact power-efficient 3-V CMOS rail-to-rail input/output operational amplifier for VLSI cell libraries," IEEE J. Solid-State Circuits, vol. SC-29, no.12, pp.1505-1513, 1994.
- de Langen, K.-J. and Huijsing, J.H., "Compact low-voltage power-efficient CMOS operational amplifier cells for VLSI," IEEE J. Solid-State Circuits vol. SC-33, no.10, pp.1482-1496, 1998.
- EPFL, "Advanced Engineering Course on Low-Power/Low-Voltage Analog IC Design", Lausanne, Switzerland, 1996.
- Giustolisi, G., Palmisano, G., Palumbo, G. and Segreto, T., "1.2-V CMOS op-amp with a dynamically biased output stage," IEEE J. Solid-State Circuits, vol. SC-35, no. 4, pp. 632-636, 2000.
- Torralba, A., Carvajal, R.G., Martinez-Heredia, J. and Ramirez-Angulo, J., "Class-AB output stage for low-voltage CMOS op-amps with accurate quiescent current control," Electronics Letters, vol.36, no.21, pp.1753-1754, 2000.

88