

Multi-stage amplifier compensation techniques for very low-voltage operational amplifiers

- Operational amplifiers must supply a large enough gain for achieving high precision in linear (*negative feedback*) applications.
- At the same time, the speed must be high enough; in other words, the a large bandwidth is desired (**i.e.** a large enough gain bandwidth product : **GB**).
- The stability of the opamp (*when connected in local feedback configuration*) must also be guaranteed for the worst type of feedback (*this is usually the **unity-gain** configuration*)

Single- or two-stage amplifiers (usually bringing **not** more than **2** effective poles) can be kept stable by applying simple techniques; the most complex one being the “**Miller compensation technique**”. Therefore, using one or two gain stages is usually preferred for keeping the design simple. (**Note:** the “effective” poles are those appearing dominantly in the open-loop transfer function. The remaining “far-away” poles/zeros which are due to negligible effects are usually not considered, - !!! they can modify the phase margin by a few degrees though !!!)

89

There exist **3** dominant approaches for multi-stage amplifier compensation:

- Nested Miller Compensation (**NMC**)
- Multi-path Nested Miller Compensation (**MNMC**)
- Nested G_m -C Compensation (**NGCC**)

Before starting to explain these approaches, it will be helpful revisiting the *conventional Miller compensation technique*.

Miller compensation

A 2-stage amplifier can be compensated by connecting a capacitor across the output and input of nodes of the second -inverting- amplifier.

Without compensation, a generalized view of the amplifier is given in **(a)** in the figure below (the gains are *naturally* negative, since the best amplifier stage supplying a large gain with a large input impedance level is the common source stage – *with a negative gain*). In **(b)** and **(c)**, two possible transistor-level realizations are supplied (+ *parasitics*).


91

Unfortunately, simple gain stages (**e.g.** *common source stage*) cannot supply sufficient voltage gain (*When using MOSFETs as active devices, this becomes even worse ☹*). Nevertheless, by using **cascoding** and/or **gain boosting** (*regulated cascode*), it is possible to obtain a large gain from a single stage ☺, *but this costs a lot of voltage headroom* ☹.

It is possible to use the **vertical** connections (**e.g.** *cascoding*) for V_{DD} values down to, for example, **2V** ; however, as V_{DD} tends to lower values, cascoding and other **vertical** gain boosting techniques can **no longer** be applied. Then, **horizontal** connections (**cascading**) must be used.

When simple gain stages are *cascaded* in an opamp, more than two stages (*typically, **three** or **four***) must be used so as to obtain a large enough open-loop gain. However, in this case, the number of effective poles in the open-loop transfer function will be increased (*typically, to **3** or **4***) making the compensation process very complicated ☹. Therefore, several compensation techniques have been proposed to simplify the compensation of multi-stage low-voltage operational amplifiers.

90

 

Such an amplifier will supply a **DC** (*low-frequency*) gain of

$$H(0)=g_{m1}r_{o1}g_{m2}r_{o2}$$

Assuming the input voltage source ideal, typically, two poles will be coming; one due to C_p and the other due to C_L (☺ *This must include both the capacitive load and the parasitic output capacitance*):


$$\omega_{p1}=1/(r_{o1}C_p) \quad , \quad \omega_{p2}=1/(r_{o2}C_L)$$

It is well-known that, so as to obtain a large enough phase margin (**e.g.** **60°**), the **non-dominant** (the much larger) pole must be located after (*must be larger than*) the unity-gain frequency (*if this is satisfied, the **unity-gain frequency** and the **GB** become equal*).

92

Very typically, this condition does not hold *naturally*, therefore, one of the poles is *artificially* made **dominant** by increasing the node capacitance corresponding to that pole, such that the unity-gain frequency comes before the second (*non-dominant*) pole.

- The simplest method to make a pole **dominant** is, to connect a capacitor between the corresponding node and ground (or AC ground). However, usually a **large** capacitor value is required for most of the cases, in turn increasing the consumed chip area ☹ (nevertheless, this method is used for some applications).
- The “Miller multiplication” idea can be used to obtain large capacitance values (**in effect**) while using tolerable capacitance values. This is simply done by connecting the artificial capacitor in between the input and output of a *negative-gain* amplifier. It is obvious that, for a 2-stage amplifier, this can be applied to the second amplifier (see the figure); thus the first pole ω_{p1} will be made dominant (it can be shown that ω_{p2} will be moving even further ☺).

 

93

It is obvious that, so as to be able to use this method, the second stage must be an **inverting-type** amplifier. The sign of the gain of the first stage does not have an effect (a *positive-gain* amplifier is used since the multi-stage compensation requires this. ... will be clear shortly).

Without any compensation, the transfer function of the given 2-stage amplifier will be,

$$H(s) = \frac{V_o(s)}{V_i(s)} \cong \frac{H(0) \omega_{p1} \omega_{p2}}{(s + \omega_{p1})(s + \omega_{p2})} = \frac{+ \frac{g_{m1}g_{m2}}{C_p C_L}}{s^2 + s \left(\frac{g_{o1}}{C_p} + \frac{g_{o2}}{C_L} \right) + \frac{g_{o1}g_{o2}}{C_p C_L}}$$

where $g_{o1} = 1/r_{o1}$ and $g_{o2} = 1/r_{o2}$.

On the other hand, for the 2-stage amplifier using a Miller compensation capacitor C_{m1} , an additional capacitive contribution of value $(|A_{v_{o2}}| + 1)C_{m1}$ will come in parallel to C_p , where, $|A_{v_{o2}}| = g_{m2}r_{o2}$ is the absolute value of the *low-freq.* voltage gain of the second stage. (Typically, this contribution dominates; thus C_p can be omitted in remaining analyses. On the other hand, the contribution of C_{m1} to

94

the output node capacitance is approximately C_{m1} , typically small enough with respect to C_L)

Using a thorough analysis, it can be shown that the transfer function for the compensated 2-stage amplifier is

$$H(s) = \frac{g_{m1}(g_{m2} - sC_{m1})/C_L C_{m1}}{s^2 + s(g_{o1}(C_L + C_{m1})/C_L C_p + g_{m2}/C_L + g_{o2}/C_L) + g_{o1}g_{o2}/C_L C_{m1}}$$

Note that the **DC gain** remains unchanged (the sign of the gain discarded for brevity) The new locations of the poles are

$$\omega_{p1} \cong \left(\frac{g_{o1}}{C_{m1}} \right) \frac{g_{o2}}{g_{m2}} = \left(\frac{g_{o1}}{C_{m1}} \right) \frac{1}{A_{v_{o2}}}, \quad \omega_{p2} \cong (g_{m2} + g_{o2})/C_L$$

It is obvious that ω_{p1} has been pushed to much lower frequencies (made dominant), whereas ω_{p2} is pushed to higher frequencies with respect to their original locations. This is called “pole splitting”.

Unfortunately, a *real* zero ($\omega_z = -g_{m2}C_{m1}$) is formed on the **right half plane** of the s-plane ☹. This may be a problem (precautions needed).

95

- Usually a resistor is used in series with C_{m1} to force the zero to the *left half plane*. It is also possible to coincide this zero with the *non-dominant* pole ω_{p2} so as to improve the phase margin further.

The effect of the zero can be explained with a *physical* point of view:

As frequency increases, the mentioned zero inverts the gain (change the phase of the gain by **-180°**). This is because the compensation capacitor is forming a *feedforward path*, eventually becoming **short-circuit** for high frequencies to form a direct path from the input of the second stage to the output.


- An alternative method to prevent the effect of the zero is to use a buffer between the output node and C_{m1} to supply a **one-way** (feedback-only) path along C_{m1} .
- A third method is based on addition of a *feedforward* amplifier (This will be analysed when we explain the “Nested G_m -C Compensation” method).

→ Now, we can explain the multi-stage amplifier compensation methods.

96

Nested Miller Compensation (NMC)

The main idea in this compensation approach is that, “**at the each new step of compensation, an *already-compensated* two-stage amplifier can be treated as an ordinary single-stage amplifier**”. In this way, starting from the last two stages, the whole system is step-by-step compensated by applying the Miller compensation in a **nested** fashion, as shown in the figure below, where a 4-pole system is compensated with three capacitors.

 


By connecting C_{m3} , A **local** dominant pole (f_{p3}) is created at node **3** for the amplifier formed by g_{m3} and $-g_{m4}$. Thus, down to its own unity-gain frequency,

this 2-stage amplifier will behave like a **single-pole** system. Then, connecting C_{m2} will achieve *pole splitting* for the poles f_{p2} and f_{p3} , such that f_{p2} and f_{p3} will take smaller and larger values, respectively,

97

with respect to their last values. Eventually, with help of connecting C_{m1} the pole at node **1** (f_{p1}) will be the dominant pole.

 The typical evolution of the pole frequency locations (for a **3-stage** amplifier to which **NMC** is applied) while the compensation capacitors are being connected, is depicted by the Bode plot below.



98

As a rule of thumb, at each compensation step (*connection of a new compensation capacitor*) the new non-dominant pole must be **buried** at least 3dB below the 0dB level to achieve a good phase margin and for *this* non-dominant pole as not to be affected badly (not to be driven *complex*) by the next compensation step. This approach, however, in turn degrades the final overall **GB** value (*this is also apparent from the above Bode plot*).

Generalizing the scheme to an N-stage amplifier, it can be shown that, the above approach for obtaining a good phase margin requires the following conditions to be satisfied:

$$\frac{g_{m(i)}}{C_{m(i)}} \cdot \frac{1}{2} \frac{g_{m(i+1)}}{C_{m(i+1)}} \quad , \quad i = 1, \dots, N-1$$

$$g_{m(N)} \gg g_{m(i)} \quad , \quad i = 1, \dots, N-1$$

In this way, the non-dominant poles can be approximated by

$$\omega_{p(i)} = g_{m(i)} / C_{m(i)} \quad i = 2, \dots, N$$

If the above conditions were not satisfied, the calculation of the non-dominant poles would be rather complex.

99

It is no doubt that, the dominant pole will come from the first node. Assuming a four-stage amplifier, it can be approximated as,


$$\omega_{p1} = g_{o1}g_{o2}g_{o3}g_{o4} / (C_{m1}g_{m2}g_{m3}g_{m4})$$

This pole must be at low enough frequencies, such that the Bode plot drop with **-20dB/dec** down to the unity-gain frequency.


The effort to *bury* each non-dominant pole 3dB below the 0dB level is required to make sure that the next step *does not affect/is not affected by* these previous non-dominant poles badly, as far as possible. Using an independent *feedforward* amplifier can solve this problem. ☺

Multi-path Nested Miller Compensation (MNMN)

 The **MNMN** adds an independent parallel input stage to transform the **NMC** structure to the **MNMN** structure, as shown in the figure. At low frequencies, the gain stages formed by g_{m1} , g_{m2} and g_{m3} dominate from the



input to the node **3**, whereas, for high frequencies (when the compensation capacitors C_{m1} and C_{m2} reduce the overall gain of the 3-stage amplifier $g_{m1}g_{m2}g_{m3}$), the feedforward amplifier g_{mf} supplies the dominant signal path from the input to node **3**. Thus, the overall system behaves similar to a typical miller compensated 2-stage amplifier (formed by g_{mf} , g_{m4} and C_{m3}). If design is made properly, then a Bode plot like the one given on the right is achievable. (the plot is for a 3-stage **MNMC** amplifier)

 

101


It is obvious that, in this case, the **GB** degradation is almost fully prevented. It can be shown that, so as to achieve this improvement, we must choose g_{m2} as low as possible. Unfortunately, the feedforward path inserts a zero to the transfer function ☺;

nevertheless, this zero can be coincided with one of the non-dominant poles if g_{m3}/C_{m2} and g_{m4}/C_{m1} are set **equal**. That is, matching g_{m3} with g_{m4} and C_{m2} with C_{m1} will be sufficient (fortunately, this is not a hard work when we are designing an integrated circuit ☺).

Nested G_m -C Compensation (NGCC)

Recall that we had mentioned (but postponed the explanation of) a **third** method for conventional Miller compensation so as to avoid the *right-half-plane* zero. The startpoint of NGCC approach is that method; therefore we'd better examine that first.

 The alternative method to avoid the zero in a Miller compensated 2-stage amplifier is to use an *inverting* feedforward amplifier from the input to the node which forms the dominant pole. The method is visualized in the figure on the right. If g_{mf} is chosen equal to g_{m1} , the




102

transfer function is obtained with a simple form as

$$H(s) = \frac{-g_{m1}g_{m2}}{s^2C_{m1}C_L + sC_{m1}g_{m2} + g_{01}g_{02}} \quad \text{with } g_{mf} = g_{m1}$$

It is obvious that there exists no zero in the transfer function ☺.

 Using this structure as a core, it is much easier and more efficient to apply a **nested** compensation procedure. The concept is supplied in the figure on the right, where a 3-stage **NGCC** amplifier is shown. For this amplifier, setting $g_{mf1} = g_{m1}$ and $g_{mf2} = g_{m2}$ is sufficient to avoid the zero(s). When a general case is considered, the overall transfer function is



103

$$H(s) = - \frac{g_{m1}g_{m2}g_{m3} + sg_{m1}(g_{mf2} - g_{m2})C_{m2} + s^2(g_{mf1} - g_{m1})C_{m1}C_{m2}}{g_{o1}g_{o2}g_{o3} + sg_{m2}g_{m3}C_{m1} + s^2(g_{m3} + g_{mf2} - g_{m2})C_{m1}C_{m2} + s^3C_LC_{m1}C_{m2}}$$

So, it's obvious that setting $g_{mf1} = g_{m1}$ and $g_{mf2} = g_{m2}$ will yield the simplified form below.

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{-g_{m1}g_{m2}g_{m3}}{g_{o1}g_{o2}g_{o3} + sg_{m2}g_{m3}C_{m1} + s^2g_{m3}C_{m1}C_{m2} + s^3C_LC_{m1}C_{m2}}$$

This transfer function can be rewritten as

$$H(s) = \frac{-A_0}{\left(1 + s\frac{A_0}{f_1}\right) \left(1 + \frac{s}{f_2} + \frac{s^2}{f_2f_3}\right)}$$

where,

$$A_0 = \frac{g_{m1}g_{m2}g_{m3}}{g_{o1}g_{o2}g_{o3}}, \quad f_1 = GB = \frac{g_{m1}}{C_{m1}}$$

$$f_2 = \frac{g_{m2}}{C_{m2}}, \quad f_2f_3 = \frac{g_{m2}g_{m3}}{C_{m2}C_L}; \quad f_1 = \frac{g_{m1}}{C_{m1}}$$

104

The dominant pole, on the other hand, is

$$P_1 = \frac{f_1}{A_0} = \frac{\frac{g_{m1}}{C_{m1}}}{\frac{g_{m1}g_{m2}g_{m3}}{g_{m2}g_{m3}C_{m1}}} = \frac{g_{01}g_{02}g_{03}}{g_{m2}g_{m3}C_{m1}} = \left(\frac{g_{01}}{C_{m1}} \right) \frac{1}{A_{V02}A_{V03}}$$

For a 4-stage NGCC amplifier, it can be shown that, the design is very easy, such that, for example guaranteeing $f_1 < f_2 < f_3 < f_4$ together with the condition

$$f_4 > \frac{f_2}{1 - f_2/f_3}$$


is sufficient for efficient application of the method. Note that, whatever the number cascaded stages is, the bandwidth is not reduced due to the applied nested compensation. ☺

Below is the generalized transfer function for an ***N*-stage NGCC** amplifier when $g_{mf(i)} = g_{m(i)}$ ($i=1 \dots N-1$) matchings are all satisfied.


105

$$H(s) = \frac{-\prod_{j=1}^N g_{mj} / g_{oj}}{\left(1 + \frac{-\prod_{j=1}^N g_{mj}}{f_1} \right) \cdot \left(1 + \frac{s}{f_2} + \frac{s^2}{f_2 f_3} + \dots + \frac{s^{n-1}}{\prod_{i=2}^N f_i} \right)}$$

 
Below on the left is the conceptual circuit and on the right is an implementation of a **2-stage NGCC** amplifier. (Notice how the **positive** g_m is obtain by supplying a current inversion via the current mirror M12-M13)



106

 

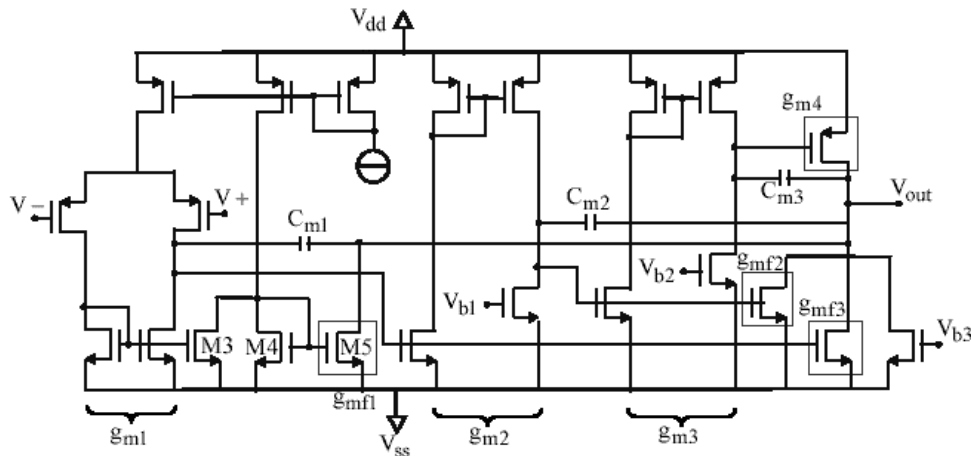For concluding, a **4-stage NGCC operational amplifier** implementation is given below. The function of each block is clearly observed.



107