

Desirable characteristics of LV current mirrors


- low AC input resistance (r_{in})
- small DC voltage drop at the input node (V_{IN})
- high output resistance (r_{out})
- low output compliance voltage (V_{OUTmin})
- good frequency response (*for high frequency applications*)
- a linear (*usually constant and accurate*) current transfer ratio

The **basic current mirror** is a good choice for low voltage operation (low r_{in} , low V_{IN} and low V_{OUTmin}) but r_{out} and accuracy are poor.

$$V_{IN} = V_{GS1} = \sqrt{2 I_{IN} / \beta_1} + V_{TH} \quad (\beta = (W/L)\mu C_{ox})$$

$$r_{in} = 1/g_{m1} = [\beta_1(V_{GS1} - V_{TH})]^{-1} = [\sqrt{2\beta_1 I_{IN}}]^{-1}, \quad r_{out} = (\lambda I_{OUT})^{-1}$$
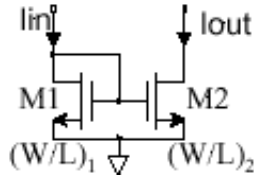
$$V_{OUTmin} = V_{DSsat2} = V_{GS2} - V_{TH} = \sqrt{2 I_{OUT} / \beta_2}$$




21

The **low-voltage cascode current mirror** is a good alternative to the basic current mirror.

☺ The output resistance and tracking accuracy are much better.

☹ V_{OUTmin} is worse and additional biasing (V_B ; sometimes an *automatic biasing*) is required.

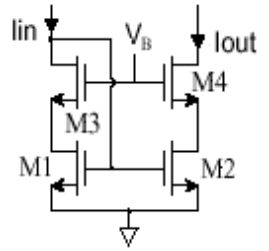Consumed area may sometimes be a drawback (Also, additional care is required in design so as to keep **M3** in saturation).



$$r_{out} = g_{m4} r_{O4} r_{O2} \quad (\text{body effect ignored}), \quad r_{in} = 1/g_{m1} = [\beta_1(V_{GS1} - V_{TH})]^{-1}$$

$$V_{IN} = V_{GS1}, \quad V_{OUTmin} = V_{DSsat4} + V_{DS2} = V_{DSsat4} + V_B - V_{GS4} = V_B - V_{TH}$$

$$V_{OUTmin, best} = V_{DSsat2} + V_{DSsat4} \quad (\text{achieved if } "V_B = V_{GS4} + V_{DSsat2}" \text{ is satisfied})$$

It is also worth mentioning that frequency behavior will be better wrt the basic current mirror since the input node capacitor is less (*the feedback capacitance C_{GD2} is no longer multiplied by a large gain to contribute to C_{in} .*)

22


It is not possible to improve all performance characteristics at the same time, without sacrificing the speed, power and area consumption.

The reported improvements are usually focused on **one or two** of the following items.

- increasing the output resistance
- lowering the output compliance
- lowering the DC input voltage drop
- increasing the tracking accuracy (*actually, this one is usually aimed to be as good as possible !*)

The **regulated cascode** stage (see the figure on the next page) can supply a much larger output resistance ($r_{out} = A_{reg} g_{m4} r_{O4} r_{O2}$) than the classical cascode stages. A current mirror implementation suitable for low voltage operation is also supplied here.

23

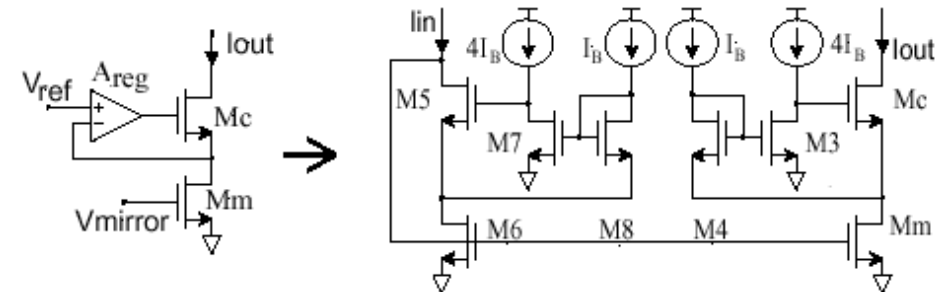

The diode connected MOSFET supplies a DC voltage shift to set V_{DSm} close to (but above) $V_{DSsat, m}$. Assuming $\beta_3 = \beta_{diode} = \beta$,

$$V_{DSm} = V_{GS3} - V_{GS, diode} = (2 \times 4I_B / \beta_3)^{1/2} - (2 \times I_B / \beta_{diode})^{1/2} = (2 \times I_B / \beta)^{1/2} = V_{DSsat3}$$

I_B , β_3 and β_{diode} must be chosen such that $V_{DSsat3} > V_{DSsat, m}$ condition is fulfilled for the largest possible I_{OUT} level.

Without the level shifter, V_{DSm} would be equal to V_{GS3} and this would create a large V_{OUTmin} , limiting the output swing severely.

24

It is possible to keep the DC voltage drop V_{IN} less than a V_{GS} (i.e. less than V_{TH}). The **active-input current mirror** is a good conceptual example.



The opamp and **M1** build an active feedback system to keep the input voltage V_{IN} fixed at V_{ref} .

This voltage can be set close **zero**, provided that $V_{ref} > V_{DSsat1}$ and the opamp common-mode range can go down to the **GND** level.

Also, thanks to the feedback, the input resistance r_{in} is also lower wrt other current mirrors: $r_{in} = 1/(A_{act} g_{m1})$

⊗ Because the feedback is active, extra stability precautions are usually required (along the feedback loop, the opamp is followed by **another** amplifier stage formed by M1, bringing additional gain and another dominant pole).

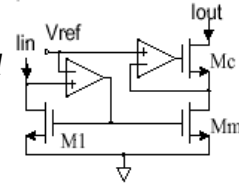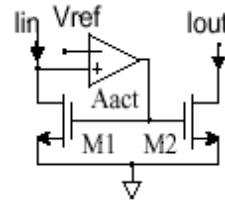So as to improve r_{out} and accuracy, the **regulated cascode** scheme can be utilized here as well. ($V_{ref} > V_{DSsatm}$ must be achieved to keep M_m in sat.)



25



We can use other techniques to set V_{IN} to value less than a V_{GS} . An example is given on the right.

This is a real class-A current mirror. With a sufficiently large I_B , it can handle **negative** input currents as well.

The bias voltage V_{cas} can be adjusted such that, " $V_{IN} > V_{DSsat1}$ " is satisfied for all I_{IN} values.

!!! The tracking accuracy and r_{out} will not be at sufficient levels unless some additional precautions are taken.

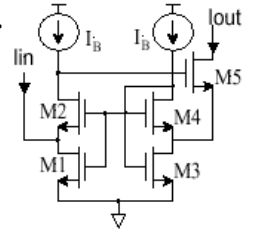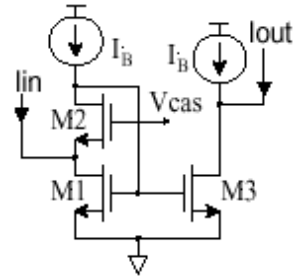M1 and M2 could have been connected in a **"self cascode"** structure as well. Then, the need for a biasing would fade away (However, keeping M1 in saturation would be very difficult). The feedback supplied by M5 on the right improves r_{out} and the tracking accuracy, even when M1 and M3 operate in triode region.



26

The **self cascode current mirror** is worth discussing on. It has a simple structure but keeping M1 and M2 in saturation is not easy.



$$V_{DS1} = V_{GS1} - V_{GS3} \text{ (less than } V_{GS1} - V_{TH} \text{)}$$

Keeping $W_3 \gg W_1$ (and $W_4 \gg W_2$) helps a bit but body effect on M3 spoils this help.

Nevertheless, "It'll find a way". ☺

The same structure can be modified to obtain a **regulated self cascode** current mirror as shown on the right. This structure will work properly even when M1 and M2 are in triode region (thanks to the opamp).

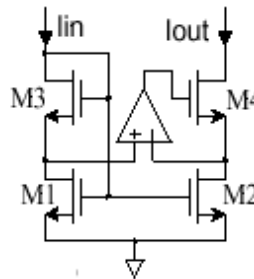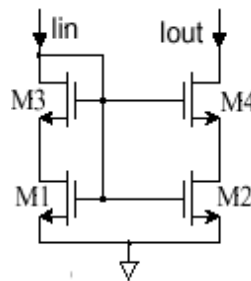
!!! The opamp must be able to operate for low common mode input voltages.



27


Actually, most of the V_{IN} -reducing techniques employ a DC level shifter (usually with a unity AC gain) to virtually form the diode connection (The active-input current mirror structure is different; it supplies a large gain along the diode connection for both AC and DC).

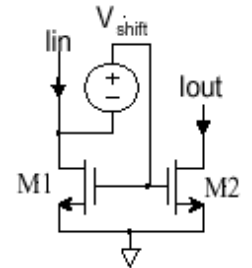Choosing $V_{shift} = V_{TH}$ (or a bit smaller) helps keeping V_{IN} as low as possible while guaranteeing saturation for M1.



An alternative for such a level shifting could be a simple differential pair in **buffer** connection, as shown on the right.

$$V_{shift} = |V_{GS3}| - |V_{GS4}|$$

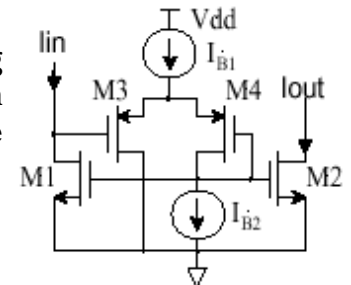

28