



## Who should attend ?

... those graduate students planning to learn low-voltage IC design considerations and techniques, so as to improve their **already acquired** knowledge and/or experience in *bipolar and MOS analog integrated circuit design*.



## Who should NOT attend ?

... those who DON'T have a sufficient background about analog integrated circuit design.

1



The student is expected to be **closely familiar** with each of the topics listed below.

- BJT and MOS device physics
- BJT and MOS I/V characteristics
- Second-order effects and parasitics
- Device models
- Basic microelectronic amplifier stages
- Small-signal and large-signal analysis/behavior of amplifiers
- Current mirrors
- DC and high-frequency response of amplifiers
- Operational amplifiers
- Feedback, stability and compensation
- Sampled-data and continuous-time filters
- BJT/CMOS/BiCMOS processing Technologies
- Layout considerations and techniques

2

## Outline (subject to modification)

- Why *analog* ?
- Why *integrated* analog circuits ?
- Why *low-voltage* analog ICs ?
- Low voltage limitations for MOSFETs and BJTs
- Solutions to obtain rail-to-rail amplification
  - Stability issues
  - Constant- $g_m$  rail-to-rail input stages
  - Rail-to-rail output stages
- Compensation of low-voltage multistage opamps
- Other low-voltage analog building blocks and techniques
  - Low-voltage current mirrors
  - Low-voltage transconductors
  - Low-voltage analog multipliers
- Current-mode techniques for low-voltage operation
- Other low voltage design techniques (e.g. differential approach, log-domain filters, etc.)

3

## REFERENCES


- **Edgar Sanchez-Sinencio & Andreas G. Andreou (Editors)**, "Low-voltage/low-power integrated circuits and systems: low-voltage mixed-signal circuits", IEEE Press, New York, 1999.
- **Klaas-Jan de Langen & Johan H. Huijsing**, "Compact low-voltage and high-speed CMOS, BiCMOS, and bipolar operational amplifiers", Kluwer Academic Publishers, Boston, 1999.
- **Satoshi Sakurai & Mohammed Ismail**, "Low-voltage CMOS operational amplifiers: theory, design, and implementation", Kluwer Academic Publishers, Boston, 1995.
- **Johan Huijsing, Rudy van de Plassche & Willy Sansen (editors)**, "Analog circuit design: volt electronics, mixed-mode systems, low-noise and RF power amplifiers for telecommunication", Kluwer Academic Publishers, Boston, 1999.

4

 
# Why Analog?

Analog circuits are fundamentally necessary for

- ① processing of natural signals
- ② digital communications
- ③ disk-drive electronics
- ④ wireless receivers
- ⑤ optical receivers
- ⑥ sensors
- ⑦ microprocessors and memories



5

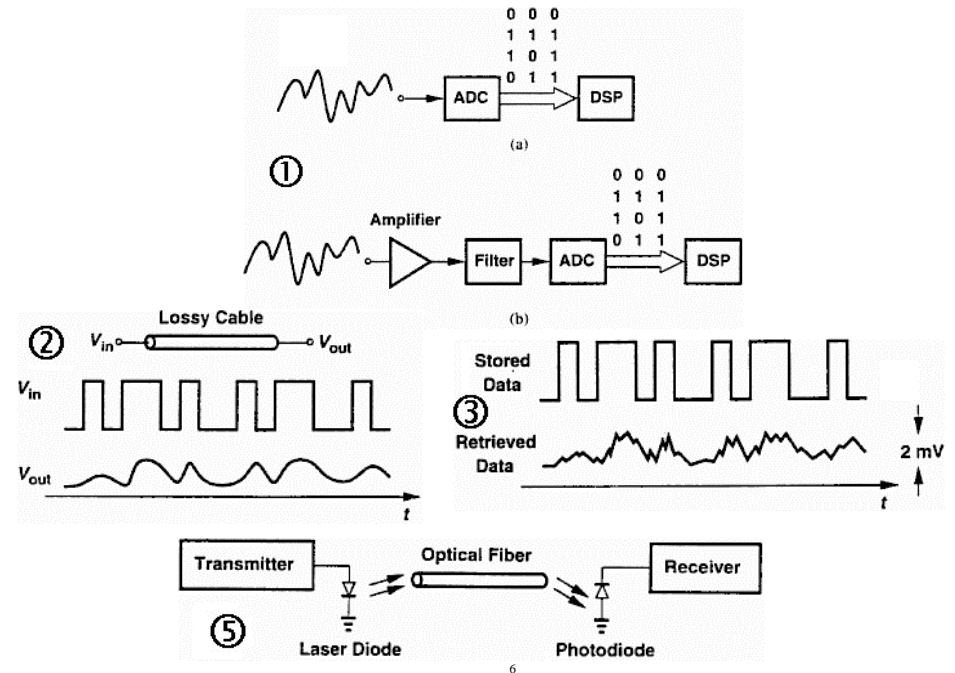

6

Analog design is much more difficult with respect to digital design, because

- multidimensional trade-off considerations (unlike digital design wherein one primary trade-off is dealt with)
- analog signals are much more sensitive to noise, crosstalk and other interferers
- 2<sup>nd</sup> order effects influence performance much more heavily
- design automation is not easy (almost every device hand-crafted)
- modeling and simulation of many effects bring difficulties (evaluation of simulation results requires experience & intuition)
- analog circuits fabricated in a digital (low-cost) process show low performance (proposal of novel structures is required)



7

## Why integrated analog circuits?

Great improvement  
in integration  
density and speed !

1960 2000

Min. feature size: 25μm → 0.18μm



The complexity of **on-chip** analog circuits/systems can **no longer** be achieved by **discrete** analog circuits/systems.

There is a large demand for analog ICs for discrete use (close to logic IC demand)

**A large portion of the total IC market is occupied by expensive analog ICs.**

8

## Why low-voltage analog ICs ?

- power consumption of CMOS digital ICs proportional to  $V_{DD}^2$   
→  $V_{DD}$  **lowered to reduce power consumption**
- Diminishing device geometries  
→ a thinner “thin oxide” has a lower breakdown voltage  
→  $V_{DD}$  **lowered**  
  
→ ☹ *in mixed-mode ICs, performance of analog circuits degrade !*  
(limited voltage headroom to operate properly or even to “operate”)
- Portable devices (e.g. medical devices, telemetry systems) supplied from 1V-1.5V (**low-voltage** + **low-power** techniques)

**Alternative analog blocks and design methods required !**

9

- Bipolar transistors are much more suitable for low-voltage operation ( $V_{BE} \sim 0.6V$ ), **but**
  - ☹ bipolar digital circuits draw much current
  - ☹ bipolar transistors are not good switches (*SC filters !*)
- BiCMOS seems to be a better choice, **but**
  - ☹ BiCMOS processes are costly. Also, typically npn transistors are worth to be utilized
- How about CMOS ? Well, standard CMOS processes are more economical, **but**
  - ☹  $V_{GS}$  starts from above the threshold ( $\sim 0.8V$ ) for low currents and may tend to **several volts** for large currents.



**OPTIMISTIC:** “Let’s lower the thresholds (*down to zero* ☺) ! Then we can supply significant headroom for the MOSFETs.”

**PESSIMISTIC:** “Digital circuits require some non-zero thresholds to be able to decide on TRUEs and FALSEs. Moreover, a **very low**  $V_{Th}$  means a large *subthreshold leakage*, increasing the *standby* power consumption of digital circuits.”

10

• Nevertheless, dual-threshold (or multi-threshold) CMOS processes do exist (high-speed/low-leakage • low-speed/high-leakage), though costly.

→ Special techniques are being developed to get rid of the leakage in digital circuits utilizing low- $V_{Th}$  MOSFETs (Search the literature using the keywords **MTCMOS**, **DTCMOS** and **VTMOS**).



**OPTIMISTIC:** “By the way... Don’t we have the opportunity to operate the MOSFETs in subthreshold ? That can help.”

**PESSIMISTIC:** “Right ! That IS done for **low-voltage low-power (LV-LP)** applications. Actually, “**LV-LP-LS**” would be a much better abbreviation (LS: Low-speed). I’m sorry !”

**LV-LP** techniques can find application in integrated systems which process *slow-changing* analog signals (e.g. heart beat → portable medical devices). For the sake of speed, **LP techniques** (i.e. subthreshold operation) will be kept **out of scope** of this course.

11


## Low voltage limitations for MOSFETs and BJTs

In amplifiers, the transistors normally must achieve a large  $r_o$ , a large  $r_i$  and a large  $g_m$ .


**MOSFETs** → saturation

**BJTs** → forward active region

 MOSFET in saturation  
(strong inversion)



BJT in forward active region

 

**A MOSFET in saturation**

$$V_{GS} > V_{Th} \quad \& \quad V_{DS} > V_{GS} - V_{Th}$$

**A BJT in forward active region**

$$V_{BE} > 0 \quad (\sim 0.7V) \quad \& \quad V_{CE} > V_{CEsat}$$

**BJT :**  $V_{BE} < 1V$ ,  $V_{CEsat} < 0.5V$ , even for large current levels.

**MOSFET:**  $V_{GS}$  may take values up to *several volts* for large currents. Then  $V_{DSsat}$  will also be large.

→ Therefore, **BJTs** are much more suitable for **LV** analog ICs.

12

The output swing of a CMOS active-loaded common-source gain stage can be almost **rail-to-rail**, if the transistors have large enough **W/L** ratios.



$$I_D = \frac{1}{2} (W/L) \mu_n C_{ox} \cdot (V_{GS} - V_{Th})^2$$

→  $W/L = 2I_D / (\mu_n C_{ox} \cdot V_{DSsat}^2)$  i.e. For a **REAL rail-to-rail** output swing, we must use large MOSFETs

Nevertheless, this stage is suitable to be used as a **rail-to-rail** output stage.

A basic MOS current mirror also have some limitations.

  - $V_{OUT}$  should not drop below  $V_{DSsat2}$ 
  - $V_{IN} = V_{GS1} > V_{Th1}$ . This voltage drop limits the output voltage swing of the preceding stage. (much worse topologies exist – e.g. cascodes)




13

**Common-mode input voltage swing** of the differential pair is very good in one direction, but poor in the other direction.


Widening this range is vital for low-voltage operational amplifiers whose input stage is a differential pair.

Also, transconductance stages (transconductors) which are utilized in continuous-time  $G_m$ -C filters require a wide voltage swing at the input.

 ☺ Combining one pMOS-input and one nMOS-input differential pair helps obtaining an almost **rail-to-rail** input common-mode voltage swing. ☹ However, this inserts additional difficulties to the design of the operational amplifier; as will be obvious shortly.



15

 

A cascode current mirror of this type consumes a lot of voltage headroom.


- $V_{IN} = V_{GS3} + V_{GS1} > 2V_{Th1}$
- $V_{OUTmin} = V_{DSsat4} + V_{GS2} > V_{Th1}$

Happily, good alternatives exist

This “**low-voltage cascode current mirror**” → has an input voltage drop equal to that of the basic current mirror ( $V_{IN} = V_{GS1}$ ). ☺



Output voltage limitation ( $V_{OUTmin}$ ) can be adjusted down to  $2 V_{DSsat}$

 The bias voltage  $V_B$  can also be adjusted *automatically* so as to achieve  $V_{OUTmin} = 2 V_{DSsat}$  for **any** current level.



**HOMEWORK #1** : Carry out a literature search about “**automatic biasing of cascode stages or current mirrors**”. Find **at least 5**, summarize the operation and mention significant advantages and drawbacks of **3** of them.

14

  

In the figure above, in (a), it is shown how the pMOS-input and nMOS-input differential pairs must be connected. In (b), combination of two common-mode input ranges are shown. It is obvious that a **rail-to-rail** common-mode swing is achieved.

16

$V_{CM}$  close to **GND** : **pMOS** pair operates, **nMOS** pair **OFF**  
 $V_{CM}$  close to  $V_{DD}$ : **nMOS** pair operates, **pMOS** pair **OFF**  
 $V_{CM}$  close to  $\frac{1}{2}V_{DD}$  : **both** pairs operate

**Therefore**, there are **3** regions along which small-signal transconductance ( $G_m$ ) of such a differential input stage takes **3** different values.



This is a **critical problem** since it means that, the **gain-bandwidth** (thus **speed**, and moreover, **stability**) of the opamp is strongly dependent on the common-mode input level.

**“Constant- $g_m$  rail-to-rail input stages”** come as a solution for this problem. There are several different techniques trying to “*regulate*” the transconductance of such an input stage along the *rail-to-rail* input common-mode range. Those techniques will occupy an important part of this course. **SOON !..**

17



It may seem as if we are NOT taking into consideration bipolar transistors. **This not true.**

The investigations so far focused mainly on CMOS because,

- CMOS is a standardized technology which avails cheaper production; therefore precedence is given to MOSFETs.
- MOSFETs degrade the low-voltage performance much worse with respect to BJTs; therefore MOSFETs deserve more care.


Later on, we will focus on BiCMOS **LV** techniques, but we must first cover some of the techniques devoted to CMOS.

It would be better starting with **“low-voltage current mirrors”** since they are extensively employed in integrated analog circuits.

18
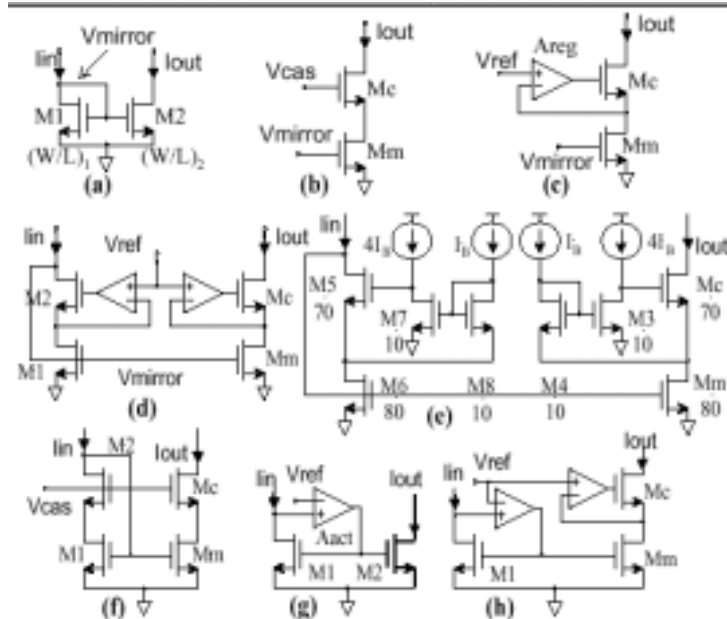
## Widely-used Current Mirrors

- a:** basic CM  
**b:** cascode stage  
**c:** regulated cascode stage  
**d:** regulated cascode CM  
**e:** a low-voltage implementation of (d)  
**f:** low-voltage cascode CM  
**g:** active-input CM  
**h:** regulated cascode active-input CM




19

Some of the above current mirrors are only conceptual. Those suitable for **LV** operation are **(a)**, **(e)** and **(g)**. Also, combining **(e)** and **(g)** could supply a **LV** version for the conceptual CM given in **(h)**.

The circuits on the right are very good examples for low-voltage current mirrors.

 Analysis and design issues of these CMs would be helpful.



20