

# Introduction to Electronics

## Mid-Term Exam #1


Ali Zeki

(105 minutes)

March, 8<sup>th</sup>, 2004

Important parameters of the devices used in **Figure 1** are as follows:

- Resistors :  $R_X=1.5k\Omega$  ,  $R_Y=3.3k\Omega$
- For **all** diodes ( $D_1, D_2, D_3, D_4$ ) :  
 $I_S=5.10^{-15}A$  ,  $P_{d,max}=75mW$
- For the Zener diodes  $D_3$  and  $D_4$  :  
 $V_{Zk}=4.7V$  ,  $I_{Zmin}=0.3mA$  ,  $r_z=7\Omega$
- $V_T=25.9mV$  [ $T=300K$ ]

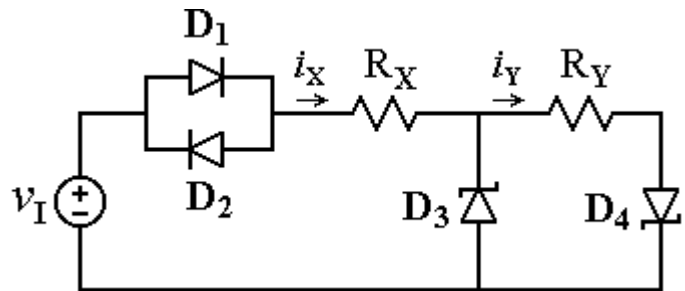

**Figure 1**

**NOTE:** Use  $r_z$  only in small signal analysis.


a) By making use of the **constant voltage drop** model (with  $V_{D0}=0.6V$ ) for the **forward-biased** diodes, determine the range for  $v_I$  along which  $D_3$  operates securely in Zener region (Name the limits of the range as  $V_{I,min}$  and  $V_{I,max}$ ). [20p]

b) By using the **accurate model** “ $i_D=I_S(e^{v_D/V_T}-1)$ ” for the diodes (except for the Zener region), determine the currents  $i_X$  and  $i_Y$  for each of the input voltage values below:

i)  $v_I=3V$  , ii)  $v_I=9V$  , iii)  $v_I=-3V$  , iv)  $v_I=-9V$

[40p]

c) If the input voltage  $v_I$  is as shown in **Figure 2**, use **small signal** approximation and the corresponding **DC** diode currents found in (b) to draw the waveforms of the currents  $i_X$  and  $i_Y$ . [40p]

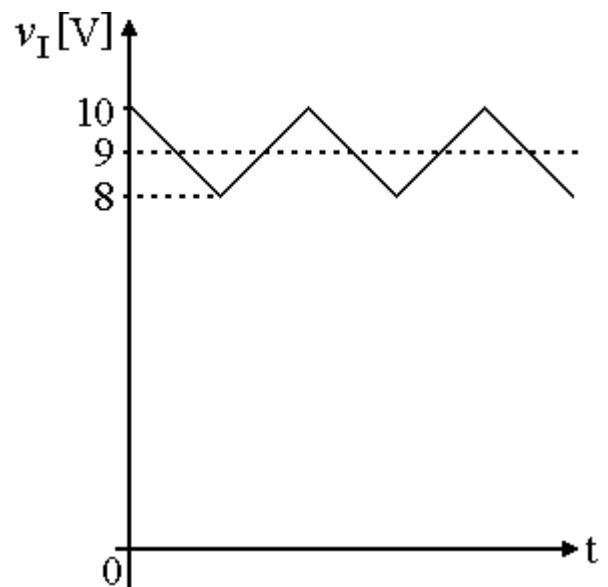

**Figure 2**

**Note for (c):** If you **couldn't** obtain the required **DC** diode currents in (b), then you can still obtain them by using the **constant voltage drop** model, **BUT** you will get less points from (c) ☹.

**GOOD LUCK**