

# Basic of Electrical Circuits

## EHB 211E

Prof. Dr. Müştak E. Yalçın

Istanbul Technical University  
Faculty of Electrical and Electronic Engineering

[mustak.yalcin@itu.edu.tr](mailto:mustak.yalcin@itu.edu.tr)

### Lecture 14

# Contents I

- Solution of State Equations
  - First-Order Linear System
  - Zero-input and Zero-state Responses
  - Homogeneous and Particular Solutions
  - Solution of Second Order State Equations
  - Solution of the Homogeneous Second-Order Equation

# Solution of State Equations

A first-order differential equation, which may be written in a standard form as

$$\dot{x} = ax + be$$

where  $a, b \in R$  and  $e \in R$  is independent source.

Given initial condition  $x(t_0) = x_0$  at  $t_0$  DE has a unique solution.

In order to obtain  $x(t)$ , let's multiply the eqn. by  $e^{-at}$

$$\begin{aligned}e^{-at}\dot{x} &= e^{-at}(ax + be) \\e^{-at}\dot{x} - e^{-at}ax &= e^{-at}be \\ \frac{d}{dt}(e^{-at}x) &= e^{-at}be\end{aligned}$$

Then integrate the eqn.

$$\int_{t_0}^t \frac{d}{dt}(e^{-at}x) = \int_{t_0}^t e^{-at}be(\tau)d\tau$$

# Solution of State Equations

The solution of the 1st order differential equation

$$x(t) = e^{a(t-t_0)}x(t_0) + \int_{t_0}^t e^{a(t-\tau)}be(\tau)d\tau$$


Zero-input response;

$$x_{zi}(t) = e^{a(t-t_0)}x(t_0)$$

Zero-state response;

$$x_{zs}(t) = \int_{t_0}^t e^{a(t-\tau)}be(\tau)d\tau$$

# Example

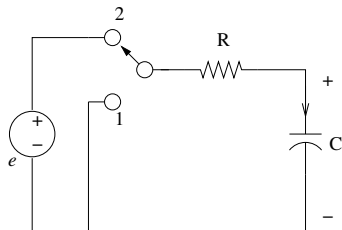

The switch is in 1, the current of capacitor


$$C \frac{dV_C}{dt} = -G(V_C)$$

The state equation;

$$\frac{dV_C}{dt} = -\frac{1}{RC} V_C$$

Zero-input response
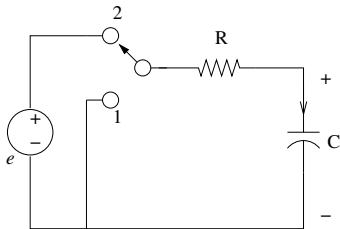
$$V_C(t) = e^{-\frac{1}{RC}(t-t_0)} V_C(0)$$



The switch is in 2, the state equation of the circuit

$$C \frac{dV_C}{dt} = G(e - V_C)$$

in standart form

$$\frac{dV_C}{dt} = -\frac{1}{RC} V_C + \frac{1}{RC} e$$

The solution of  $V_C(t)$ ;

$$V_C(t) = e^{-\frac{1}{RC}(t-t_0)} V_C(0) + \int_0^t e^{-\frac{1}{RC}(t-\tau)} \frac{1}{RC} e(\tau) d\tau$$

# Homogeneous Solution

The homogeneous solution is also called the natural response is the general solution of DE when the input is set to zero;

$$\dot{x} = ax.$$

The homogeneous solution has the form

$$x_h(t) = Ke^{at}$$

Particular Solution (Forced response)  $x_p(t)$  is depend on the source  $e$  and it will be picked up from the Table. Substituting  $x_p(t)$  into DE eqn. we will obtain the parameters of the  $x_p(t)$ .

$$\dot{x}_p = ax_p + be$$

# Particular Solutions

| SOURCE  | PARTICULAR SOLUTION  |
|---|--|
| $E$   | $K$  |
| $Ee^{\alpha t}$                               | $Ke^{\alpha t}$  |
| $Ee^{at}$                                     | $K_1e^{at} + K_2te^{at}$   |
| $Et$  | $K_1 + K_2t$   |
| $E \cos(\omega t)$                            | $K_1 \cos(\omega t) + K_2 \sin(\omega t)$  |
| $E \sin(\omega t)$                            | $K_1 \cos(\omega t) + K_2 \sin(\omega t)$  |
| $E_1 \sin(\omega_1 t) + E_2 \cos(\omega_2 t)$ | $K_1 \cos(\omega_1 t) + K_2 \sin(\omega_2 t)$<br>$+ K_3 \cos(\omega_2 t) + K_4 \sin(\omega_2 t)$ |



# The complete response

The complete response is the sum of natural response and forced response.

$$x(t) = x_h(t) + x_p(t)$$

Using initial condition  $x(t_0)$

$$x_0 = Ke^{at_0} + x_p(t_0)$$

Parameter for the natural response can be obtained  $K = \frac{x_0 - x_p(t_0)}{e^{at_0}}$ .

The complete response

$$x(t) = \underbrace{(x_0 - x_p(t_0))e^{a(t-t_0)}}_{\text{Natural response}} + \underbrace{x_p(t)}_{\text{Particular solution}}$$

Zero-input and zero-state (forced response) responses express in term of natural response and Particular solution.

$$x(t) = \underbrace{x_0 e^{a(t-t_0)}}_{\text{zero-input response}} + \underbrace{x_p(t) - x_p(t_0)e^{a(t-t_0)}}_{\text{zero-state response}}$$

A first-order differential equation is given by

$$\dot{x} = -2x + e(t)$$

where  $e(t) = e^{-t}u(t)$  and  $x(0) = 2$ . Find  $x(t)$  for  $t > 0$ . The homogeneous solution is

$$x_h(t) = Ke^{-2t}$$

and the particular solution is

$$x_p(t) = Ee^{-t}$$

Substituting the particular solution into the DE

$$-Ee^{-t} = -2Ee^{-t} + e^{-t}$$

then  $E = 1$ , we obtain the complete the solution

$$x(t) = Ke^{-2t} + e^{-t}$$

Applying the initial condition to the above equation, we obtain  $K = 1$ .  
Then

$$x(t) = (e^{-2t} + e^{-t})u(t)$$

The zero-input response is


$$x_{zi}(t) = 2e^{-2t}$$

and the zero-state response is

$$\begin{aligned}x_{zs}(t) &= \int_0^t e^{-2(t-\tau)} e^{-\tau} d\tau \\ &= e^{-2t} \int_0^t e^{\tau} d\tau \\ &= e^{-2t}(e^t - 1)\end{aligned}$$

The complete solution
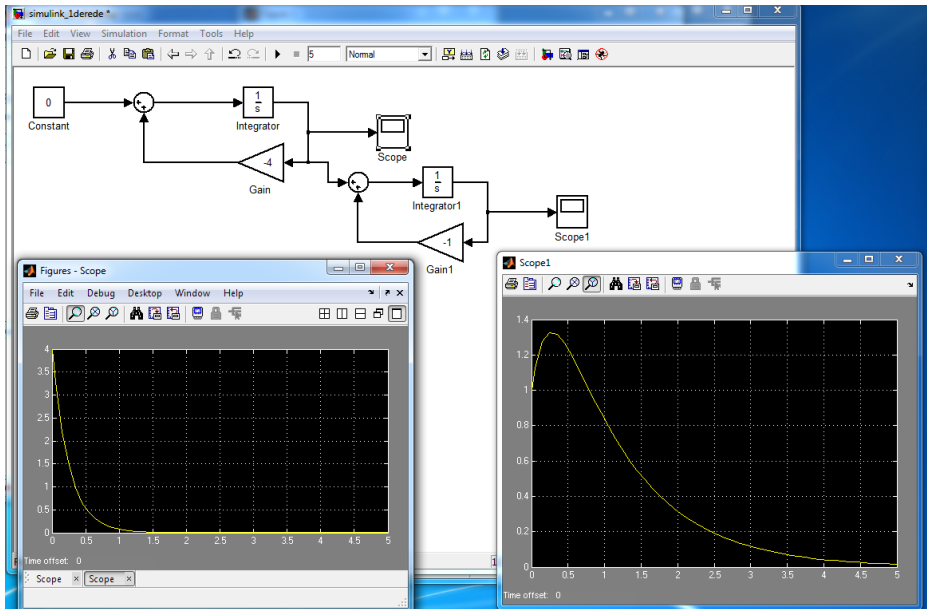
$$x(t) = 2e^{-2t}u(t) + e^{-t} - e^{-2t}$$



A first-order differential equation is given by  $\dot{x} = -4x$  where  $x(0) = 4$ . Find  $x(t)$  for  $t > 0$ . The homogeneous solution is  $x(t) = Ke^{-4t}$ . Applying the initial condition to the above equation, we obtain  $K = 4$ . Then  $x(t) = 4e^{-4t}u(t)$

It's connected to a second first order system which is

$$\dot{z} = -z + x(t)$$

where  $z(0) = 1$ . Find  $z(t)$  for  $t > 0$ .

The homogeneous and the particular solutions are

$$z_h(t) = Ke^{-t} \quad z_p(t) = Ee^{-4t}$$

Substituting the particular solution into the DE


$$-4Ee^{-4t} = -Ee^{-4t} + 4e^{-4t}$$



then  $E = -4/3$ , we obtain the complete the solution

$z(t) = Ke^{-t} - 4/3e^{-4t}$ . Applying the initial condition to the above equation, we obtain  $K = 7/3$ . Then

$$z(t) = (7/3e^{-t} - 4/3e^{-4t})u(t)$$
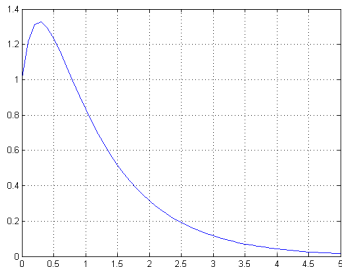
```
>> t=0:0.1:5;  
>> plot(t,7*exp(-t)/3-4*exp(-4*t)/3);
```



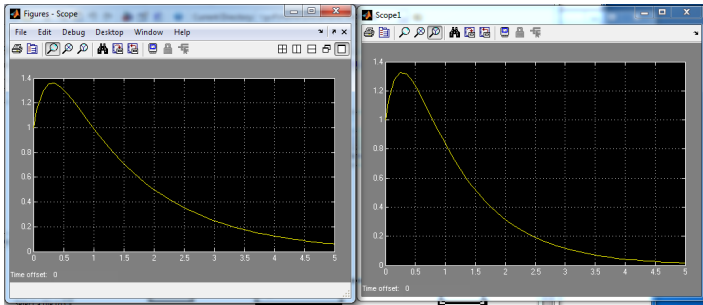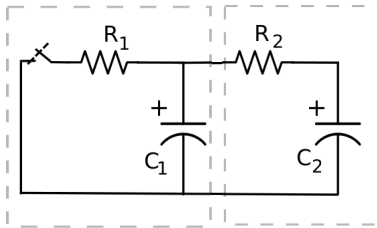

# Solution of Second Order State Equations

A second order state equation is given by standard form such as

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} e$$

or

$$\begin{aligned} \frac{dx_1}{dt} &= a_{11}x_1 + a_{12}x_2 + b_1e \\ \frac{dx_2}{dt} &= a_{21}x_1 + a_{22}x_2 + b_2e \end{aligned}$$

The output of this system is given by

$$y(t) = c_1x_1(t) + c_2x_2(t) + de(t)$$



In order to have differential equation in the output variable

$$\frac{d^2x_1}{dt^2} - (a_{11} + a_{22})\frac{dx_1}{dt} + (a_{11}a_{22} - a_{12}a_{21})x_1 = b_1\frac{du}{dt} + (a_{12}b_2 - a_{22}b_1)e$$

$$\frac{d^2x_2}{dt^2} - (a_{11} + a_{22})\frac{dx_2}{dt} + (a_{11}a_{22} - a_{12}a_{21})x_2 = b_2\frac{du}{dt} + (a_{21}b_1 - a_{11}b_2)e.$$

Undamped natural frequency

$$w = \sqrt{a_{11}a_{22} - a_{12}a_{21}}$$

Damping ratio

$$Q = -\frac{1}{2w}(a_{11} + a_{22})$$

With these new coefficients

$$\frac{d^2x_1}{dt^2} + 2Qw \frac{dx_1}{dt} + w^2x_1 = b_1 \frac{du}{dt} + (a_{12}b_2 - a_{22}b_1)e$$

$$\frac{d^2x_2}{dt^2} + 2Qw \frac{dx_2}{dt} + w^2x_2 = b_2 \frac{du}{dt} + (a_{21}b_1 - a_{11}b_2)e.$$

Defining

$$q_0 = c_1(-b_1a_{22} + a_{12}b_2) + c_2(-b_2a_{11} + a_{21}b_1) + d(a_{11}a_{22} - a_{12}a_{21})$$

$$q_1 = c_1b_1 + c_2b_2 - d(a_{11} + a_{22})$$

$$q_2 = d$$

The second order differential equation

$$\frac{d^2y}{dt^2} - (a_{11} + a_{22})\frac{dy}{dt} + (a_{11}a_{22} - a_{12}a_{21})y = q_2\frac{d^2e}{dt^2} + q_1\frac{de}{dt} + q_0e.$$

and it is in the term of standard parameter

$$\frac{d^2y}{dt^2} + 2Qw\frac{dy}{dt} + w^2y = q_2\frac{d^2e}{dt^2} + q_1\frac{de}{dt} + q_0e.$$

# Solution of the Homogeneous Second-Order Equation

For  $e(t) = 0$ , 2nd order equation

$$\frac{d^2y}{dt^2} + 2Qw \frac{dy}{dt} + w^2y = 0$$

$$y_h(t) = K_1e^{\lambda_1 t} + K_2e^{\lambda_2 t}$$

where  $K_1$  and  $K_2$  are constants defined by the initial conditions, and the eigenvalues  $\lambda_1$  and  $\lambda_2$  are the roots of the characteristic equation. Or  $\lambda_1$  and  $\lambda_2$  are found from

$$\lambda_i^2 + 2Qw\lambda_i + w^2 = 0$$

the eigenvalues

$$\lambda_1, \lambda_2 = -Qw \mp w\sqrt{Q^2 - 1}.$$

$K_1$  and  $K_2$  are obtain

$$y(0) = c_1x(0) + c_2x_2(0)$$

using initial conditions

$$y(0) = K_1 + K_2$$


and

$$\left. \frac{dy(t)}{dt} \right|_{t=0} = c_1(a_{11}x_1(0) + a_{12}x_2(0)) + c_2(a_{21}x_1(0) + a_{22}x_2(0)) = K_1\lambda_1 + K_2\lambda_2$$

The response of the system for  $e = 0$  is depend on

$$\lambda_1, \lambda_2 = w(-Q \mp \sqrt{Q^2 - 1}).$$

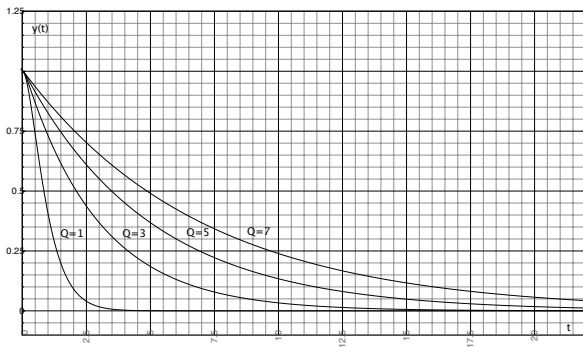- $Q > 1$  :  $\lambda < 0$  and real. In this case, the response is said to be overdamped.



- $Q = 1$ : The response is said to be critically damped.

$$\lambda_1, \lambda_2 = -w.$$

Homogenous solution is

$$y_h(t) = K_1 e^{-wt} + K_2 t e^{-wt}$$


- $0 \leq Q < 1$  : The response is said to be underdamped.

$$\lambda_1, \lambda_2 = -Q\omega \mp j\omega\sqrt{1 - Q^2}.$$

The output

$$y_h(t) = y_0 \frac{e^{-Q\omega t}}{\sqrt{1 - Q^2}} \cos(\omega_d t - \phi)$$

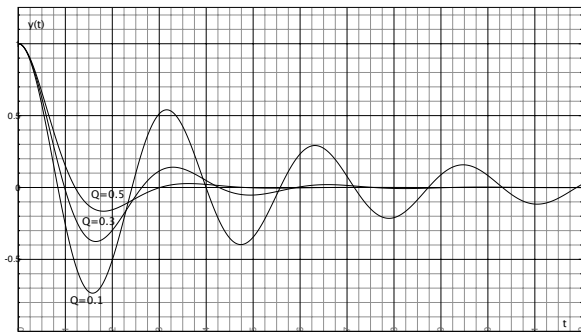
where  $\omega_d = \omega\sqrt{1 - Q^2}$  and  $\phi = \tan^{-1} \frac{Q}{\sqrt{1 - Q^2}}$ .






- $Q < 0$

$$\text{Real}\{\lambda\} > 0$$

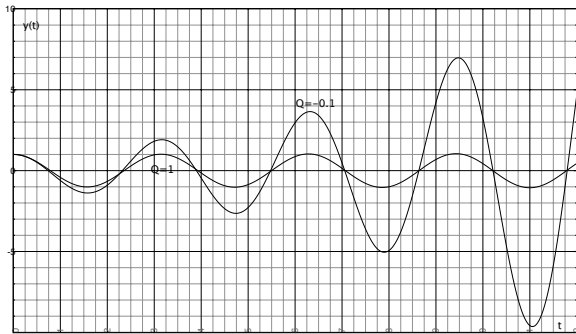
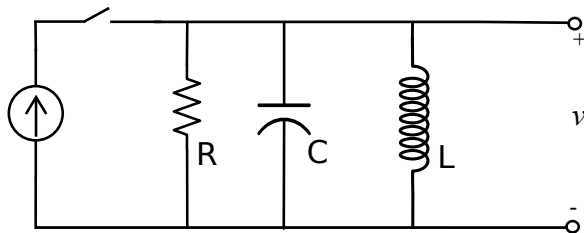
# Natural Response of a Parallel RLC Circuit



$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC}v = 0$$

$$w = \frac{1}{\sqrt{LC}}, \quad Q = \frac{\sqrt{LC}}{2RC},$$

Electric Circuits, James W. Nilsson and Susan A. Riedel, pp. 286-301

# Step response

We will find the output for  $e(t) = u(t)$  which is given by

$$y(t) = y_h(t) + y_o(t)$$

The particular solution  $y_o(t) = K$ . Substituting the particular solution into the eqn. we will have  $K = \frac{1}{w_n^2}$ . Step response is obtain such as


$$y(t) = K_1 e^{\lambda_1 t} + K_2 e^{\lambda_2 t} + \frac{1}{w_n^2}$$

$K_1$  and  $K_2$  are obtained form the initial conditions with

$$y(0) = K_1 + K_2 + \frac{1}{w_n^2}$$

$$\left. \frac{dy(t)}{dt} \right|_{t=0} = K_1 \lambda_1 + K_2 \lambda_2$$

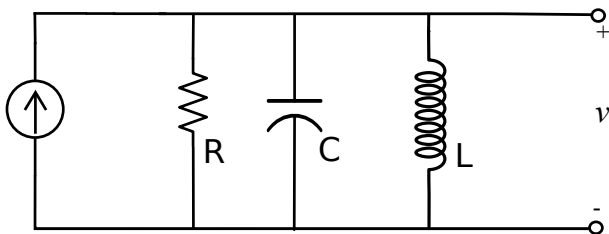
## Step Response of a Parallel RLC Circuit



$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC}v = \frac{1}{LC}i_k$$

Electric Circuits, James W. Nilsson and Susan A. Riedel, pp. 301-307

# Step response

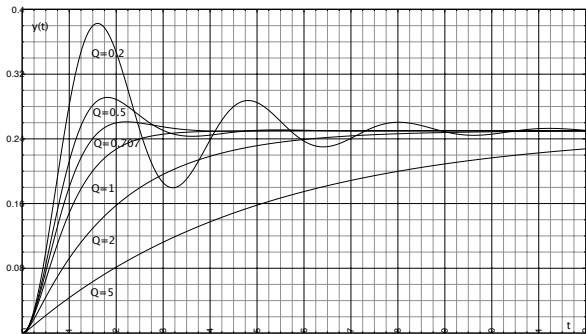

## Example

$$\dot{x} = \begin{bmatrix} 0 & 2 \\ -1 & -3 \end{bmatrix} x + \begin{bmatrix} 0 \\ 1 \end{bmatrix} e$$

where  $\begin{bmatrix} 1 \\ 0 \end{bmatrix}$  is the initial condition and the output is  $y(t) = x_1(t)$ . Let find the output for  $e(t) = 0$ ,  $e(t)=u(t)$  and  $e(t) = 10 \cos(t)$ .

We have

$$\begin{aligned}\dot{x}_1 &= 2x_2 \\ \dot{x}_2 &= -x_1 - 3x_2 + e\end{aligned}$$

The output is obtain such as

$$\begin{aligned}\ddot{x}_1 &= 2\ddot{x}_2 \\ \dot{x}_1 &= 2(-x_1 - 3x_2 + e) \\ &= -2x_1 - 6x_2 + 2e \\ &= -3\dot{x}_1 - 2x_1 + 2e\end{aligned}$$

For the homogeneous solution, we must find eigenvalues

$$\det \left\{ \lambda I - \begin{bmatrix} 0 & 2 \\ -1 & -3 \end{bmatrix} \right\} = \lambda^2 + 3\lambda + 2 = 0$$

$\lambda = -1$  ve  $\lambda = -2$  . The homogeneous solution

$$y(t) = K_1 e^{-t} + K_2 e^{-2t}$$

Using initial condition

$$\begin{aligned} y(0) &= K_1 + K_2 = 1 \\ \dot{y}(0) &= -K_1 - 2K_2 = 0 \end{aligned}$$

$K_1 = 2$  and  $K_2 = -1$  are obtained. The solution is

$$y(t) = 2e^{-t} - e^{-2t}.$$

For  $e(t) = u(t)$ , the particular solution is chosen from table which is

$$y_{\ddot{o}}(t) = E$$

Substituting the particular solution into the DE equ. We have  $E = 1$ .

$$y(t) = K_1 e^{-t} + K_2 e^{-2t} + 1$$

Using the initial conditions

$$\begin{aligned} y(0) &= K_1 + K_2 + 1 = 1 \\ y(0) &= -K_1 - 2K_2 + 1 = 0 \end{aligned}$$

we will have  $K_1 = -1$  and  $K_2 = 1$ . The complete solution is given by

$$y(t) = -e^{-t} + e^{-2t} + u(t)$$



For  $e(t) = 10 \cos(t)$ , the particular solution is chosen from table which is

$$y_{\ddot{o}}(t) = E_1 \cos t + E_2 \sin t$$

Substituting the particular solution into the DE equ.

$$-E_1 \cos t - E_2 \sin t = 3E_1 \sin t - 3E_2 \cos t - 2E_1 \cos t - 2E_2 \sin t + 20 \cos t$$

we have  $E_1 = 2$  ve  $E_2 = 6$  then


$$y(t) = K_1 e^{-t} + K_2 e^{-2t} + 2 \cos t + 6 \sin t$$

Using the initial conditions

$$\begin{aligned} y(0) &= K_1 + K_2 + 2 = 1 \\ \dot{y}(0) &= -K_1 - 2K_2 + 6 = 0 \end{aligned}$$

we will have  $K_1 = -8$  and  $K_2 = 7$ . The complete solution is given by
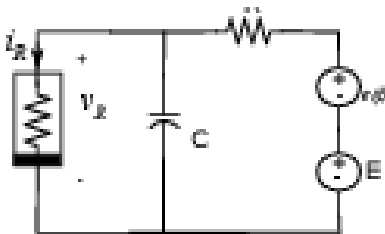
$$y(t) = -8e^{-t} + 7e^{-2t} + 2 \cos t + 6 \sin t$$



$$E = -2V, R = 2\Omega, e(t) = 0.2 \sin(\omega t), C = 1F, v_R = i_R^2$$

DC Analysis:

$$C \frac{dV_c}{dt} = i_C = 0$$

$$e = iR + v_R = -4 = 2i_R + i_R^2$$

$$i_R = -2Amps$$

AC Analysis:  $R_Q = -4\Omega$

$$CC \frac{dV_c}{dt} = \frac{(e - v_C)}{R} - \frac{v_C}{R_Q}$$

$$\frac{dv_C}{dt} = -\frac{v_C}{4} + 0.1 \sin(\omega t)$$